

Intro to Digital Design

L4: Combinational Building Blocks & Sequential Logic

Instructor: Naomi Alterman

Teaching Assistants:

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Aarjav Jain

Packard Stephenson

Administrivia

- ❖ Lab 4 out today
 - Playing with the 7-segment displays
- ❖ Quiz 1 is next week in lecture
 - Last 20 minutes, worth 10% of your course grade
 - On Lectures 1-3: ~~CL, K-maps~~, Waveforms, and Verilog
 - Past Quiz 1 (+ solutions) on website: Course Info → Quizzes
 - **NB**: we'll probably put a block diagram question on this one similar to what you've been drawing in your lab reports

Lecture Outline

- ❖ **Arithmetic (adders)**
- ❖ Sequential Logic in theory
- ❖ Sequential Logic in Verilog

Review: Unsigned Binary Integers

- ❖ n bits can represent integers 0 to $2^n - 1$
- ❖ When written in **binary**/"base 2", each digit represents a bit (eg, a signal on a wire)
- ❖ How I convert to base 2 in my head:

Binary digits: ...

	1	1	0	0	1	
	x16	+ x8	+ x4	+ x2	+ x1	= 25
	(2^4)	(2^3)	(2^2)	(2^1)	(2^0)	

Review: Binary Arithmetic

- ❖ Add and subtract using the “carry” and “borrow” rules, just in binary

#1


$$\begin{array}{r}
 63 \\
 + \underline{8} \\
 \hline
 71
 \end{array}
 \quad
 \begin{array}{r}
 0011111 \\
 + 0000100 \\
 \hline
 01000111
 \end{array}$$

Handwritten annotations: Red arrows point from the rightmost 1 of the first number to the 0s of the second number, and from the 1 of the second number to the 0 of the first number. The final 1 of the first number and the final 0 of the second number are circled in red.
 
#2

$$\begin{array}{r}
 65 \\
 - \underline{8} \\
 \hline
 57
 \end{array}
 \quad
 \begin{array}{r}
 0100001 \\
 - 0000100 \\
 \hline
 0011101
 \end{array}$$

Handwritten annotations: Red arrows point from the 0s of the first number to the 1s of the second number, and from the 1 of the first number to the 0 of the second number. The first 1 of the first number and the first 0 of the second number are circled in red.



<http://hartenstein.de/KARL/KARL-folder.pdf>

Half Adder (1 bit)


$$\begin{array}{r}
 a_3 \quad a_2 \quad a_1 \quad a_0 \\
 + \quad b_3 \quad b_2 \quad b_1 \quad b_0 \\
 \hline
 s_3 \quad s_2 \quad s_1 \quad s_0
 \end{array}$$

Carry-out bit


a_0	b_0	c_1	s_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\text{Carry} = a_0 b_0$$

$$\text{Sum} = a_0 \oplus b_0$$

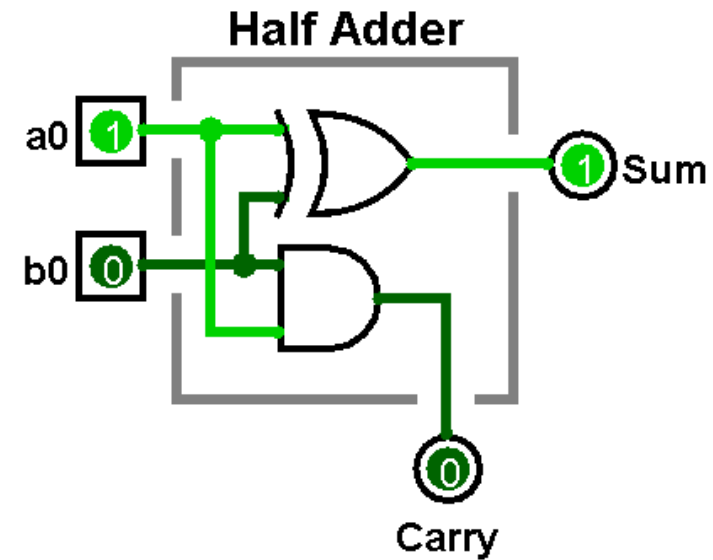

Full Adder (1 bit)

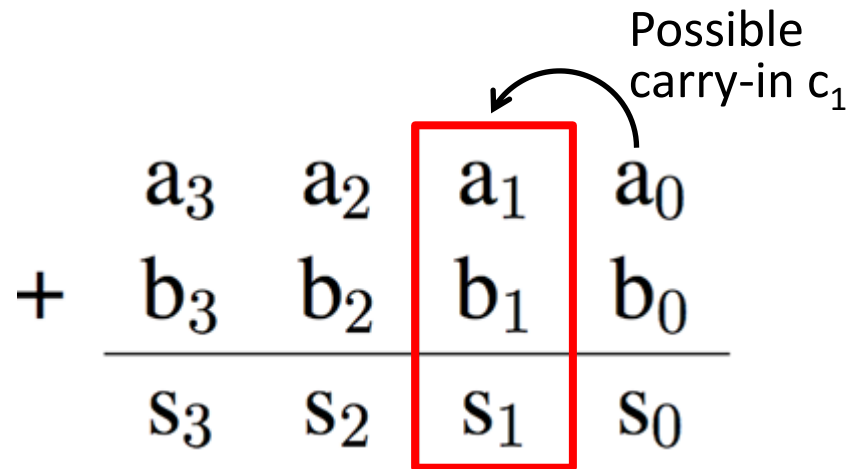


$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

if majority of a, b, c are 1 output is 1


Carry-in c_i Carry-out c_{i+1}

c_i	a_i	b_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

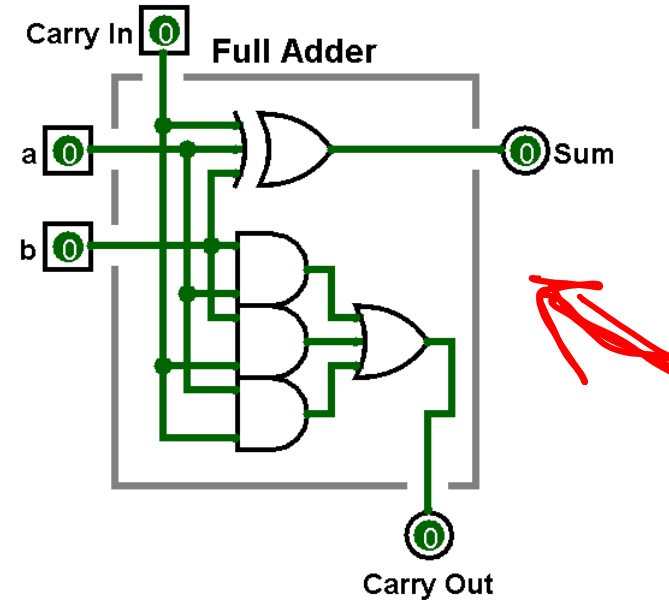


Multi-Bit Adder (N bits)

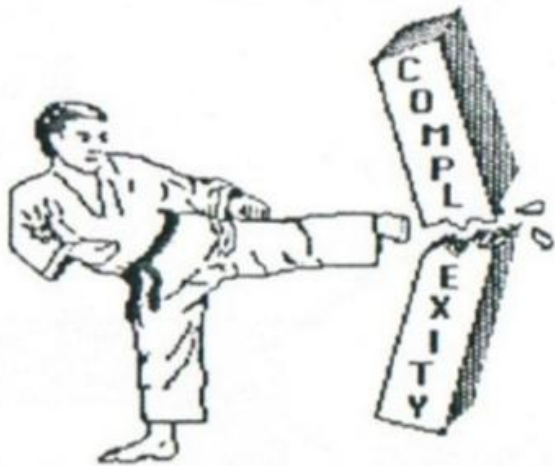- ❖ Chain 1-bit adders by connecting CarryOut_i to CarryIn_{i+1} :


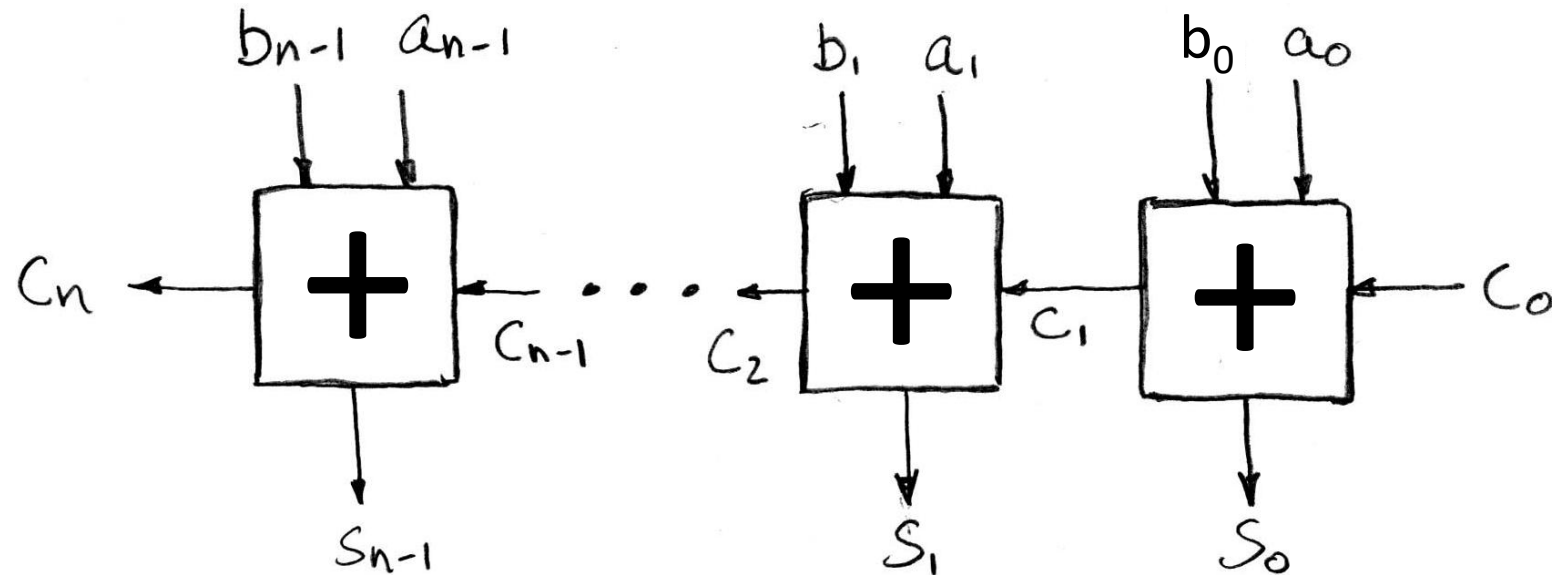
<http://hartenstein.de/KARL/KARL-folder.pdf>



1-bit Adders in Verilog

- ❖ How do we get the carry bit out of a Verilog adder?

```
module sad_add (s, a, b);  
  output logic s;  
  input  logic a, b;  
  
  always_comb begin  
    s = a + b;  
  end  
endmodule
```

- ❖ Use {sig, ..., sig} for concatenation

```
module half_add (c, s, a, b);  
  output logic c, s;  
  input  logic a, b;  
  
  always_comb begin  
    {c, s} = a + b;  
  end  
endmodule
```

Ripple-Carry Adder in Verilog

```
module fulladd (cout, s, cin, a, b);  
  output logic cout, s;  
  input  logic cin, a, b;  
  
  always_comb begin  
    {cout, s} = cin + a + b;  
  end  
endmodule
```

❖ Chain full adders?

```
module add2 (cout, s, cin, a, b);  
  output logic cout; output logic [1:0] s;  
  input  logic cin;  input  logic [1:0] a, b;  
  logic  c1;  
  
  fulladd b1 (cout, s[1], c1, a[1], b[1]);  
  fulladd b0 (c1, s[0], cin, a[0], b[0]);  
endmodule
```

instantiating
N copies of
our adder circ.

Feeling negative

- ❖ Ok, but how do we build logic to handle negative numbers?

Review: Two's Complement

- ❖ MSB's weight becomes -2^{n-1}
 - Can think of MSB as "sign bit"

1 0 1 0 1

~~1×16~~ + 0×8 + 1×4 + 0×2 + $1 \times 1 = 11$

(2^4) (2^3) (2^2) (2^1) (2^0)

$\times -16$
 $-(2^4)$

$- 11$

Review: Two's Complement (cont'd)


❖ Properties:

- In n bits, represent integers -2^{n-1} to $2^{n-1} - 1$
- Positive number encodings match unsigned numbers
- Single zero (encoding = all zeros)

❖ Negation procedure:

- Take the bitwise complement and then add one
 
$$\underline{\underline{(\sim x + 1 == -x)}}$$



Subtraction in binary

- ❖ Negate the 2nd operand and then add like usual:

$$A - B = A + (-B) = A + (\sim B + 1)$$

negate B

- ❖ **Note:** we “throw away” the last carry-out

- ❖ 4-bit examples:

#3	-	0 0 1 0	+2	U4	2
	+	1 1 0 0	-4	U4	<u>12</u>
		<u>1 1 1 0</u>	-2		

#4	+	1 0 0 0	-8	U4	8
	+	0 1 0 0	+4	U4	4
		<u>1 1 0 0</u>	-4		

#5	+	0 1 1 0	+6	U4	6
	+	0 0 1 0	+2	U4	2


** (6+2) = 8*

#6	-	1 1 1 1	-1	U4	15
	-	1 1 1 0	-2	U4	14
		<u>1 1 1 1</u>			

+	<u>1 1 1 0</u>	4
	<u>0 1 0 0</u>	

Subtraction in circuitry

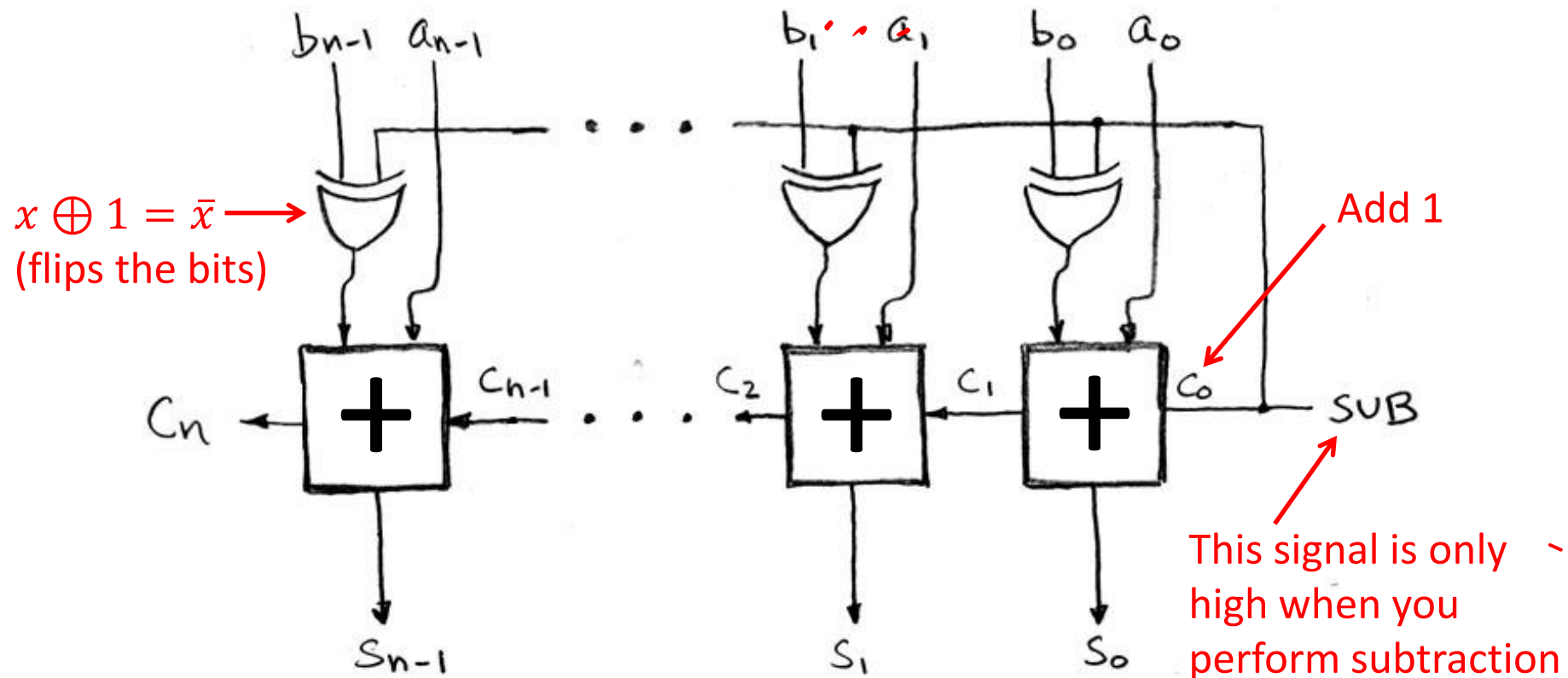- ❖ How do we modify our circuit to subtract numbers too?
 - Flip the bits and add 1!



Detecting Arithmetic Overflow

- ❖ **Overflow:** When a calculation produces a result that can't be represented in the current encoding scheme
 - Integer range limited by fixed width
 - Can occur in both the positive and negative directions
- ❖ **Unsigned Overflow** 2^{N-1} 0
 - Result of add/sub is $> U_{\max}$ or $< U_{\min}$
- ❖ **Signed Overflow**
 - Result of add/sub is $> T_{\max}$ or $< T_{\min}$
 - $(+) + (+) = (-)$ or $(-) + (-) = (+)$

Signed Overflow Examples

#7

	0 1 0 1	s4	+5
	+ 0 0 1 1		+3
	1 0 0 0		-8

← ← ←
u4
5
3
8
+)
+

#8

	1 0 0 1	s4	-7
	+ 1 1 1 0		-2
	0 1 1 1		7

← ← ←
(4)(2)(1)
+)
+


#9

	0 1 0 1	s4	+5
	+ 0 0 1 0		+2

#10

	1 1 0 0	s4	-4
	+ 0 1 0 0		4

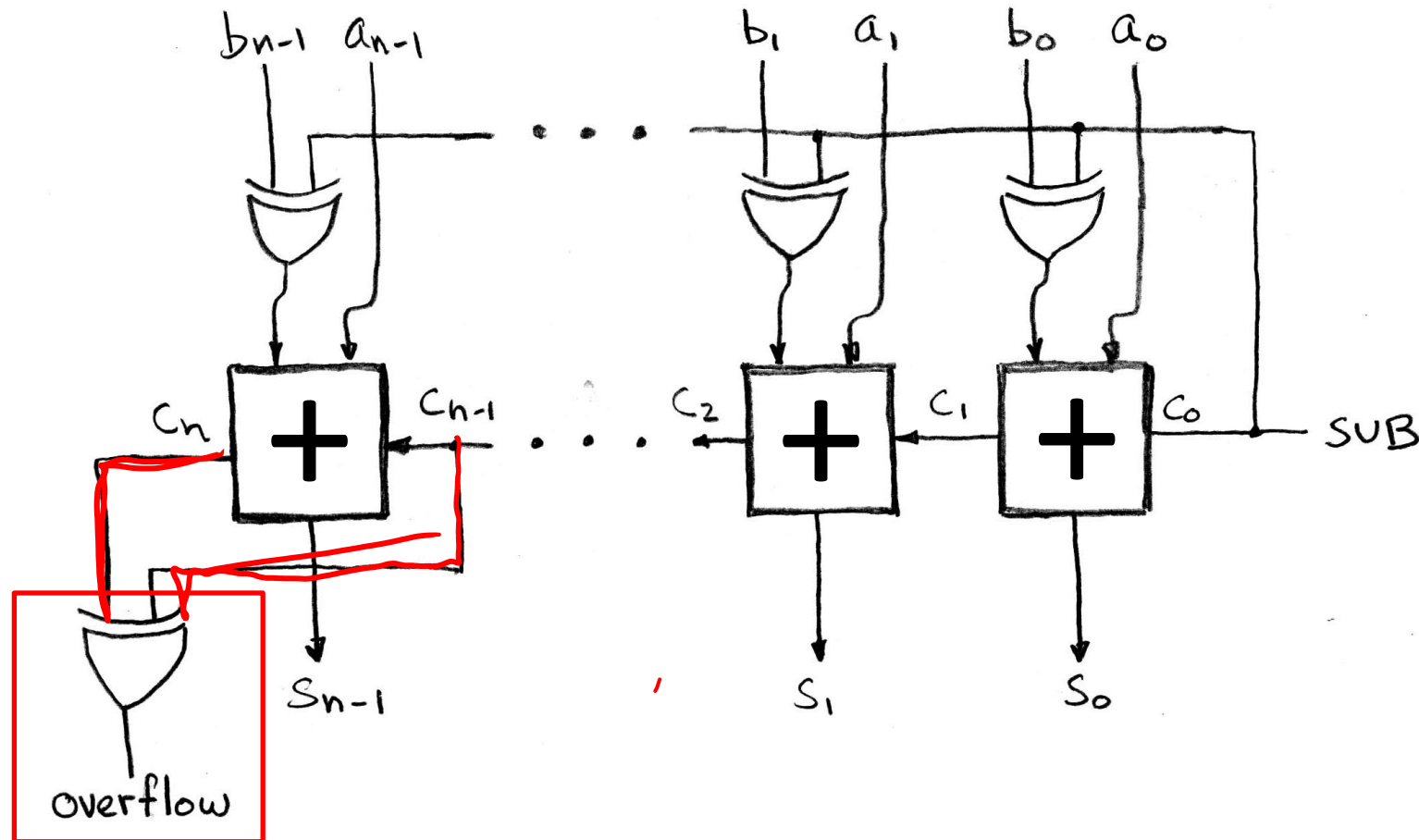Two's Complement Adder/Subtractor with Overflow



Add/Sub in Verilog (parameterized)

#define
templates < >

❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (overflow, carry_out, out, subtract, A, B);  
  output logic overflow, carry_out;  
  output logic [N-1:0] out;  
  input logic subtract;  
  input logic [N-1:0] A, B;
```

carry-in

add up to the
last col of
bits

```
endmodule // addN
```

Add/Sub in Verilog (parameterized)

❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (overflow, carry_out, out, subtract, A, B);
  output logic          overflow, carry_out;
  output logic [N-1:0] out;
  input  logic          subtract;
  input  logic [N-1:0] A, B;
  logic  [N-1:0]      B_prime;    // possibly bit-flipped B
  logic          carry_in;      // eg, second-to-last carry-out

  always_comb begin
    B_prime = B ^ {N{subtract}}; // replication operator
    {C2, out[N-2:0]} = A[N-2:0] + B_prime[N-2:0] + subtract;
    {carry_out, out[N-1]} = A[N-1] + B_prime[N-1] + carry_in;
    overflow = carry_out ^ carry_in;
  end
endmodule // addN
```

- “overflow” is the x86-64 CPU’s **OF** flag, “carry_out” is **CF** flag

Add/Sub in Verilog (parameterized)

```

module addN_tb ();
  logic          subtract;
  logic [N-1:0] A, B;
  logic          overflow, carry_out;
  logic [N-1:0] out;

  addN #(.N(4)) dut (.overflow, .carry_out, .out, .subtract, .A, .B);
  params port list
  initial begin
    #100; subtract = 0; A = 4'b0101; B = 4'b0010; // 5 + 2
    #100; subtract = 0; A = 4'b1101; B = 4'b1011; // -3 + -5
    #100; subtract = 0; A = 4'b0101; B = 4'b0011; // 5 + 3
    #100; subtract = 0; A = 4'b1001; B = 4'b1110; // -7 + -2
    #100; subtract = 1; A = 4'b0101; B = 4'b1110; // 5 - (-2)
    #100; subtract = 1; A = 4'b1101; B = 4'b0101; // -3 - 5
    #100; subtract = 1; A = 4'b0101; B = 4'b1101; // 5 - (-3)
    #100; subtract = 1; A = 4'b1001; B = 4'b0010; // -7 - 2
    #100;
  end
endmodule // addN_tb

```

Miso Moment




Lecture Outline

- ❖ Arithmetic (adders)
- ❖ **Sequential Logic in theory**
- ❖ Sequential Logic in Verilog

Synchronous Digital Systems (SDS)


Combinational Logic (CL)

 

Network of logic gates without feedback.

Outputs are functions only of inputs.

Sequential Logic (SL)

 

The presence of feedback introduces the notion of “state.”



Circuits can “remember” or store information.

Uses for Sequential Logic

- ❖ Place to store values for some amount of time:
 - Registers
 - Memory
- ❖ *Help control flow of information between combinational logic blocks*
 - Hold up the movement of information to allow for orderly passage through CL


Control Flow of Information

❖ Remember the hazards?

 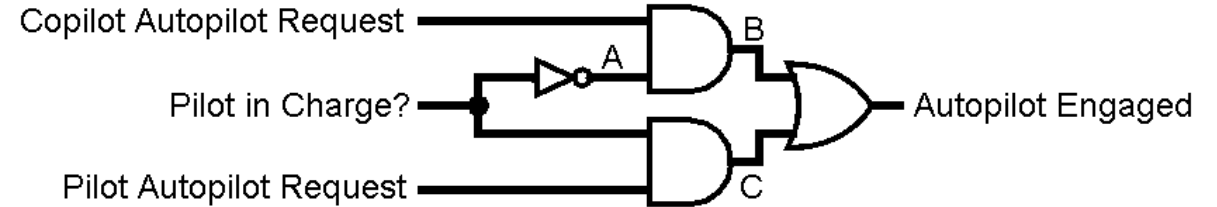

Design example: Perpetual Timer

 - ❖ A circuit that counts up from 0 over time
 - ❖ When time is up, stops counting and beeps incessantly
 - ❖ Needs to “remember” previous value to calculate next value




- ❖ Want:

```
s = 0;
while (true) {
    s = s + 1;
}
```

Timer: First Try

Does this work?

No

 


- 1) How do we say: 'S=0'?
- 2) How to control the next iteration of the 'for' loop?

Timer: Second Try


We'll add a "reset" signal
Does this work?



Still No!

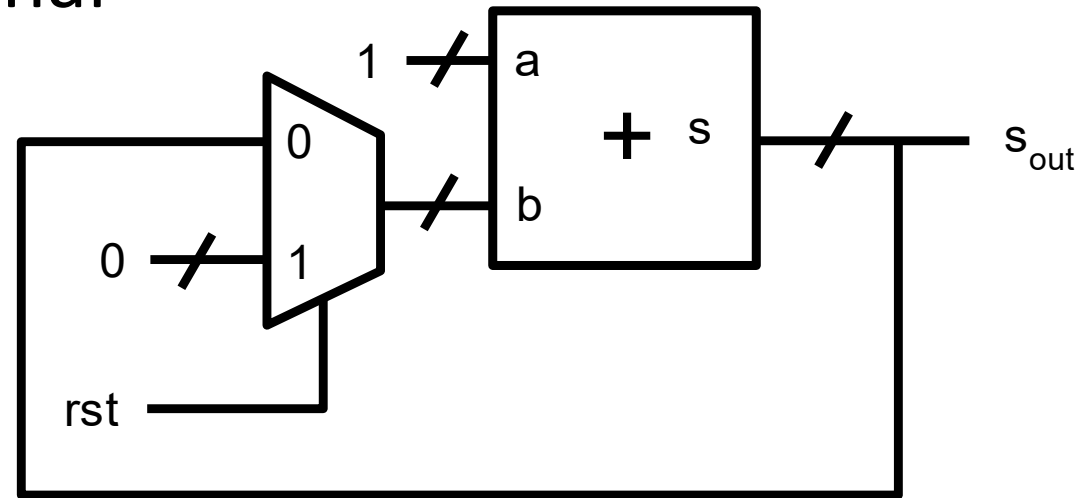


How to control the next iteration of
the 'for' loop?

State Element: Flip-Flop

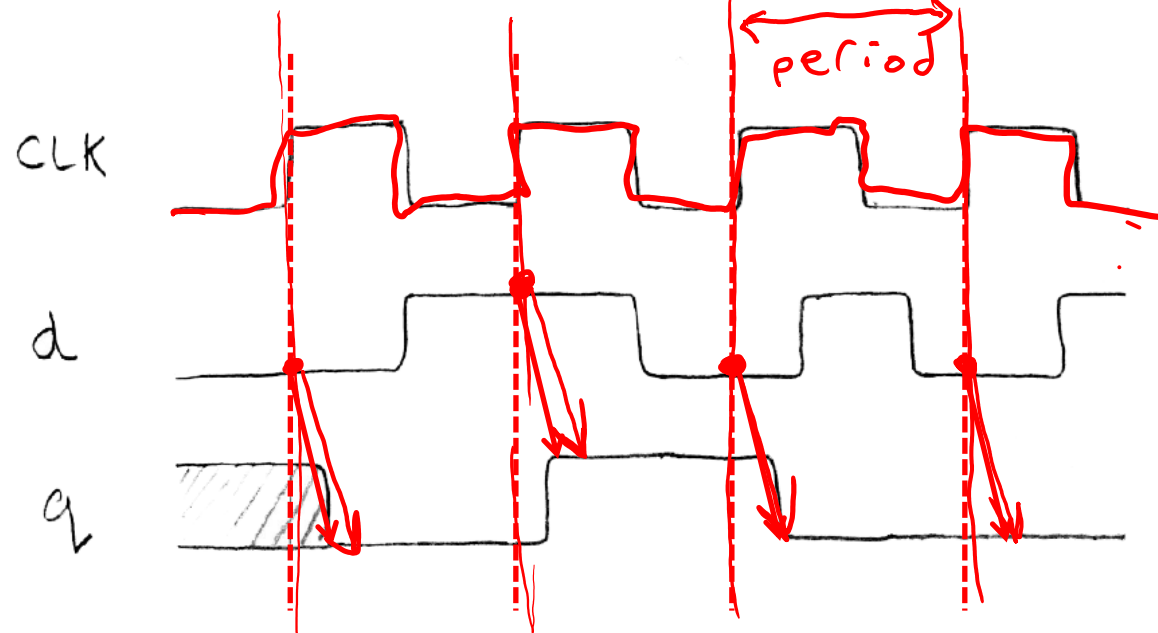 - ❖ Positive edge-triggered D-type flip flop
 - On the rising edge of the clock (), input d is **sampled** and held as the output " q " until the next clock edge
 - All other times, the input d is ignored



State Element: Register

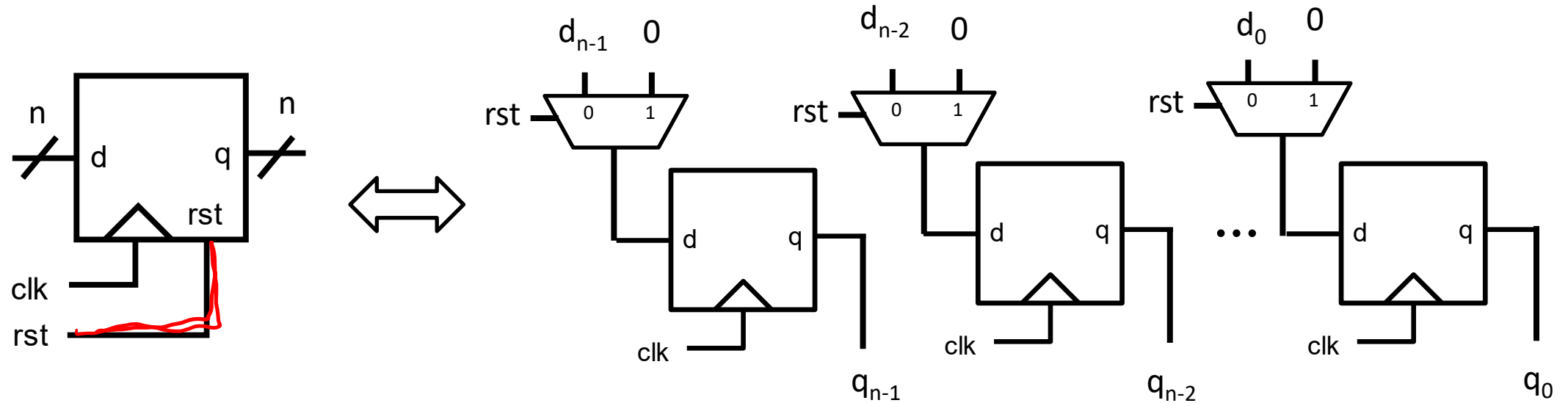


- ❖ A row of n flip-flops to store n bits
 - One for every bit in input/output bus width
- ❖ Optional RESET input
 - Forces Q to 0 when asserted
 - “Synchronous”: only detected if high on clock edge
 - “Asynchronous”: happens immediately

Timer: Third try

We happy?



We happy :3

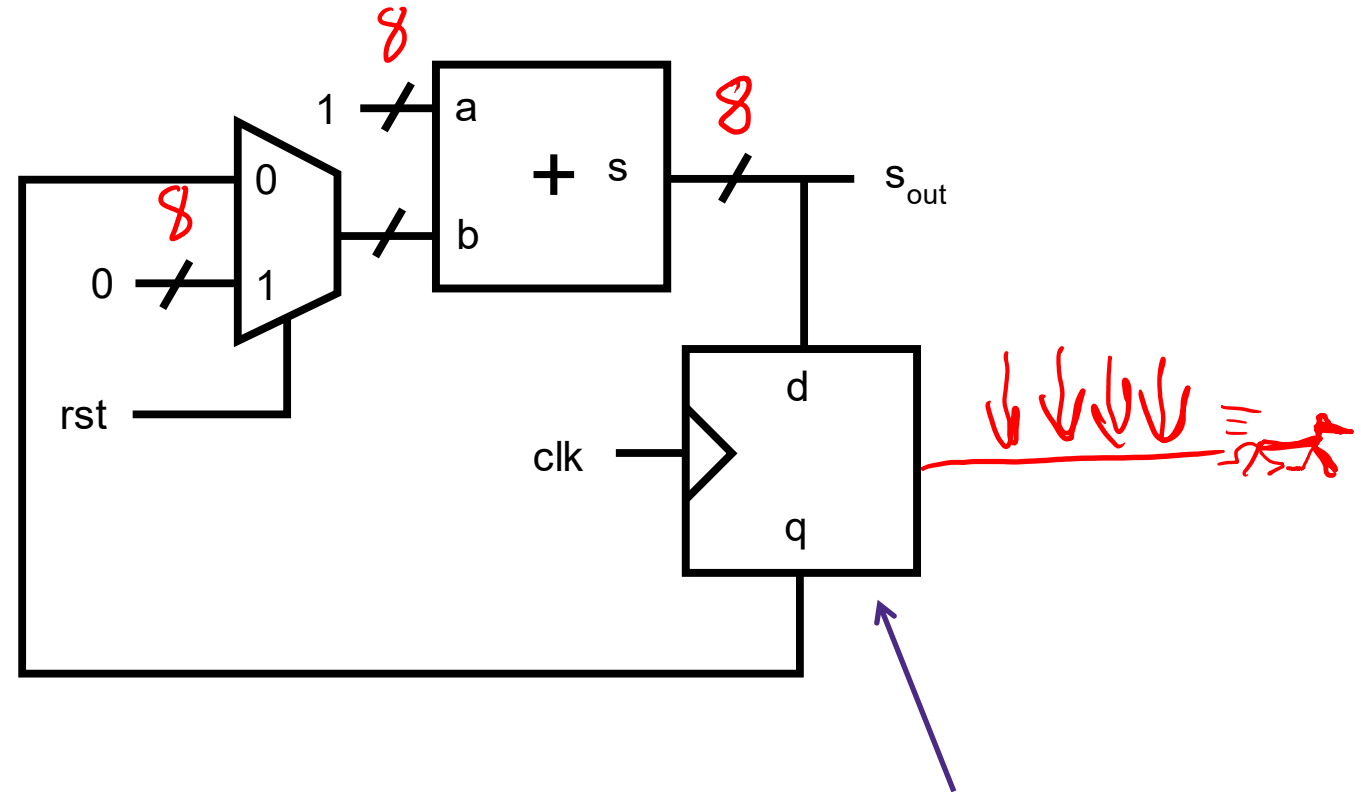

Register holds up the transfer of data to adder



Synchronous waveforms

Start by assuming no propagation delays

  



Synchronous waveforms

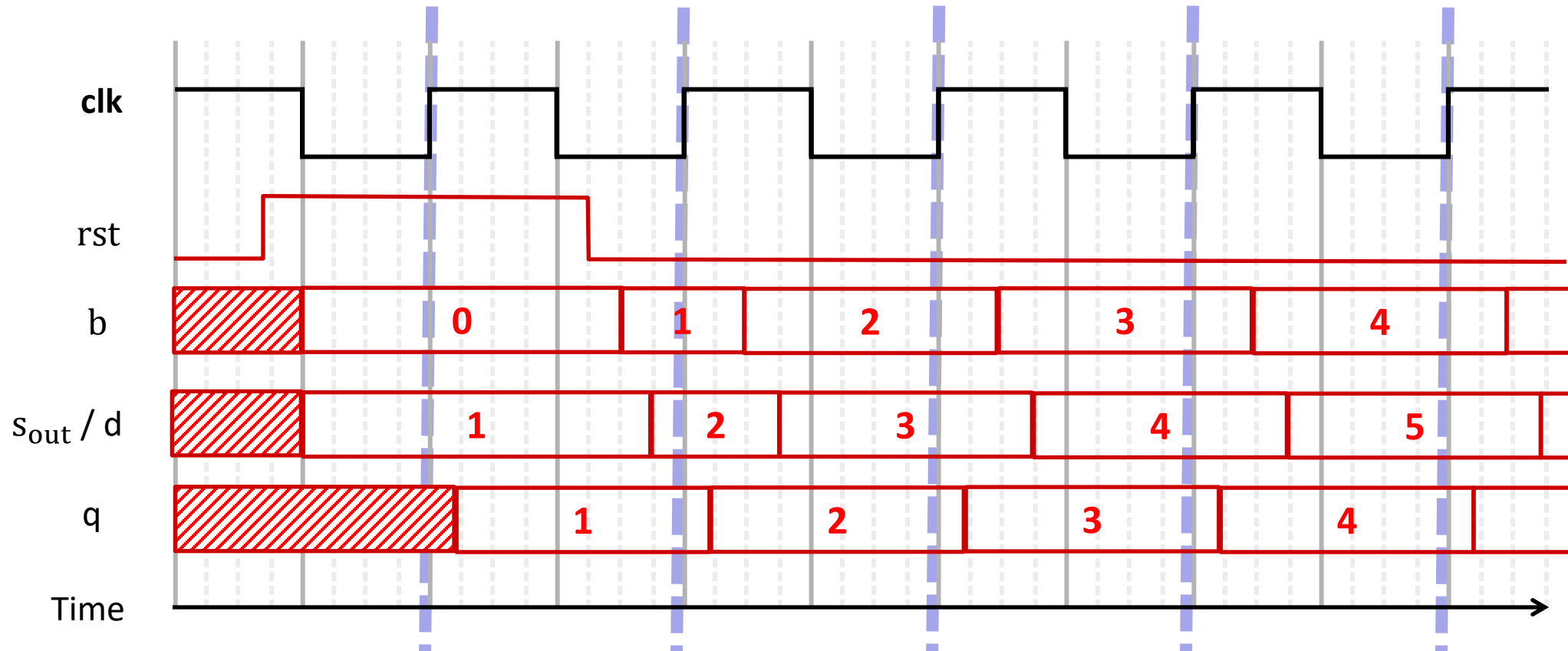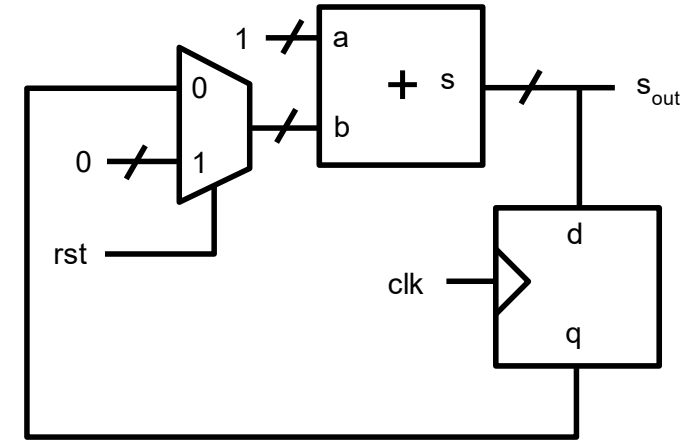Now a propagation delay of 3ns
(1 tick) per block





Autopilot Revisited

 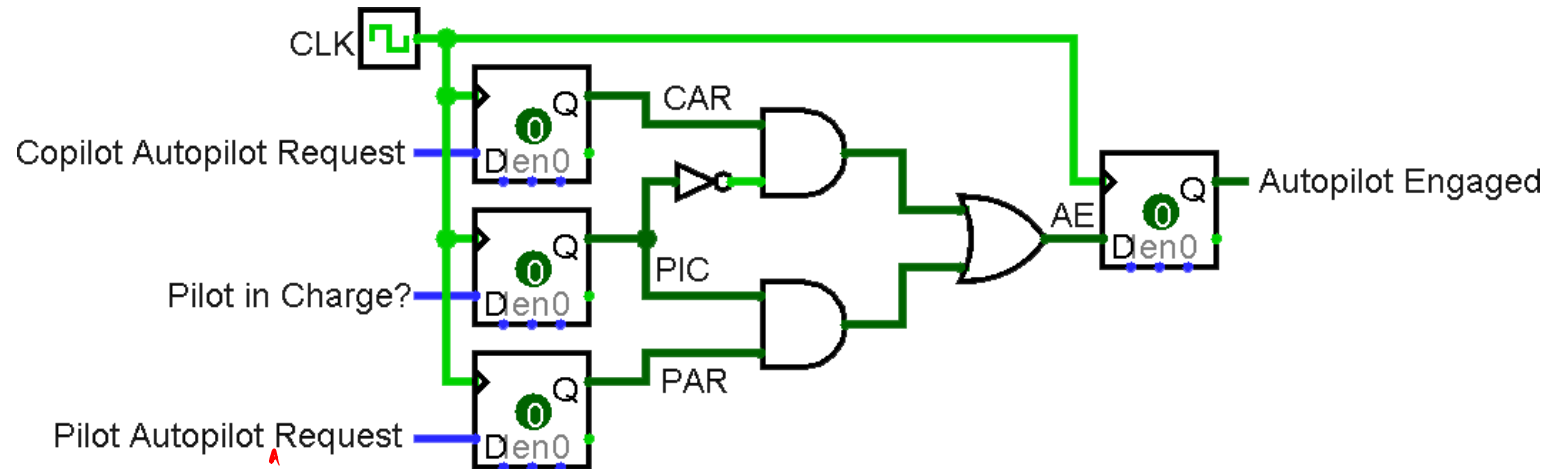- ❖ Flip-flops “filter out” circuit hazards!



Safe Sequential Circuits

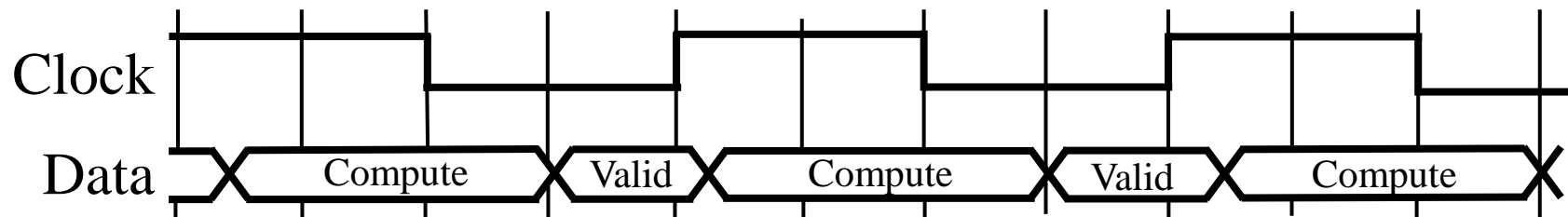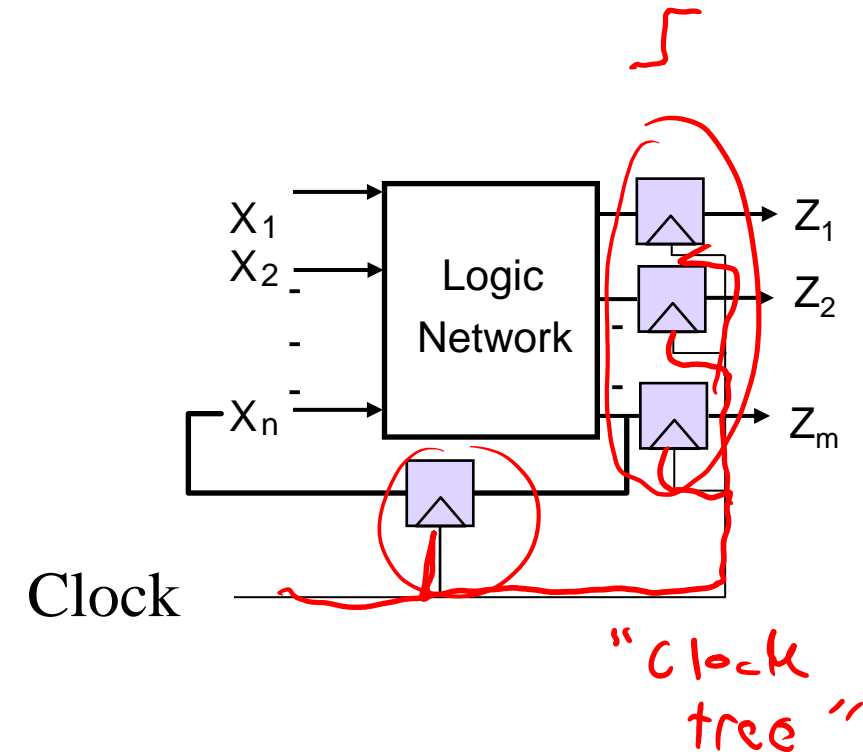- ❖ Clocked elements on feedback, perhaps outputs
 - Clock signal synchronizes operation
 - Clocked elements hide glitches/hazards
 - Output can wiggle with hazards as much as it wants as long as it's **stable around the positive clock edge**
 - More on this in a few weeks ;)



Lecture Outline

- ❖ Arithmetic (adders)
- ❖ Sequential Logic in theory
- ❖ **Sequential Logic in Verilog**

Reminder: “always_comb” blocks

- ❖ Verilog requires us to wrap control flow statements in an **always_comb** block
 - Block defines the full set of circuits that *may* drive the value on a **logic** variable
 - Idea: the last assignment in an always block to a given variable is the result that gets used
- ❖ But I promised there were more species of “**always**” block...



Verilog: Basic D Flip-Flop, Register

```

module basic_D_FF (q, d, clk);
  output logic q; // q is state-holding
  input logic d, clk;

  always ff @(posedge clk)
    q <= d; // use <= for clocked elements
endmodule

```



sensitivity list

```

module basic_reg (q, d, clk);
  output logic [7:0] q;
  input logic [7:0] d;
  input logic clk;

  always_ff @(posedge clk)
    q <= d;
endmodule


```

  

Sequential “always” blocks

- ❖ General `always` blocks:
 - “Always” running, but its output only gets sampled when signals in the *sensitivity list* change:

```
always @ (posedge clk)
```


- ❖ `always_ff`: 
 - Forces SystemVerilog to use flip flops as the stateful element in the circuit
 - **Only** use `always_ff` for sequential logic in this class, never `always`

```
always_ff @ (posedge clk)
```


Blocking vs. Nonblocking

- ❖ **Blocking** statement (\equiv):
statements executed sequentially
 - Resembles programming languages
- ❖ **Nonblocking** statement (\leftarrow):
statements executed “in parallel”
 - Resembles hardware
 
```
always_ff @ (posedge clk)
begin
    b = a;
    c = b;
end
```


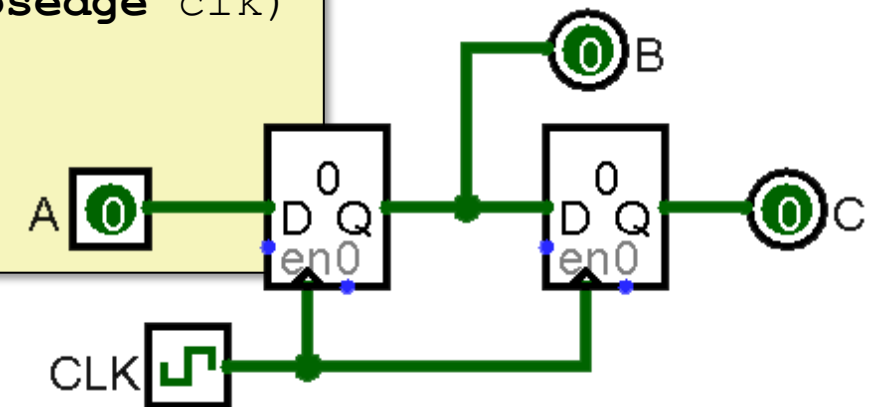
```
always_ff @ (posedge clk)
begin
    b <= a;
    c <= b;
end
```




SystemVerilog Coding Guidelines

- 1) When modeling sequential logic with an `always_ff` block, use ***nonblocking*** assignments (`<=`)
- 2) When modeling combinational logic with an `always_comb` block, use ***blocking*** assignments (`=`)
- 3) When modeling both sequential and combinational logic within the same `always_ff` block, use ***nonblocking*** assignments
- 4) Do not mix ***blocking*** and ***nonblocking*** assignments in the same `always_*` block
- 5) Do not make assignments to the same variable from more than one `always_*` block

Verilog: Reset Functionality

❖ Option 1: synchronous reset

 
```
module DFFR (q, d, reset, clk);  
    output logic q; // q is state-holding  
    input  logic d, reset, clk;  
  
    always_ff @(posedge clk)  
        if (reset)  
            q <= 0; // on reset, set to 0  
        else  
            q <= d; // otherwise pass d to q  
  
endmodule
```



Verilog: Reset Functionality


❖ Option 2: asynchronous reset
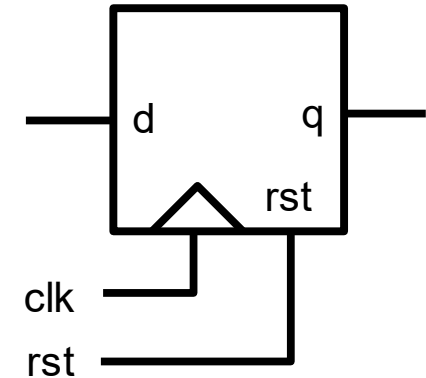
```
module DFFaR (q, d, reset, clk);  
    output logic q; // q is state-holding  
    input  logic d, reset, clk;  
  
    always_ff @(posedge clk or posedge reset)  
        if (reset)  
            q <= 0; // on reset, set to 0  
        else  
            q <= d; // otherwise pass d to q  
  
endmodule
```



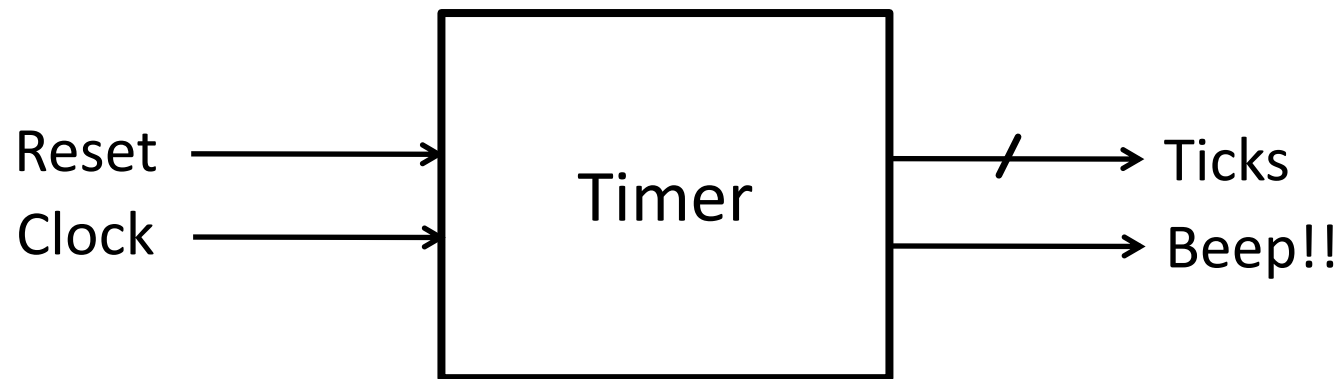Exercise for the reader: Advanced Timer

- ❖ Draw a circuit diagram for a block that counts up from 0 to parameter N
 - ❖ Very similar to our “perpetual timer” example, but it’ll need another mux and a block to compare if two numbers are equal
 - ❖ Can use a black box for the comparator
 - ❖ (but you know enough to design that too, if you wanted to 😊)



Summary

- ❖ Binary addition and subtraction can be performed with chained full adders
 - Two's complement allows us to use the same hardware
 - We can detect signed overflow by XORing the carry-in and carry-out of the sign bit
- ❖ State elements: 1-bit “flip-flops” and multi-bit “registers”
 - Can be initialized with “reset”
 - Used to store data and control the flow of information between stages of combinational logic
 - Triggered by rising edge of clock signal
- ❖ State in Verilog implemented with `always_ff` blocks
 - Clock indicated through sensitivity list `@(posedge clock)`
 - Non-blocking assignment with `<=`