

Intro to Digital Design

L5: Finite State Machines

Instructor: Naomi Alterman

Teaching Assistants:

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Aarjav Jain

Packard Stephenson

Administrivia

- ❖ Quiz 1 today, grades out Friday
 - Both the quiz and solutions will be added to the question bank on the course website

- ❖ Lab 5 – Verilog implementation of FSMs
 - Step up in difficulty from Labs 1-4 (worth 100 points)
 - Bonus points for minimal logic
 - Simplification through *design* (Verilog does the rest)


Outline

- ❖ **Sequential Logic in Verilog (wrap-up)**
- ❖ Finite State Machines
- ❖ FSMs in Verilog

Reminder: Flip Flops

- ❖ A single bit of memory
- ❖ Copy d to q on the rising edge of the clock signal
 
```
module DFF (q, d, clk);  
    output logic q; // q is state-holding  
    input  logic d, reset, clk;  
  
    always_ff @(posedge clk) begin  
        q <= d;  
    end  
  
endmodule
```



Verilog: Simulated Clock, three ways

- ❖ In our testbenches we need to generate a clock signal
 - Use “forever” block to loop testbench code for whole simulation

Explicit Edges:

```
initial begin
  clk = 0;
  forever begin
    #50 clk = 1;
    #50 clk = 0;
  end
end
```

Toggle:

```
initial begin
  clk = 0;
  forever begin
    #50 clk = ~clk;
  end
end
```

Parameterized clock period:

```
parameter period = 100;
initial begin
  clk = 0;
  forever begin
    #(period/2) clk = ~clk;
  end
end
```

Verilog Testbench with Clock

```
module D_FF_testbench;
  logic CLK, reset, d;
  logic q;

  parameter PERIOD = 100;

  D_FF dut (.q, .d, .reset, .CLK); // Instantiate the D_FF


  initial CLK = 0; // Set up clock
  forever #(PERIOD/2) CLK = ~CLK;

  initial begin // Set up signals
    d <= 0; reset <= 1;
    @(posedge CLK); reset <= 0;
    @(posedge CLK); d <= 1;
    @(posedge CLK); d <= 0;
    @(posedge CLK); #(PERIOD/4) d <= 1;
    @(posedge CLK);
    $stop(); // end the simulation
  end
endmodule
```

Simulation Timing Controls

- ❖ Delay: `#<time>`
 - Delays by a specific amount of simulation time
 - Can do calculations in `<time>`
 - Examples: `#(PERIOD/4)`, `#50`
- ❖ Edge-sensitive: `@(<pos/negedge> signal)`
 - Delays next statement until specified transition on signal
 - Example: `@(posedge CLK)`
- ❖ Level-sensitive Event: `wait(<expression>)`
 - Delays next statement until `<expression>` evaluates to TRUE
 - Example: `wait(enable == 1)`

ModelSim Waveforms

 


```
initial begin
    d <= 0; reset <= 1;
    @(posedge CLK);      reset <= 0;
    @(posedge CLK); d <= 1;
    @(posedge CLK); d <= 0;
    @(posedge CLK); #(PERIOD/4) d <= 1;
    @(posedge CLK);
    $stop();
end
```

Outline

- ❖ Sequential Logic in Verilog
- ❖ **Finite State Machines**
- ❖ FSMs in Verilog

Finite State Machines (FSMs)

- ❖ A convenient way to conceptualize computation over time
 - Function can be represented with a *state transition diagram*
 - The state represents “what step we’re at” in a procedure
 - The transitions represent time advancing (in units of clock cycles)
 - You’ve seen these before in CSE311
- ❖ **New for CSE369:** Implement FSMs in hardware as synchronous digital systems
 - Flip-flops/registers hold “state”
 - Controller (state update, I/O) implemented in combinational logic

 


State Diagrams

- ❖ Our digital logic state diagrams are defined by:
 - A set of *states* S (circles)
 - A *transition function* that maps from the current input and current state to the output and the next state (arrows between states)
 - An *initial state* s_0 (only arrow not between states)
- ❖ State transitions are controlled by the clock:
 - On each clock cycle the machine checks the inputs and generates a new state (could be same) and new output
- ❖ **Note:** We cover Mealy machines here; Moore machines put outputs on states, not transitions

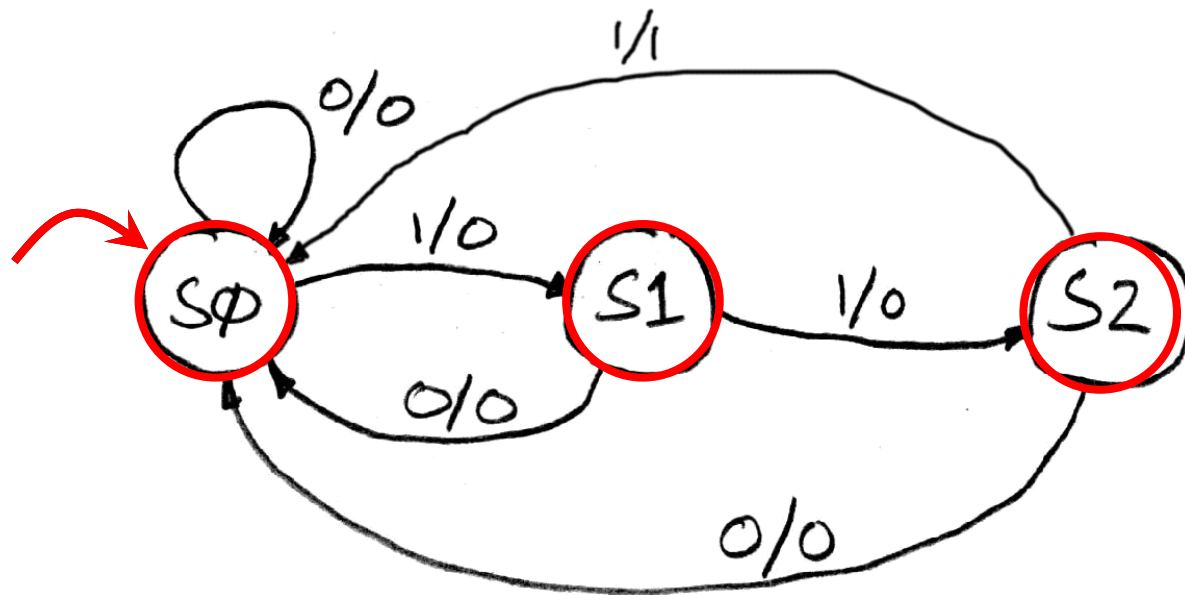Example: Buggy 3 Ones FSM


- ❖ FSM to detect 3 consecutive 1's in the Input




States: S0, S1, S2

Initial State: S0

 Transition label format:
"input bits/output bits"




State diagrams, historical example!

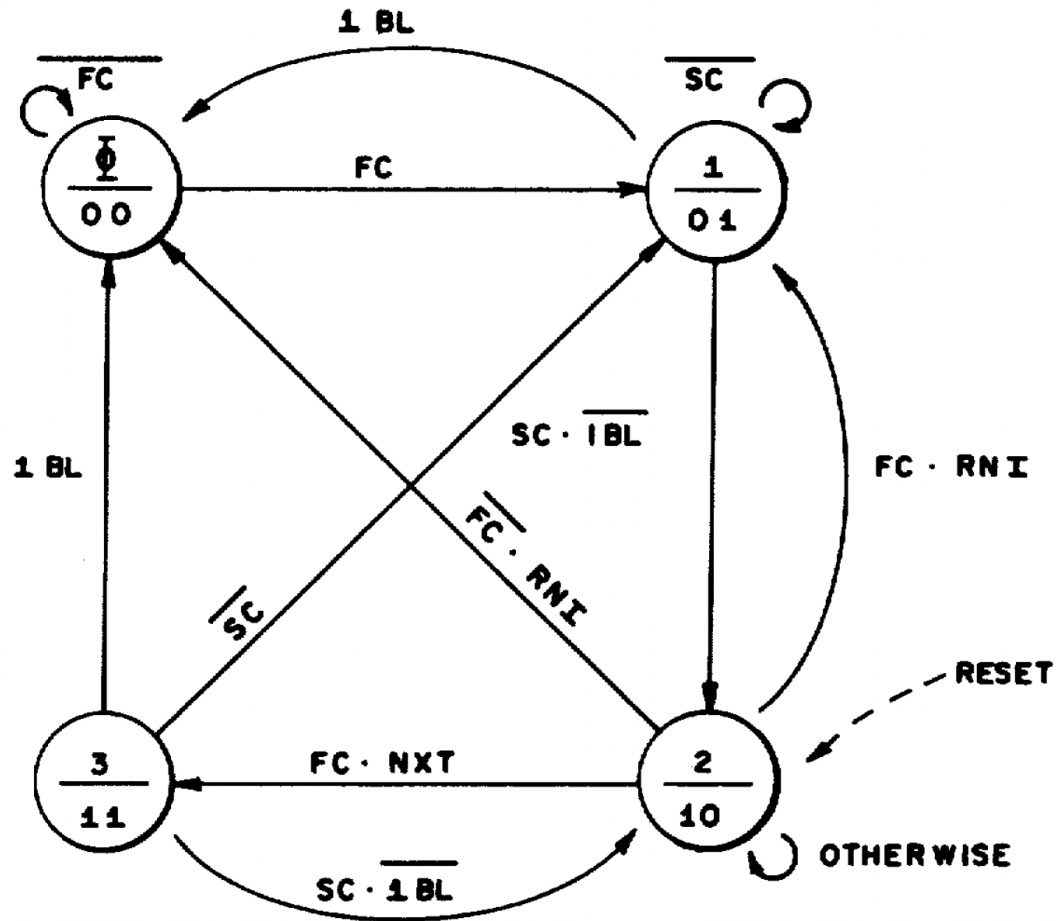

- ❖ The first x86 processor (the Intel 8086) used this state machine to know when to fetch instruction bytes from memory
- ❖ This diagram was submitted as a part of Intel's patent
- ❖ Note, this is a Moore machine (outputs on states)


Hardware Implementation of FSM

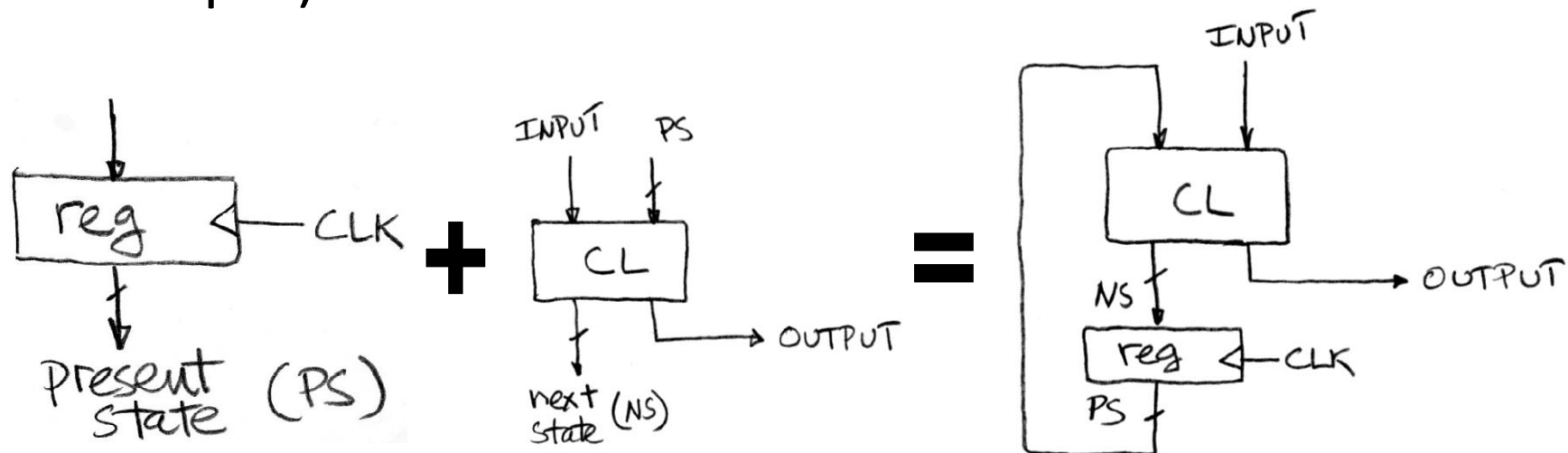- ❖ Register holds a representation of the FSM's state
 - Must assign a *unique* bit pattern for each state
 - Output is *present/current state* (PS/CS)
 - Input is *next state* (NS)
- ❖ Combinational Logic implements transition function (state transitions + output)




FSM: Combinational Logic

 - ❖ Read off transitions into Truth Table!
 - **Inputs:** Present State (PS) and Input (In)
 - **Outputs:** Next State (NS) and Output (Out)






PS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

 

- ❖ Implement logic for *EACH* output (2 for NS, 1 for Out)

FSM: Logic Simplification

PS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1
11	0	XX	X
11	1	XX	X

   

State Diagram Properties

- ❖ For S states, how many state bits do I use?
- ❖ For I inputs, what is the *maximum* number of transition arrows on the state diagram?
 - Can sometimes combine transition arrows
 - Can sometimes omit transitions (don't cares)
- ❖ For s state bits and I inputs, how big is the truth table?

Outline

- ❖ Sequential Logic in Verilog (wrap-up)
- ❖ Finite State Machines
- ❖ **FSM Design Example**


FSM Design Process

- 1) Understand the problem
- 2) Draw the state diagram and a block diagram for any dependent combinational logic
- 3) Use state diagram to produce truth table
- 4) Use truth table to implement combinational logic

Vending Machine Example

❖ Vending machine description/behavior:

 - Single coin slot for dimes and nickels
- Releases gumball after ≥ 10 cents deposited
- Gives no change



❖ State Diagram:

Vending Machine State Table


PS	N	D	NS	Open
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

PS,N

D	00	01	11	10
0				
1				

PS,N


D	00	01	11	10
0				
1				

 

Vending Machine Implementation


- ❖ $Open = D + PS \cdot N$
- ❖ $NS = \overline{PS} \cdot N + PS \cdot \overline{N} \cdot \overline{D}$

Open 

 

Vending Machine Implementation

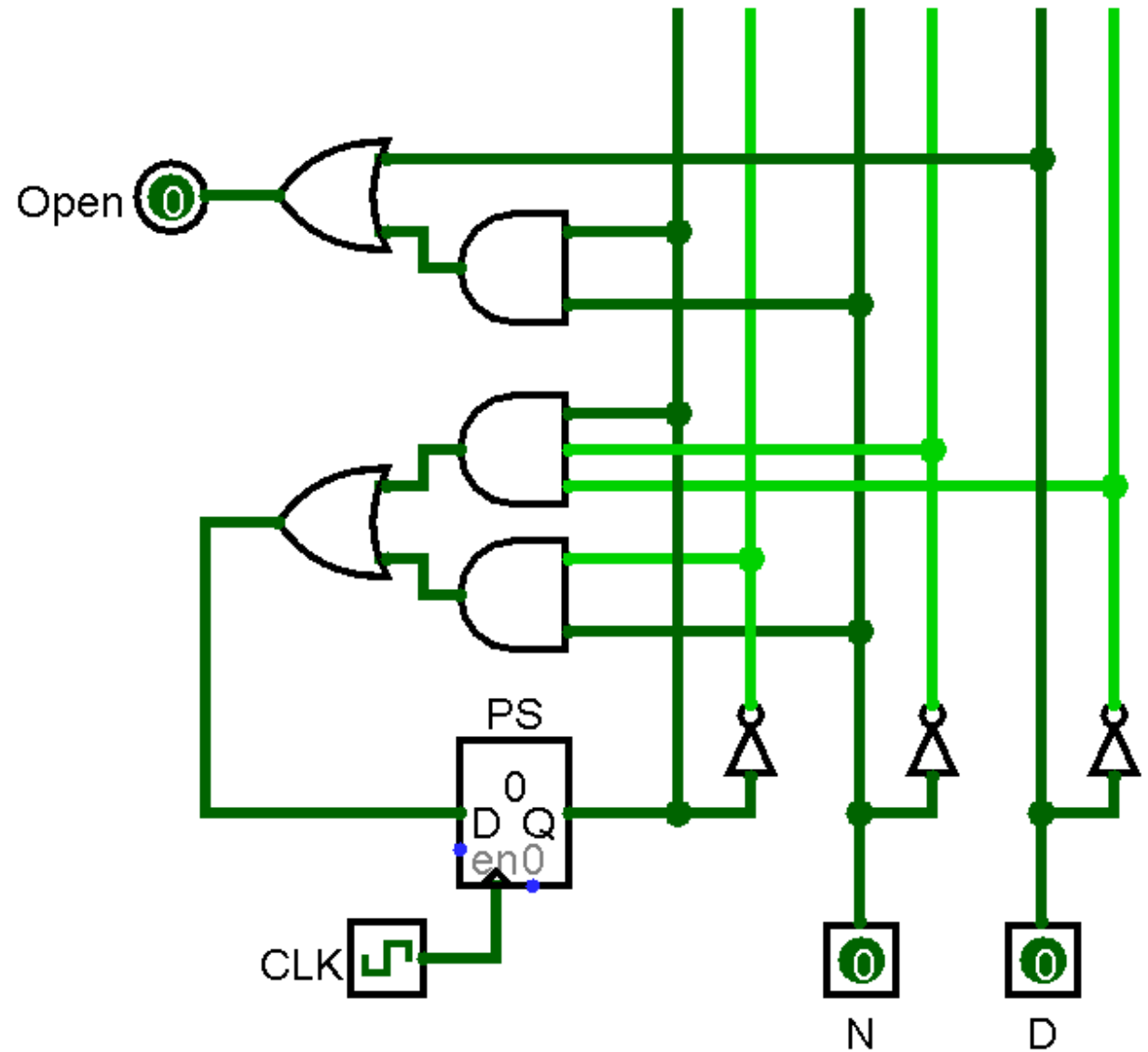- ❖ $Open = D + PS \cdot N$
- ❖ $NS = \overline{PS} \cdot N + PS \cdot \overline{N} \cdot \overline{D}$



FSMs in Verilog (1/3) : Declarations

- ❖ Let's examine the components of the Verilog FSM example module on the next few slides

```
module vendingMachineFSM (clk, reset, n, d, open);  
  input logic clk, reset, n, d;  
  output logic open;  
  
  // State Encodings and variables  
  // ps = Present State, ns = Next State  
  enum logic {C0 = 1'b0, C5 = 1'b1} ps, ns;  
  
  ...
```

FSMs in Verilog (2/3) : Combinational Logic

```
...

// Next State Logic
always_comb
  case (ps)
    C0: if (n & ~d) ns = C5;
        else          ns = C0;
    C5: if (n | d) ns = C0;
        else          ns = C5;
  endcase

// Output Logic - could have been in "always" block
// or part of Next State Logic.
assign open = ((ps == C0) & d) | ((ps == C5) & (n | d)) ;

...
```

FSMs in Verilog (3/3) : State

```
...  
  
// Sequential Logic (DFFs)  
always_ff @(posedge clk)  
    if (reset)  
        ps <= C0;  
    else  
        ps <= ns;  
  
endmodule
```


FSM Testbench (1/2)

```
module vendingMachineFSM_tb();  
  logic clk, reset, n, d;  
  logic open;  
  
  vendingMachineFSM dut (.clk, .reset, .n, .d, .open);  
  
  // Set up the clock  
  parameter CLOCK_PERIOD=100;  
  
  initial begin  
    clk <= 0;  
    forever #(CLOCK_PERIOD/2) clk <= ~clk;  
  end  
  
  ...
```

FSM Testbench (2/2)

```
// Set up the inputs to the design (each line is a clock cycle)
initial begin
    reset <= 1; n <= 0; d <= 0; @(posedge clk);
        reset <= 0; @(posedge clk);
            @(posedge clk);
            @(posedge clk);
                d <= 1; @(posedge clk);
                d <= 0; @(posedge clk);
                    n <= 1; @(posedge clk);
                    n <= 0; @(posedge clk);
                        n <= 1; @(posedge clk);
                            @(posedge clk);
                                n <= 0; d<=1; @(posedge clk);
                                    d<=0; @(posedge clk);
                                        $stop; // End the simulation
end
```

Testbench Waveforms

 

- ❖ What is the min # of clock cycles to *completely* test this FSM? 🤔

