

Intro to Digital Design

L6: Synchronous Timing Constraints

Instructor: Naomi Alterman

Teaching Assistants:

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Aarjav Jain

Packard Stephenson

Administrivia

❖ Lab 6 out later today - Tug of War game

★ *Bigger* step up in difficulty from Lab 5

- Putting together complex system built of multiple FSMs – interconnections!
- Bonus points for smaller resource usage

Diagrams!
Start earlier



Outline

- ❖ **Synchronous Timing Constraints**

Reminder: Flip Flops

- ❖ A single bit of memory
- ❖ Copy d to q on the rising edge of the clock signal
  
```
module DFF (q, d, clk);  
    output logic q; // q is state-holding  
    input  logic d, reset, clk;  
  
    always_ff @(posedge clk) begin  
        q <= d;  
    end  
  
endmodule
```




Flip-Flop Timing Terminology (1/2)

- ❖ Camera Analogy: motion blur in photos
 - *Don't move* while camera shutter is opening
 - *Don't move* while camera shutter is closing
 - *Check for blurriness* once image appears on the display



Flip flop
sampling
its input

 


Flip-Flop Timing Terminology (2/2)





❖ Now applied to sequential logic elements:

 - ➔ **Setup Time:** how long the input must be stable *before* the CLK trigger for proper input read
- ➔ **Hold Time:** how long the input must be stable *after* the CLK trigger for proper input read
- **"CLK-to-Q" Delay:** how long it takes the output to change, measured from the CLK trigger





Flip-Flop Timing Behavior

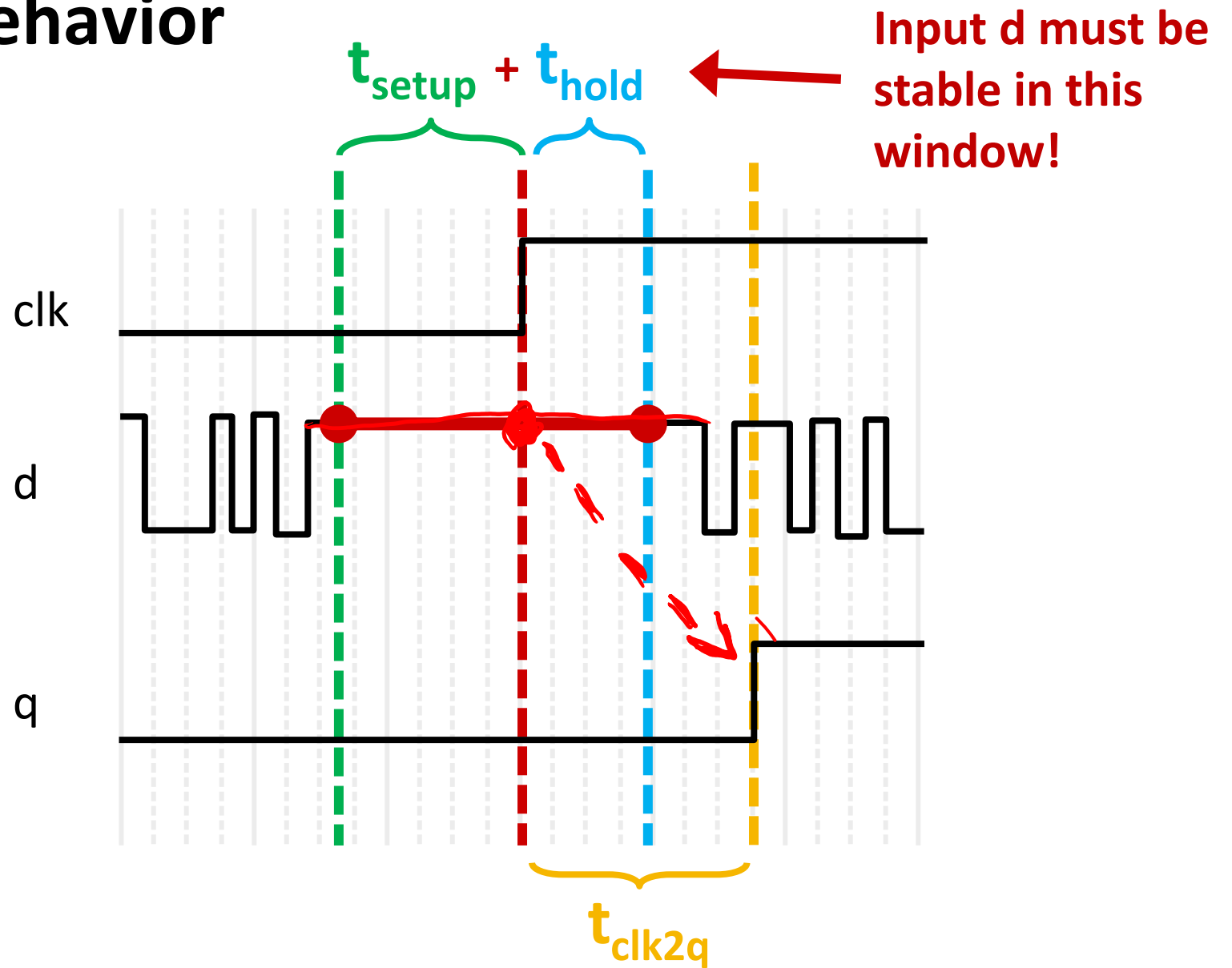 


Stopwatch: timing analysis

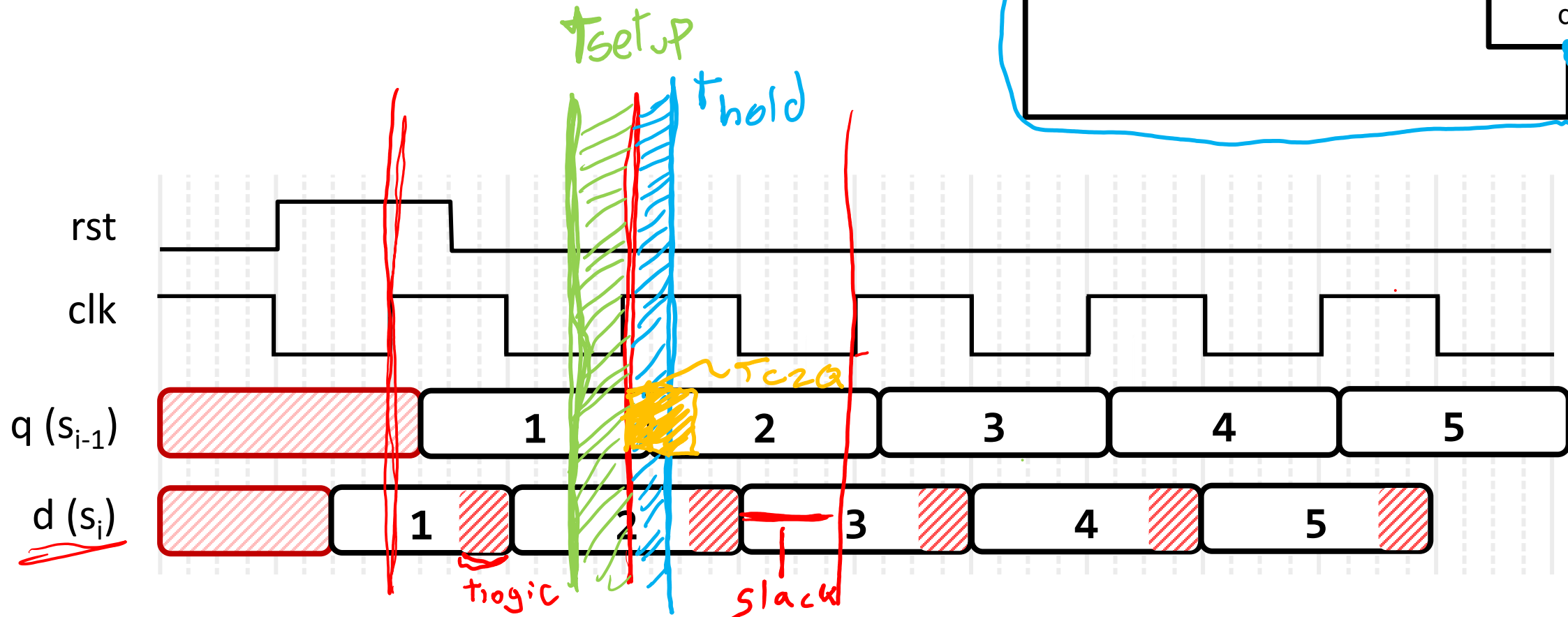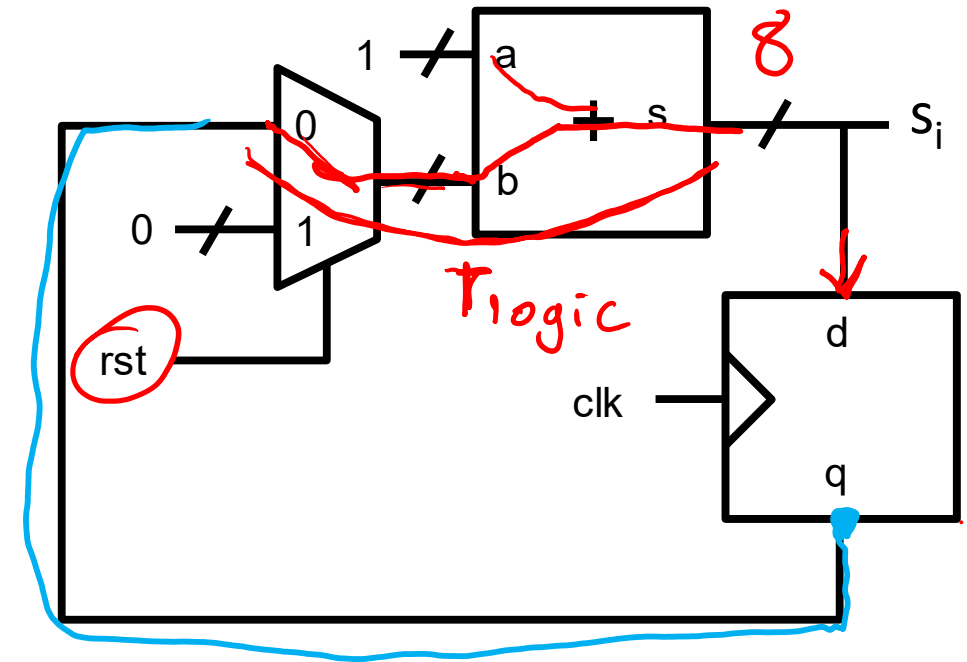- As bits ripple through adder, S_i is temporarily wrong!
- BUT! Register always captures correct value
- In good circuits, signal stays constant around the rising edge of CLK




Model for Synchronous Digital Systems

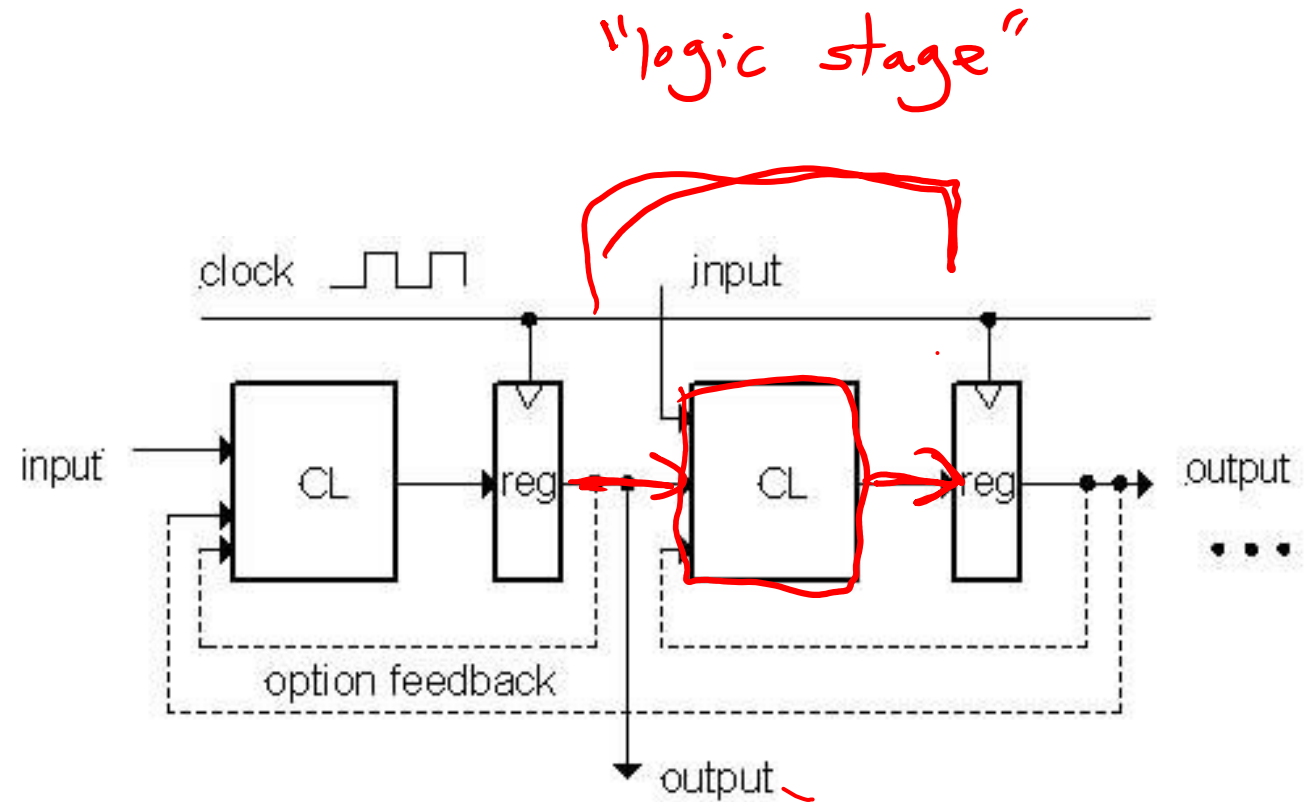
- ❖ Combinational logic blocks separated by registers
 - Clock signal connects only to sequential logic elements
 - Feedback is optional depending on application
- ❖ How do we know if things are going to break?!



Minimum and Maximum Delay

 

Race around the clock

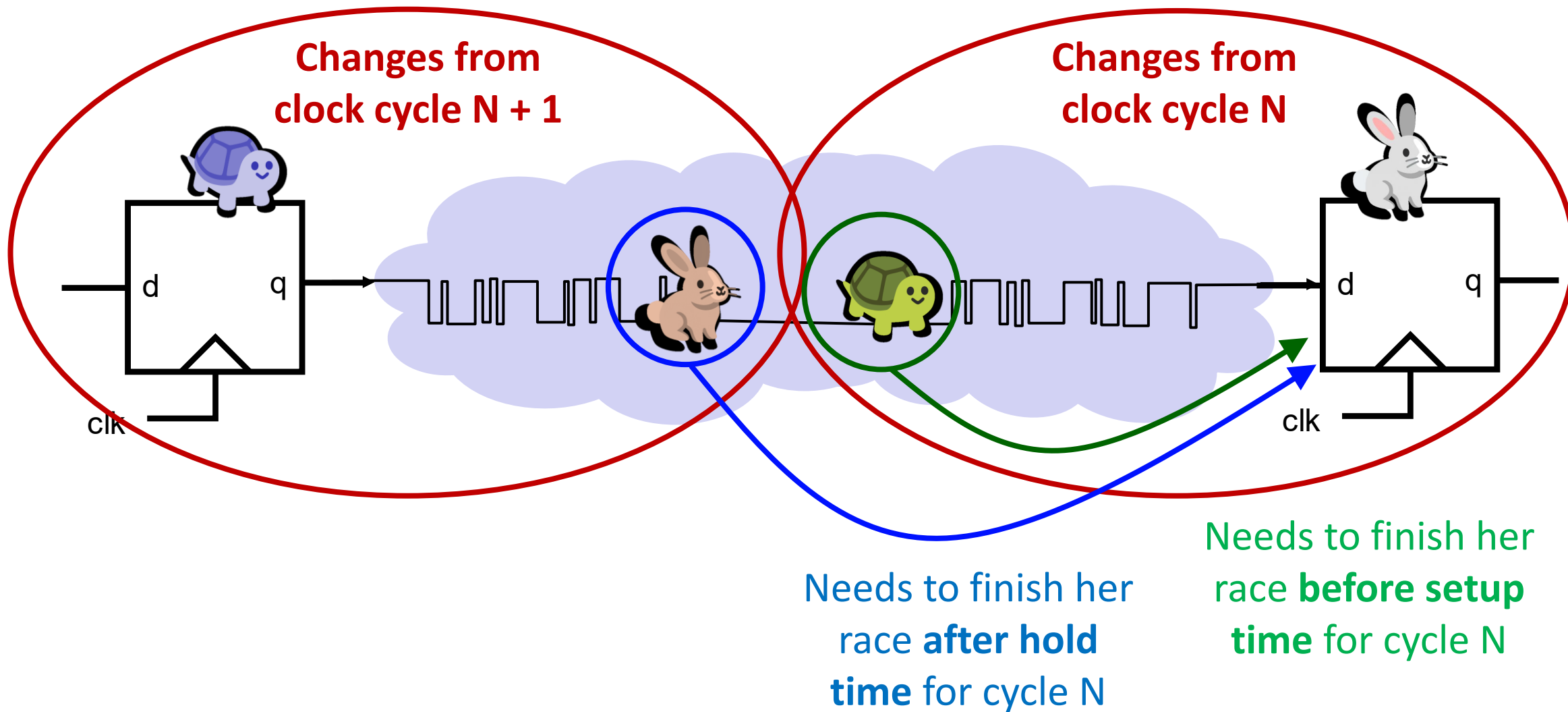


Timing equations

❖ Within a given clock period (t_{period}), the short paths 🐰 shouldn't violate hold time (t_{hold}) and the long paths 🐢 shouldn't violate setup time (t_{setup})

❖ Let $t_{input,i}$ be the time it takes for the input of a register to change for the i^{th} time in a single clock cycle, measured from the CLK trigger:

 
- ② $t_{hold} \leq t_{input,i} \leq t_{period} - t_{setup}$ for all i
- Two separate constraints! ①





Minimum Delay

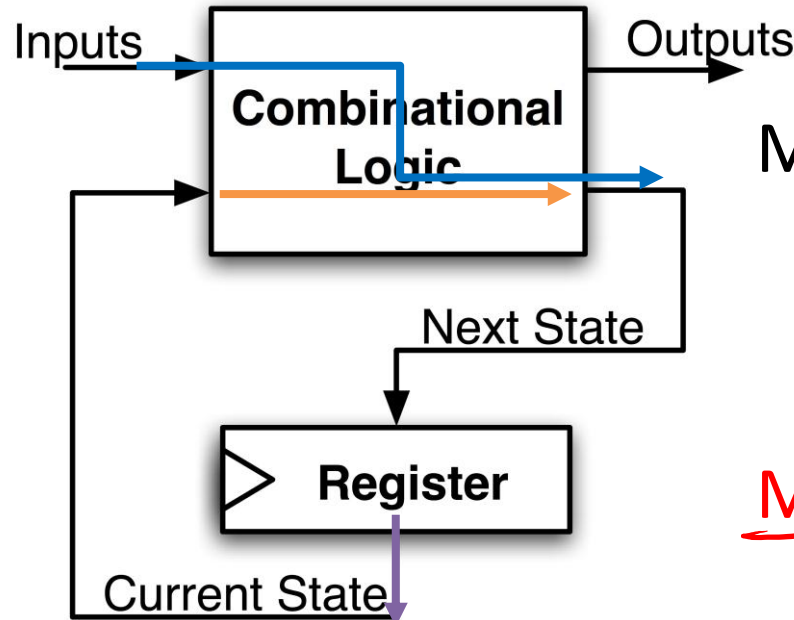- ❖ If shortest path to register input is too short, might violate hold time constraint
 - Input could change before state is “locked in”
 - Particularly problematic with *asynchronous* signals



"worst case"


$$\text{Min Delay} = \min(\text{CLK-to-Q Delay} + \text{Min CL Delay}, \text{Min CL Delay})$$

Min Delay ≥ Hold Time



Maximum Clock Frequency

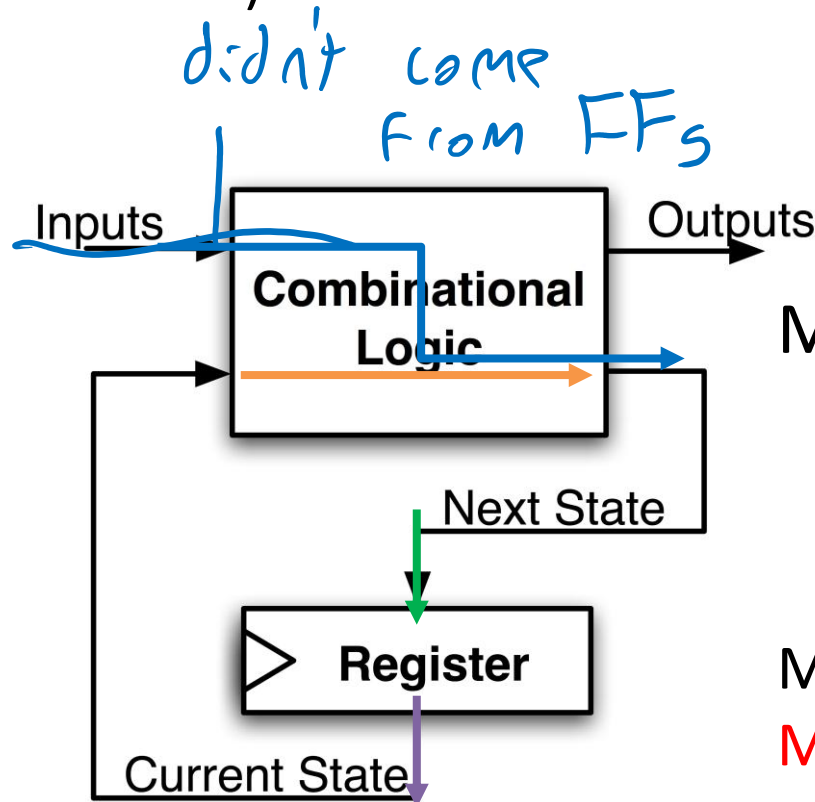- ❖ What is the max frequency of this circuit?
 - Limited by how much time needed to get correct Next State to Register (t_{setup} constraint)




$$\text{Max Delay} = \max(\text{CLK-to-Q Delay} + \text{Max CL Delay}, \text{Max CL Delay})$$

$$\text{Min Period} = \text{Max Delay} + \text{Setup Time}$$
$$\text{Max Freq} = 1/\text{Min Period}$$

The Critical Path

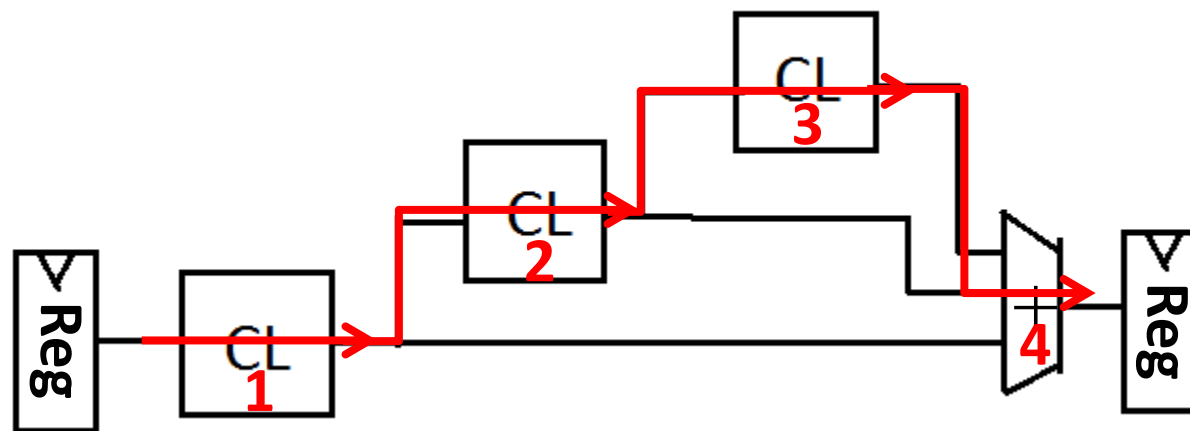- ❖ The *critical path* is the longest delay between *any* two registers in a circuit
- ❖ The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register




Critical Path =

CLK-to-Q Delay
+ CL Delay 1
+ CL Delay 2
+ CL Delay 3
+ Adder Delay
+ Setup Time

Well, what can we do then?

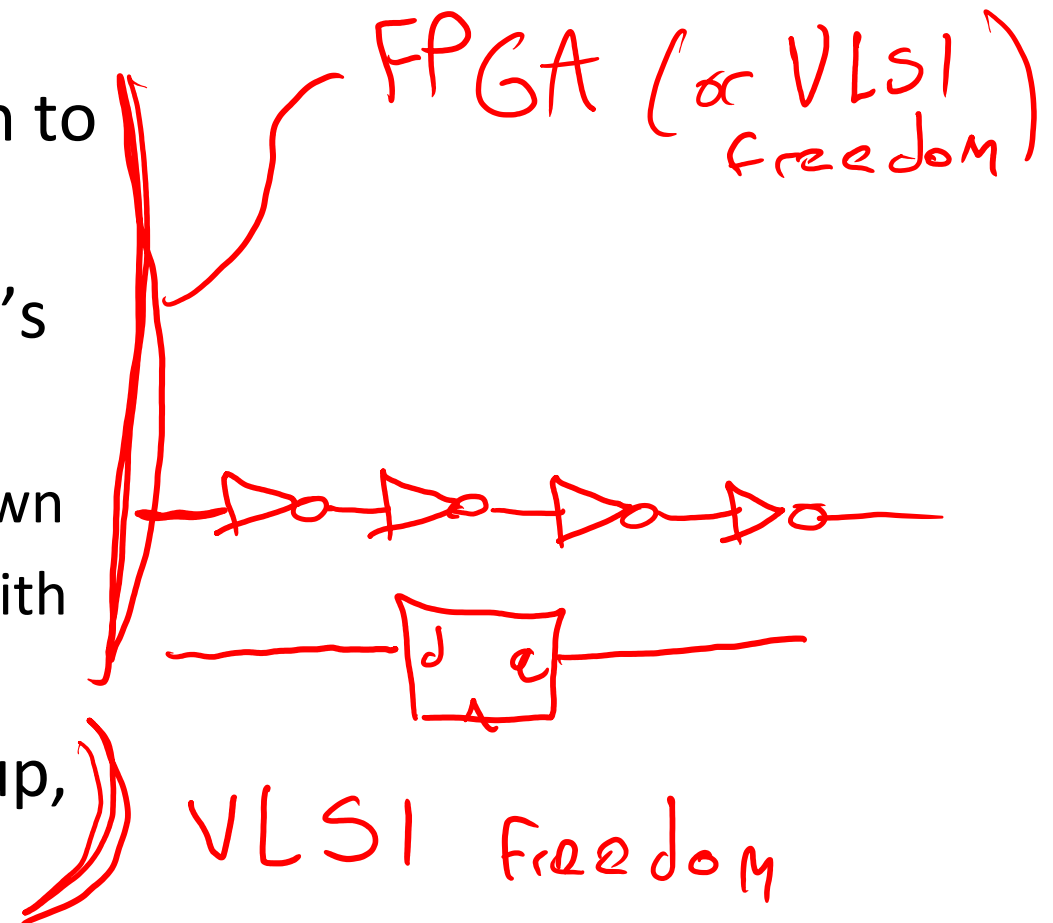- ❖ Choose a **clock period** that's long enough to allow for the critical path
- ❖ Design our **combinational logic** so that it's neither too fast nor too slow
 - Too fast: put **delay elements** in to slow it down
 - Too slow: **split up** the logic into **two stages** with a **register in the middle**
- ❖ Design our **flip-flops** to have smaller setup, hold and clock-to-Q times



1 Practice Question

We want to run our CPU at 1 GHz. Assume:
 $t_{add} = 100$ ps, $t_{mult} = 200$ ps, $t_{setup} = t_{hold} = 50$ ps.
 What is the maximum $t_{clk-to-q}$ we can allow?

$$t_{hold} \leq t_{CLmin}$$


$$\rightarrow t_{CLmax} \leq \frac{1000ps}{1 \times 10^9} - \frac{50ps}{1 \times 10^9}$$

$$t_{clkMax} \leq 950$$

$$t_{cq} + t_{add} + t_{mult} + t_{add} \leq 950$$

$$t_{cq} + 400 \leq 950$$

$$t_{cq} \leq 550ps$$

 


- (A) 550 ps
- (B) 750 ps
- (C) 500 ps
- (D) 700 ps

2 Another practice question

❖ The circuit below has the following timing parameters

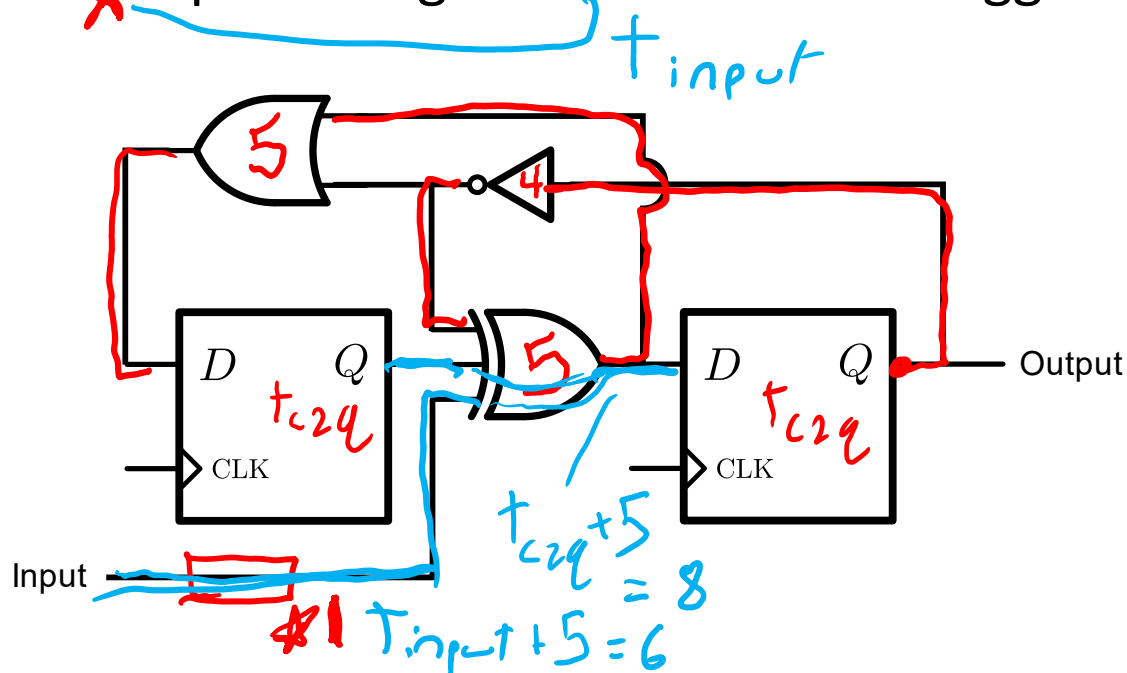- $t_{\text{period}} = 20 \text{ ns}$, $t_{\text{setup}} = 2 \text{ ns}$
- $t_{\text{XOR}} = t_{\text{OR}} = 5 \text{ ns}$, $t_{\text{NOT}} = 4 \text{ ns}$
- ~~*~~ Input changes 1 ns after clock trigger



$$\underline{t_{\text{hold}} \leq t_{\text{CLmin}}}$$

$$t_{\text{CLmax}} \leq t_{\text{period}}^{20} - t_{\text{setup}}^2$$

1. What is the max allowable t_{C2Q} ?

$$t_{\text{max}} \leq 18$$

$$\Downarrow$$

$$t_{\text{C2Q}} + t_{\text{not}} + t_{\text{xor}} + t_{\text{or}} \leq 18$$

$$t_{\text{C2Q}} + 14 \leq 18 \Rightarrow \boxed{t_{\text{C2Q}} \leq 4}$$

2. If $t_{\text{C2Q}} = 3 \text{ ns}$, what is the max allowable t_{hold} ?

$$t_{\text{hold}} \leq t_{\text{input}} + t_{\text{xor}}$$

$$\leq 1 + 5$$



$$\boxed{t_{\text{hold}} \leq 6}$$

Miso Moment



Where Do Timing Constraints Come From?


Edge-triggered
D flip-flop:

 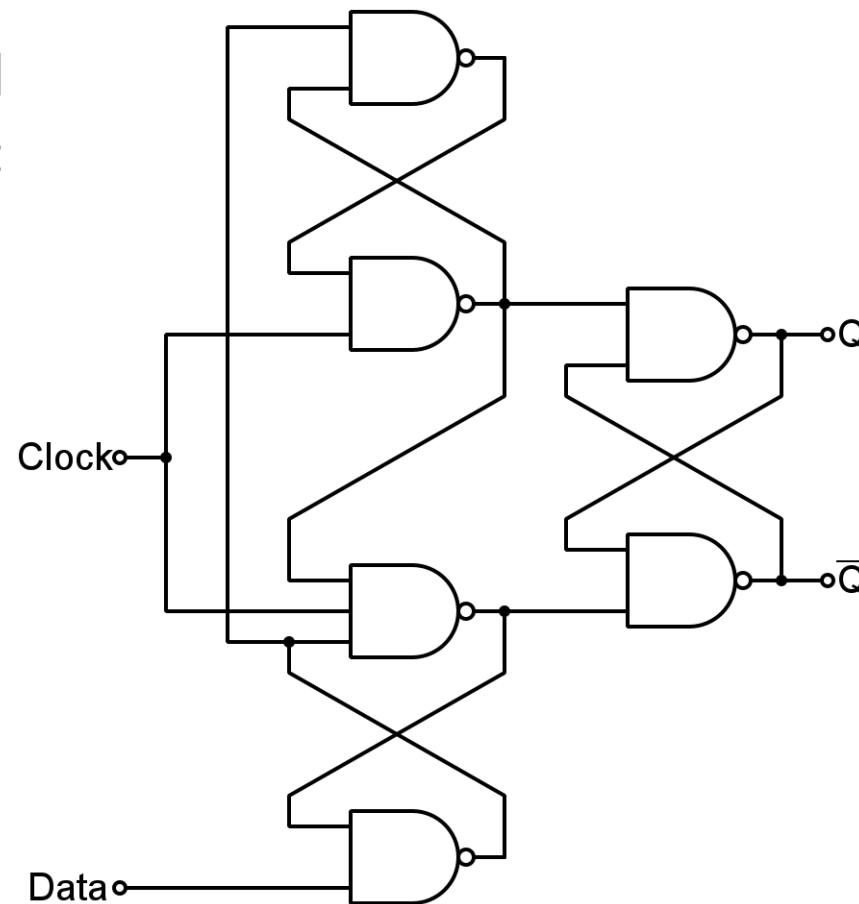

By Nolanjshettle at English Wikipedia, CC BY-SA 3.0,
<https://commons.wikimedia.org/w/index.php?curid=40852354>

DFF feedback loop simulator

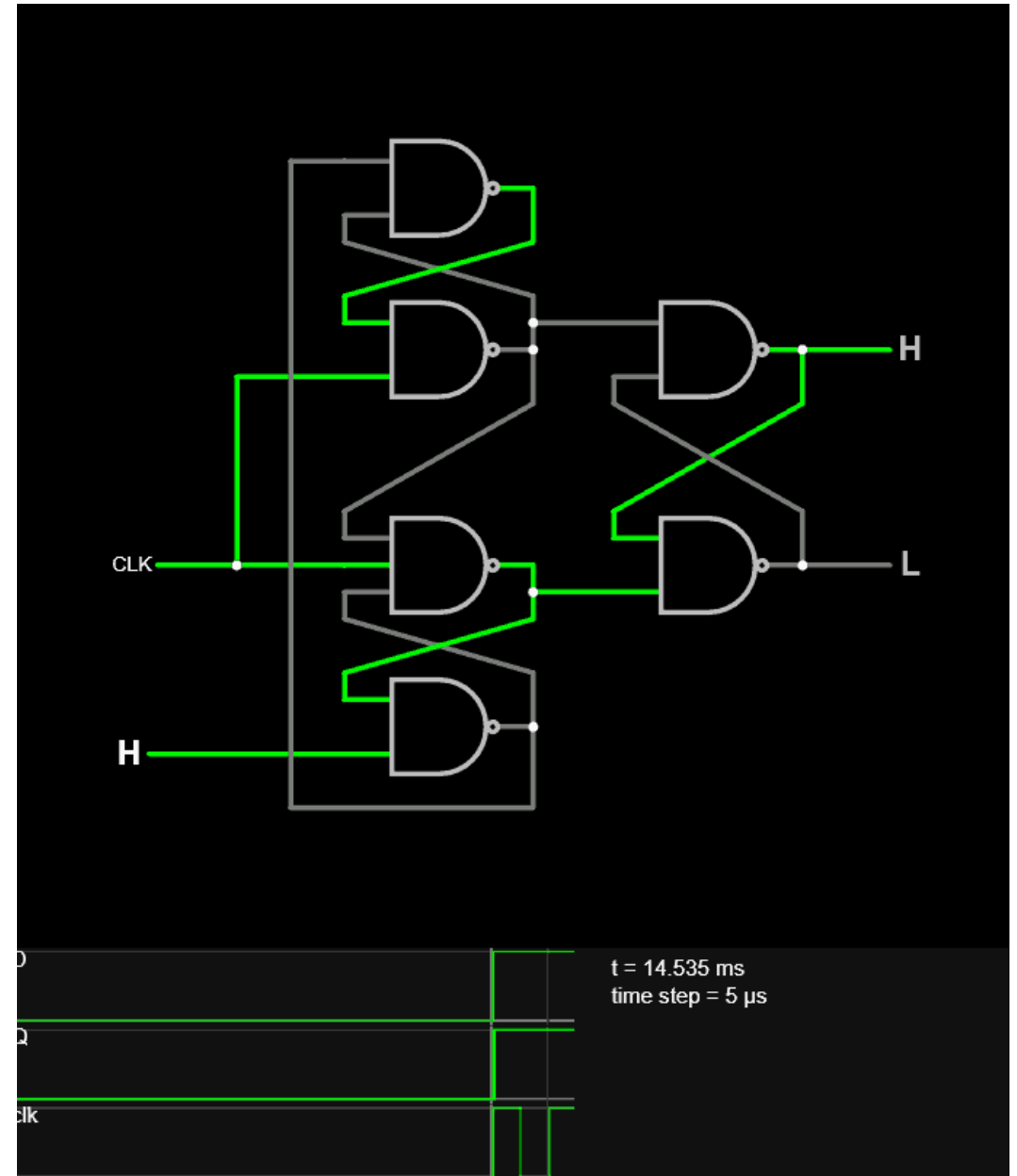- ❖ <https://www.falstad.com/circuit/e-edgedff.html>
- ❖ This is **way** outside the scope of this class. Only worry about this if you're curious




clk →

3 More timing Practice

❖ For an n -bit ripple-carry adder, what is the **earliest** and **latest** time that the output will change after clock edge?

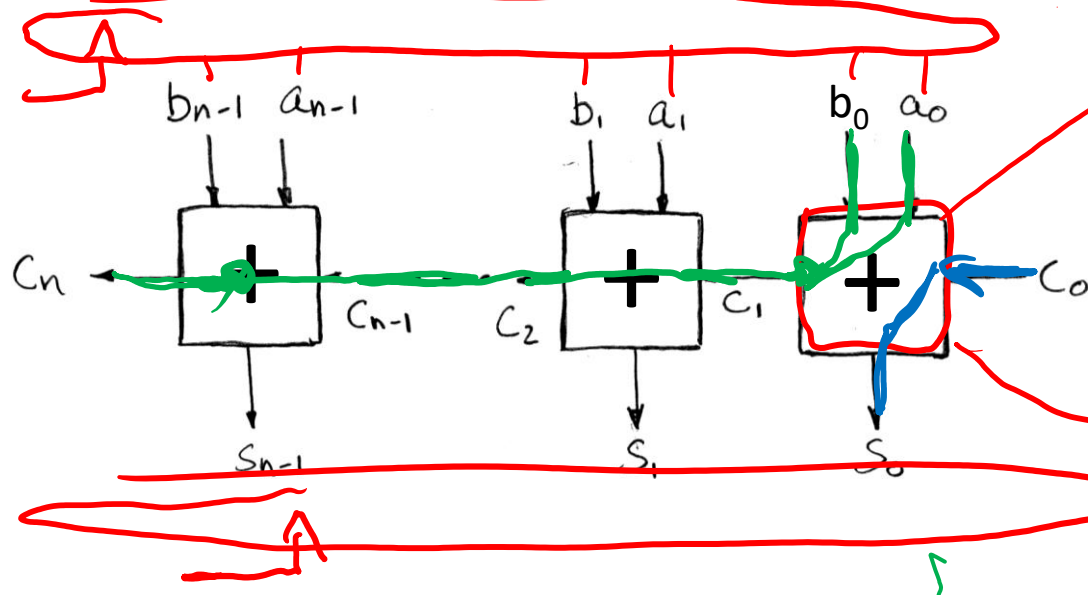- Assume gate delay of 1 ns
- Assume A, B, c_0 straight from register output (eg, change at t_{c20})




$$t_{early} = t_{c2Q} + t_{xor}$$

$$\boxed{= t_{c2Q} + 1}$$

← Not the "right" answer for that bit just the earliest change


$$t_{late} = \underbrace{t_{c2Q} + t_{or} + t_{and} + t_{or}}_{\text{stage 1}} + \underbrace{(N-1)(t_{and} + t_{or})}_{\text{stages 2} \rightarrow N}$$

$$\boxed{= t_{c2Q} + 3 + (N-1)(2)}$$

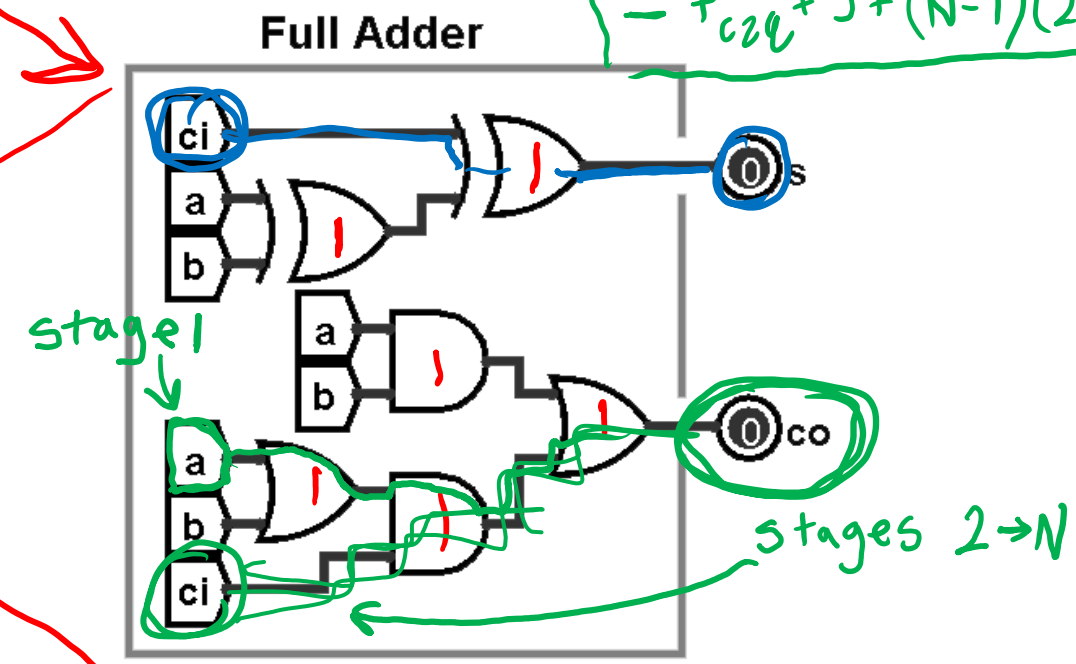

Flip-Flop Realities: External Inputs

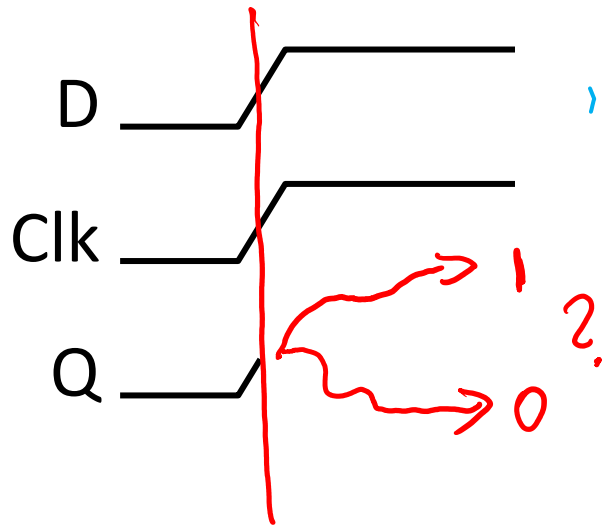
- ❖ External inputs aren't synchronized to the clock
 - If not careful, can violate timing constraints
- ❖ What happens if input changes around clock trigger?




Flip-Flop Realities: Metastability

- ❖ **Metastability** occurs when a digital feedback loop settles into an **unstable equilibrium** storing a **non-binary** voltage
 - Can last for a potentially unbounded amount of time
 - Will randomly decay to a '0' or a '1'....probably

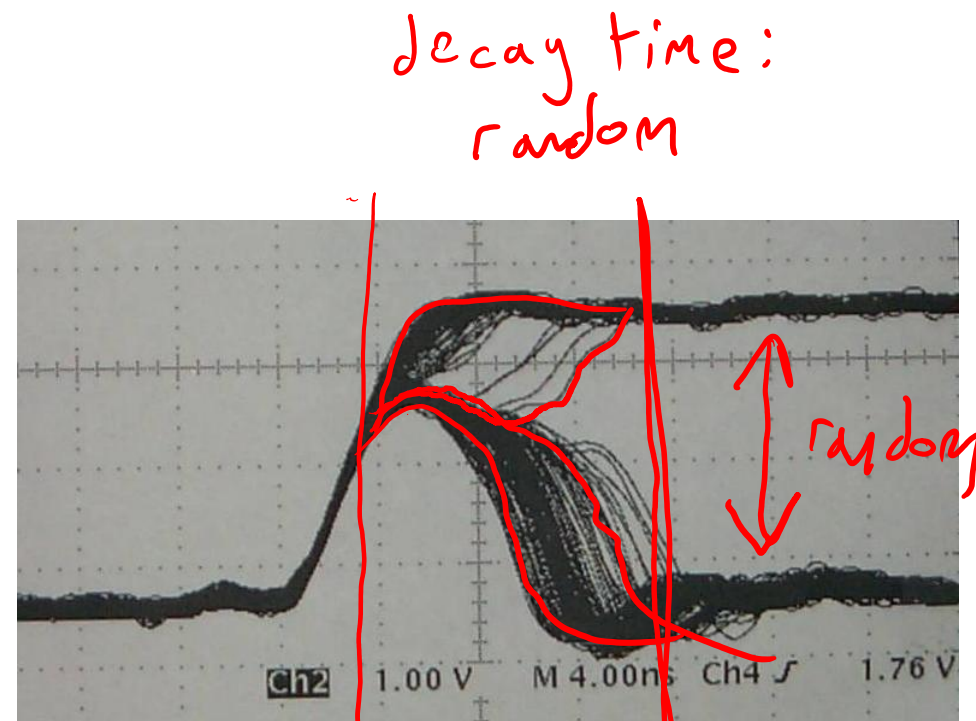- ❖ Flip flops help reject transients
 - Longer chains = higher chance of filtering out all metastability, but longer signal delay



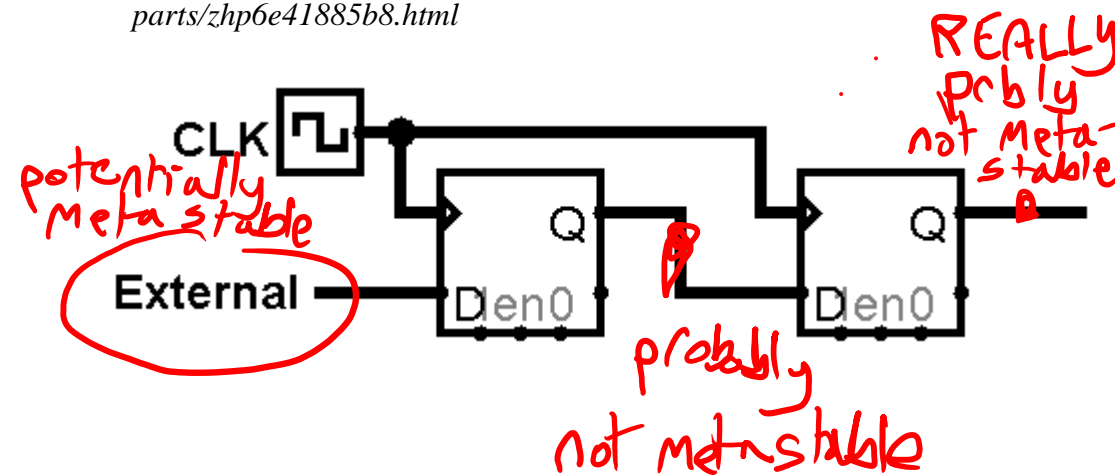
<https://www.cl.cam.ac.uk/teaching/1011/SysOnChip/slides/sp3soc/parts/zhp6e41885b8.html>



>

Flip-Flop Realities: NEVER GATE THE CLOCK!!!

 - ❖ Don't do it
- ❖ Introduces unnecessary **clock skew** into design
- ❖ Makes timing equations *exceptionally* hard to model



Summary of Timing Terms

- ❖ **Clock:** steady square wave that synchronizes system
- ❖ **Flip-flop:** one bit of state that samples every rising edge of CLK (positive edge-triggered)
- ❖ **Register:** several bits of state that samples on rising edge of CLK (positive edge-triggered); often has a RESET
- ❖ **Setup Time:** when input must be stable *before* CLK trigger
- ❖ **Hold Time:** when input must be stable *after* CLK trigger
- ❖ **CLK-to-Q Delay:** how long it takes output to change from CLK trigger

Extra: Unrelated to SDS, just more FSM practice

❖ Recognize the string 101 with the following behavior

- Input: 1 0 0 1 0 1 0 1 1 0 0 1 0
- Output: 0 0 0 0 0 1 0 1 0 0 0 0 0

❖ State diagram to implementation:

