

Intro to Digital Design

L8: Memory, Useful Doodads

Instructor: Naomi Alterman

Teaching Assistants:

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Aarjav Jain

Packard Stephenson

Administrivia

❖ Lab 8 – Project!

- 2 weeks to work on it – **don't wait to start!**

- **Milestone 1:** Check-in during lab demo next week

- Submission **required!** Block diagram of your overall system design and at least one new module in Verilog

- **Milestone 2:** Turn in code + report + bitfile by end of dead week

- **Milestone 3:** Demo your bitfile and turn in your lab kit

- 8 suggested projects, or get your own approved

- Not all are worth the same number of points (“full credit” is 160)
- Think carefully about what you want to tackle

~~(e.g., complex FSM, LED board, multiple “clock speeds”)~~

- Bonus points for adding cool features and early finish

- Up to **20 points for extra features**; up to **10 points for early finish**

Outline

- ❖ **Memory**
 - ROM
 - RAM
- ❖ Useful Doodads

7

Storage Element: Idealized ROM

❖ “Read Only Memory”

- NxM: An array of N M-Bit words
- Address input selects the word driven on the output

➔ Data “burned in” by the manufacturer (or your bitfile) and retained even if power is lost



❖ Difference between a ROM and your seven segment decoder is density

- (and thus underlying circuit implementation)

❖ What can we do with a truly *read-only* memory?

- ➔ Math look-up tables (trig functions) “a lookup table”
- ➔ FSM state transitions “a LUT”
- ➔ Bitmap images and other simple patterns

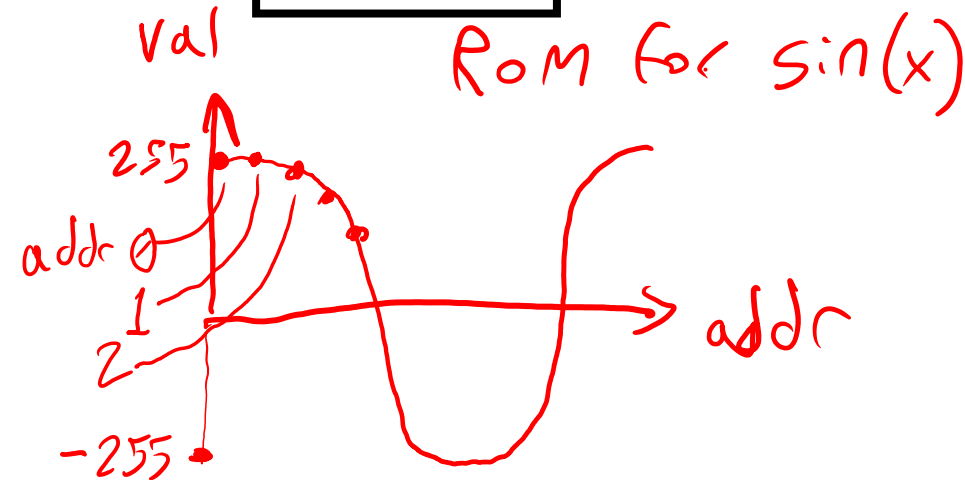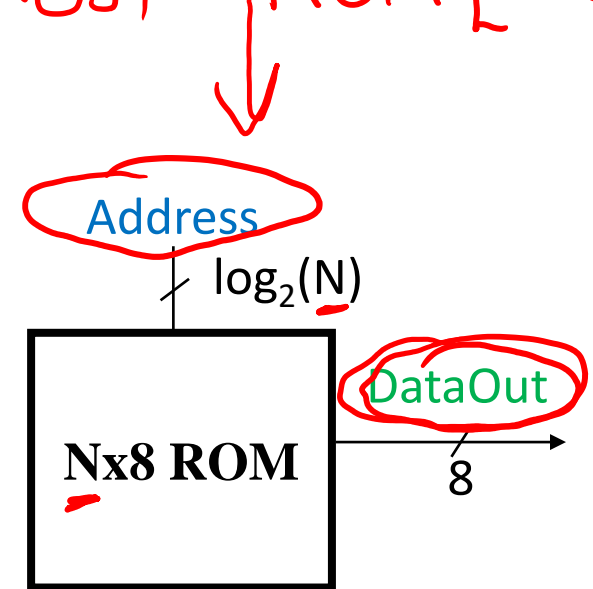
$u8 \text{ DataOut} = \text{ROM}[\text{Address}]$



Storage Element: Idealized RAM

❖ “Random Access Memory”



- Can now write as well as read
 - Data lost on reset or power-off
 - On clock edge, **DataIn** written to memory cell at **Address** if **WriteEnable** = 1
 - **DataOut** is still completely combinational (changes to **Address** immediately change the data output)
-
- ❖ Simplest and most robust implementation: “SRAM” – implemented as an array of flip flops with muxed inputs and outputs
 - ❖ Higher-density but more touchy: “DRAM” – implemented with circuit wizardry

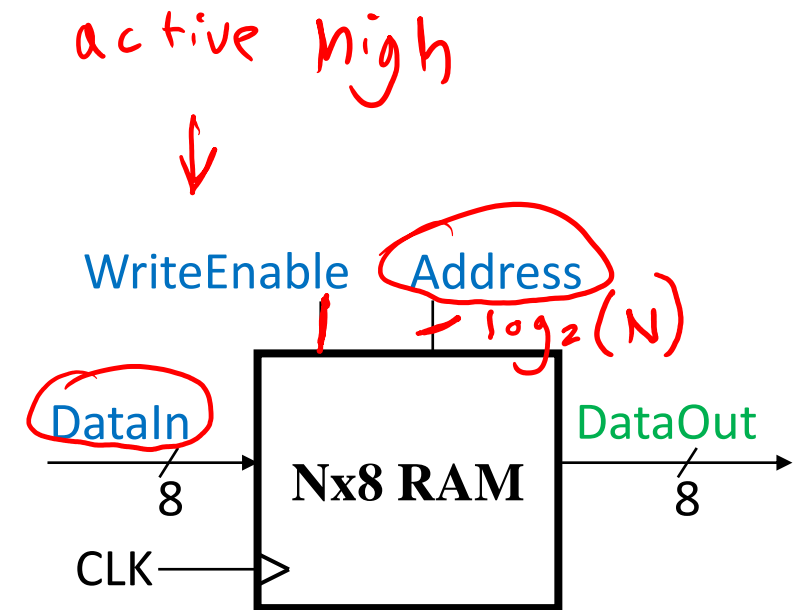

```
if (WriteEn) {  
    RAM[Addr] = DataIn;  
}
```

8x4 SRAM

WriteEnable

 
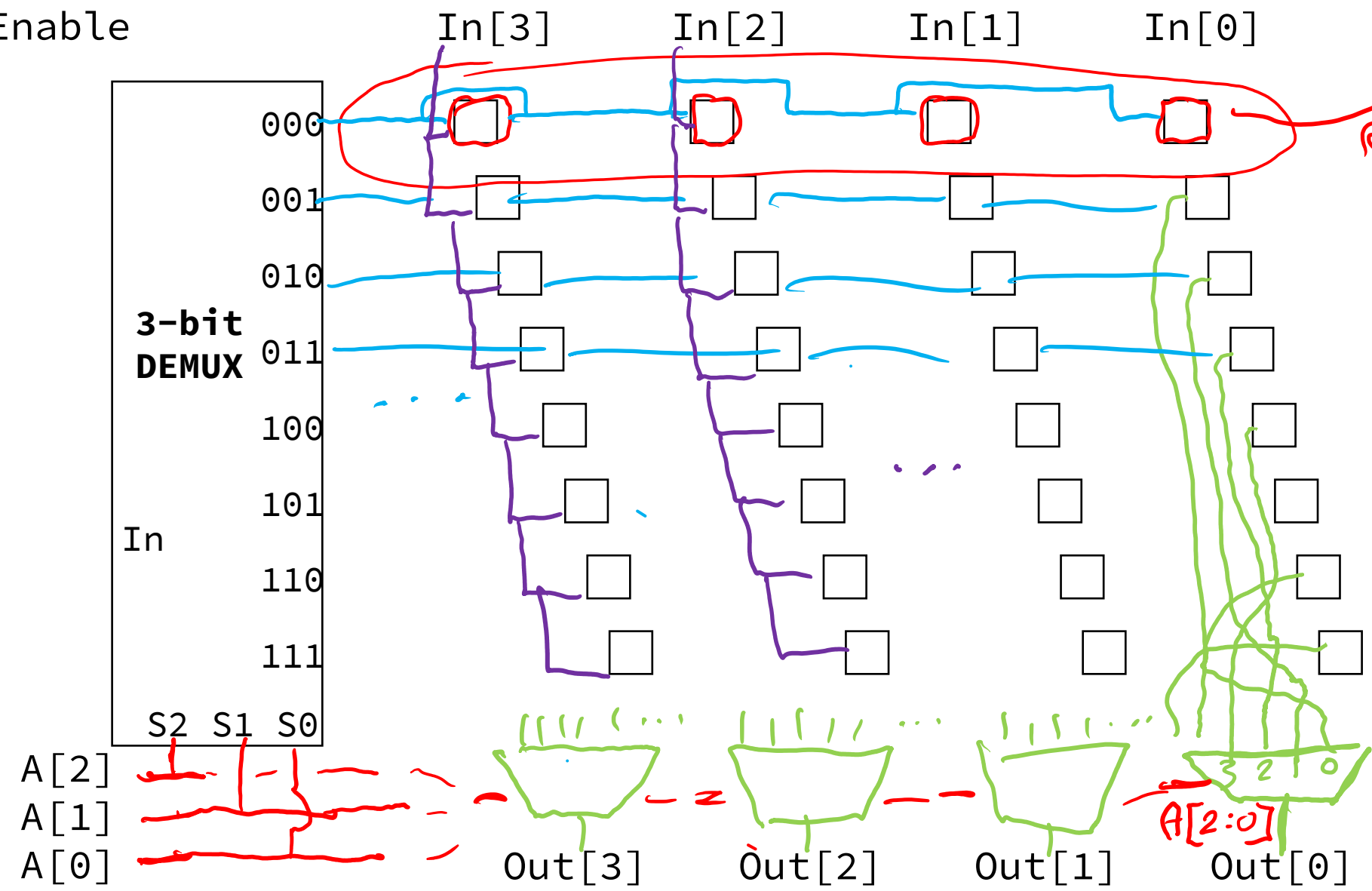


Sneaky Peaky: DRAM

DRAM: 1 cap + 1 transistor


SRAM: 1 flip flop & a mux (~12-30 trans. input)

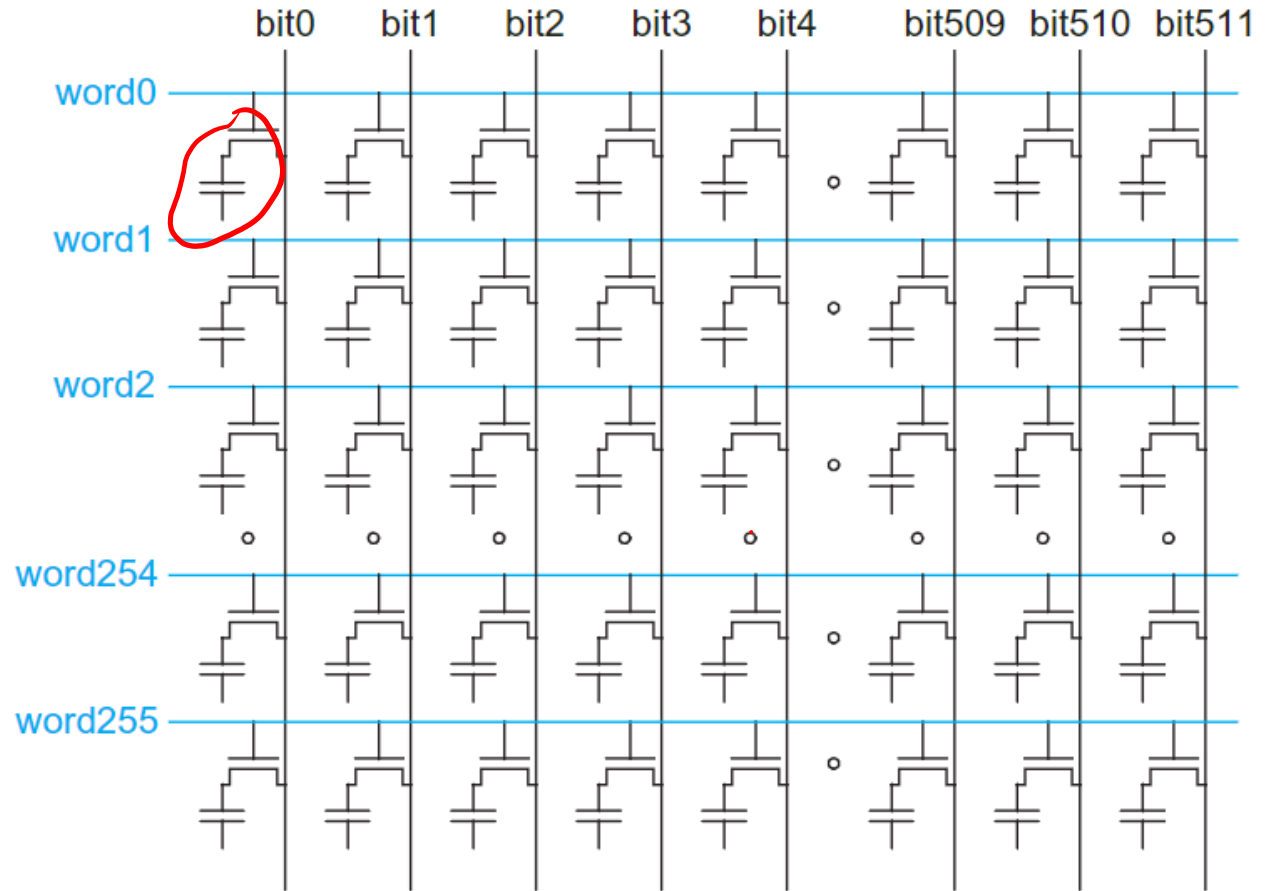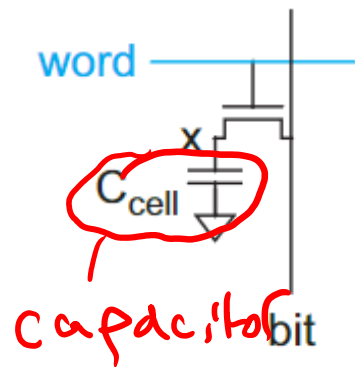- ❖ Highest memory density, but very touchy
- ❖ Bits “decay” over time and need to be refreshed (read and written)
- ❖ One bit cell:



Diagrams from CMOS VLSI Design: A Circuits and Systems Perspective (4th ed) by Weste & Harris

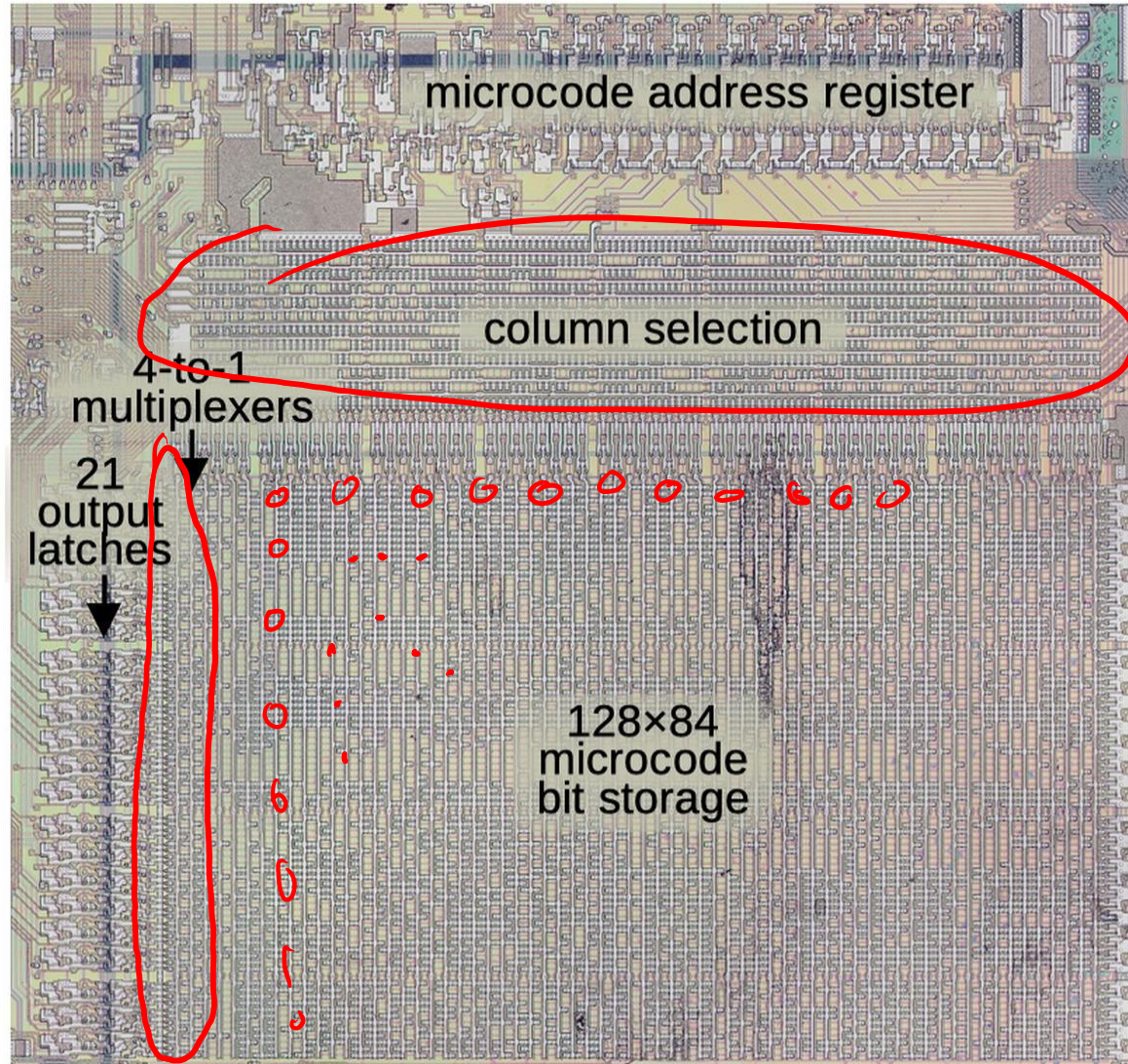Memory IRL: Microcode ROM in the original x86



Outline

- ❖ Memory
- ❖ **Useful Doodads**
 - Comparators
 - Clock domains

Comparators (Multibit)

- ❖ Zero comparator $A == 0$
 - NOR all of A's bits
- ❖ Equality ($A == B$)
 - XNOR corresponding bits of A and B, then AND together
 - Compute $A - B$, then check if it $== 0$
- ❖ Comparator ($A < B$, $A == B$, $A > B$)
 - $A < B$: MSB of $A - B$
 - $A == B$: NOR of all bits of $A - B$
 - $A > B$: NOT of MSB of $A - B$

“Multiple Clocks” Via Enable Signals and Counters

❖ Even with that `clock_divider` module, we **only ever want to run our circuit on one clock if we can help it**

- Logic stages that share a clock are called a clock domain
- Crossing clock domains carelessly is a recipe for metastability

❖ So how can we slow things down?

- Use flip flops with an Enable signal
- Comparator on counter output generates an Enable pulse once every N cycles
- Keeps all logic technically on the same clock domain, while allowing some things to happen “more slowly” than others

