

---

---

# Section 1

— Boolean Algebra Review —


---

---
 
# Meet your TAs!

Derek de Leuw (he/him)

- 4<sup>th</sup> year Computer Engineering student
- Took 369 in Autumn 2024
- 2<sup>nd</sup> time TAing this class, have TAed 333 previously as well



# Meet your TAs!

Isabel Froelich (she/her)

- 4<sup>th</sup> year Computer Engineering student
- Took 369 in Autumn 2024
- 2<sup>nd</sup> time TAing this class, have TAed 390Z and 390T previously
- This is my roommate's cat, Willow, playing a very intense game of bananagrams



# Meet each other!

In groups of 3-5, introduce yourselves:

- Name
- Year
- Favorite class so far
- Why you are taking this class?
- How would you say DE1-SoC?

# Administrivia

- **Pre-course survey:** Due today (4/3, [link](#)).
- **Lab kits:** If you didn't pick up a kit, come to OH ASAP so you can get started on the lab. There are always **LOTS** of hardware and software issues to figure out.
- **Lab 1:** Report due next Wednesday (4/8) @ 2:30 pm, demo during your assigned slot of the same week your lab report is due.
  - Lab demo slots will be assigned on Monday (4/6) via Canvas.

# What to expect from section

- **When:** Every Friday at 1:30pm in CSE2 271
  - Recordings will be made available afterward on Panopto
  - Different TAs each week!
- **What:** SystemVerilog is a tricky language and we don't have much time to talk about it during lectures (only 80 min/week), so we are introducing optional sections focused on it.
- Please come and share your feedback! Let us know if there is anything you would like to focus on!

# 369 Workflow

More on this in Lecture 2

# Quartus



- The Intel Quartus Software is a tool for designing, synthesizing, and programming FPGAs.
- With it, you are able to (1) **write SystemVerilog code**, (2) **synthesize it**, and (3) **program your DE1-SoC board**.
- More information: [Quartus Tutorial](#)

# ModelSim ModelSim

- ModelSim is a simulation and debugging tool for a variety of hardware description languages, including SystemVerilog.
- With it, you are able to run simulations to **verify your code's logical behavior** without endangering your hardware.
  - This is your main tool for **debugging!**
- More information: [ModelSim Usage Guide](#)

1. Write SystemVerilog in

**Quartus**



2. Test


**ModelSim ModelSim.**

3. Fix bugs

4. Synthesize and program the board

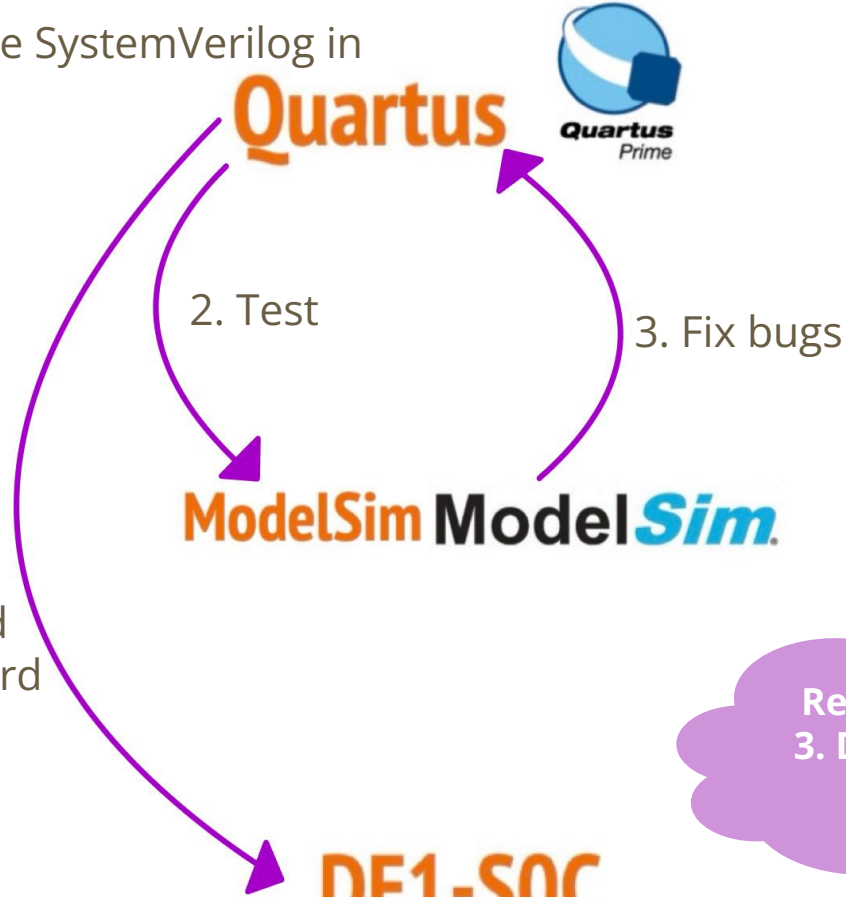**DE1-SOC**


Repeat steps 2 and 3. Do NOT debug on hardware pls



Some details on how FPGAs work will be covered Lecture 9
 
# DE1-SoC Overview

- The DE1-SoC is a development kit built around an FPGA.
  - An FPGA is a large array of logical elements with reprogrammable connections. This means we can use it to build many different kinds of hardware all on the same chip!
  - The kit also contains other functionalities that we will use in our labs.
- More information: [FPGA overview](#)



# Logic Review

# Boolean Algebra


- Represent inputs and outputs as variables
  - Each variable can only take on the value of 0 or 1
- Overbar is NOT: “logical complement”
  - If A is 0, then  $\bar{A}$  is 1 and vice-versa
- Plus (+) is 2-input OR: “logical sum”
- Product ( $\cdot$ ) is 2-input AND: “logical product”
- All other gates and logical expressions can be built from combinations of these
  - e.g.,  $A \text{ XOR } B = A \oplus B = \bar{A}B + B\bar{A}$

# Truth Tables

- Table relating inputs to a combinational logic (CL) circuit to its output
  - Outputs *only* depend on current inputs
  - Use 0/1 instead of low/high voltage
  - Show output for *every* possible combination of inputs (“black box” approach)
  - For  $N$  inputs,  $2^N$  rows required to map all outputs


# Logic Gates

NOT

 


A	Out
0	1
1	0

AND

 


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR

 


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

NAND

 


A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

XOR

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

# Truth Table to Boolean Expression

- Read off of table
  - For 1, write variable name
  - For 0, write complement of variable
- *Sum of Products (SoP)*
  - Take rows with 1's in output column, sum products of inputs
- *Product of Sums (PoS)*
  - Take rows with 0's in output column, product the sum of the complements of the inputs

# Basic Boolean Equivalences

- Identity:  $X + 0 = X$     $X \cdot 1 = X$
- Domination:  $X \cdot 0 = 0$     $X + 1 = 1$
- Idempotent:  $X + X = X$     $X \cdot X = X$
- Negation:  $\bar{\bar{X}} + X = 1$     $\bar{\bar{X}} \cdot X = 0$
- Double Negation:  $\bar{\bar{X}} = X$

# Basic Boolean Laws


- Commutative:  $X + Y = Y + X$                        $X \cdot Y = Y \cdot X$
- Associative:     $X + (Y + Z) = (X + Y) + Z$      $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$
- Distributive:    $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$      $X + YZ = (X + Y) \cdot (X + Z)$

# Boolean Absorption

- $X + XY = X$
- $XY + X\bar{Y} = X$
- $X + \bar{X}Y = X + Y$
- $X(X + Y) = X$
- $(X + Y)(X + \bar{Y}) = X$
- $X(\bar{X} + Y) = XY$


# Exercise 1

 - a) Write out the Boolean Algebra expression for Q for the following circuit.
- b) Simplify the expression for Q.



# Exercise 1 (Solution)

 - a) Write out the Boolean Algebra expression for Q for the following circuit.



# Exercise 1 (Solution)

- b) Simplify the expression for Q.

$$AB + BC(B+C)$$

$$AB + BC + BC$$

$$AB + BC$$

$$B(A + C)$$

# Not All Logic Gates Are Created Equally!

- Can recreate all other gates using only NAND or only NOR gates
  - Called “universal” gates
  - *e.g.* A NAND A =  $\bar{A}$ , B NOR B =  $\bar{B}$
  - DeMorgan’s Law helps us here!

2-Input Gate Type	# of CMOS Transistors
NOT	2
AND	6
OR	6
NAND	4
NOR	4
XOR	8
XNOR	8

# Logic Minimization

- Reduce complexity at gate level
  - Allows us to build smaller and faster hardware
  - Care about # of gates, # of literals (gate inputs), “depth” of gate levels, and types of logic gates


# Logic Minimization

- Reduce complexity at gate level
  - Allows us to build smaller and faster hardware
  - Care about # of gates, # of literals (gate inputs), “depth” of gate levels, and types of logic gates
- Faster hardware?
  - Fewer inputs implies faster gates in some technologies
  - Fan-ins (# of gate inputs) are limited in some technologies
  - Fewer levels of gates implies reduced signal propagation delays
  - # of gates influences manufacturing costs
  - Simpler Boolean expressions means smaller transistor networks, which means smaller circuit delays, which gives us faster hardware
 
# DeMorgan's Law


If you remember one thing from section, it should be this pretty pls!

- In Boolean Algebra, converts between AND-OR and OR-AND expressions
  - $\overline{X+Y} = \bar{X} \cdot \bar{Y}$
  - $\overline{X \cdot Y} = \bar{X} + \bar{Y}$
- At gate level, can convert from AND/OR to NAND/NOR gates
  - “Flip” all input/output bubbles and “switch” gate (Bubble Pushing)



 
## Exercise 2

- Find the simplified Boolean expression for the following diagram:


 
## Exercise 2 (Solution)


- Find the simplified Boolean expression for the following diagram:



$$X = \overline{A + B} + A\overline{B} + \overline{C}D$$
 
## Exercise 2 (Solution)

- Find the simplified Boolean expression for the following diagram:




$$X = \overline{A + B} + A\overline{B} + \overline{C}D$$

$$X = \overline{A}B + A\overline{B} + \overline{C}D$$
 
## Exercise 2 (Solution)

- Find the simplified Boolean expression for the following diagram:




$$X = \overline{A + B} + A\overline{B} + \overline{C}D$$

$$X = \overline{A}B + A\overline{B} + \overline{C}D$$

$$X = \overline{B} + \overline{C}D$$
 
## Exercise 2 (Solution)

- Find the simplified Boolean expression for the following diagram:



$$X = \overline{A + B} + \overline{A\overline{B}} + \overline{\overline{C}D}$$


$$X = \overline{A\overline{B}} + \overline{A\overline{B}} + \overline{\overline{C}D}$$

$$X = \overline{B} + \overline{\overline{C}D}$$

$$X = \overline{B} + \overline{C + D}$$
 
## Exercise 2 (Solution)

- Find the simplified Boolean expression for the following diagram:



$$X = \overline{A + B} + A\bar{B} + \bar{C}\bar{D}$$

$$X = \overline{A}\bar{B} + A\bar{B} + \bar{C}\bar{D}$$

$$X = \bar{B} + \bar{C}\bar{D}$$

$$X = \bar{B} + \overline{C + D}$$


$$\mathbf{X = B(C + D)}$$

## Exercise 3


- Implement the Boolean expression  $B(A + C)$  with the fewest number of a single universal gate. What does your solution look like?
  - Universal gates are NAND and NOR

# Exercise 3 (Solution)


NAND

 


NOR

 

NAND (alternative)

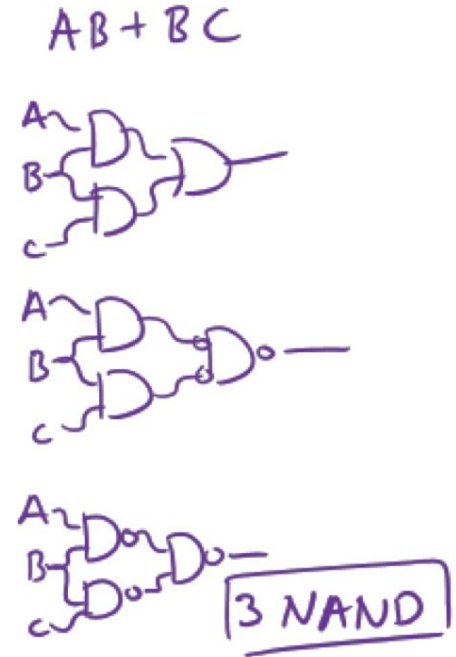

# CL General Form

 

A	B	C	Y
0	0	0	$F(0,0,0)$
0	0	1	$F(0,0,1)$
0	1	0	$F(0,1,0)$
0	1	1	$F(0,1,1)$
1	0	0	$F(1,0,0)$
1	0	1	$F(1,0,1)$
1	1	0	$F(1,1,0)$
1	1	1	$F(1,1,1)$

For  $N$  inputs, function  $F$  maps each row to 0 or 1, so  $2^{(2^N)}$  possible functions.

# Installation Process

# Installing Quartus and ModelSim

- If you wish to skip installation altogether, you can use the lab computers in CSE 003.
- Follow the installation tutorial on the website: [link](#)
  - This class only supports the **Windows** version of Quartus and ModelSim.
  - For **MacOS**, you can use a Windows virtual machine (described in the tutorial).
- Installation tips:
  - All 3 downloaded files need to be in the same directory so that ModelSim and Cyclone V options are available during Quartus installation.
  - Try not to miss the USB Blaster II driver installation option at the end.


# Workflow Demo

Shortened version of the [Quartus Tutorial](#)

# File Organization

- Unzip Lab1\_files\_Q17.zip to get started.
  - Download from the Lab 1&2 specs.
  - Can be unzipped again to start any new project or you can copy an existing project directory.
- Create subdirectories for each lab within a class directory (e.g., CSE369/Lab1).
  - All project SystemVerilog files should be placed in this directory and added to Quartus project.
- Every Verilog module should have a test bench in a *separate* file.
  - Suggested naming scheme: `new_module.sv` and `new_module_tb.sv` for test bench.


# Programming Workflow (Quartus)


- Open the Quartus project via the `.qpf` file in the project directory (double-click or find using File → Open Project...).
- In the Project Navigator “Files” tab, need to right-click and select “Set as Top-Level Entity” on the proper file/module.
  - The top-level entity should NOT be a test bench.
- When done coding a module, save the file and then run the Analysis and Synthesis tool: 
  - Quartus’ interface for compilation warnings and errors is better than ModelSim’s.
  - Use this tool to fix errors with syntax and signal connections before simulation.

# Simulation Workflow (ModelSim)

- Double-click `Launch_ModelSim.bat` in the project directory.
- In a text editor, modify `runlab.do` for your project:
  - Add files to compile (modules + test benches).
  - Change which test bench you wish to simulate.
  - Change the waveform script file (`*_wave.do`) – this won't exist at first.
- Execute `do runlab.do` in the *Transcript* pane.
  - Use waveforms to verify/debug logical behavior of your module(s).
- Update waveform script file as desired.
  - Click on different modules in the *sim* pane to access different signals.
  - Drag signals from the *Objects* pane into the *Wave* pane.
  - With the *Wave* pane selected, `Ctrl+S` to overwrite your waveform script file.
 
# Hardware Workflow (Quartus)

- Make sure the board is off before connecting to the computer's USB, then power the board on (red push button).
- In Quartus, ensure that your top-level module is set as the project's top-level module then use the **Compilation tool**: 
  - This typically takes a while to run (2-10 minutes).
- Use File → Open... to open the **Programmer interface** via ProgramTheDE1\_SoC.cdf.
  - Need to change the file type to "Programming Files":



- Assuming no issues, click "**Start**" to program your DE1-SoC!