

Exercise 1 –

- a) Parameterize the Guessing Game module for bit-width N and secret number S :

```
// Game to check user's N-bit input guess against a hard-coded
// secret #, S
// - SW[2:0] is the guess, KEY[0] allows input to be checked
// - LEDR[0] is <, LEDR[1] is ==, LEDR[2] is >
module guessing_game
  (output logic [9:0] LEDR,
   input logic [3:0] KEY, input logic [9:0] SW);

  logic is_lt, is_eq, is_gt;


  comparator      number_comparator(
    .A(SW[2:0]),
    .B(3'b001),
    .is_lt, .is_eq, .is_gt
  );

  assign LEDR[0] = is_lt & ~KEY[0];
  assign LEDR[1] = is_eq & ~KEY[0];
  assign LEDR[2] = is_gt & ~KEY[0];

endmodule // guessing_game
```

 Exercise 2 – Creating a String of Lights

Finish the module called `string_lights` that implements the system shown below (a string of 10 flip-flops/1-bit registers tied to the LEDRs) for the DE1-SoC.



- Use `SW[9]` as the reset, `SW[0]` as `In`, and `KEY[0]` as `clk`.
 - Since we are using a `KEY` for the clock, no need for `clock_divider`.
- Hint: flip-flops can be module instances or inferred from an `always_ff` block.

```
// flip-flop that samples d on the rising edge of the clk
// and transfers it to q
module D_FF1 (output logic q,
  input logic d, reset, clk);
  always_ff @(posedge clk)
  if (reset)
    q <= 0;
  else
    q <= d;
endmodule // D_FF1

module string_lights (output logic [9:0] LEDR,
  input logic [3:0] KEY,
  input logic [9:0] SW);
  logic clk, reset, in;
  // TODO: Finish creating the string of lights with or without the D_FF1 module!

endmodule // string_lights
```

Exercise 3 – Sequential Logic Test Bench

Finish the test bench for string_lights.

```
module string_lights_tb();
    logic [9:0] LEDR;
    logic [3:0] KEY;
    logic [9:0] SW;

    string_lights dut (.*);

    // TODO: Finish the test bench!
    // Remember that KEY[0] is acting as a clock for this system.

endmodule // string_lights_tb
```