

# Intro to Digital Design

## L4: Combinational Building Blocks & Sequential Logic

**Instructor:** Naomi Alterman

**Teaching Assistants:**

Derek de Leuw

Isabel Froelich

Kevin Hernandez

Sathvik Kanuri

Aadithya Manoj

# Administrivia


- ❖ Lab 3 Demos due during your assigned demo slots
  - Don't forget to submit your lab materials *before* Wednesday at 2:30 pm, regardless of your demo time
  - Come to lab with your reports open and bitfiles ready to load up
- ❖ Lab 4 – 7-segment displays
- ❖ Quiz 1 is next week in lecture
  - Last 20 minutes, worth 10% of your course grade
  - On Lectures 1-3: CL, K-maps, Waveforms, and Verilog
  - Past Quiz 1 (+ solutions) on website: Course Info → Quizzes

# Lecture Outline

- ❖ Multiplexors
- ❖ Adders
- ❖ Sequential Logic in theory
- ❖ Sequential Logic in Verilog

 
# Data Multiplexor

- ❖ Multiplexor (“MUX”) is a *selector*
  - Use an  $s$ -bit “select signal” to direct one of  $2^s$   $n$ -bit wide inputs to output
  - Called a  $n$ -bit,  $N$ -to-1 MUX
- ❖ Example:  $n$ -bit 2-to-1 MUX
  - Input  $S$  ( $s$  bits wide) selects between two inputs of  $n$  bits each



# Review: Implementing a 1-bit 2-to-1 MUX

❖ **Schematic:**

 


❖ **Boolean Algebra:**

$$\begin{aligned}c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\&= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\&= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\&= \bar{s}(a(1) + s((1)b) \\&= \bar{s}a + sb\end{aligned}$$

❖ **Truth Table:**


s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

❖ **Circuit Diagram:**

 

# 1-bit 4-to-1 MUX

- ❖ **Schematic:**

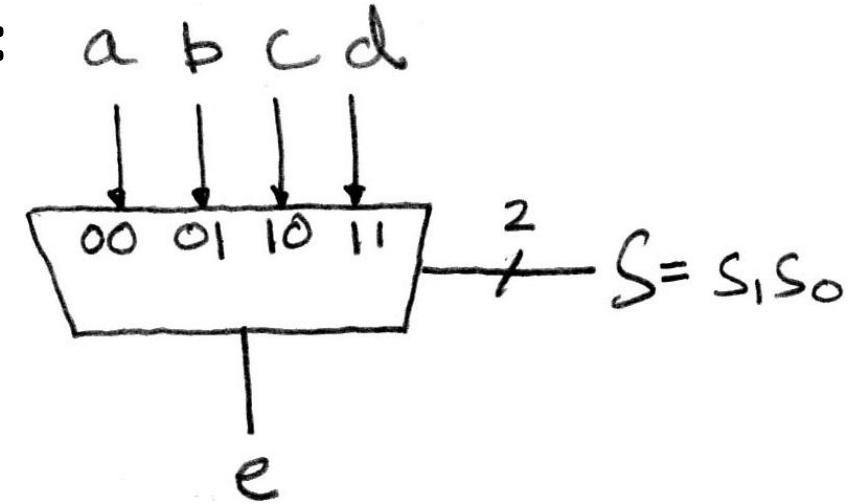


- ❖ **Truth Table:** How many rows?

- ❖ **Boolean Expression:**

$$e = \bar{s}_1 \bar{s}_0 a + \bar{s}_1 s_0 b + s_1 \bar{s}_0 c + s_1 s_0 d$$

 
# 1-bit 4-to-1 MUX

- ❖ Can we leverage what we've previously built?
  - Alternative hierarchical approach:


 
# Multiplexers in General Logic

- ❖ Implement  $F = X\bar{Y}Z + Y\bar{Z}$  with a 8:1 MUX



# Lecture Outline

- ❖ Multiplexors
- ❖ **Adders**
- ❖ Sequential Logic in theory
- ❖ Sequential Logic in Verilog


# Review: Unsigned Integers

- ❖ Unsigned values follow the standard base 2 system
  - $b_7b_6b_5b_4b_3b_2b_1b_0 = b_72^7 + b_62^6 + \dots + b_12^1 + b_02^0$
- ❖ In  $n$  bits, represent integers 0 to  $2^n-1$
- ❖ Add and subtract using the “carry” and “borrow” rules, just in binary

$$\begin{array}{r} 63 \\ + 8 \\ \hline 71 \end{array} \quad \begin{array}{r} 00111111 \\ + 00001000 \\ \hline 01000111 \end{array}$$

$$\begin{array}{r} 64 \\ - 8 \\ \hline 56 \end{array} \quad \begin{array}{r} 01000000 \\ - 00001000 \\ \hline 00111000 \end{array}$$

# Review: Two's Complement (Signed)

 


## ❖ Properties:

- In  $n$  bits, represent integers  $-2^{n-1}$  to  $2^{n-1} - 1$
- Positive number encodings match unsigned numbers
- Single zero (encoding = all zeros)
 
## ❖ Negation procedure:

- Take the bitwise complement and then add one  
 $( \sim x + 1 == -x )$



# Addition and Subtraction in Hardware

- ❖ The same bit manipulations work for both unsigned and two's complement numbers!

- Perform subtraction via adding the negated 2<sup>nd</sup> operand:

$$A - B = A + (-B) = A + (\sim B) + 1$$

- ❖ 4-bit examples:


		Two's	Un		Two's	Un
0	0	1	0	+2	2	
+ 1	1	0	0	-4	12	
<hr/>				<hr/>		
0	1	1	0	+6	6	
- 0	0	1	0	+2	2	
<hr/>				<hr/>		
1	1	1	1	-1	15	
- 1	1	1	0	-2	14	

# Half Adder (1 bit)


$$\begin{array}{r} a_3 \quad a_2 \quad a_1 \quad a_0 \\ + \quad b_3 \quad b_2 \quad b_1 \quad b_0 \\ \hline s_3 \quad s_2 \quad s_1 \quad s_0 \end{array}$$

$$\text{Carry} = a_0 b_0$$
$$\text{Sum} = a_0 \oplus b_0$$

$a_0$	$b_0$	$c_1$	$s_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


# Full Adder (1 bit)

 

Carry-in  $c_i$  and Carry-out  $c_{i+1}$  are indicated in red.


$c_i$	$a_i$	$b_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
 
$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) \\ = a_i b_i + a_i c_i + b_i c_i$$


 
# Multi-Bit Adder (N bits)

- ❖ Chain 1-bit adders by connecting  $\text{CarryOut}_i$  to  $\text{CarryIn}_{i+1}$ :



# 1-bit Adders in Verilog

- ❖ What's wrong with this?
  - Truncation!

```
module halfadd1 (s, a, b);
  output logic s;
  input logic a, b;

  always_comb begin
    s = a + b;
  end
endmodule
```

- ❖ Fixed:
  - Use of `{sig, ..., sig}` for *concatenation*

```
module halfadd2 (c, s, a, b);
  output logic c, s;
  input logic a, b;

  always_comb begin
    {c, s} = a + b;
  end
endmodule
```

# Ripple-Carry Adder in Verilog

```
module fulladd (cout, s, cin, a, b);
  output logic cout, s;
  input logic cin, a, b;

  always_comb begin
    {cout, s} = cin + a + b;
  end
endmodule
```


- ❖ Chain full adders?

```
module add2 (cout, s, cin, a, b);
  output logic cout; output logic [1:0] s;
  input logic cin;  input logic [1:0] a, b;
  logic c1;


  fulladd b1 (cout, s[1], c1, a[1], b[1]);
  fulladd b0 (c1, s[0], cin, a[0], b[0]);
endmodule
```
 
# Subtraction?

- ❖ Can we use our multi-bit adder to do subtraction?
  - Flip the bits and add 1?
    - $X \oplus 1 = \bar{X}$
    - CarryIn<sub>0</sub> (using full adder in all positions)



# Multi-bit Adder/Subtractor

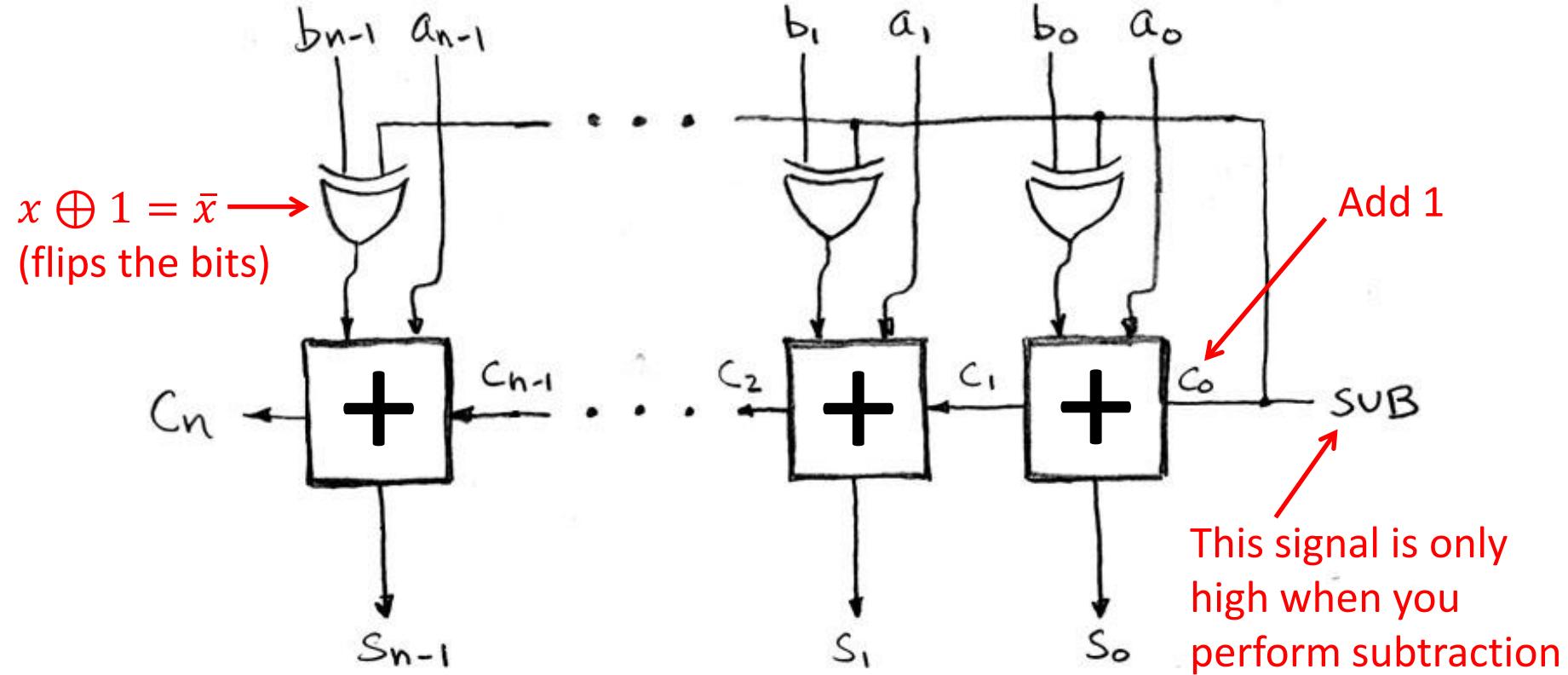

# Detecting Arithmetic Overflow

- ❖ **Overflow:** When a calculation produces a result that can't be represented in the current encoding scheme
  - Integer range limited by fixed width
  - Can occur in both the positive and negative directions
- ❖ **Unsigned Overflow**
  - Result of add/sub is  $> \text{UMax}$  or  $< \text{Umin}$
- ❖ **Signed Overflow**
  - Result of add/sub is  $> \text{TMax}$  or  $< \text{TMin}$
  - $(+) + (+) = (-)$  or  $(-) + (-) = (+)$

# Signed Overflow Examples

Two's

$$\begin{array}{r} 0101 \quad +5 \\ + 0011 \quad +3 \\ \hline \end{array}$$

Two's

$$\begin{array}{r} 1001 \quad -7 \\ + 1110 \quad -2 \\ \hline \end{array}$$


Two's

$$\begin{array}{r} 0101 \quad +5 \\ + 0010 \quad +2 \\ \hline \end{array}$$

Two's

$$\begin{array}{r} 1100 \quad -4 \\ + 0100 \quad 4 \\ \hline \end{array}$$
 
# Multi-bit Adder/Subtractor with Overflow



# Add/Sub in Verilog (parameterized)

- ❖ Variable-width add/sub (with overflow, carry)

```
module addN #(parameter N=32) (OF, CF, S, sub, A, B);
    output logic      OF, CF;
    output logic [N-1:0] S;
    input  logic       sub;
    input  logic [N-1:0] A, B;
    logic   [N-1:0] D;    // possibly flipped B
    logic   C2;        // second-to-last carry-out

    always_comb begin
        D = B ^ {N{sub}}; // replication operator
        {C2, S[N-2:0]} = A[N-2:0] + D[N-2:0] + sub;
        {CF, S[N-1]} = A[N-1] + D[N-1] + C2;
        OF = CF ^ C2;
    end
endmodule // addN
```

- Here using OF = overflow flag, CF = carry flag (from condition flags in x86-64 CPUs)

# Add/Sub in Verilog (parameterized)

```
module addN_tb ();
    logic      sub;
    logic [N-1:0] A, B;
    logic      OF, CF;
    logic [N-1:0] S;

    addN #(N(4)) dut (.OF, .CF, .S, .sub, .A, .B);

    initial begin
        #100; sub = 0; A = 4'b0101; B = 4'b0010; // 5 + 2
        #100; sub = 0; A = 4'b1101; B = 4'b1011; // -3 + -5
        #100; sub = 0; A = 4'b0101; B = 4'b0011; // 5 + 3
        #100; sub = 0; A = 4'b1001; B = 4'b1110; // -7 + -2
        #100; sub = 1; A = 4'b0101; B = 4'b1110; // 5 -(-2)
        #100; sub = 1; A = 4'b1101; B = 4'b0101; // -3 - 5
        #100; sub = 1; A = 4'b0101; B = 4'b1101; // 5 -(-3)
        #100; sub = 1; A = 4'b1001; B = 4'b0010; // -7 - 2
        #100;
    end
endmodule // addN_tb
```

# Miso Moment




# Lecture Outline

- ❖ Multiplexors
- ❖ Adders
- ❖ **Sequential Logic in theory**
- ❖ Sequential Logic in Verilog

# Synchronous Digital Systems (SDS)


## ❖ Combinational Logic (CL)

 

Network of logic gates without feedback.

Outputs are functions only of inputs.

## ❖ Sequential Logic (SL)

 

The presence of feedback introduces the notion of “state.”



Circuits can “remember” or store information.

# Uses for Sequential Logic

- ❖ Place to store values for some amount of time:
  - Registers
  - Memory
- ❖ *Help control flow of information between combinational logic blocks*
  - Hold up the movement of information to allow for orderly passage through CL

  
# Control Flow of Information?

- ❖ Circuits can temporarily go to incorrect states!


 
# Design example: Perpetual Timer

- ❖ A circuit that counts up from 0 over time
  - ❖ When time is up, stops counting and beeps incessantly
  - ❖ Needs to “remember” previous value to calculate next value




- ❖ Want:  

```
s = 0;  
while (true) {  
    s = s + 1;  
}
```

# Timer: First Try

Does this work?


No

 

- 1) How do we say: 'S=0'?
- 2) How to control the next iteration of the 'for' loop?

 
# Timer: Second Try



We'll add a “reset” signal  
Does this work?




How to control the next iteration of  
the ‘for’ loop?

# State Element: Flip-Flop

   - ❖ Positive edge-triggered D-type flip flop
  - On the rising edge of the clock (  ), input  $d$  is **sampled** and held as the output “ $q$ ” until the next clock edge
  - All other times, the input  $d$  is ignored



# State Element: Register

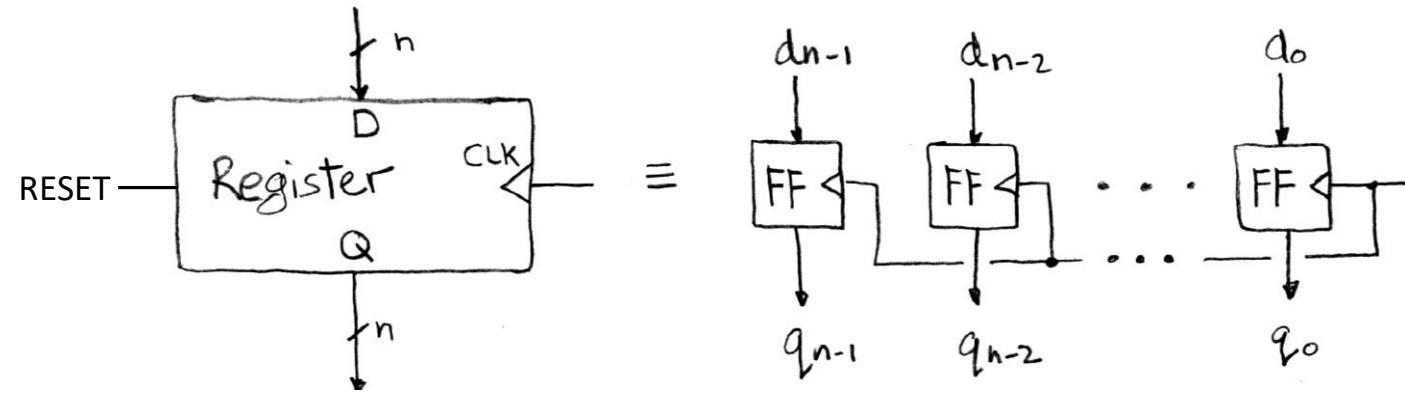


- ❖  $n$  instances of flip-flops together
  - One for every bit in input/output bus width
- ❖ Optional synchronous RESET input
  - Forces  $Q$  to 0 when asserted
  - Just shorthand for adding a mux to the FF's input

# Timer: Third try

We happy?



We happy :3

 

Register holds up the transfer  
of data to adder



# Synchronous waveforms

Start by assuming no propagation delays

  

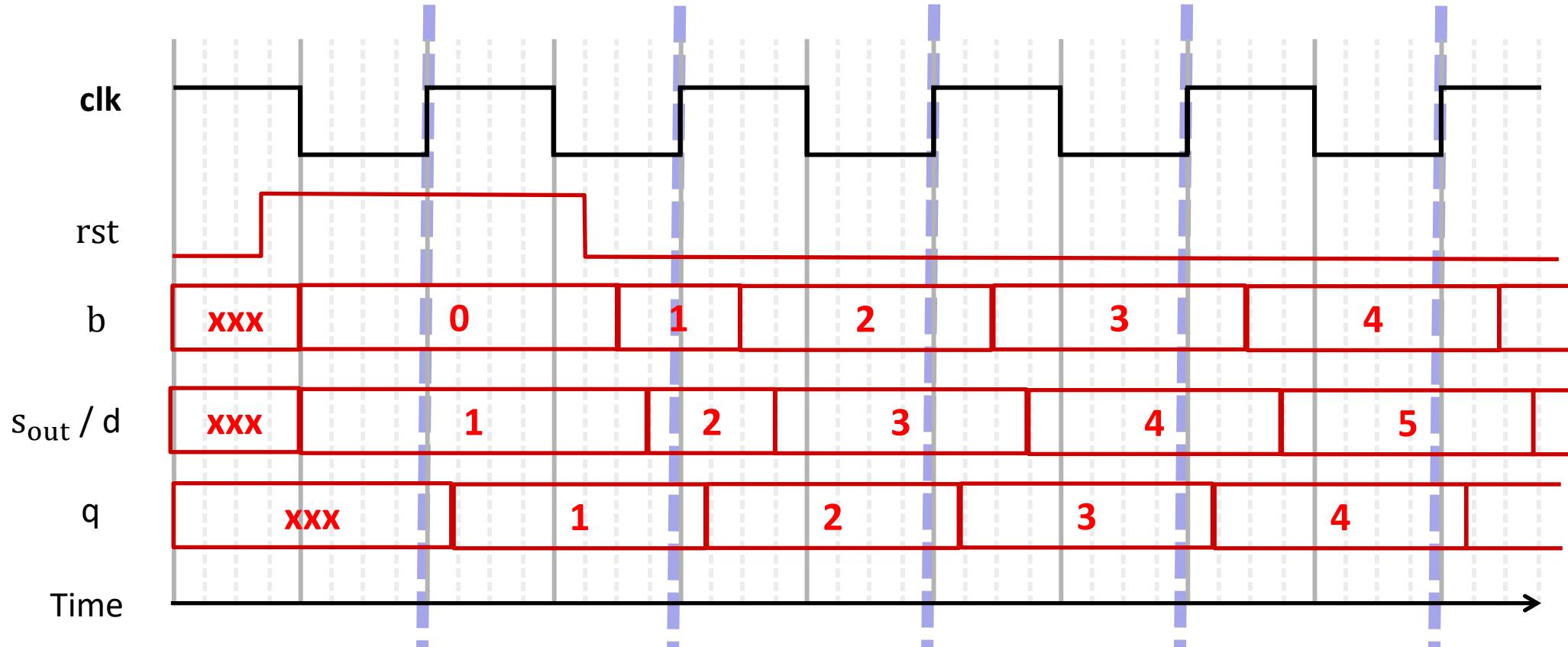
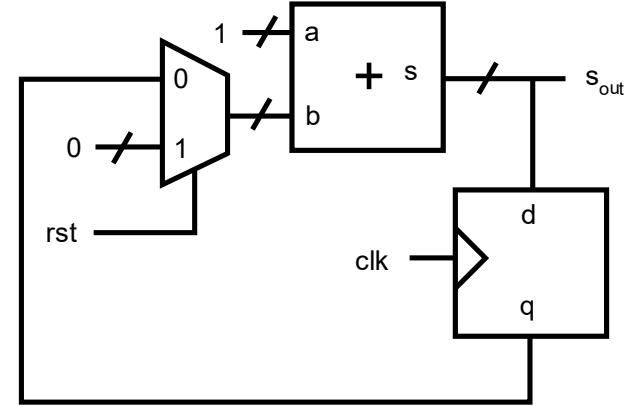
# Synchronous waveforms

Now a propagation delay of 3ns  
(1 tick) per block



 
 
# Autopilot Revisited

- ❖ Flip-flops “filter out” circuit hazards!


  
# Safe Sequential Circuits

- ❖ Clocked elements on feedback, perhaps outputs
  - Clock signal synchronizes operation
  - Clocked elements hide glitches/hazards
  - Output can wiggle with hazards as much as it wants as long as it's **stable around the positive clock edge**
    - More on this in a few weeks ;)



# Lecture Outline

- ❖ Multiplexors
- ❖ Adders
- ❖ Sequential Logic in theory
- ❖ **Sequential Logic in Verilog**



# Verilog: Basic D Flip-Flop, Register

```
module basic_D_FF (q, d, clk);
    output logic q; // q is state-holding
    input logic d, clk;

    always_ff @ (posedge clk)
        q <= d; // use <= for clocked elements
endmodule
```

```
module basic_reg (q, d, clk);
    output logic [7:0] q;
    input logic [7:0] d;
    input logic clk;

      always_ff @ (posedge clk)
        q <= d;
endmodule
```




# Reminder: “always\_comb” blocks

- ❖ Verilog requires us to wrap control flow statements in an **always\_comb** block
  - Block defines the full set of circuits that *may* drive the value on a `logic` variable
  - Idea: the last assignment in an always block to a given variable is the result that gets used
- ❖ But I promised there were more species of “**always**” block...
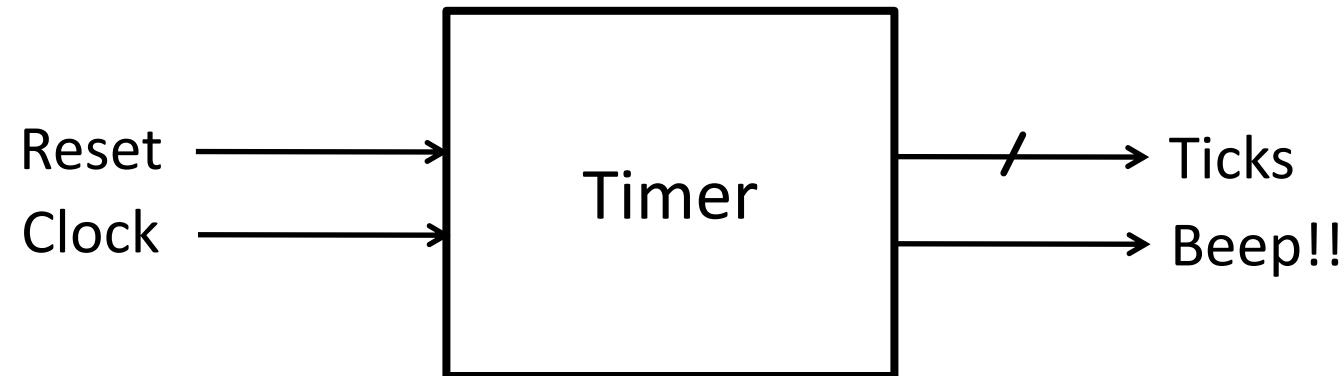
# Exercise for the reader: Advanced Timer

- ❖ Draw a circuit diagram for a block that counts up from 0 to parameter N
  - ❖ Very similar to our “perpetual timer” example, but it’ll need another mux and a block to compare if two numbers are equal
    - ❖ Can use a black box for the comparator
    - ❖ (but you know enough to design that too, if you wanted to 😊)



# Summary (1/2)

- ❖ Multiplexors switch signals to the output
  - Illustrated in block diagrams as trapezoids with labelled inputs and a select signal
- ❖ Binary addition and subtraction can be performed with chained full adders
  - Two's complement allows us to use the same hardware
  - We can detect signed overflow by XORing the carry-in and carry-out of the sign bit

# Summary (2/2)

- ❖ State elements controlled by clock
  - Store information
  - Control the flow of information between other state elements and combinational logic
- ❖ Registers implemented from flip-flops
  - Triggered by CLK, pass input to output, can reset