

Intro to Digital Design

L10: Course Wrap-up

Instructor: Naomi Alterman

Teaching Assistants:

Derek de Leuw

Isabel Froelich

Kevin Hernandez


Sathvik Kanuri

Aadithya Manoj


Outline

- ❖ **TTL & Breadboarding**
- ❖ Course Wrap-up
- ❖ Quiz 3


TTL computers

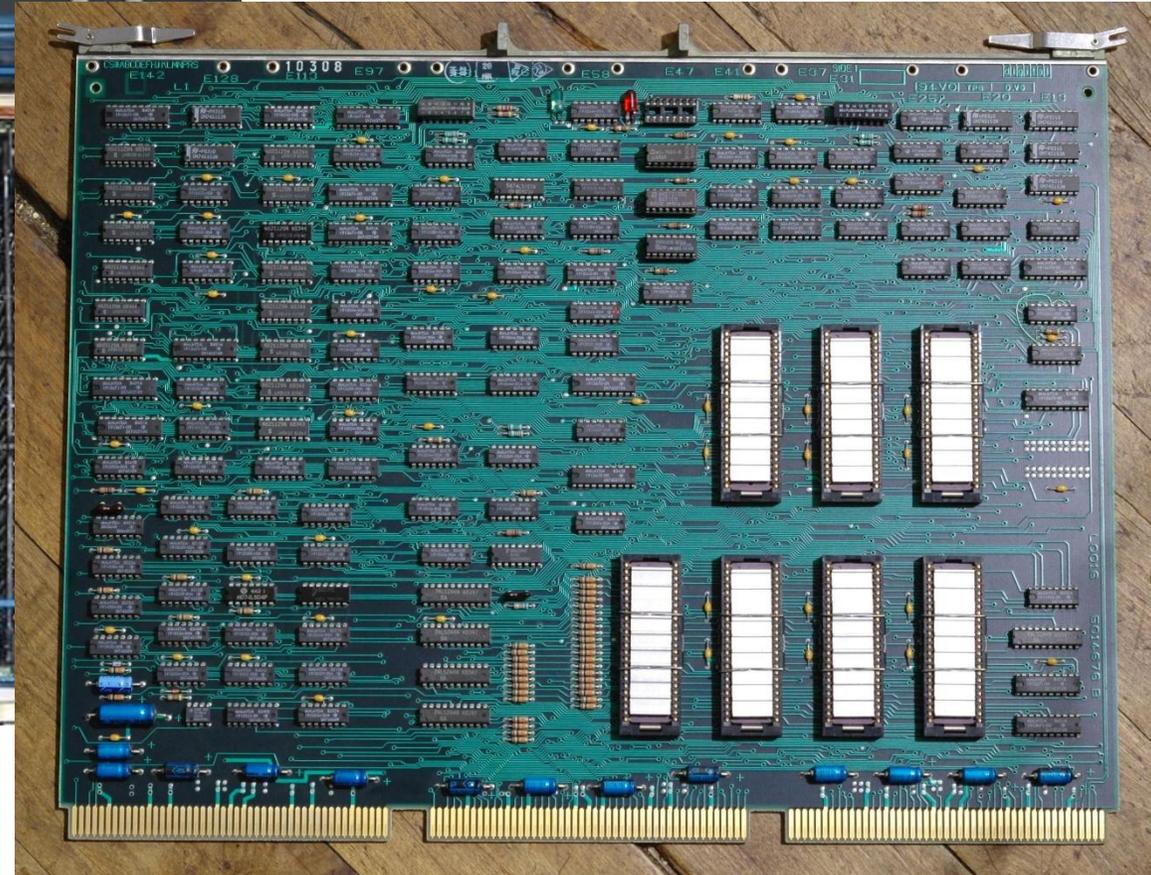

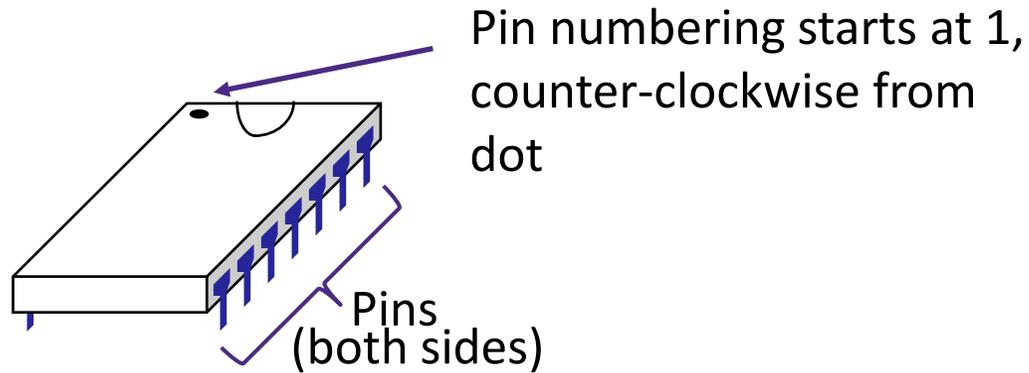Transistor-Transistor Logic (TTL) Packages




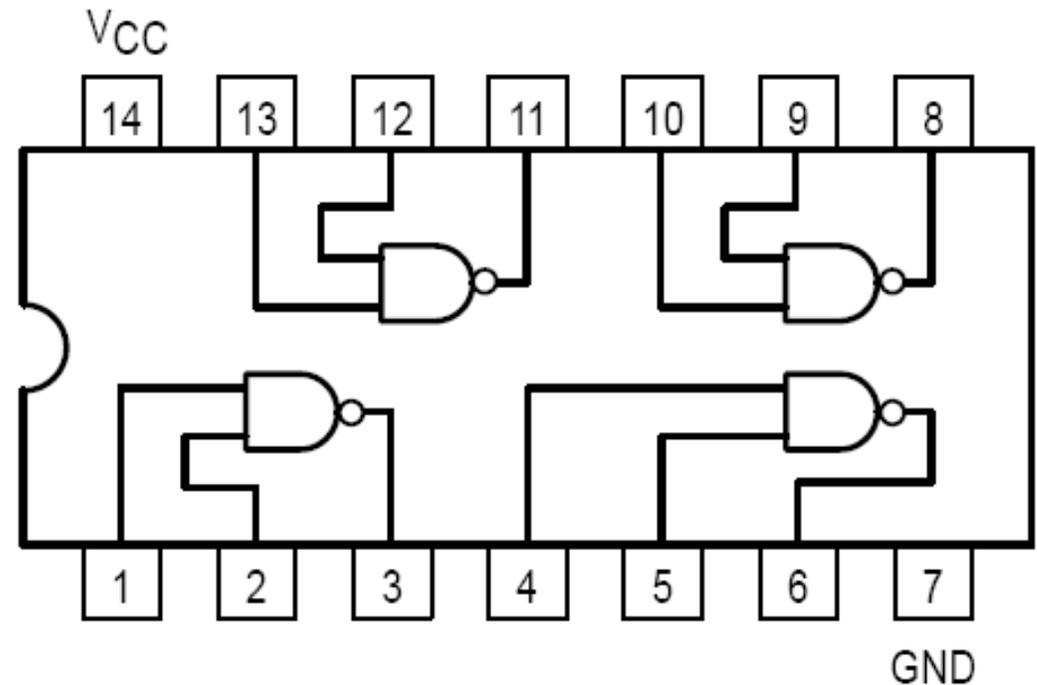- ❖ Diagrams like these and other useful/helpful information can be found on part **data sheets**
 - It's really useful to learn how to read these




Mapping truth tables to circuit boards

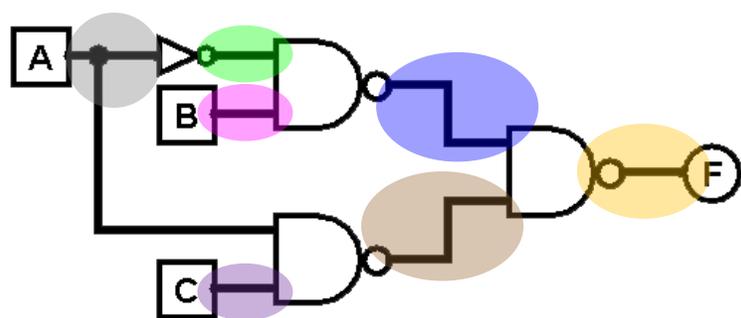- ❖ Given a truth table:
 - 1) Write the Boolean expression
 - 2) Minimize the Boolean expression
 - 3) Draw as gates
 - 4) Map to available gates
 - 5) Determine # of packages and their connections




7 nets (wires) in this design



(4)

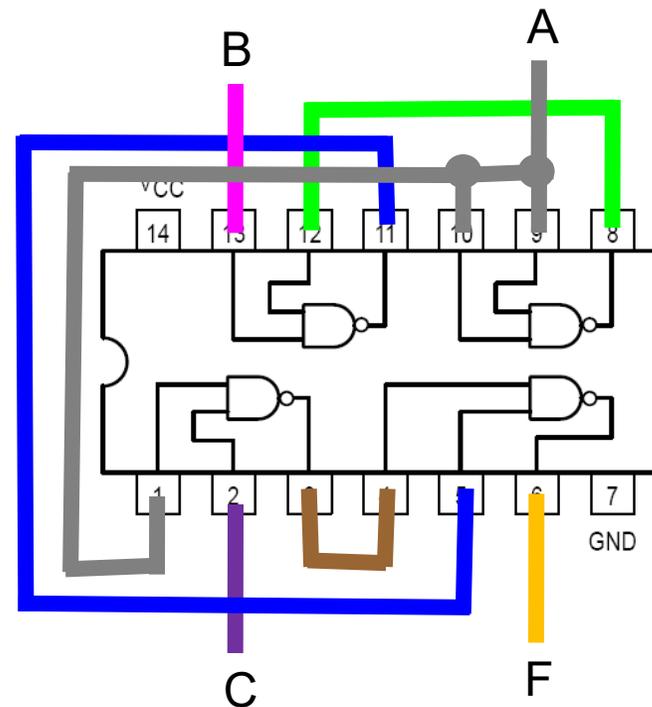


Prototyping with breadboards

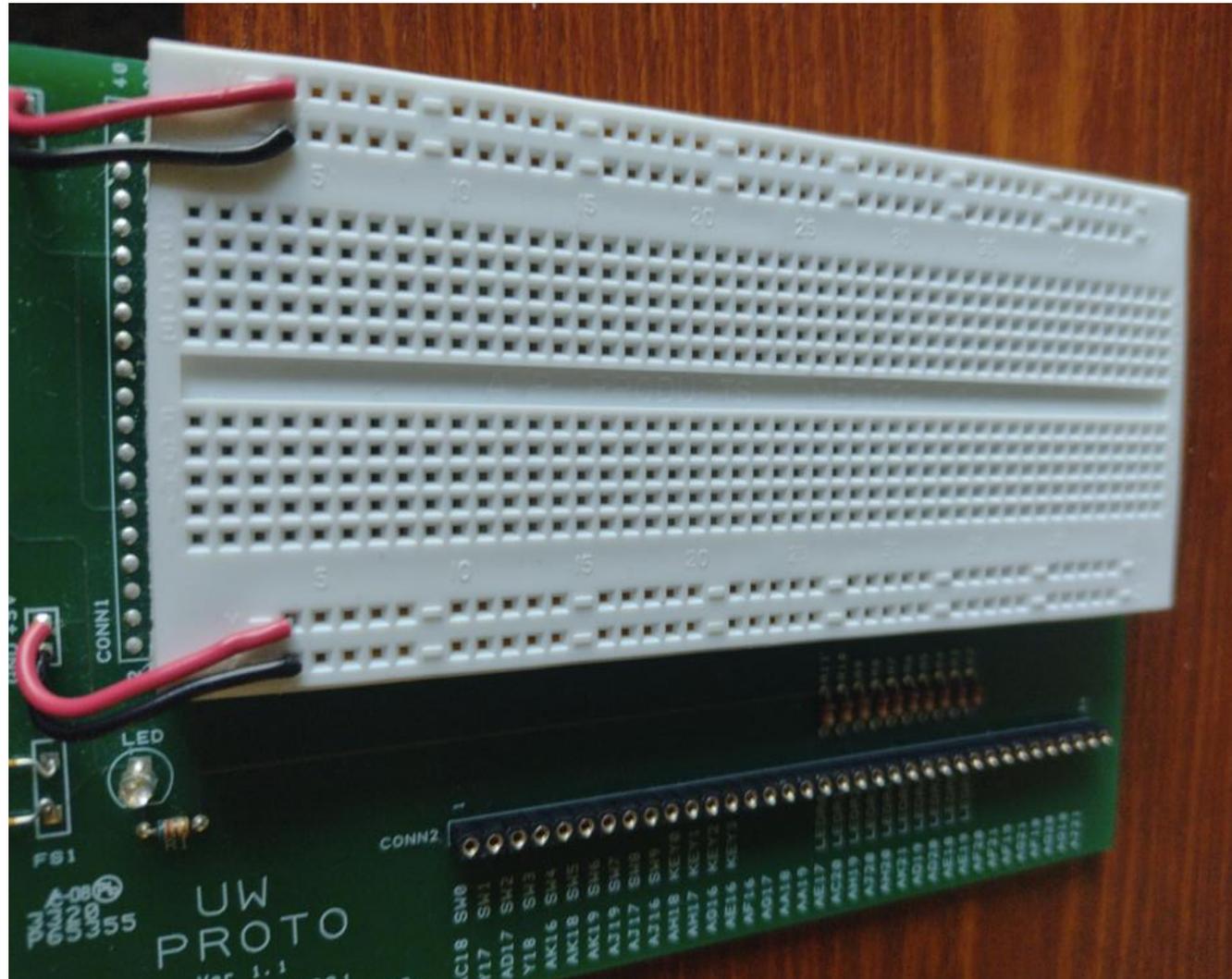


Breadboarding circuits

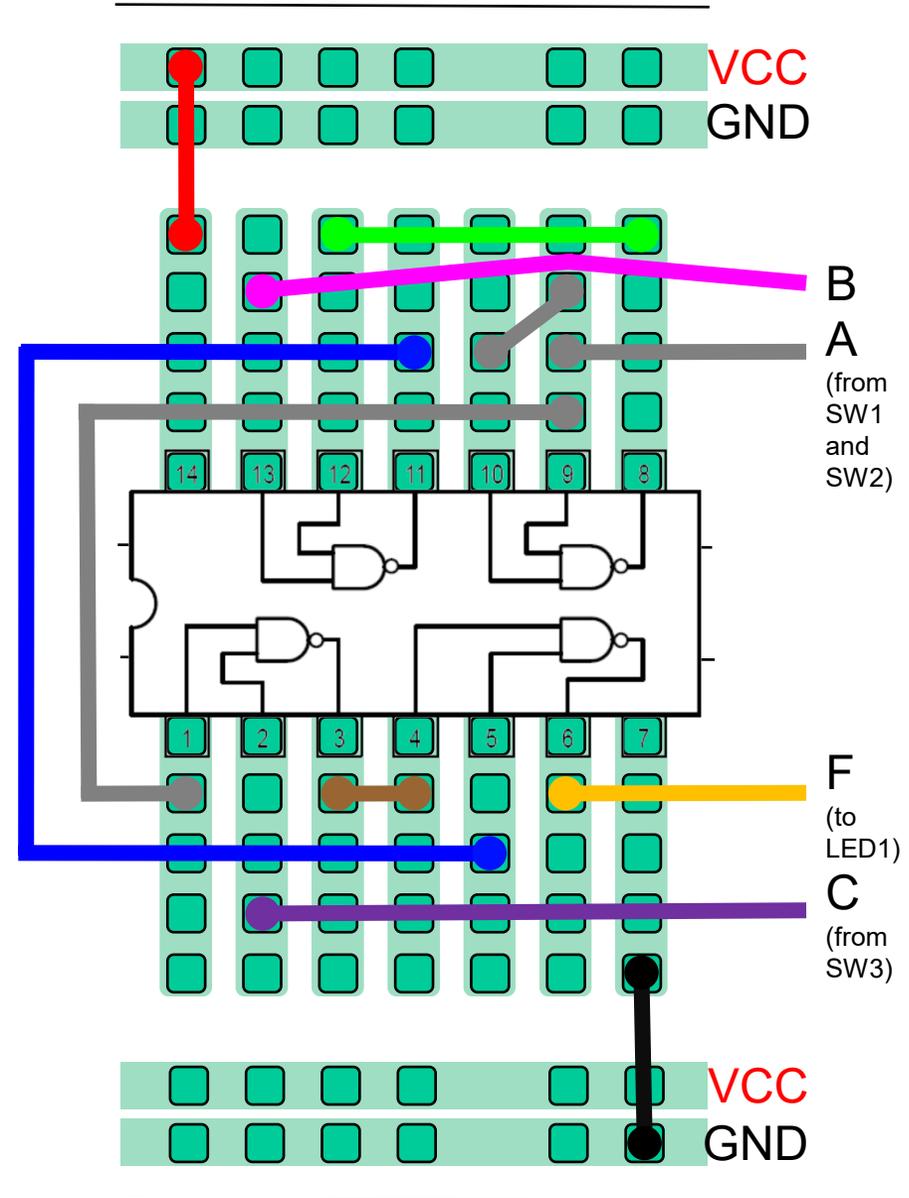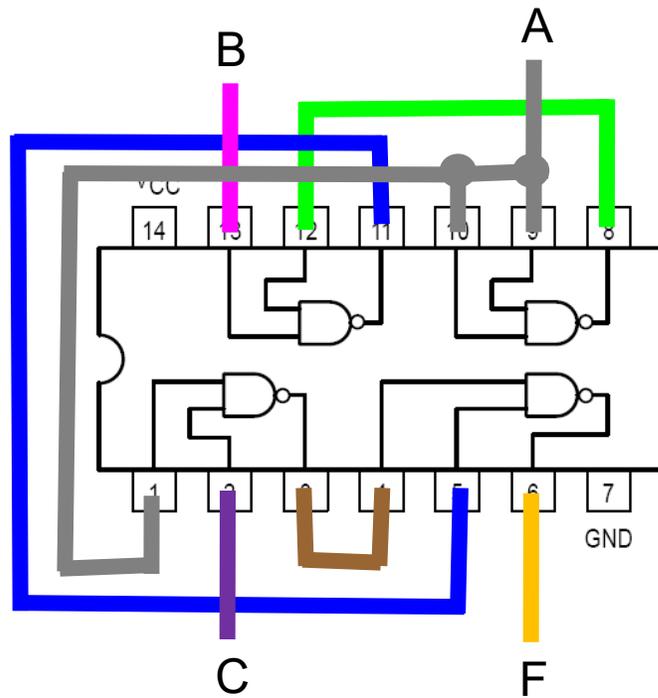

Breadboarding Modern Components

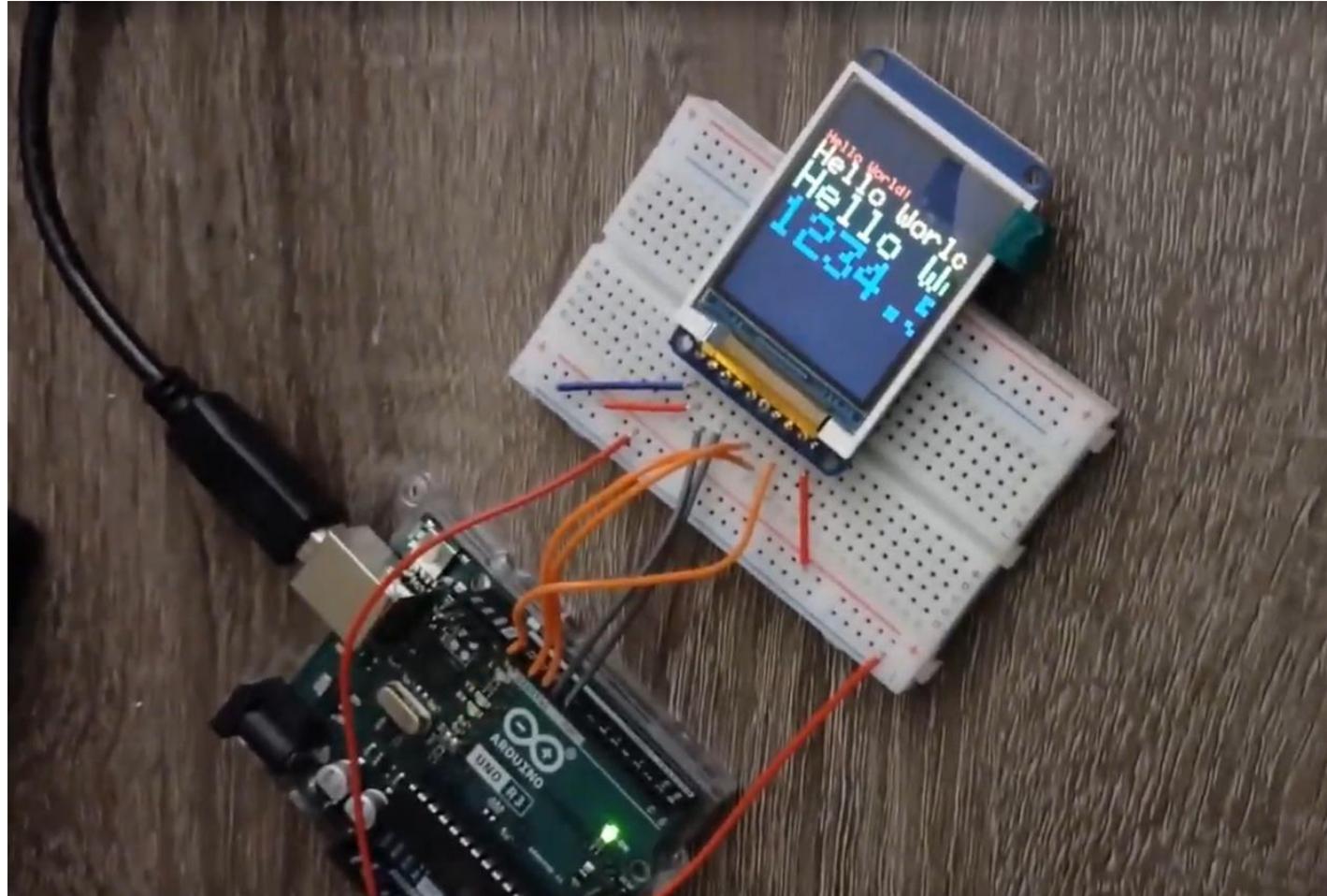

Breadboarding Modern Fashion

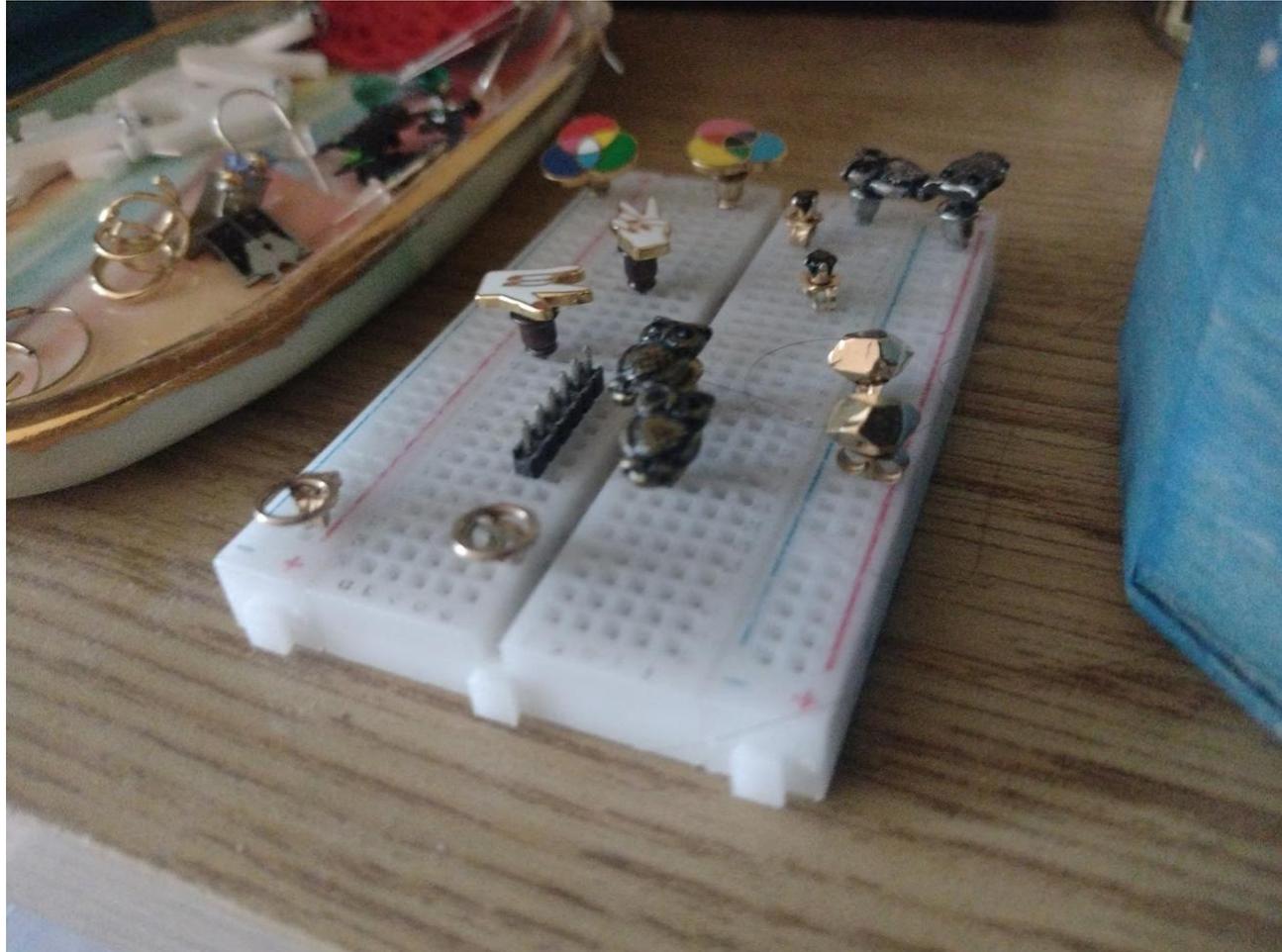

Outline

- ❖ TTL & Breadboarding
- ❖ **Course Wrap-up**
- ❖ Quiz 3

Course Wrap-Up

- ❖ Combinational Logic
 - Karnaugh Maps
- ❖ Sequential Logic
 - Timing Considerations
- ❖ Finite State Machines
- ❖ Routing Elements
 - Multiplexor, Encoder, Decoder, Demultiplexor
- ❖ Computational Building Blocks
 - Adders, Registers, Shift Registers, Counters
- ❖ *SystemVerilog*

Digital Workhorses

❖ Multiplexors

- Logic – can implement arbitrary logic as LUTs
- Routing – select between many simultaneous computations

❖ Flip-flops

- Store information
 - registers, shift registers, counters, FSMs, RAM cells
- Synchronization of system
 - “Holds up” signals so feedback loops only iterate once per clock cycle
- Filter out circuit hazards and glitches
- Gotta watch out for metastability

Takeaways

- ❖ Hardware design is all about computation in space rather than computation in time
- ❖ Modern EE tools and design methods let us do a lot without needing to know much about actual circuitry
 - Verilog is a “high level” way to produce the “lowest level” of computing components!
 - Sufficient level of abstraction for many cases
- ❖ ... but it's a leaky abstraction, and the hardware details are important
 - Timing especially – synchronization, metastability
 - Design affects speed, power, size

Takeaways

- ❖ You now know how to design and implement complex digital circuits!
 - DE1-SoC (\$377): <http://www.terasic.com.tw/cgi-bin/page/archive.pl?Language=English&No=836>


Final Words




- ❖ Please fill out [course evaluation](#) before the end of the week!
 - Due by the 15th; let's improve this class together 🙏
- ❖ Future classes
 - EE 205/215 – details of electronics
 - EE/CSE 371 – digital design techniques and considerations (algorithms, communication, complexity)
 - EE/CSE 469 – computer architecture (CPU design)
- ❖ Hope you had fun this quarter!
- ❖ Huge thanks to your TAs!



Isabel

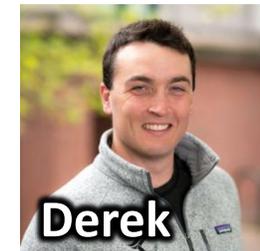

Derek

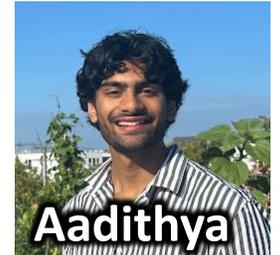

Aadithya



Kevin



Sathvik