

# CSE 369 QUIZ 1

Name: \_\_\_\_\_ **Molly Model** \_\_\_\_\_  
Student ID Number: \_\_\_\_\_ **1234567** \_\_\_\_\_

**Please do not turn the page until 12:30.**

## Instructions

- This quiz contains 3 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 20 (+5) minutes to complete this quiz.


## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) CL Gates	8	<b>8</b>
(2) K-map	5	<b>5</b>
(3) Waveforms & Verilog	13	<b>13</b>
<b>Total:</b>	<b>26</b>	<b>26</b>


**Question 1: Combinational Logic Gates [8 pts]**

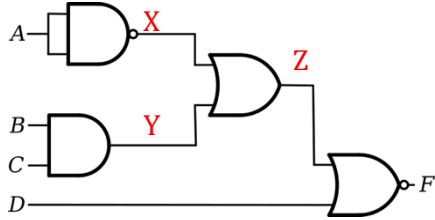- (A) Write out a Boolean expression for the circuit diagram below. *No need to simplify.* Remember to use + (OR), · (AND), and  $\bar{\phantom{x}}$  (NOT) as well as any necessary parentheses to make your answer unambiguous. [2 pts]  $F = \overline{(\bar{A} + BC) + D}$



- $X = \bar{A}$  [0.5 pt]
- $Y = BC$  [0.5 pt]
- $Z = X + Y$  [0.5 pt]
- $F = \overline{D + Z}$  [0.5 pt]

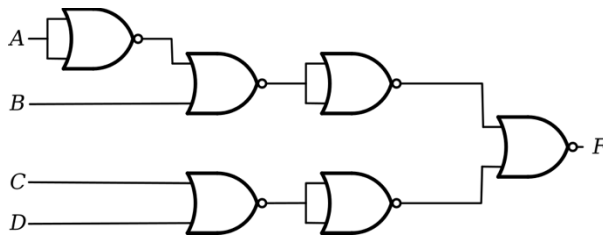
- (B) Find a minimal implementation of the function below using only **2-input NOR gates**. We will only accept circuit diagrams. [6 pts]  
 $F = \overline{AB(C + D)}$



- [1 pt] Valid gate conversion from expression
- [2 pt] DeMorgan's applications (either in expression or gates)
- [3 pt] Conversion of extra NOTs to NORs

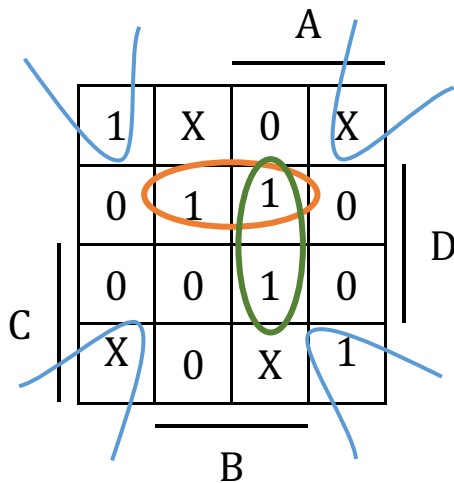**Question 2: Karnaugh Maps [5 pts]**

Find the *minimum sum-of-products solution* for the K-map shown below.



$$F = \overline{B}\overline{D} + ABD + B\overline{C}D$$


$$\text{Or } + ABD + \overline{A}B\overline{C}$$

$$\text{Or } + ABC + B\overline{C}D$$

- [2 pt] X choices
- [1 pt each] correct term/grouping
- [-0.5 pt each] smaller grouping used
- [-0.5 pt each] extra grouping included

### Question 3: Waveforms & Verilog [13 pts]

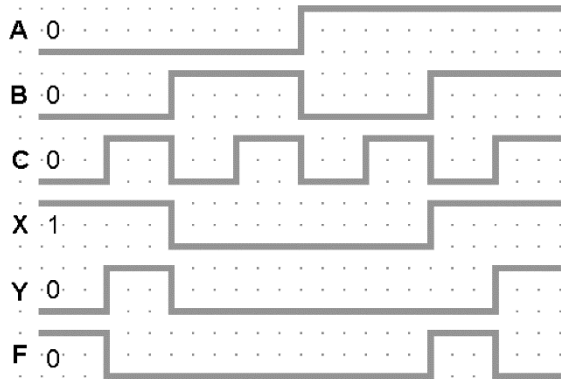- (A) Consider the Verilog simulated testbench waveforms shown. If we know that X and Y are outputs of 2-input logic gates, complete the module `Mystery` below. [7 pts]



```

module Mystery (F, A, B, C);
  output logic F;
  input logic A, B, C;
  logic X, Y;

  xnor G1 (X, A, B);
  // or assign X = ~(A ^ B);

  and G2 (Y, C, X);
  // or assign Y = C & X;

  xor G3 (F, X, Y);
endmodule

```

- (B) A testbench for the `Mystery` module (with inputs A, B, C) is shown below. Which input combinations are NOT currently being tested? You may not need all of the blanks. [3 pts]

```

module Mystery_testbench ();
  logic F, A, B, C;

  initial begin

    A = 0; B = 0; C = 0; #10; // XXX
    A = 1;                #10; // 000
      B = 1;                #10; // 110
        C = 1; #10; // 111
    A = 0; B = 0;          #10; // 001
      B = 1; C = 0; #10; // 010
        B = 0;          #10; // 000
    A = 1;                #10; // 100

  end
endmodule

```

Missing combinations:

1. {A,B,C} = 3'b011;
2. {A,B,C} = 3'b101;
3. {A,B,C} = 3'b\_\_\_\_;
4. {A,B,C} = 3'b\_\_\_\_;

- (C) Circle the value of A at the beginning of the simulation of `Mystery_testbench`: [1 pt]

0

1

X

Z

- (D) Give a brief piece of advice on how to improve the above testbench. [2 pts]

Many acceptable answers here:

- Use a for-loop (from 0 to 7) to guarantee going through all combinations.
- Go through combinations more systematically (e.g., 000 → 001 → 002 → ...).
- Explicitly write out the A, B, and C values on each line for readability.
- Define signals from the start (i.e., eliminate the first #10;).