

CSE 369 QUIZ 2

Name: Perry_Perfect

UWNetID: perfect

Please do not turn the page until 10:30.

Instructions

- This quiz contains 4 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 25 minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) SL & Timing	6	6
(2) FSM Implementation	10	10
(3) FSM Design	10	10
Total:	26	26

 Question 1: Sequential Logic & Timing [6 pts]

Consider the following circuit diagram with $t_{setup} = 50 \text{ ps}$ (10^{-12} s), $t_{hold} = 20 \text{ ps}$, $t_{c2Q} = 70 \text{ ps}$, $t_{NOT} = 15 \text{ ps}$, $t_{OR} = 80 \text{ ps}$, and $t_{XOR} = 100 \text{ ps}$. Consider each part below *independently* and fill in your answers in the boxes below, making sure to *include units*.



- (A) If the input In changes exactly on clock triggers, what is the minimum clock period that we can use and still ensure proper behavior? [4 pts]

300 ps

The critical path is shown above in red and goes through the XOR and OR gates.

So we need $t_{c2Q} + t_{XOR} + t_{OR} \leq t_{period} - t_{setup}$.

Then $t_{period} \geq 70 + 100 + 80 + 50 = 300 \text{ ps}$.

- (B) If the input In changes **10 ps** after each clock trigger, what is the minimum t_{XOR} delay we need to prevent a *hold time violation*? [2 pts]


10 ps

Shortest path is shown above in blue and goes from In through the XOR gate.

So we need $10 \text{ ps} + t_{XOR} \geq t_{hold}$ and $t_{XOR} \geq 20 - 10 = 10 \text{ ps}$.

Question 2: Finite State Machine Implementation [10 pts]


 
(A) Fill in the provided truth table based on the FSM shown. [2 pts]




PS ₁	PS ₀	In	NS ₁	NS ₀	Out ₁	Out ₀
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	1	1	0	1
0	1	1	0	1	0	1
1	0	0	X	X	X	X
1	0	1	X	X	X	X
1	1	0	0	0	1	1
1	1	1	1	1	1	1

(B) Complete the circuit diagram below using *minimal logic* based on the truth table shown below. You are welcome to use 2- and 3-input logic gates. [8 pts]


PS	In ₁	In ₀	NS	Out
0	0	0	1	1
0	0	1	0	1
0	1	0	X	X
0	1	1	1	1
1	0	0	0	1
1	0	1	0	0
1	1	0	X	X
1	1	1	1	0

  
 
$$NS = In_1 + \overline{In_0} \overline{PS}$$



$$Out = \overline{PS} + In_0$$

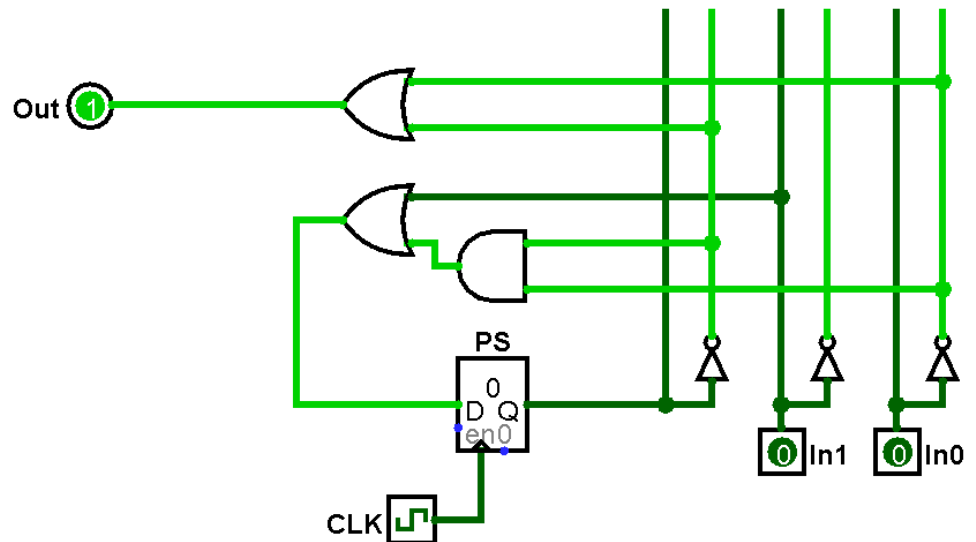

Question 3: Finite State Machine Design [10 pts]

- (A) If we have an FSM with five states and a transition arrow from each state to all the other states (20 transitions total), how many bits does our system require? [2 pt]

5 states and 4 transitions per state.


State Bits: **3**

Input Bits: **2**

- (B) The following FSM takes a stream of inputs and removes the *second* 1 from every consecutive string of 1's.

Input: 1 0 1 1 0 1 1 1 0 1 1 1 1

Output: 1 0 1 0 0 1 0 1 0 1 0 1 1

 

Complete the testbench initial block to *thoroughly* test the FSM. You are welcome to fill out the Verilog comments to help you keep track of state, but these will not be graded. [3 pts]

```

initial begin
    In <= 1; // state: 00

    @(posedge clk); In <= 0; // state: 01
    @(posedge clk); In <= 0; // state: 00
    @(posedge clk); In <= 1; // state: 00

    @(posedge clk); In <= 1; // state: 01
    @(posedge clk); In <= 1; // state: 10

    @(posedge clk); In <= 0; // state: 10
    @(posedge clk); // state: 00
    $stop();
end
  
```

- (C) Draw a state diagram for an FSM that removes the *third* 1 from every consecutive string of 1's: [5 pt]

