

# CSE 369 QUIZ 2

Name: \_\_\_\_\_

UWNetID: \_\_\_\_\_

**Please do not turn the page until 10:30.**

## Instructions

- This quiz contains 4 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 25 minutes to complete this quiz.


## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) SL & Timing	6	
(2) FSM Implementation	10	
(3) FSM Design	10	
<b>Total:</b>	<b>26</b>	

 **Question 1: Sequential Logic & Timing [6 pts]**

Consider the following circuit diagram with  $t_{setup} = 50 \text{ ps}$  ( $10^{-12} \text{ s}$ ),  $t_{hold} = 20 \text{ ps}$ ,  $t_{c2Q} = 70 \text{ ps}$ ,  $t_{NOT} = 15 \text{ ps}$ ,  $t_{OR} = 80 \text{ ps}$ , and  $t_{XOR} = 100 \text{ ps}$ . Consider each part below *independently* and fill in your answers in the boxes below, making sure to *include units*.




- (A) If the input In changes exactly on clock triggers, what is the minimum clock period that we can use and still ensure proper behavior? [4 pts]

- (B) If the input In changes **10 ps** after each clock trigger, what is the minimum  $t_{XOR}$  delay we need to prevent a *hold time violation*? [2 pts]

**Question 2: Finite State Machine Implementation [10 pts]**


 
(A) Fill in the provided truth table based on the FSM shown. [2 pts]



PS <sub>1</sub>	PS <sub>0</sub>	In	NS <sub>1</sub>	NS <sub>0</sub>	Out <sub>1</sub>	Out <sub>0</sub>
0	0	0		0	0	0
0	0	1		1	0	0
0	1	0		1	0	1
0	1	1		1	0	1
1	0	0	X	X	X	
1	0	1	X	X	X	
1	1	0	0	0	1	
1	1	1	1	1	1	

(B) Complete the circuit diagram below using *minimal logic* based on the truth table shown below. You are welcome to use 2- and 3-input logic gates. [8 pts]

PS	In <sub>1</sub>	In <sub>0</sub>	NS	Out
0	0	0	1	1
0	0	1	0	1
0	1	0	X	X
0	1	1	1	1
1	0	0	0	1
1	0	1	0	0
1	1	0	X	X
1	1	1	1	0

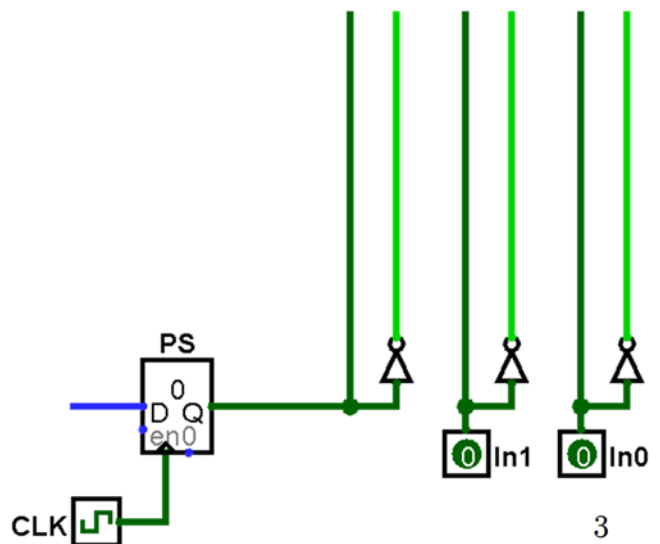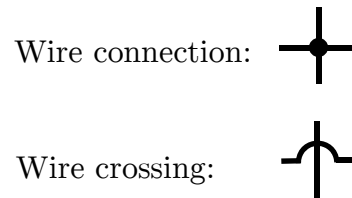

### Question 3: Finite State Machine Design [10 pts]


- (A) If we have an FSM with five states and a transition arrow from each state to all the other states (20 transitions total), how many bits does our system require? [2 pt]

State Bits:	Input Bits:
-------------	-------------

- (B) The following FSM takes a stream of inputs and removes the *second* 1 from every consecutive string of 1's.

Input: 1 0 1 1 0 1 1 1 0 1 1 1 1

Output: 1 0 1 0 0 1 0 1 0 1 0 1 1

 

Complete the testbench `initial` block to *thoroughly* test the FSM. You are welcome to fill out the Verilog comments to help you keep track of state, but these will not be graded. [3 pts]

```

initial begin
    In <= 1;           // state: 00

    @(posedge clk);  In <= ____; // state: ____
    @(posedge clk);  In <= 0;    // state: ____
    @(posedge clk);  In <= 1;    // state: ____

    @(posedge clk);  In <= ____; // state: ____
    @(posedge clk);  In <= 1;    // state: ____

    @(posedge clk);  In <= ____; // state: ____
    @(posedge clk);  // state: ____
    $stop();
end
  
```

- (C) Draw a state diagram for an FSM that removes the *third* 1 from every consecutive string of 1's: [5 pt]