

CSE 369 QUIZ 2

Name: _____

Student ID
Number: _____

Please do not turn the page until 2:20.

Instructions

- This quiz contains 4 pages, including this cover page. You may use the backs of the pages for scratch work.
- Please clearly indicate (box, circle) your final answer.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 30 (+5) minutes to complete this quiz.


Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) SL & Timing	6	
(2) FSM Implementation	10	
(3) FSM Design	11	
Total:	27	

 Question 1: Sequential Logic & Timing [6 pts]

Consider the following circuit diagram with $t_{\text{setup}} = 8 \text{ ns}$ (10^{-9} s), $t_{\text{C2Q}} = 10 \text{ ns}$, $t_{\text{AND}} = 20 \text{ ns}$, $t_{\text{NOR}} = 16 \text{ ns}$, $t_{\text{NOT}} = 6 \text{ ns}$, and $t_{\text{XOR}} = 22 \text{ ns}$.



- (A) Calculate the **minimum clock period** that will allow the circuit to function correctly. [3 pts]


ns

- (B) Calculate the **maximum hold time** (t_{hold}) that will allow the circuit to function correctly. [3 pts]

ns

Question 2: Finite State Machine Implementation [10 pts]



 
(A) Fill in the provided truth table based on the FSM shown. [2 pts]



PS ₁	PS ₀	In	NS ₁	NS ₀	Out ₁	Out ₀
0	0	0	X	X	X	X
0	0	1	X	X		
0	1	0	1	0	0	1
0	1	1	1	1	1	1
1	0	0			1	0
1	0	1	1	1		
1	1	0	0	1	0	0
1	1	1			0	0


(B) Complete the circuit diagram below using *minimal logic* based on the truth table shown below. Use only 2-input logic gates. [8 pts]

PS	In ₁	In ₀	NS	Out
0	0	0	0	1
0	0	1	X	X
0	1	0	0	0
0	1	1	0	0
1	0	0	1	0
1	0	1	X	X
1	1	0	1	0
1	1	1	0	1

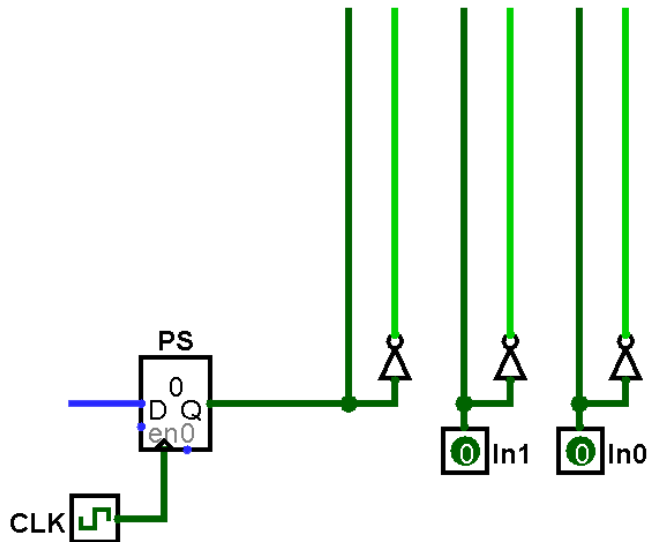  

 Question 3: Finite State Machine Design [11 pts]

The following FSM represents a *Red Light, Green Light* game, where a player is only allowed to move forward ($M = 1$) when the light is green ($L = 1$). Here, the player wins (output $W = 1$) after successfully moving twice; moving when the light is red ($L = 0$) results in returning to the start.



- (A) How many total rows are in the truth table for this FSM? How many of the rows are filled with Don't Cares?

Rows:	Don't Care Rows:
-------	------------------

- (B) Complete the testbench `initial` block to *thoroughly* test JUST the Start and Mid states. You need to fill in all bolded blanks. You are welcome to fill out the Verilog comments to help you keep track of state, but these will not be graded. [7 pts]

```

initial begin
    L <= 0;      M <= 0;      // state: 0
    @(posedge clk); L <= ____; M <= ____; // state: ____
    @(posedge clk); L <= 1;   M <= 0;   // state: ____
    @(posedge clk); L <= 0;   M <= 1;   // state: ____
    @(posedge clk); L <= ____; M <= ____; // state: ____
    @(posedge clk); L <= 1;   M <= 0;   // state: ____
    @(posedge clk); L <= 1;   M <= 1;   // state: ____
    @(posedge clk); L <= ____; M <= ____; // state: ____
    @(posedge clk); L <= 1;   M <= 1;   // state: 1
    @(posedge clk);
    ... // test the Win state
    @(posedge clk);
    $stop();
end
  
```

- (C) If we change the game so that it takes THREE successful moves to win, what would your updated answers be for Part A? [2 pt]

Rows:	Don't Care Rows:
-------	------------------