

# CSE 369 QUIZ 3

Name: \_\_\_\_\_

UWNetID: \_\_\_\_\_

**Please do not turn the page until 10:30.**

## Instructions

- This quiz contains 4 pages, including this cover page.
- Show scratch work for partial credit, but put your final answers in the boxes and blanks provided.
- The quiz is closed book and closed notes.
- Please silence and put away all cell phones and other mobile or noise-making devices.
- Remove all hats, headphones, and watches.
- You have 35 minutes to complete this quiz.


## Advice

- Read questions carefully before starting. Read *all* questions first and start where you feel the most confident to maximize the use of your time.
- There may be partial credit for incomplete answers; please show your work.
- Relax. You are here to learn.

Question	Points	Score
(1) Building Blocks	12	
(2) Shift Registers	9	
(3) Rotate Right	11	
<b>Total:</b>	<b>32</b>	
 
### Question 1: Building Blocks [12 pts]

We want to build a **binary-to-braille decoder circuit**. Braille is represented by 6 dots, as shown below. Circles that are black/white represent LEDs that are on (1)/off (0), respectively. The binary-coded digit is given in bits  $N_3$ - $N_0$ .



Implement the *simplest* two-level logic for an *enabled* circuit below for the **left-middle dot (LM)**. You may use any 1- to 3-input logic gates discussed in the class.


- The dot should always be off (0) if Enable = 0
- Your truth table *will be graded*.

$N_3$	$N_2$	$N_1$	$N_0$	LM
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	



**Question 2: Shift Registers [9 pts]**

 - (A) We are designing a 3-bit LFSR to use as a pseudo-random number generator, but we only have a 2-input XOR gate available. Assuming we start in state **111**, which state bit ( $q_1$  or  $q_0$ ) should we connect along with  $q_2$  to the XOR gate in order to get the longest possible cycle? What is the length of the cycle we end up in? [5 pt]



Bits:	$q_2$ and _____
Cycle length:	

- (B) The Verilog code below is supposed to implement an *enabled* version of the LFSR above with bits  **$q_1$  and  $q_0$**  connected to the XOR gate. Find errors in the code and rewrite the offending *lines* in the boxes. [4 pt]

```

module LFSR (Q, enable, reset, clk);
  input          enable, reset, clk;
  output reg [2:0] Q;

  always_ff @(negedge clk)
    if ( reset )
      Q <= 3'b000;
    else if ( enable )
      Q <= { Q[0] ^ Q[1], Q[1], Q[0] };

endmodule

```

1)	
2)	
3)	

### Question 3: Rotate Right [11 pts]

A **rotate right** circuit is similar to a right shift, except that bits that are “shifted off” wrap around and get “shifted in” on the other side. For example, 0b1110 rotated right by 1 is 0b0111.

- (A) Below we show two *splitters*, which are used to “break out” busses into wires and vice-versa. Pay special attention to the wire numbering! Wire up the diagram below to perform the **rotate right by 1** operation between In and Out. [2 pts]



- (B) Assume the circuit from Part A can be represented as a block labeled “**rotr1**.” Using these blocks and routing elements, implement a **4-bit rotate right circuit** that takes in a 4-bit input and 2 select bits indicating how many times to rotate right (0-3). Make sure it is clear what the ports and directions are. [6 pts]



- (C) Chaining blocks together often leads to slower circuits, so Harry the Husky is arguing that we should re-implement our Part B circuit without the **rotr1** blocks. Do you agree with him? Why or why not? [3 pt]