

## Today

- Design Works Demo
- Sum of Products
- DeMorgan's Law
- Boolean simplification
- Reverse Engineering Example

Monday, April 10, 2000

1

CSE-370 Section

## Sum-of-Product & Product-of-Sum

- Sum of Product
  - see entries with value 1.
  - Ensure output 1 for those inputs. So **OR**
  - $A'B + AB'$
- Product of Sum
  - see entries with value 0
  - Ensure output 0 for those input. So **AND**
  - $(A+B)(A'+B')$

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

Monday, April 10, 2000

2

CSE-370 Section

## DeMorgan's Law

$$\overline{X + Y} = \overline{X} \cdot \overline{Y}$$

- Thus, the inversion doesn't distribute directly: it also changes the "or" to an "and"
- Dual:

$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$

Monday, April 10, 2000

3

CSE-370 Section

## DeMorgan's Examples

- Simplify:  $(A' + B + C)'$   
 $(A' + B + C)'$   
 $= AB'C'$
- Simplify:  $((A'B) + C)'$   
 $(A(B'C + D))'$   
 $= A' + (B'C + D)'$   
 $= A' + (B'C)'D'$   
 $= A' + (B + C)D'$


Monday, April 10, 2000

4

CSE-370 Section
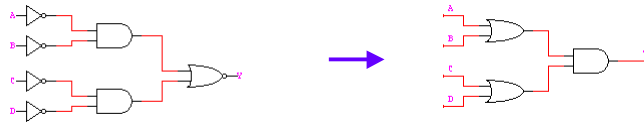
## DeMorgan's law on circuits

- You can do DeMorgan's law directly on the circuit:



Monday, April 10, 2000

5

CSE-370 Section

## Simplification

- Some important rules for simplification (how do you prove these?):
  - $AB + AB' = A$
  - $A + AB = A$
- Note that you can use the rules in either direction, to remove terms, or to add terms. Indeed, sometimes you need to add some terms in order to get to the simplest solution.

Monday, April 10, 2000

6

CSE-370 Section

## Examples

- Simplify:  $ab'c + abc + a'bc$   
 $ab'c + abc + a'bc$   
 $= ab'c + abc + abc + a'bc = ac + bc$
- Show that  $X + X'Y = X + Y$   
 $X + X'Y$   
 $= X(1 + Y) + X'Y$   
 $= X + XY + X'Y$   
 $= X + Y$

Monday, April 10, 2000

7

CSE-370 Section

## Examples (cont'd)

- Simplify:  $WX + XY + X'Z' + WY'Z'$   
 $WX + XY + X'Z' + WY'Z'$   
 $= WX + XY + X'Z' + WY'Z'X + WY'Z'X'$   
 $= WX(1 + Y'Z') + XY + X'Z'(1 + WY')$   
 $= WX + XY + X'Z'$

Monday, April 10, 2000

8

CSE-370 Section

## Long example

### Simplify:

$$\begin{aligned} & A'B'C'D' + A'BC'D' + A'BD + A'BC'D + ABCD + ACD' + B'CD' \\ &= A'C'D'(B' + B) + A'BD(1 + C') + ABCD + ACD' + B'CD' \\ &= A'C'D' + A'BD + ABCD + ACD' + B'CD' \\ &= A'C'D' + BD(A' + AC) + ACD' + B'CD' \\ &= A'C'D' + BD(A' + C) + ACD' + B'CD' \text{ (Since } X + X'Y = X + Y\text{)} \\ &= A'C'D' + A'BD + (BCD + ACD') + B'CD' \\ &= A'C'D' + A'BD + (BCD + ACD' + ABC) + B'CD' \\ &\quad \text{(Added } ABC \text{ by consensus)} \\ &= A'C'D' + (A'BD + ABC + BCD) + (ABC + B'CD' + ACD') \\ &= A'C'D' + A'BD + ABC + B'CD' \end{aligned}$$


Monday, April 10, 2000

9

CSE-370 Section

## Reverse Engineering Example

### Write down the Boolean expression:

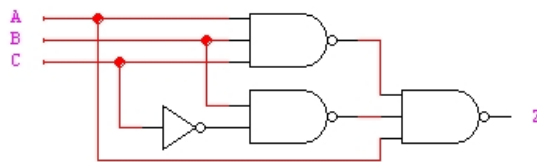

$$f(A, B, C) = \overline{ABC} \cdot \overline{BC} \cdot A$$

Monday, April 10, 2000

10

CSE-370 Section

## Reverse Engineering Ex (cont.)

- Simplify the function using Boolean algebra:

$$\begin{aligned} f(A, B, C) &= \overline{\overline{ABC}} \cdot \overline{\overline{BC}} \cdot \overline{\overline{A}} \\ &= ABC + \overline{BC} + \overline{A} && \text{DeMorgan's/Involution} \\ &= B(AC + \overline{C}) + \overline{A} && \text{Distributive} \\ &= B(A + \overline{C}) + \overline{A} && \text{Simplification} \\ &= AB + \overline{BC} + \overline{A} && \text{Distributive} \\ &= \overline{A} + B + \overline{BC} && \text{Simplification} \\ &= \overline{A} + B && \text{Simplification} \end{aligned}$$

Monday, April 10, 2000

11

CSE-370 Section

## Reverse Engineering Ex (cont.)

- Write the complete truth table for the circuit.

A	B	C	Z
0	0	0	1
	0	1	1
	1	0	1
	1	1	1
1	0	0	0
	0	1	0
	1	0	1
	1	1	1

Monday, April 10, 2000

12

CSE-370 Section

## Reverse Engineering Ex (cont.)

- Write the canonical SOP form.

$$f(A, B, C) = \overline{\overline{A}BC} + \overline{\overline{A}\overline{B}C} + \overline{\overline{A}B\overline{C}} + \overline{\overline{A}\overline{B}\overline{C}} + \overline{A\overline{B}\overline{C}} + \overline{A\overline{B}C}$$


Monday, April 10, 2000

13

CSE-370 Section

## Reverse Engineering Ex (cont.)

- Re-implement the better design.

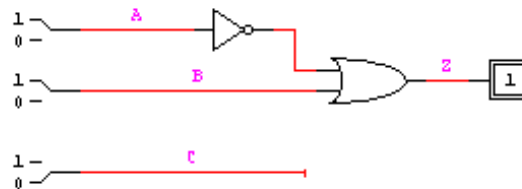

Monday, April 10, 2000

14

CSE-370 Section