


Combinational logic topics

- Logic functions, truth tables, and switches
 - NOT, AND, OR, NAND, NOR, XOR, ...
 - minimal set
- Axioms and theorems of Boolean algebra
 - proofs by re-writing
 - proofs by perfect induction
- Gate logic
 - networks of Boolean functions
 - time behavior
- Canonical forms
 - two-level
 - incompletely specified functions
- Simplification
 - Boolean cubes and Karnaugh maps
 - two-level simplification

CSE 370 - Spring 2001 - Combinational Logic - 1

Possible logic functions of two variables

- There are 16 possible functions of 2 input variables:
 - in general, there are 2^{2^n} functions of n inputs

 

CSE 370 - Spring 2001 - Combinational Logic - 2

Cost of different logic functions

- Different functions are easier or harder to implement
 - each has a cost associated with the number of switches needed
 - 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
 - X (F3) and Y (F5): require 0 switches, output is one of inputs
 - X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
 - X nor Y (F4) and X nand Y (F14): require 4 switches
 - X or Y (F7) and X and Y (F1): require 6 switches
 - X = Y (F9) and X \oplus Y (F6): require 16 switches
- thus, because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice

CSE 370 - Spring 2001 - Combinational Logic - 3

Minimal set of functions

- Can we implement all logic functions from NOT, NOR, and NAND?
 - For example, implementing X and Y is the same as implementing not (X nand Y)
 - In fact, we can do it with only NOR or only NAND
 - NOT is just a NAND or a NOR with both inputs tied together
- | X | Y | X nor Y | X | Y | X nand Y |
|---|---|---------|---|---|----------|
| 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 |
- NOR and NAND are "duals", that is, its easy to implement one using the other
 - $X \text{ nand } Y = \text{not} (\text{not } X \text{ nor } \text{not } Y)$
 - $X \text{ nor } Y = \text{not} (\text{not } X \text{ nand } \text{not } Y)$
 - But let's not move too fast. . .
 - let's look at the mathematical foundation of logic

CSE 370 - Spring 2001 - Combinational Logic - 4

An algebraic structure

- An algebraic structure consists of
 - a set of elements B
 - binary operations { + , \cdot }
 - and a unary operation { ' }
 - such that the following axioms hold:
- the set B contains at least two elements, a, b, such that $a \neq b$
 - closure: $a + b$ is in B $a \cdot b$ is in B
 - commutativity: $a + b = b + a$ $a \cdot b = b \cdot a$
 - associativity: $a + (b + c) = (a + b) + c$ $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
 - identity: $a + 0 = a$ $a \cdot 1 = a$
 - distributivity: $a + (b \cdot c) = (a + b) \cdot (a + c)$ $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
 - complementarity: $a + a' = 1$ $a \cdot a' = 0$

CSE 370 - Spring 2001 - Combinational Logic - 5

Boolean algebra

- Boolean algebra
 - $B = \{0, 1\}$
 - + is logical OR, \cdot is logical AND
 - ' is logical NOT
- All algebraic axioms hold

CSE 370 - Spring 2001 - Combinational Logic - 6

Logic functions and Boolean algebra

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: ', +, and •

X	Y	X+Y	X	Y	X'	X'•Y
0	0	0	0	0	1	0
0	1	1	0	1	1	1
1	0	1	1	0	0	0
1	1	1	1	1	0	0

X	Y	X'	Y'	X•Y	X'•Y'	(X•Y) + (X'•Y')
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \bullet Y) + (X' \bullet Y') = X = Y$$

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

X, Y are Boolean algebra variables

CSE 370 – Spring 2001 – Combinational Logic – 7

Axioms and theorems of Boolean algebra

- identity
 - $X + 0 = X$
 - $X \bullet 1 = X$
- null
 - $X + 1 = 1$
 - $X \bullet 0 = 0$
- idempotency:
 - $X + X = X$
 - $X \bullet X = X$
- involution:
 - $(X')' = X$
- complementarity:
 - $X + X' = 1$
 - $X \bullet X' = 0$
- commutativity:
 - $X + Y = Y + X$
 - $X \bullet Y = Y \bullet X$
- associativity:
 - $(X + Y) + Z = X + (Y + Z)$
 - $(X \bullet Y) \bullet Z = X \bullet (Y \bullet Z)$

CSE 370 – Spring 2001 – Combinational Logic – 8

Axioms and theorems of Boolean algebra (cont'd)

- distributivity:
 - $X \bullet (Y + Z) = (X \bullet Y) + (X \bullet Z)$
 - $X + (Y \bullet Z) = (X + Y) \bullet (X + Z)$
- uniting:
 - $X \bullet Y + X \bullet Y' = X$
 - $(X + Y) \bullet (X + Y') = X$
- absorption:
 - $X + X \bullet Y = X$
 - $X \bullet (X + Y) = X$
 - $(X + Y') \bullet Y = X \bullet Y$
 - $(X \bullet Y') + Y = X + Y$
- factoring:
 - $(X + Y) \bullet (X' + Z) = X \bullet Z + X' \bullet Y$
 - $X \bullet Y + X' \bullet Z = (X + Z) \bullet (X' + Y)$
- consensus:
 - $(X \bullet Y) + (Y \bullet Z) + (X' \bullet Z) = X \bullet Y + X' \bullet Z$
 - $(X + Y) \bullet (Y + Z) \bullet (X' + Z) = (X + Y) \bullet (X' + Z)$

CSE 370 – Spring 2001 – Combinational Logic – 9

Axioms and theorems of Boolean algebra (cont')

- de Morgan's:
 - $(X + Y + \dots)\' = X' \bullet Y' \bullet \dots$
 - $(X \bullet Y \bullet \dots)\' = X' + Y' + \dots$
- generalized de Morgan's:
 - $f(X_1, X_2, \dots, X_n, 0, 1, +, \bullet) = f(X_1', X_2', \dots, X_n', 1, 0, \bullet, +)$
- establishes relationship between • and +

CSE 370 – Spring 2001 – Combinational Logic – 10

Axioms and theorems of Boolean algebra (cont')

- Duality
 - a dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
 - any theorem that can be proven is thus also proven for its dual!
 - a meta-theorem (a theorem about theorems)
- duality:
 - $X + Y + \dots \Leftrightarrow X \bullet Y \bullet \dots$
- generalized duality:
 - $f(X_1, X_2, \dots, X_n, 0, 1, +, \bullet) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \bullet, +)$
- Different than deMorgan's Law
 - this is a statement about theorems
 - this is not a way to manipulate (re-write) expressions

CSE 370 – Spring 2001 – Combinational Logic – 11

Proving theorems (rewriting)

- Using the axioms of Boolean algebra:
 - e.g., prove the theorem: $X \bullet Y + X \bullet Y' = X$

distributivity (8)	$X \bullet Y + X \bullet Y' = X \bullet (Y + Y')$
complementarity (5)	$X \bullet (Y + Y') = X \bullet (1)$
identity (1D)	$X \bullet (1) = X$
 - e.g., prove the theorem: $X + X \bullet Y = X$

identity (1D)	$X + X \bullet Y = X \bullet 1 + X \bullet Y$
distributivity (8)	$X \bullet 1 + X \bullet Y = X \bullet (1 + Y)$
identity (2)	$X \bullet (1 + Y) = X \bullet (1)$
identity (1D)	$X \bullet (1) = X$

CSE 370 – Spring 2001 – Combinational Logic – 12

Proving theorems (perfect induction)

- Using perfect induction (complete truth table):
 - e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND
 with inputs complemented

X	Y	X'	Y'	(X + Y)'	X' · Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR
 with inputs complemented

X	Y	X'	Y'	(X · Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

A simple example

- 1-bit binary adder
 - inputs: A, B, Carry-in
 - outputs: Sum, Carry-out



A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

Apply the theorems to simplify expressions

- The theorems of Boolean algebra can simplify Boolean expressions
 - e.g., full adder's carry-out function (same rules apply to any function)

Cout = $A' B Cin + A B' Cin + A B Cin' + A B Cin$
 = $A' B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin$
 = $A' B Cin + A B Cin + A B' Cin + A B Cin' + A B Cin$
 = $(A' + A) B Cin + A B' Cin + A B Cin' + A B Cin$
 = $(1) B Cin + A B' Cin + A B Cin' + A B Cin$
 = $B Cin + A B' Cin + A B Cin' + A B Cin + A B Cin$
 = $B Cin + A B' Cin + A B Cin + A B Cin' + A B Cin$
 = $B Cin + A (B' + B) Cin + A B Cin' + A B Cin$
 = $B Cin + A (1) Cin + A B Cin' + A B Cin$
 = $B Cin + A Cin + A B (Cin' + Cin)$
 = $B Cin + A Cin + A B (1)$
 = $B Cin + A Cin + A B$

From Boolean expressions to logic gates

- NOT $X' \quad \bar{X} \quad \sim X$
- AND $X \cdot Y \quad XY \quad X \wedge Y$
- OR $X + Y \quad X \vee Y$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

From Boolean expressions to logic gates (cont'd)

- NAND $X \cdot Y$
- NOR $(X + Y)'$
- XOR $X \oplus Y$
- XNOR $X = Y$

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

From Boolean expressions to logic gates (cont'd)


- More than one way to map expressions to gates

 e.g., $Z = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$



Waveform view of logic functions


- Just a sideways truth table
 - but note how edges don't line up exactly
 - it takes time for a gate to switch its output!

 

CSE 370 - Spring 2001 - Combinational Logic - 19

Choosing different realizations of a function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

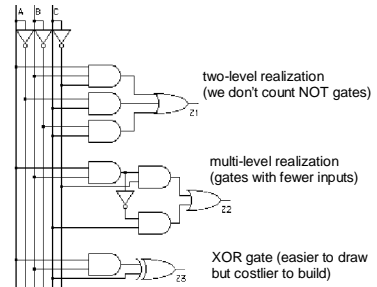

CSE 370 - Spring 2001 - Combinational Logic - 20

Which realization is best?

- Reduce number of inputs
 - literal: input variable (complemented or not)
 - can approximate cost of logic gate as 2 transistors per literal
 - why not count inverters?
 - fewer literals means less transistors
 - smaller circuits
 - fewer inputs implies faster gates
 - gates are smaller and thus also faster
 - fan-ins (# of gate inputs) are limited in some technologies
- Reduce number of gates
 - fewer gates (and the packages they come in) means smaller circuits
 - directly influences manufacturing costs

CSE 370 - Spring 2001 - Combinational Logic - 21


Which is the best realization? (cont'd)

- Reduce number of levels of gates
 - fewer level of gates implies reduced signal propagation delays
 - minimum delay configuration typically requires more gates
 - wider, less deep circuits
- How do we explore tradeoffs between increased circuit delay and size?
 - automated tools to generate different solutions
 - logic minimization: reduce number of gates and complexity
 - logic optimization: reduction while trading off against delay

CSE 370 - Spring 2001 - Combinational Logic - 22

Are all realizations equivalent?

- Under the same input stimuli, the three alternative implementations have almost the same waveform behavior
 - delays are different
 - glitches (hazards) may arise
 - variations due to differences in number of gate levels and structure
- The three implementations are functionally equivalent

 

CSE 370 - Spring 2001 - Combinational Logic - 23

Implementing Boolean functions

- Technology independent
 - canonical forms
 - two-level forms
 - multi-level forms
- Technology choices
 - packages of a few gates
 - regular logic
 - two-level programmable logic
 - multi-level programmable logic

CSE 370 - Spring 2001 - Combinational Logic - 24

Canonical forms

- Truth table is the unique signature of a Boolean function
- Many alternative gate realizations may have the same truth table
- Canonical forms
 - standard forms for a Boolean expression
 - provides a unique algebraic signature

Sum-of-products canonical forms

- Also known as disjunctive normal form
- Also known as minterm expansion

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = 001 \ 011 \ 101 \ 110 \ 111$
 $F = A'B'C' + A'BC' + AB'C' + ABC' + ABC$
 $F' = A'B'C' + A'BC' + AB'C'$

Sum-of-products canonical form (cont'd)

- Product term (or minterm)
 - ANDed product of literals – input combination for which output is true
 - each variable appears exactly once, in true or inverted form (but not both)

A	B	C	minterms
0	0	0	A'B'C' m0
0	0	1	A'B'C m1
0	1	0	A'BC' m2
0	1	1	A'BC m3
1	0	0	AB'C' m4
1	0	1	AB'C m5
1	1	0	ABC' m6
1	1	1	ABC m7

F in canonical form:
 $F(A, B, C) = \Sigma m(1,3,5,6,7)$
 $= m1 + m3 + m5 + m6 + m7$
 $= A'B'C + A'BC + AB'C + ABC' + ABC$
 canonical form \neq minimal form
 $F(A, B, C) = A'B'C + A'BC + AB'C + ABC' + ABC$
 $= (A'B' + A'B + AB' + AB)C + ABC'$
 $= ((A' + A)(B' + B))C + ABC'$
 $= C + ABC'$
 $= ABC' + C$
 $= AB + C$

short-hand notation for minterms of 3 variables

Product-of-sums canonical form

- Also known as conjunctive normal form
- Also known as maxterm expansion

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = 000 \ 010 \ 100$
 $F = (A + B + C) (A + B' + C) (A' + B + C)$
 $F' = (A + B + C) (A + B' + C) (A' + B + C) (A' + B' + C)$

Product-of-sums canonical form (cont'd)

- Sum term (or maxterm)
 - ORed sum of literals – input combination for which output is false
 - each variable appears exactly once, in true or inverted form (but not both)

A	B	C	maxterms
0	0	0	A+B+C M0
0	0	1	A+B+C' M1
0	1	0	A+B'+C M2
0	1	1	A+B'+C' M3
1	0	0	A'+B+C M4
1	0	1	A'+B+C' M5
1	1	0	A'+B'+C M6
1	1	1	A'+B'+C' M7


F in canonical form:
 $F(A, B, C) = \Pi M(0,2,4)$
 $= M0 \cdot M2 \cdot M4$
 $= (A + B + C) (A + B' + C) (A' + B + C)$
 canonical form \neq minimal form
 $F(A, B, C) = (A + B + C) (A + B' + C) (A' + B + C)$
 $= (A + B + C) (A + B' + C)$
 $= (A + B + C) (A' + B + C)$
 $= (A + C) (B + C)$

short-hand notation for maxterms of 3 variables

S-o-P, P-o-S, and de Morgan's theorem

- Sum-of-products
 - $F' = A'B'C' + A'BC' + AB'C'$
- Apply de Morgan's
 - $(F')' = (A'B'C' + A'BC' + AB'C')$
 - $F = (A + B + C) (A + B' + C) (A' + B + C)$
- Product-of-sums
 - $F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C')$
- Apply de Morgan's
 - $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C'))'$
 - $F = A'B'C + A'BC + AB'C + ABC$


Four alternative two-level implementations of $F = AB + C$

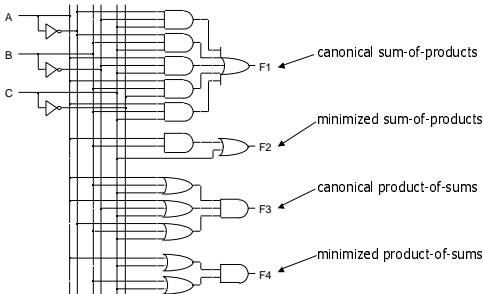

CSE 370 – Spring 2001 – Combinational Logic – 31

Waveforms for the four alternatives

- Waveforms are essentially identical
 - except for timing hazards (glitches)
 - delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)

 

CSE 370 – Spring 2001 – Combinational Logic – 32

Mapping between canonical forms

- Minterm to maxterm conversion
 - use maxterms whose indices do not appear in minterm expansion
 - e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7) = \Pi M(0,2,4)$
- Maxterm to minterm conversion
 - use minterms whose indices do not appear in maxterm expansion
 - e.g., $F(A,B,C) = \Pi M(0,2,4) = \Sigma m(1,3,5,6,7)$
- Minterm expansion of F to minterm expansion of F'
 - use minterms whose indices do not appear
 - e.g., $F(A,B,C) = \Sigma m(1,3,5,6,7)$ $F'(A,B,C) = \Sigma m(0,2,4)$
- Maxterm expansion of F to maxterm expansion of F'
 - use maxterms whose indices do not appear
 - e.g., $F(A,B,C) = \Pi M(0,2,4)$ $F'(A,B,C) = \Pi M(1,3,5,6,7)$

CSE 370 – Spring 2001 – Combinational Logic – 33

Incompletely specified functions

- Example: binary coded decimal increment by 1
 - BCD digits encode the decimal digits 0 – 9 in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0
0	0	1	0	0	1	1	0
0	0	1	1	1	0	0	0
0	1	0	0	1	0	1	0
0	1	0	1	1	1	0	0
0	1	1	0	1	0	1	0
0	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Annotations:

- off-set of W: (0,0,0,1), (0,0,1,0), (0,1,0,0), (0,1,0,1)
- on-set of W: (0,1,1,0), (0,1,1,1), (1,0,0,0), (1,0,0,1)
- don't care (DC) set of W: (1,0,1,0), (1,0,1,1), (1,1,0,0), (1,1,0,1), (1,1,1,0), (1,1,1,1)

 these inputs patterns should never be encountered in practice – "don't care" about associated output values, can be exploited in minimization

CSE 370 – Spring 2001 – Combinational Logic – 34

Notation for incompletely specified functions

- Don't cares and canonical forms
 - so far, only represented on-set
 - also represent don't-care-set
 - need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 - $Z = \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$

CSE 370 – Spring 2001 – Combinational Logic – 35


Simplification of two-level combinational logic

- Finding a minimal sum of products or product of sums realization
 - exploit don't care information in the process
- Algebraic simplification
 - not an algorithmic/systematic procedure
 - how do you know when the minimum realization has been found?
- Computer-aided design tools
 - precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - to understand automatic tools and their strengths and weaknesses
 - ability to check results (on small examples)

CSE 370 – Spring 2001 – Combinational Logic – 36

The uniting theorem


- Key tool to simplification: $A(B' + B) = A$
- Essence of simplification of two-level logic
 - find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

 

CSE 370 – Spring 2001 – Combinational Logic – 37

Boolean cubes


- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n-dimensional "cube"

 

CSE 370 – Spring 2001 – Combinational Logic – 38

Mapping truth tables onto Boolean cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:

 


CSE 370 – Spring 2001 – Combinational Logic – 39

Three variable example

- Binary full-adder carry-out logic


A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

CSE 370 – Spring 2001 – Combinational Logic – 40

Higher dimensional cubes

- Sub-cubes of higher dimension than 2

 

CSE 370 – Spring 2001 – Combinational Logic – 41

m-dimensional cubes in a n-dimensional Boolean space

- In a 3-cube (three variables):
 - a 0-cube, i.e., a single node, yields a term in 3 literals
 - a 1-cube, i.e., a line of two nodes, yields a term in 2 literals
 - a 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
 - a 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
 - an m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals

CSE 370 – Spring 2001 – Combinational Logic – 42

Karnaugh maps

- Flat map of Boolean cube
 - wrap-around at edges
 - hard to draw and visualize for more than 4 dimensions
 - virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
 - guide to applying the uniting theorem
 - on-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

	A	0	1	
B	0	1	1	
0	0	1	1	
1	0	0	0	

	A	B	F
0	0	0	1
0	0	1	0
1	0	1	1
1	1	1	0

CSE 370 – Spring 2001 – Combinational Logic – 43

Karnaugh maps (cont'd)


- Numbering scheme based on Gray-code
 - e.g., 00, 01, 11, 10
 - only a single bit changes in code for adjacent map cells

	AB	00	01	11	10
C	0	2	6	4	
1	3	7	5		

	A		
0	4	12	8
1	5	13	9
3	7	15	11
2	6	14	10

13 = 1101 = ABC'D


CSE 370 – Spring 2001 – Combinational Logic – 44

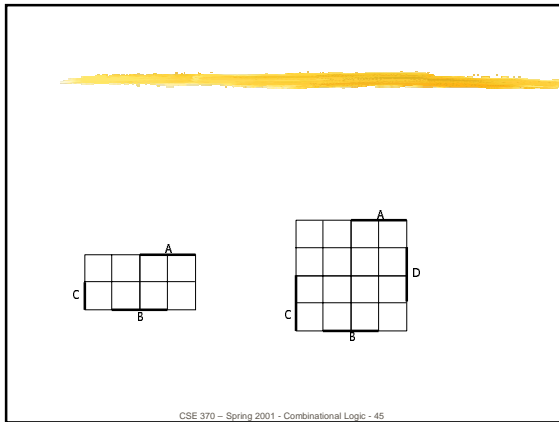

CSE 370 – Spring 2001 – Combinational Logic – 45

Adjacencies in Karnaugh maps

- Wrap from first to last column
- Wrap top row to bottom row

 

CSE 370 – Spring 2001 – Combinational Logic – 46

Karnaugh map examples

- $F =$
- Cout =
- $f(A,B,C) = \sum m(0,4,6,7)$

obtain the complement of the function by covering 0s with subcubes

CSE 370 – Spring 2001 – Combinational Logic – 47

More Karnaugh map examples


- $G(A,B,C) = A$
- $F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$
- F' simply replace 1's with 0's and vice versa
 $F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$

CSE 370 – Spring 2001 – Combinational Logic – 48

Karnaugh map: 4-variable example

$f(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$

$F = C + A'BD + B'D'$

 


find the smallest number of the largest possible subcubes to cover the ON-set (fewer terms with fewer inputs per term)

Karnaugh maps: don't cares

$f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

 
- without don't cares
- $f = A'D + B'C'D$



Karnaugh maps: don't cares (cont'd)

$f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

 
- $f = A'D + B'C'D$ without don't cares
- $f = A'D + C'D$ with don't cares



by using don't care as a "1" a 2-cube can be formed rather than a 1-cube to cover this node

don't cares can be treated as 1s or 0s depending on which is more advantageous

Design example: two-bit comparator

 


A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
0	0	1	1	0	0	0
0	1	0	0	1	0	0
0	1	1	1	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	0	1	0	1	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1


block diagram and truth table

we'll need a 4-variable Karnaugh map for each of the 3 output functions

 
Design example: two-bit comparator (cont'd)



K-map for LT

 

K-map for EQ

 

K-map for GT


$LT = A'B'D + A'C + B'CD$

$EQ = A'B'C'D' + A'B'C'D + ABCD + AB'CD' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$


$GT = B'C'D' + A'C + ABD'$

LT and GT are similar (flip A/C and B/D)

 Design example: two-bit comparator (cont'd)




 two alternative implementations of EQ with and without XOR



XNOR is implemented with at least 3 simple gates





Design example: 2x2-bit multiplier

 


A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	1

4-variable K-map for each of the 4 output functions

    Design example: 2x2-bit multiplier (cont'd)




Design example: BCD increment by 1

 


I8	I4	I2	I1	O8	O4	O2	O1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	1	0	0	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	1	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	0	0
1	0	0	1	X	X	X	X
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

4-variable K-map for each of the 4 output functions

 Design example: BCD increment by 1 (cont'd)




 
O8 = I4 I2 I1 + I8 I1'
O4 = I4 I2' + I4 I1' + I4' I2 I1
O2 = I8' I2' I1 + I2 I1'
O1 = I1'



Definition of terms for two-level simplification

- Implicant
 - single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- Prime implicant
 - implicant that can't be combined with another to form a larger subcube
- Essential prime implicant
 - prime implicant is essential if it alone covers an element of ON-set
 - will participate in ALL possible covers of the ON-set
 - DC-set used to form prime implicants but not to make implicant essential
- Objective:
 - grow implicant into prime implicants (minimize literals per term)
 - cover the ON-set with as few prime implicants as possible (minimize number of product terms)

Examples to illustrate terms

  


Algorithm for two-level simplification

- Algorithm: minimum sum-of-products expression from a Karnaugh map
 - Step 1: choose an element of the ON-set
 - Step 2: find "maximal" groupings of 1s and Xs adjacent to that element
 - consider top/bottom row, left/right column, and corner adjacencies
 - this forms prime implicants (number of elements always a power of 2)
 - Repeat Steps 1 and 2 to find all prime implicants
 - Step 3: revisit the 1s in the K-map
 - if covered by single prime implicant, it is essential, and participates in final cover
 - 1s covered by essential prime implicant do not need to be revisited
 - Step 4: if there remain 1s not covered by essential prime implicants
 - select the smallest number of prime implicants that cover the remaining 1s

CSE 370 – Spring 2001 – Combinational Logic – 61

Algorithm for two-level simplification (example)

 

CSE 370 – Spring 2001 – Combinational Logic – 62

Combinational logic summary

- Logic functions, truth tables, and switches
 - NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Axioms and theorems of Boolean algebra
 - proofs by re-writing and perfect induction
- Gate logic
 - networks of Boolean functions and their time behavior
- Canonical forms
 - two-level and incompletely specified functions
- Simplification
 - two-level simplification
- Later
 - automation of simplification
 - multi-level logic
 - design case studies
 - time behavior

CSE 370 – Spring 2001 – Combinational Logic – 63