


## Computer organization

- Computer design – an application of digital logic design procedures
- Computer = processing unit + memory system
- Processing unit = control + datapath
- Control = finite state machine
  - inputs = machine instruction, datapath conditions
  - outputs = register transfer control signals, ALU operation codes
  - instruction interpretation = instruction fetch, decode, execute
- Datapath = functional units + registers
  - functional units = ALU, multipliers, dividers, etc.
  - registers = program counter, shifters, storage registers

CSE 370 – Spring 2001 – Computer Organization - 1

## Structure of a computer


- Block diagram view

 

CSE 370 – Spring 2001 – Computer Organization - 2
 
## Registers

- Selectively loaded – EN or LD input
- Output enable – OE input
- Multiple registers – group 4 or 8 in parallel




OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)  
LD asserted during a b-to-hi clock transition loads new data into FFs


CSE 370 – Spring 2001 – Computer Organization - 3
 
## Register transfer: Some possibilities


- Point-to-point connection
  - dedicated wires
  - muxes on inputs of each register



 - Common input from multiplexer
  - load enables for each register
  - control signals for multiplexer




- Common bus with output enables
  - output enables and load enables for each register

 

CSE 370 – Spring 2001 – Computer Organization - 4

## Register files


- Collections of registers in one package
  - two-dimensional array of FFs
  - address used as index to a particular word
  - can have separate read and write addresses so can do both at same time
- 4 by 4 register file
  - 16 D-FFs
  - organized as four words of four bits each
  - write-enable (load)
  - read-enable (output enable)
- Register "indexes" are sometimes visible (to assembly language programmers)

 

CSE 370 – Spring 2001 – Computer Organization - 5

## Memories

- Larger collections of storage elements
  - implemented not as FFs but as much more efficient latches
  - high-density memories use 1 to 5 switches (transistors) per memory bit
- Static RAM – 1024 words each 4 bits wide
  - once written, memory holds forever (not true for denser dynamic RAM)
  - address lines to select word (10 lines for 1024 words)
  - read enable
    - same as output enable
    - often called chip select
    - permits connection of many chips into larger array
  - write enable (same as load enable)
  - bi-directional data lines
    - output when reading, input when writing

 

CSE 370 – Spring 2001 – Computer Organization - 6

## Instruction sequencing

- Example – an instruction to add the contents of two registers (Rx and Ry) and place result in a third register (Rz)
- Step 1: get the ADD instruction from memory into an instruction register
- Step 2: decode instruction
  - instruction in IR has the code of an ADD instruction
  - register indices used to generate output enables for registers Rx and Ry
  - register index used to generate load signal for register Rz
- Step 3: execute instruction
  - enable Rx and Ry output and direct to ALU
  - setup ALU to perform ADD operation
  - direct result to Rz so that it can be loaded into register

CSE 370 – Spring 2001 - Computer Organization - 7

## Instruction types

- Data manipulation instructions
  - arithmetic: add, subtract, increment, decrement
  - multiply/divide
  - shifts, bit-string ops, complements, etc.
  - floating point? usually a separate datapath
  - operands (data) may be from memory, from registers, or "immediate"*
- Data staging instruction
  - load/store data to/from memory
  - register-to-register move
- Control instructions
  - conditional/unconditional branches in program flow
  - subroutine call and return
- A different categorization of instructions: no-operands, 1 operand, etc.

CSE 370 – Spring 2001 - Computer Organization - 8


## Elements of the control unit (aka instruction unit)

- Control unit inputs/outputs
  - outputs control signals data path
  - inputs from data path used to alter flow of program (test if zero)
- Standard FSM elements
  - state register
  - next-state logic
  - output logic (datapath/control signaling)
  - Moore or synchronous Mealy machine to avoid loops unbroken by FF
- Plus additional "control" registers
  - instruction register (IR)
  - program counter (PC)

CSE 370 – Spring 2001 - Computer Organization - 9

## Instruction execution


- Control state diagram (for each diagram)
  - reset
  - fetch instruction (from memory)
  - decode
  - execute (perform operation)
- Instructions partitioned into three classes
  - branch
  - load/store
  - register-to-register
- Different sequence through diagram for each instruction type

 

CSE 370 – Spring 2001 - Computer Organization - 10

## Data path (hierarchy)


- Arithmetic circuits constructed in hierarchical and iterative fashion
  - each bit in datapath is functionally identical
  - 4-bit, 8-bit, 16-bit, 32-bit datapaths

 

CSE 370 – Spring 2001 - Computer Organization - 11

## Data path: Arithmetic Logic Unit


- ALU block diagram
  - input: data and operation to perform
  - output: result of operation and status information

 

CSE 370 – Spring 2001 - Computer Organization - 12

## Data path (ALU + registers)


- Accumulator (AC or A register)
  - special register found in many architectures
  - one of the inputs to ALU
  - output of ALU stored back in accumulator
- One-address instructions
  - operation and address of one operand
  - other operand and destination is accumulator register
  - $AC \leftarrow AC \text{ op Mem}[addr]$
  - "single address instructions" (AC implicit operand)
- Multiple registers
  - part of instruction used to choose register operands

 

CSE 370 – Spring 2001 - Computer Organization - 13

## Data path (bit-slice)

- Bit-slice concept – iterate to build n-bit wide datapaths

 

CSE 370 – Spring 2001 - Computer Organization - 14

## Instruction path

- Program counter (PC) [or Instruction Counter (IC)]
  - keeps track of program execution
  - address of next instruction to read from memory
  - may have auto-increment feature or use ALU
- Instruction register (IR)
  - current instruction
  - includes ALU operation and address of operand
  - also holds target of jump instruction
  - immediate operands
- Relationship to data path
  - PC may be incremented through ALU
  - contents of IR may also be required as input to ALU

CSE 370 – Spring 2001 - Computer Organization - 15

## Data path: memory interface

- Two Possible Memory Arrangements
  - separate data and instruction memory (Harvard architecture)
    - two address buses, two data buses
  - single combined memory (Princeton architecture)
    - single address bus, single data bus
- Common concepts
  - Memory Address Register (MAR): tells memory unit which *address* to read/write
  - Memory Buffer Register (MBR): contains *data* to/from memory
  - MAR and MBR might be separate registers labeled as such, or might be existing registers used for the purpose

CSE 370 – Spring 2001 - Computer Organization - 16


## Separate vs. Single Memory Organizations

- Separate memory
  - ALU output goes to data memory input
  - register input from data memory output
  - data memory address from instruction register
  - instruction register from instruction memory output
  - instruction memory address from program counter
- Single memory
  - address from PC or IR
  - memory output to instruction and data registers
  - memory input from ALU output

CSE 370 – Spring 2001 - Computer Organization - 17

## Block diagram of processor


- "Register transfer view" of Princeton architecture
  - emphasizes which register outputs are connected to which register inputs
  - arrows represent data-flow, other are control signals from control FSM
  - MAR may be a simple multiplexer rather than separate register
  - MBR is split in two (REG and IR)
  - load control for each register

 

CSE 370 – Spring 2001 - Computer Organization - 18

## Block diagram of processor


- Register transfer view of Harvard architecture
  - arrows represent data-flow, other are control signals from control FSM
  - PC and IR serve as MARs
  - REG and IR serve as MBRs
  - load control for each register

 

CSE 370 - Spring 2001 - Computer Organization - 19

## CSE370 processor data-path and memory


- Princeton architecture
- Register file
- Instruction register
- PC incremented through ALU
- Modeled after MIPS r1000 (used in 378 textbook by Patterson & Hennessy)
  - really a 32 bit machine
  - we'll do a 16 bit version

 

CSE 370 - Spring 2001 - Computer Organization - 20

## CSE370 processor control

- Synchronous Mealy machine
- Multiple cycles per instruction

 

CSE 370 - Spring 2001 - Computer Organization - 21

## CSE370 processor instructions

- Three principal types (1.6 bits in each instruction)

type	op	rs	rt	rd	funct
R(register)	3	3	3	3	4
I(mediate)	3	3	3	7	
J(jump)	3	13			

- Instructions we'll implement

	op	rs	rt	rd	offset	funct
R	add	0	rs	rt	rd	0
	sub	0	rs	rt	rd	1
	and	0	rs	rt	rd	2
	or	0	rs	rt	rd	3
	slt	0	rs	rt	rd	4
I	lw	1	rs	rt	offset	rt = mem[rs + offset]
	sw	2	rs	rt	offset	mem[rs + offset] = rt
	beq	3	rs	rt	offset	pc = pc + offset, if (rs == rt)
	addi	4	rs	rt	offset	rt = rs + offset
J	j	5			target address	pc = target address
	halt	7				stop execution until reset

CSE 370 - Spring 2001 - Computer Organization - 22

## Tracing an instruction's execution

- Instruction:  $r3 = r1 + r2$
- | R                     | 0 | ns=r1 | rt=r2 | rd=r3 | funct=0 |
|-----------------------|---|-------|-------|-------|---------|
| 1. instruction fetch  |   |       |       |       |         |
|                       |   |       |       |       |         |
| 2. instruction decode |   |       |       |       |         |
|                       |   |       |       |       |         |

CSE 370 - Spring 2001 - Computer Organization - 23

## Tracing an instruction's execution (cont'd)


- Instruction:  $r3 = r1 + r2$
- | R                      | 0 | ns=r1 | rt=r2 | rd=r3 | funct=0 |
|------------------------|---|-------|-------|-------|---------|
| 3. instruction execute |   |       |       |       |         |
|                        |   |       |       |       |         |

CSE 370 - Spring 2001 - Computer Organization - 24



### FSM controller for CPU (skeletal Moore FSM)


- First pass at deriving the state diagram (Moore or Mealy machine)
- these will be further refined into sub-states

 

CSE 370 - Spring 2001 - Computer Organization - 31

### FSM controller for CPU (skeletal sync. Mealy FSM)

- First pass at deriving the state diagram (synchronous Mealy machine)
- these will be further refined into sub-states

 


CSE 370 - Spring 2001 - Computer Organization - 32

### FSM controller for CPU (reset and inst. fetch)

- Assume Moore machine
- outputs associated with states rather than arcs
- Reset state and instruction fetch sequence
- On reset (go to Fetch state)
- start fetching instructions
- PC will set itself to zero


$mabus \leftarrow PC;$   
 $memory\ read;$   
 $IR \leftarrow memory\ data\ bus;$   
 $PC \leftarrow PC + 1;$

 

CSE 370 - Spring 2001 - Computer Organization - 33

### FSM controller for CPU (decode)


- Operation decode state
- next state branch based on operation code in instruction
- read two operands out of register file
- what if the instruction doesn't have two operands?

 

CSE 370 - Spring 2001 - Computer Organization - 34

### FSM controller for CPU (instruction execution)


- For add instruction
- configure ALU and store result in register
- $rd \leftarrow A + B$
- other instructions may require multiple cycles

 

CSE 370 - Spring 2001 - Computer Organization - 35

### FSM controller for CPU (add instruction)

- Putting it all together and closing the loop
- the famous instruction fetch decode execute cycle

 

CSE 370 - Spring 2001 - Computer Organization - 36

## FSM controller for CPU

- Now we need to repeat this for all the instructions of our processor
  - fetch and decode states stay the same
  - different execution states for each instruction
    - some may require multiple states