

## Hardware description languages

- ⌘ Describe hardware at varying levels of abstraction
- ⌘ Structural description
  - ☒ textual replacement for schematic
  - ☒ hierarchical composition of modules from primitives
- ⌘ Behavioral/functional description
  - ☒ describe what module does, not how
  - ☒ synthesis generates circuit for module
- ⌘ Simulation semantics

## HDLs

- ⌘ Abel (circa 1983) - developed by Data-I/O
  - ☒ targeted to programmable logic devices
  - ☒ not good for much more than state machines
- ⌘ ISP (circa 1977) - research project at CMU
  - ☒ simulation, but no synthesis
- ⌘ Verilog (circa 1985) - developed by Gateway (now part of Cadence)
  - ☒ similar to Pascal and C
  - ☒ delays is only interaction with simulator
  - ☒ fairly efficient and easy to write
  - ☒ IEEE standard
- ⌘ VHDL (circa 1987) - DoD sponsored standard
  - ☒ similar to Ada (emphasis on re-use and maintainability)
  - ☒ simulation semantics visible
  - ☒ very general but verbose
  - ☒ IEEE standard

## Verilog

- ⌘ Supports structural and behavioral descriptions
- ⌘ Structural
  - ☒ explicit structure of the circuit
  - ☒ e.g., each logic gate instantiated and connected to others
- ⌘ Behavioral
  - ☒ program describes input/output behavior of circuit
  - ☒ many structural implementations could have same behavior
  - ☒ e.g., different implementation of one Boolean function
- ⌘ We'll only be using behavioral Verilog
  - ☒ rely on schematic for structural constructs

## Structural model

```
module xor_gate (out, a, b);
  input    a, b;
  output   out;
  wire     abar, bbar, t1, t2;

  inverter invA (abar, a);
  inverter invB (bbar, b);
  and_gate and1 (t1, a, bbar);
  and_gate and2 (t2, b, abar);
  or_gate  or1 (out, t1, t2);

endmodule
```

## Simple behavioral model

⌘ Continuous assignment

```
module and_gate (out, in1, in2);
  input          in1, in2;
  output         out;
  reg            out;

  assign #2 out = in1 & in2;
endmodule
```

delay from input change  
to output change

## Simple behavioral model

⌘ always block

```
module and_gate (out, in1, in2);
  input          in1, in2;
  output         out;
  reg            out;

  always @(in1 or in2) begin
    #2 out = in1 & in2;
  end
endmodule
```

simulation register -  
keeps track of  
value of signal

specifies when block is executed  
ie. triggered by which signals

## Driving a simulation

```
module stimulus (a, b);  
  output      a, b;  
  reg [1:0]   cnt;  
  
  initial begin  
    cnt = 0;  
    repeat (4) begin  
      #10 cnt = cnt + 1;  
      $display ("@ time=%d, a=%b, b=%b, cnt=%b",  
        $time, a, b, cnt); end  
    #10 $finish;  
  end  
  
  assign a = cnt[1];  
  assign b = cnt[0];  
endmodule
```

2-bit vector

initial block executed only once at start of simulation


print to a console

directive to stop simulation

CSE 370 - Winter 200 - Hardware Description Languages - 7

## Complete Simulation

⌘ Instantiate stimulus component and device to test in a schematic

 

CSE 370 - Winter 200 - Hardware Description Languages - 8

## Comparator Example

```
module Compare1 (A, B, Equal, Alarger, Blarger);
  input      A, B;
  output     Equal, Alarger, Blarger;

  assign #5 Equal = (A & B) | (~A & ~B);
  assign #3 Alarger = (A & ~B);
  assign #3 Blarger = (~A & B);
endmodule
```

## Hardware Description Languages vs. Programming Languages

- ⌘ Program structure
  - ☒ instantiation of multiple components of the same type
  - ☒ specify interconnections between modules via schematic
  - ☒ hierarchy of modules (only leaves can be HDL in DesignWorks)
- ⌘ Assignment
  - ☒ continuous assignment (logic always computes)
  - ☒ propagation delay (computation takes time)
  - ☒ timing of signals is important (when does computation have its effect)
- ⌘ Data structures
  - ☒ size explicitly spelled out - no dynamic structures
  - ☒ no pointers
- ⌘ Parallelism
  - ☒ hardware is naturally parallel (must support multiple threads)
  - ☒ assignments can occur in parallel (not just sequentially)