


Timing methodologies

- ⌘ Rules for interconnecting components and clocks
 - ☑ guarantee proper operation of system when strictly followed
- ⌘ Approach depends on building blocks used for memory elements
 - ☑ we'll focus on systems with edge-triggered flip-flops
 - ☑ found in programmable logic devices
 - ☑ many custom integrated circuits focus on level-sensitive latches
- ⌘ Basic rules for correct timing:
 - ☑ (1) correct inputs, with respect to time, are provided to the flip-flops
 - ☑ (2) no flip-flop changes state more than once per clocking event

CSE 370 - Spring 2001 - Sequential Logic - 1


Timing methodologies (cont'd)

- ⌘ Definition of terms
 - ☑ clock: periodic event, causes state of memory element to change can be rising edge or falling edge or high level or low level
 - ☑ setup time: minimum time before the clocking event by which the input must be stable (T_{su})
 - ☑ hold time: minimum time after the clocking event until which the input must remain stable (T_h)

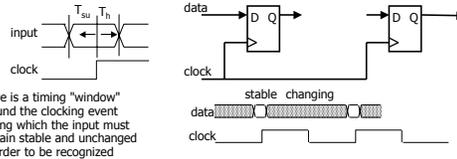

CSE 370 - Spring 2001 - Sequential Logic - 2

Comparison of latches and flip-flops

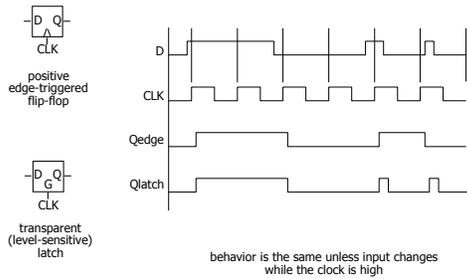

CSE 370 - Spring 2001 - Sequential Logic - 3


Comparison of latches and flip-flops (cont'd)

Type	When inputs are sampled	When output is valid
unclocked latch	always	propagation delay from input change
level-sensitive latch	clock high (T_{su}/T_h around falling edge of clock)	propagation delay from input change or clock edge (whichever is later)
master-slave flip-flop	clock high (T_{su}/T_h around falling edge of clock)	propagation delay from falling edge of clock
negative edge-triggered flip-flop	clock hi-to-lo transition (T_{su}/T_h around falling edge of clock)	propagation delay from falling edge of clock

CSE 370 - Spring 2001 - Sequential Logic - 4

Typical timing specifications


- ⌘ Positive edge-triggered D flip-flop
 - ☑ setup and hold times
 - ☑ minimum clock width
 - ☑ propagation delays (low to high, high to low, max and typical)

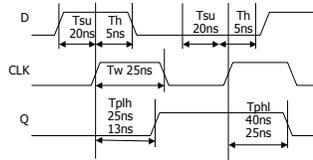

CSE 370 - Spring 2001 - Sequential Logic - 5

Cascading edge-triggered flip-flops

- ⌘ Shift register
 - ☑ new value goes into first stage
 - ☑ while previous value of first stage goes into second stage
 - ☑ consider setup/hold/propagation delays (prop must be > hold)

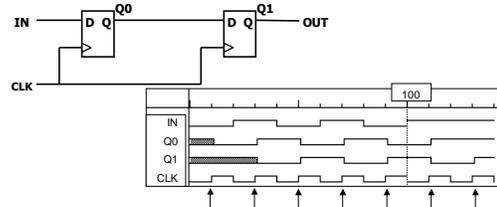


CSE 370 - Spring 2001 - Sequential Logic - 6

Cascading edge-triggered flip-flops (cont'd)

Why this works

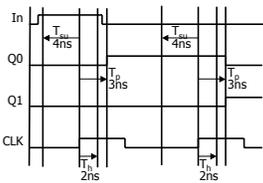- ☑ propagation delays exceed hold times
- ☑ clock width constraint exceeds setup time
- ☑ this guarantees following stage will latch current value before it changes to new value



timing constraints guarantee proper operation of cascaded components


assumes infinitely fast distribution of the clock

CSE 370 - Spring 2001 - Sequential Logic - 7

Clock skew

The problem

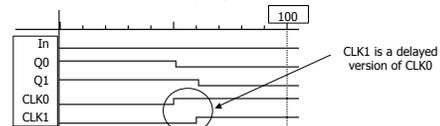- ☑ correct behavior assumes next state of all storage elements determined by all storage elements at the same time
- ☑ this is difficult in high-performance systems because time for clock to arrive at flip-flop is comparable to delays through logic
- ☑ effect of skew on cascaded flip-flops:



original state: IN = 0, Q0 = 1, Q1 = 1
due to skew, next state becomes: Q0 = 0, Q1 = 0, and not Q0 = 0, Q1 = 1

CSE 370 - Spring 2001 - Sequential Logic - 8

Summary of latches and flip-flops

Development of D-FF

- ☑ level-sensitive used in custom integrated circuits
 - ☑ can be made with 4 switches
- ☑ edge-triggered used in programmable logic devices
 - ☑ good choice for data storage register
- ☑ Historically J-K FF was popular but now never used
 - ☑ similar to R-S but with 1-1 being used to toggle output (complement state)
 - ☑ good in days of TTL/SSI (more complex input function: $D = JQ' + KQ$)
 - ☑ not a good choice for PALs/PLAs as it requires 2 inputs
 - ☑ can always be implemented using D-FF
- ☑ Preset and clear inputs are highly desirable on flip-flops
 - ☑ used at start-up or to reset system to a known state

CSE 370 - Spring 2001 - Sequential Logic - 9

Metastability and asynchronous inputs

Clocked synchronous circuits

- ☑ inputs, state, and outputs sampled or changed in relation to a common reference signal (called the clock)
- ☑ e.g., master/slave, edge-triggered

Asynchronous circuits

- ☑ inputs, state, and outputs sampled or changed independently of a common reference signal (glitches/hazards a major concern)
- ☑ e.g., R-S latch

Asynchronous inputs to synchronous circuits


- ☑ inputs can change at any time, will not meet setup/hold times
- ☑ dangerous, synchronous inputs are greatly preferred
- ☑ cannot be avoided (e.g., reset signal, memory wait, user input)

CSE 370 - Spring 2001 - Sequential Logic - 10


Synchronization failure

Occurs when FF input changes close to clock edge

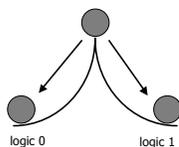- ☑ the FF may enter a metastable state - neither a logic 0 nor 1 -
- ☑ it may stay in this state an indefinite amount of time
- ☑ this is not likely in practice but has some probability



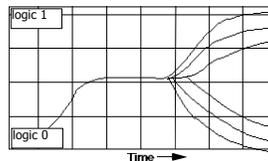small, but non-zero probability that the FF output will get stuck in an in-between state




oscilloscope traces demonstrating synchronizer failure and eventual decay to steady state

CSE 370 - Spring 2001 - Sequential Logic - 11

Dealing with synchronization failure

Probability of failure can never be reduced to 0, but it can be reduced


- (1) slow down the system clock
 - this gives the synchronizer more time to decay into a steady state; synchronizer failure becomes a big problem for very high speed systems
- (2) use fastest possible logic technology in the synchronizer
 - this makes for a very sharp "peak" upon which to balance
- (3) cascade two synchronizers
 - this effectively synchronizes twice (both would have to fail)

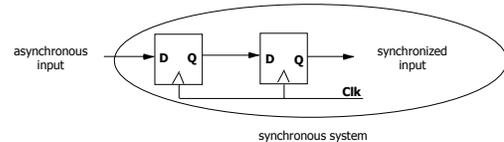

CSE 370 - Spring 2001 - Sequential Logic - 12

Handling asynchronous inputs


- ⌘ Never allow asynchronous inputs to fan-out to more than one flip-flop
- ☑ synchronize as soon as possible and then treat as synchronous signal

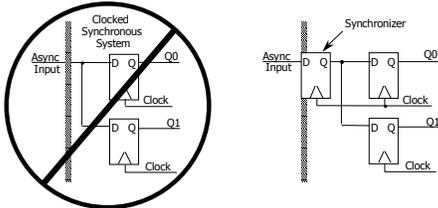

CSE 370 - Spring 2001 - Sequential Logic - 13

Handling asynchronous inputs (cont'd)

- ⌘ What can go wrong?
- ☑ input changes too close to clock edge (violating setup time constraint)

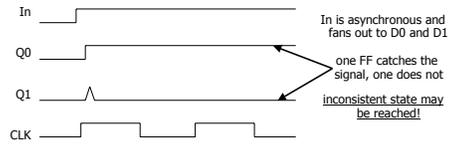

CSE 370 - Spring 2001 - Sequential Logic - 14