

## Combinational Logic Technologies

- ⌘ Standard gates
  - ☒ gate packages
  - ☒ cell libraries
- ⌘ Regular logic
  - ☒ multiplexers
  - ☒ decoders
- ⌘ Two-level programmable logic
  - ☒ PALs
  - ☒ PLAs
  - ☒ ROMs

## Random logic

- ⌘ Transistors quickly integrated into logic gates (1960s)
- ⌘ Catalog of common gates (1970s)
  - ☒ Texas Instruments Logic Data Book – the yellow bible
  - ☒ all common packages listed and characterized (delays, power)
  - ☒ typical packages:
    - ☒ in 14-pin IC: 6-inverters, 4 NAND gates, 4 XOR gates
- ⌘ Today, very few parts are still in use
- ⌘ However, parts libraries exist for chip design
  - ☒ designers reuse already characterized logic gates on chips
  - ☒ same reasons as before
  - ☒ difference is that the parts don't exist in physical inventory – created as needed

## Random logic


- ⌘ Too hard to figure out exactly what gates to use
  - ☒ map from logic to NAND/NOR networks
  - ☒ determine minimum number of packages
    - ☒ slight changes to logic function could decrease cost
- ⌘ Changes to difficult to realize
  - ☒ need to rewire parts
  - ☒ may need new parts
  - ☒ design with spares (few extra inverters and gates on every board)

## Regular logic

- ⌘ Need to make design faster
- ⌘ Need to make engineering changes easier to make
- ⌘ Simpler for designers to understand and map to functionality
  - ☒ harder to think in terms of specific gates
  - ☒ better to think in terms of a large multi-purpose block

 
## Making connections

- ⌘ Direct point-to-point connections between gates
  - ☐ wires we've seen so far
- ⌘ Route one of many inputs to a single output --- multiplexer
- ⌘ Route a single input to one of many outputs --- demultiplexer



 
## Mux and demux

- ⌘ Switch implementation of multiplexers and demultiplexers
  - ☐ can be composed to make arbitrary size switching networks
  - ☐ used to implement multiple-source/multiple-destination interconnections


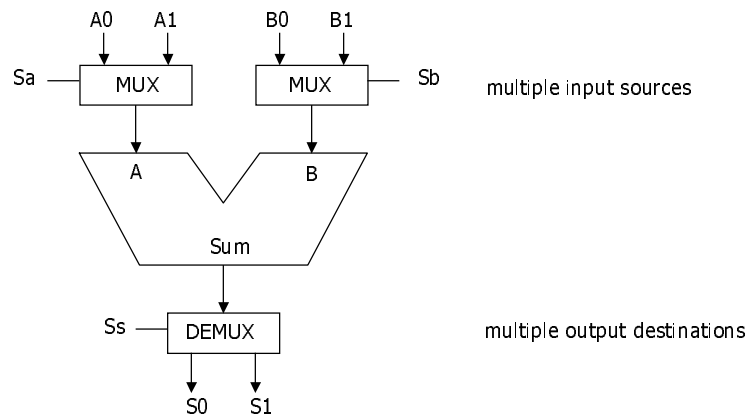
## Mux and demux (cont'd)

⌘ Uses of multiplexers/demultiplexers in multi-point connections



## Multiplexers/selectors

⌘ Multiplexers/selectors: general concept

- ☑  $2^n$  data inputs,  $n$  control inputs (called "selects"), 1 output
- ☑ used to connect  $2^n$  points to a single point
- ☑ control signal pattern forms binary index of input connected to output

$$Z = A' I_0 + A I_1$$

A	Z
0	$I_0$
1	$I_1$

functional form

logical form

$I_1$	$I_0$	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

two alternative forms for a 2:1 Mux truth table

## Multiplexers/selectors (cont'd)




⌘ 2:1 mux:  $Z = A' I_0 + A I_1$

⌘ 4:1 mux:  $Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$

⌘ 8:1 mux:  $Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$


⌘ In general:  $Z = \sum_{k=0}^{2^n-1} (m_k I_k)$

   ☒ in minterm shorthand form for a  $2^n:1$  Mux




## Gate level implementation of muxes

⌘ 2:1 mux

 


⌘ 4:1 mux

 

 
## Cascading multiplexers

⌘ Large multiplexers can be implemented by cascading smaller ones



control signals B and C simultaneously choose one of I0, I1, I2, I3 and one of I4, I5, I6, I7

 control signal A chooses which of the upper or lower mux's output to gate to Z




## Multiplexers as general-purpose logic

⌘ A  $2^n:1$  multiplexer can implement any function of  $n$  variables

- ☑ with the variables used as control inputs and
- ☑ the data inputs tied to 0 or 1
- ☑ in essence, a lookup table

⌘ Example:
 
$$\begin{aligned} \square F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\ &= A'B'C' + A'BC' + ABC' + ABC \\ &= A'B'(C') + A'B'(C) + AB'(0) + AB(1) \end{aligned}$$




## Multiplexers as general-purpose logic (cont'd)

⌘ A  $2^{n-1}:1$  multiplexer can implement any function of  $n$  variables


- ☑ with  $n-1$  variables used as control inputs and
- ☑ the data inputs tied to the last variable or its complement

⌘ Example:
 
$$\begin{aligned} \square F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\ &= A'B'C' + A'BC' + ABC' + ABC \\ &= A'B'(C') + A'B(C') + AB'(0) + AB(1) \end{aligned}$$



A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

## Multiplexers as general-purpose logic (cont'd)

⌘ Generalization

$n-1$  mux control variables  
single mux data variable

$I_0$	$I_1$	...	$I_{n-1}$	$I_n$
.	.	.	.	0
.	.	.	.	1

		F	
0	1	0	1
1	0	1	0
$I_n$	$I_n'$	1	0
0	1	0	1


four possible configurations of truth table rows can be expressed as a function of  $I_n$

⌘ Example:  $G(A,B,C,D)$  can be implemented by an 8:1 MUX

choose A,B,C as control variables

multiplexer implementation

A	B	C	D	G
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

 

## Activity

- ⌘ Map the following equation to an 4:1 multiplexer using a minimum of external gates:



## Demultiplexers/decoders

- ⌘ Decoders/demultiplexers: general concept

- single data input, n control inputs,  $2^n$  outputs
- control inputs (called "selects" (S)) represent binary index of output to which the input is connected
- data input usually called "enable" (G)

1:2 Decoder:

$$\begin{aligned} O0 &= G \cdot S' \\ O1 &= G \cdot S \end{aligned}$$

2:4 Decoder:

$$\begin{aligned} O0 &= G \cdot S1' \cdot S0' \\ O1 &= G \cdot S1' \cdot S0 \\ O2 &= G \cdot S1 \cdot S0' \\ O3 &= G \cdot S1 \cdot S0 \end{aligned}$$

3:8 Decoder:


$$\begin{aligned} O0 &= G \cdot S2' \cdot S1' \cdot S0' \\ O1 &= G \cdot S2' \cdot S1' \cdot S0 \\ O2 &= G \cdot S2' \cdot S1 \cdot S0' \\ O3 &= G \cdot S2' \cdot S1 \cdot S0 \\ O4 &= G \cdot S2 \cdot S1' \cdot S0' \\ O5 &= G \cdot S2 \cdot S1' \cdot S0 \\ O6 &= G \cdot S2 \cdot S1 \cdot S0' \\ O7 &= G \cdot S2 \cdot S1 \cdot S0 \end{aligned}$$




## Gate level implementation of demultiplexers

### ⌘ 1:2 decoders



active-high enable

 

active-low enable

 


### ⌘ 2:4 decoders

  

## Demultiplexers as general-purpose logic
 
### ⌘ A $n:2^n$ decoder can implement any function of $n$ variables

- ☑ with the variables used as control inputs
- ☑ the enable inputs tied to 1 and
- ☑ the appropriate minterms summed to form the function




demultiplexer generates appropriate minterm based on control signals (it "decodes" control signals)

## Demultiplexers as general-purpose logic (cont'd)

⌘  $F1 = A'BC'D + A'B'CD + ABCD$

⌘  $F2 = ABC'D' + ABC$

⌘  $F3 = (A' + B' + C' + D')$

 


## Cascading decoders

⌘ 5:32 decoder


☒ 1x2:4 decoder

☒ 4x3:8 decoders

 
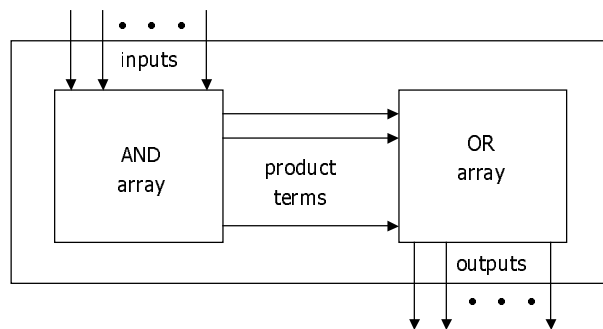
## Programmable logic arrays

- ⌘ Pre-fabricated building block of many AND/OR gates
  - ☒ actually NOR or NAND
  - ☒ "personalized" by making or breaking connections among the gates
  - ☒ programmable array block diagram for sum of products form



## Enabling concept

- ⌘ Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

personality matrix

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

input side:

1 = uncomplemented in term  
 0 = complemented in term  
 - = does not participate

output side:


1 = term connected to output  
 0 = no connection to output

reuse of terms
 
## Before programming

⌘ All possible connections are available before "programming"

☒ in reality, all AND and OR gates are NANDs




## After programming

⌘ Unwanted connections are "blown"

☒ fuse (normally connected, break unwanted ones)

 
☒ anti-fuse (normally disconnected, make wanted connections)


 
## Alternate representation for high fan-in structures

⌘ Short-hand notation so we don't have to draw all the wires


☒ × signifies a connection is present and perpendicular signal is an input to gate



notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

 

## Programmable logic array example

⌘ Multiple functions of A, B, C

☒  $F1 = A B C$

☒  $F2 = A + B + C$


☒  $F3 = A' B' C'$

☒  $F4 = A' + B' + C'$

☒  $F5 = A \text{ xor } B \text{ xor } C$

☒  $F6 = A \text{ xnor } B \text{ xnor } C$

A	B	C	F1	F2	F3	F4	F5	F6
0	0	0	0	0	1	1	0	0
0	0	1	0	1	0	1	1	1
0	1	0	0	1	0	1	1	1
0	1	1	0	1	0	1	0	0
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	0
1	1	0	0	1	0	1	0	0
1	1	1	1	1	0	0	1	1

 

## PALs and PLAs


### ⌘ Programmable logic array (PLA)

- ☑ what we've seen so far
- ☑ unconstrained fully-general AND and OR arrays
 
### ⌘ Programmable array logic (PAL)

- ☑ constrained topology of the OR array
- ☑ innovation by Monolithic Memories
- ☑ faster and smaller OR plane

a given column of the OR array has access to only a subset of the possible product terms



## PALs and PLAs: design example

### ⌘ BCD to Gray code converter

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	-	-	-	-	-
1	1	-	-	-	-	-	-

minimized functions:

$$W = A + B D + B C$$


$$X = B C'$$

$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

## PALs and PLAs: design example (cont'd)

### ⌘ Code converter: programmed PLA

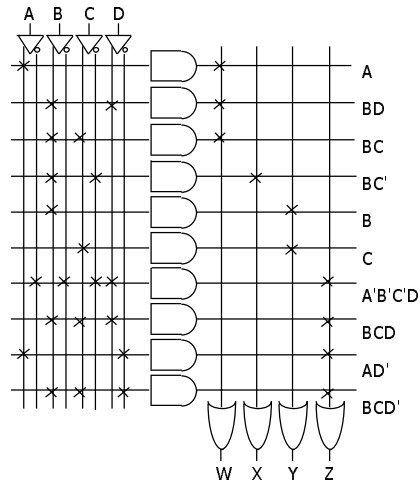

minimized functions:

$$\begin{aligned} W &= A + BD + BC \\ X &= B C \\ Y &= B + C \\ Z &= A'B'C'D + B C D + A D' + B' C D' \end{aligned}$$


not a particularly good candidate for PAL/PLA implementation since no terms are shared among outputs

however, much more compact and regular implementation when compared with discrete AND and OR gates

## PALs and PLAs: design example (cont'd)

### ⌘ Code converter: programmed PAL


4 product terms per each OR gate

 

## PALs and PLAs: design example (cont'd)
 
### ⌘ Code converter: NAND gate implementation

- ☒ loss of regularity, harder to understand
- ☒ harder to make changes



## PALs and PLAs: another design example

### ⌘ Magnitude comparator

A	B	C	D	EQ	NE	LT	GT
0	0	0	0	1	0	0	0
0	0	0	1	0	1	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	1	0	0	0
0	1	1	0	0	1	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	0	1
1	0	1	0	1	0	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	1
1	1	0	1	0	1	0	1
1	1	1	0	0	1	0	1
1	1	1	1	1	0	0	0


minimized functions:

$$EQ = A'B'C'D' + A'BC'D + ABCD + AB'CD'$$

$$LT = A'C + A'B'D + B'CD$$

$$NE = AC' + A'C + B'D + BD'$$

$$GT = AC' + ABC + BC'D'$$

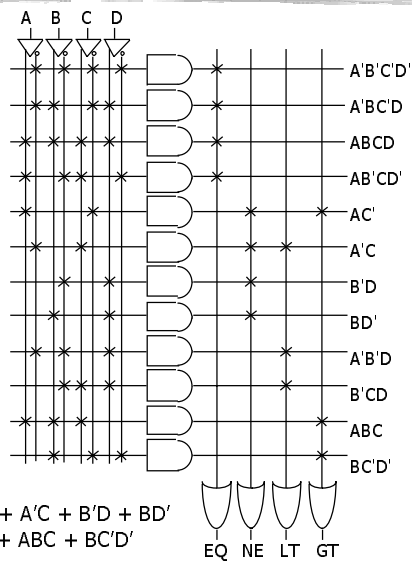




## Activity

⌘ Map the following functions to the PLA below:


$$\square W = AB + A'C' + BC'$$

$$\square X = ABC + AB' + A'B$$

$$\square Y = ABC' + BC + B'C'$$

 

## Activity (cont'd)

 


## Read-only memories

### ⌘ Two dimensional array of 1s and 0s

- ☒ entry (row) is called a "word"
- ☒ width of row = word-size
- ☒ index is called an "address"
- ☒ address is input
- ☒ selected word is output

internal organization

 

## ROMs and combinational logic

### ⌘ Combinational logic implementation (two-level canonical form) using a ROM

$$F0 = A' B' C + A B' C' + A B' C$$


$$F1 = A' B' C + A' B C' + A B C$$

$$F2 = A' B' C' + A' B' C + A B' C'$$

$$F3 = A' B C + A B' C' + A B C'$$

A	B	C	F0	F1	F2	F3
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	1	0	0
0	1	1	0	0	0	1
1	0	0	1	0	1	1
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	1	0	1	0	0


truth table

 

block diagram
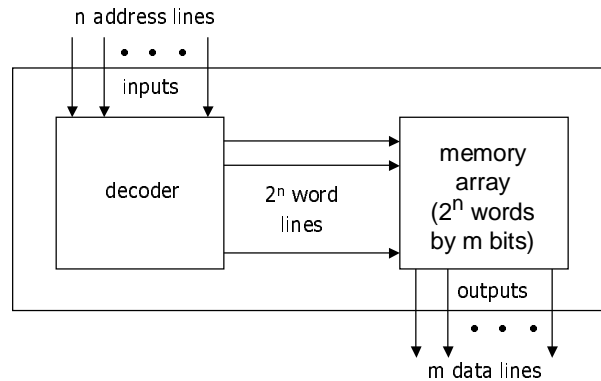
## ROM structure

- ⌘ Similar to a PLA structure but with a fully decoded AND array
  - ☑ completely flexible OR array (unlike PAL)



## ROM vs. PLA

- ⌘ ROM approach advantageous when
  - ☑ design time is short (no need to minimize output functions)
  - ☑ most input combinations are needed (e.g., code converters)
  - ☑ little sharing of product terms among output functions
- ⌘ ROM problems
  - ☑ size doubles for each additional input
  - ☑ can't exploit don't cares
- ⌘ PLA approach advantageous when
  - ☑ design tools are available for multi-output minimization
  - ☑ there are relatively few unique minterm combinations
  - ☑ many minterms are shared among the output functions
- ⌘ PAL problems
  - ☑ constrained fan-ins on OR plane

## Regular logic structures for two-level logic

- ⌘ ROM – full AND plane, general OR plane
  - ☒ cheap (high-volume component)
  - ☒ can implement any function of n inputs
  - ☒ medium speed
- ⌘ PAL – programmable AND plane, fixed OR plane
  - ☒ intermediate cost
  - ☒ can implement functions limited by number of terms
  - ☒ high speed (only one programmable plane that is much smaller than ROM's decoder)
- ⌘ PLA – programmable AND and OR planes
  - ☒ most expensive (most complex in design, need more sophisticated tools)
  - ☒ can implement any function up to a product term limit
  - ☒ slow (two programmable planes)

## Regular logic structures for multi-level logic

- ⌘ Difficult to devise a regular structure for arbitrary connections between a large set of different types of gates
  - ☒ efficiency/speed concerns for such a structure
  - ☒ in 467 you'll learn about field programmable gate arrays (FPGAs) that are just such programmable multi-level structures
    - ☒ programmable multiplexers for wiring
    - ☒ lookup tables for logic functions (programming fills in the table)
    - ☒ multi-purpose cells (utilization is the big issue)
- ⌘ Use multiple levels of PALs/PLAs/ROMs
  - ☒ output intermediate result
  - ☒ make it an input to be used in further logic

## Combinational logic technology summary

### ⌘ Random logic

- ☒ Single gates or in groups
- ☒ conversion to NAND-NAND and NOR-NOR networks
- ☒ transition from simple gates to more complex gate building blocks
- ☒ reduced gate count, fan-ins, potentially faster
- ☒ more levels, harder to design

### ⌘ Time response in combinational networks

- ☒ gate delays and timing waveforms
- ☒ hazards/glitches (what they are and why they happen)

### ⌘ Regular logic

- ☒ multiplexers/decoders
- ☒ ROMs
- ☒ PLAs/PALs
- ☒ advantages/disadvantages of each