 


## Overview

- ◆ Last lecture
  - Cascading flip-flops
  - Clock skew
  - Registers
- ◆ Today
  - Introduction to finite state machines
    - State diagrams
  - Counters as finite state machines
    - Counter design


## State machines

- ◆ Combinational logic and storage elements
  - Localized feedback loops
  - Choice of storage elements alters the logic
    - D flip-flop, T flip-flop, etc.



 
## Asynchronous versus synchronous

- ◆ Asynchronous
  - State changes occur when state inputs change
  - Feedback elements may be wires or delays
- ◆ Synchronous
  - State changes occur synchronously
  - Feedback elements are clocked



 
## Finite-state machines

- ◆ States: Possible storage-element values
- ◆ Transitions: Changes in state
  - Clock synchronizes the state changes
- ◆ Sequential logic
  - Sequences through a series of states
  - Based on inputs and present state



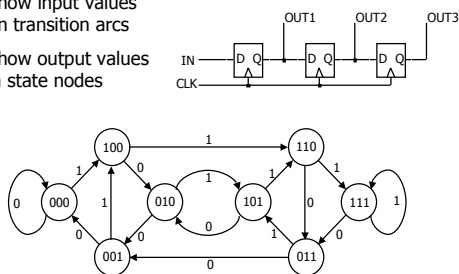
## Drawing state diagrams

- ◆ Show input values on transition arcs
- ◆ Show output values in state nodes


 
## Begin by studying counters

- ◆ Simple state machines
  - Output is the counter's state
- ◆ Next state is well defined
  - Does not depend on input (no inputs)




## Counter design procedure

1. Draw a state diagram
2. Draw a state-transition table
3. Encode the next-state functions
  - Minimize the logic using k-maps
4. Implement the design


*Example: Design the 3-bit up counter*

## 1. Draw a state diagram

 
 
## 2. Draw a state-transition table


- Like a truth-table
  - State encoding is easy for counters → Use count value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0


## 3. Encode the next state functions

- Assume D flip-flops as state elements

 
 
## 4. Implement the design


- 3 flip-flops hold state
  - Counter is synchronously clocked
- Minimized logic computes next state



## Class example


- Redesign the 3-bit up counter using T flip-flops
1. Draw a state diagram
  2. Draw a state-transition table
  3. Encode the next-state functions
    - Minimize the logic using k-maps
  4. Implement the design

### 1. Draw a state diagram

 
 
### 2. Draw a state-transition table


- ◆ Like a truth-table
  - State encoding is easy for counters → Use count value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

### 3. Encode the next state functions

T flip-flops

 

C3	C2	C1	N3	N2	N1	T3	T2	T1
0	0	0	0	0	1			
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

### 4. Implement the design:

