 


## Overview

- ◆ Last lecture
  - Timing diagrams
  - Multilevel logic
    - ▣ Multilevel NAND/NOR conversion
    - ▣ AOI and OAI gates
  - Hazards
- ◆ Today
  - "Switching-network" logic blocks
    - ▣ Multiplexers/selectors
    - ▣ Demultiplexers/decoders
  - Programmable logic devices (PLDs)
    - ▣ Regular structures for 2-level logic

## Switching-network logic blocks


- ◆ Multiplexer
  - Routes one of many inputs to a single output
  - Also called a *selector*
- ◆ Demultiplexer
  - Routes a single input to one of many outputs
  - Also called a *decoder*



We construct these devices from:  
 (1) logic gates  
 (2) networks of transistor switches
 
## Rationale: Sharing complex logic functions


- ◆ Share an adder: Select inputs; route sum



## Multiplexers


- ◆ Basic concept
  - $2^n$  data inputs;  $n$  control inputs ("selects"); 1 output
  - Connects one of  $2^n$  inputs to the output
  - "Selects" decide which input connects to output
  - Two alternative truth-tables: **Functional** and **Logical**

 Example: A 2:1 Mux    **Functional** truth table    **Logical** truth table




S	Z	In <sub>0</sub>	In <sub>1</sub>	S	Z
0	In <sub>0</sub>	0	0	0	0
1	In <sub>1</sub>	0	0	0	1
0	In <sub>0</sub>	0	1	0	1
0	In <sub>0</sub>	0	1	1	0
1	In <sub>1</sub>	1	0	0	0
1	In <sub>1</sub>	1	0	1	1
1	In <sub>1</sub>	1	1	0	1
1	In <sub>1</sub>	1	1	1	1
 
## Logic-gate implementation of multiplexers



 
## Multiplexers (con't)

- ◆ 2:1 mux:  $Z = S'In_0 + SIn_1$
- ◆ 4:1 mux:  $Z = S_0'S_1'In_0 + S_0'S_1In_1 + S_0S_1'In_2 + S_0S_1In_3$
- ◆ 8:1 mux:  $Z = S_0'S_1'S_2'In_0 + S_0'S_1'S_2In_1 + \dots$


 
## Cascading multiplexers

- Can form large multiplexers from smaller ones
  - Many implementation options



CSE370, Lecture 9


7

## Multiplexers as general-purpose logic

- A  $2^n:1$  mux can implement any function of  $n$  variables
  - A lookup table
  - A  $2^{n-1}:1$  mux also can implement any function of  $n$  variables
- Example:  $F(A,B,C) = m_0 + m_2 + m_6 + m_7$ 

$$= A'B'C' + A'BC' + ABC' + ABC$$

$$= A'B'(C') + A'B(C') + AB(0) + AB(1)$$

 


CSE370, Lecture 9

8
 
## Multiplexers as general-purpose logic

- Implementing a  $2^n:1$  mux as a function of  $n-1$  variables
  - $(n-1)$  mux control variables  $S_0 - S_{n-1}$
  - One data variable  $S_n$
  - Four possible values for each data input: 0, 1,  $S_n$ ,  $S_n'$
  - Example:  $F(A,B,C,D)$  implemented using an 8:1 mux




CSE370, Lecture 9

9
 
## Demultiplexers

- Basic concept
  - Single data input;  $n$  control inputs ("selects");  $2^n$  outputs
  - Single input connects to one of  $2^n$  outputs
  - "Selects" decide which output is connected to the input
  - When used as a decoder, the input is called an "enable" (G)




CSE370, Lecture 9


10

## Logic-gate implementation of demultiplexers

### 1:2 demux

 

### 2:4 demux

 


CSE370, Lecture 9

11
 
## Demultiplexers as general-purpose logic

- A  $n:2^n$  demux can implement any function of  $n$  variables
  - Use variables as select inputs
  - Tie enable input to logic 1
  - Sum the appropriate minterms (extra OR gate)



CSE370, Lecture 9

12


## Demultiplexers as general-purpose logic

### Example

$$F1 = A'BC'D' + A'B'CD + ABCD$$

$$F2 = ABC'D' + ABC$$

$$F3 = (A'+B'+C'+D')$$

 


CSE370, Lecture 9

13

## Cascading demultiplexers

### 5:32 demux

 


CSE370, Lecture 9

14

## Programmable logic (PLAs & PALs)
 
### Concept: Large array of uncommitted AND/OR gates

- Actually NAND/NOR gates
- You program the array by making or breaking connections
  - Programmable block for sum-of-products logic




CSE370, Lecture 9

15

## All two-level logic functions are available

### You "program" the wire connections

 

A 3-input, 5-term, 4-function PLA

CSE370, Lecture 9

16

## Sharing product terms

### Example:

$$F0 = A + B'C'$$

$$F1 = AC' + AB$$

$$F2 = B'C' + AB$$

$$F3 = B'C + A$$

inputs  
1 = asserted in term  
0 = negated in term  
- = does not participate

### Personality matrix:

product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

outputs  
1 = term connected to output  
0 = no connection to output


Reuse terms

CSE370, Lecture 9

17
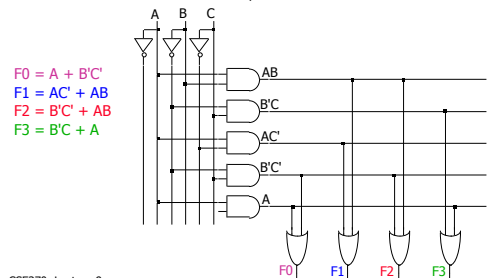
## Programming the wire connections

- Fuse: Comes connected; break unwanted connections
- Anti-fuse: Comes disconnected; make wanted connections



CSE370, Lecture 9

18