

Overview


- ◆ Last lecture
 - State encoding
 - ↳ One-hot encoding
 - ↳ Output encoding
- ◆ Today:
 - Optimizing FSMs
 - ↳ Pipelining
 - ↳ Retiming
 - ↳ Partitioning
 - Conclusion of sequential logic

Definitions

- ◆ Latency: Time to perform a computation
 - Data input to data output
- ◆ Throughput: Input or output data rate
 - Typically the clock rate
- ◆ Combinational delays drive performance
 - Define $d \equiv$ delay through slowest combinational stage
 - $n \equiv$ number of stages from input to output
 - Latency $\propto n \times d$ (in sec)
 - Throughput $\propto 1/d$ (in Hz)


Pipelining

 - ◆ What?
 - Subdivide combinational logic
 - Add registers between logic
- ◆ Why?
 - Trade latency for throughput
 - ↳ Reduce logic delays
 - ↳ Increase clock speed
 - Increased throughput
 - ↳ Takes cycles to fill the pipe
 - Increased latency
 - ↳ Increase circuit utilization
 - ↳ Simultaneous computations




Pipelining

 - ◆ When?
 - Need throughput more than latency
 - ↳ Signal processing
 - Logic delays > setup/hold times
 - Acyclic logic
- ◆ Where?
 - At natural breaks in the combinational logic
 - Adding registers makes sense




Pipelining example

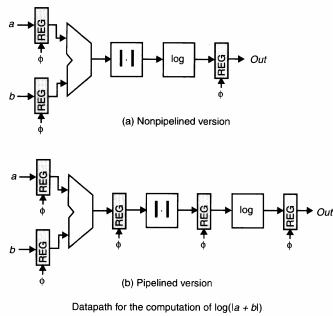

Pipelining and clock skew

- ◆ Which is faster?
- ◆ Which is safer?

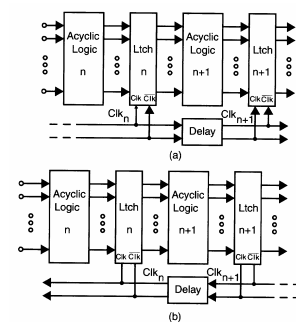


Retiming

- ◆ Pipelining adds registers
 - To increase the clock speed
- ◆ Retiming moves registers around
 - Reschedules computations to optimize performance
 - ✦ Minimize critical path
 - ✦ Optimize logic across register boundaries
 - ✦ Reduce register count
 - Without altering functionality


Retiming in a nutshell

 - ◆ Change position of FFs
 - For speed
 - To suit implementation target
- ◆ Retiming modifies state assignment
 - Preserves FSM functionality



Retiming groundrules

 - ◆ Rules:
 - Remove one register from each input and add one to each output
 - Remove one register from each output and add one to each input




Retiming examples

- ◆ Reduce register count




- ◆ Change output delays

 


Optimal pipelining

 - Add registers
- Use retiming to optimize location



 
Example: Digital correlator

- ◆ $y_t = \delta(x_t, a_0) + \delta(x_{t-1}, a_1) + \delta(x_{t-2}, a_2) + \delta(x_{t-3}, a_3)$
 - $\delta(x, a) = 1$ if $x = a$; 0 otherwise



Example: Digital correlator (cont'd)

- ◆ Delays: Comparator = 3; adder = 7

 

CSE370, Lecture 25

13

FSM partitioning

- ◆ Break a large FSM into two or more smaller FSMs

◆ Rationale

- Less states in each partition
 - ↳ Simpler minimization and state assignment
 - ↳ Smaller combinational logic
 - ↳ Shorter critical path
- But more logic overall

◆ Goal

- Minimize communication between partitions
 - ↳ Minimize wires & I/O

◆ Partitions are synchronous


- Same clock!!!

CSE370, Lecture 25

14

Example: Partition the machine

- ◆ Partition into two halves

 


CSE370, Lecture 25

15

Introduce idle states

 - ◆ SA and SB handoff control between machines




CSE370, Lecture 25


16

Partitioning rules

 - Rule #1: Source-state transformation
Replace by transition to idle state (SA)



 - Rule #2: Destination state transformation
Replace with exit transition from idle state




CSE370, Lecture 25


17

Partitioning rules (cont')

 - Rule #3: Multiple transitions with same source or destination
Source \Rightarrow Replace by transitions to idle state (SA)
Destination \Rightarrow Replace with exit transitions from idle state



 - Rule #4: Hold condition for idle state
OR exit conditions and invert



CSE370, Lecture 25


18

Mealy versus Moore partitions

- ◆ Mealy machines **undesirable**
 - Inputs can affect outputs immediately
 - ↳ "output" can be a handoff to another machine!!!
 - Inputs can ripple through several machines in one clock cycle
- ◆ Moore or synchronized Mealy **desirable**
 - Input-to-output path always broken by a flip-flop
 - But...may take several clocks for input to propagate to output
 - ↳ Output may derive from other side of a partition


Example: Six-state up/down counter

- ◆ Break into 2 parts

 

 Example: 6 state up/down counter (con't)

- ◆ Count sequence $S_0, S_1, S_2, S_3, S_4, S_5$
 - S_2 goes to S_A and holds, leaves after S_5
 - S_5 goes to S_B and holds, leaves after S_2
 - Down sequence is similar



Minimize communication between partitions

- ◆ Ideal world: Two machines handoff control
 - Separate I/O, states, etc.
- ◆ Real world: Minimize handoffs and common I/O
 - Minimize number of state bits that cross boundary
 - Merge common outputs
- ◆ Look for:
 - Disjoint inputs used in different regions of state diagram
 - Outputs active in only one region of state diagram
 - Isomorphic portions of state diagram
 - ↳ Add states, if necessary, to make them so
 - Regions of diagram with a single entry and single exit point

Sequential logic: What you should know

- ◆ Sequential logic building blocks
 - Latches (R-S and D)
 - Flip-flops (master/slave D, edge-triggered D & T)
 - Latch and flip-flop timing (setup/hold time, prop delay)
 - Timing diagrams
 - Flip-flop clocking
 - Asynchronous inputs and metastability
 - Registers

Sequential logic: What you should know

- ◆ Counters
 - Timing diagrams
 - Shift registers
 - Ripple counters
 - State diagrams and state-transition tables
 - Counter design procedure
 1. Draw a state diagram
 2. Draw a state-transition table
 3. Encode the next-state functions
 4. Implement the design
 - Self-starting counters

Sequential logic: What you should know

◆ Finite state machines

- Timing diagrams (synchronous FSMs)
- Moore versus Mealy versus registered Mealy
- FSM design procedure
 1. Understand the problem (state diagram & state-transition table)
 2. Determine the machine's states (minimize the state diagram)
 3. Encode the machine's states (state assignment)
 4. Design the next-state logic (minimize the combinational logic)
 5. Implement the FSM
- FSM design guidelines
 - ✦ Separate datapath and control
- One-hot encoding
- Pipelining and retiming basics