

## Combinational logic

- Number Representations
- Basic logic
  - Boolean algebra, proofs by re-writing, proofs by perfect induction
  - logic functions, truth tables, and switches
  - NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Logic realization
  - two-level logic and canonical forms
  - incompletely specified functions
- Simplification
  - uniting theorem
  - grouping of terms in Boolean functions
- Alternate representations of Boolean functions
  - cubes
  - Karnaugh maps

## Digital

- Digital = discrete
  - Binary codes (example: BCD)
  - Decimal digits 0-9
  - DNA nucleotides
- Binary codes
  - Represent symbols using binary digits (bits)
- Digital computers:
  - I/O is digital
    - ASCII, decimal, etc.
  - Internal representation is binary
    - Process information in bits

<u>Decimal Symbols</u>	<u>BCD Code</u>
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

## The basics: Binary numbers

- Bases we will use
  - Binary: Base 2
  - Octal: Base 8
  - Hexadecimal: Base 16
- Positional number system
  - $101_2 = 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$
  - $63_8 = 6 \times 8^1 + 3 \times 8^0$
  - $A1_{16} = 10 \times 16^1 + 1 \times 16^0$
- Addition and subtraction

$$\begin{array}{r} 1011 \\ + 1010 \\ \hline 10101 \end{array} \qquad \begin{array}{r} 1011 \\ - 0110 \\ \hline 0101 \end{array}$$

## Binary $\rightarrow$ hex/decimal/octal conversion

- Conversion from binary to octal/hex
  - Binary: 10011110001
  - Octal: 10 | 011 | 110 | 001 =  $2361_8$
  - Hex: 100 | 1111 | 0001 =  $4F1_{16}$
- Conversion from binary to decimal
  - $101_2 = 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 5_{10}$
  - $63.4_8 = 6 \times 8^1 + 3 \times 8^0 + 4 \times 8^{-1} = 51.5_{10}$
  - $A1_{16} = 10 \times 16^1 + 1 \times 16^0 = 161_{10}$



## Sign-and-magnitude

- The most-significant bit (msb) is the sign digit
  - 0 ≡ positive
  - 1 ≡ negative
- The remaining bits are the number's magnitude
- Problem 1: Two representations for zero
  - 0 = 0000 and also -0 = 1000
- Problem 2: Arithmetic is cumbersome

Add		Subtract			Compare and subtract		
4	0100	4	0100	0100	- 4	1100	1100
+ 3	+ 0011	- 3	+ 1011	- 0011	+ 3	+ 0011	- 0011
= 7	= 0111	= 1	≠ 1111	= 0001	- 1	≠ 1111	= 1001

## Ones-complement

- Negative number: Bitwise complement positive number
  - 0011 ≡ 3<sub>10</sub>
  - 1100 ≡ -3<sub>10</sub>
- Solves the arithmetic problem

Add		Invert, add, add carry		Invert and add	
4	0100	4	0100	- 4	1011
+ 3	+ 0011	- 3	+ 1100	+ 3	+ 0011
= 7	= 0111	= 1	1 0000	- 1	1110
		add carry:	+1		
			= 0001		

- Remaining problem: Two representations for zero
  - 0 = 0000 and also -0 = 1111

## Twos-complement

- Negative number: Bitwise complement **plus one**


- $0011 \equiv 3_{10}$
- $1101 \equiv -3_{10}$

- Number wheel

- Only one zero!

- msb is the sign digit

 - $0 \equiv$  positive
- $1 \equiv$  negative



## Twos-complement (con't)

- Complementing a complement  $\Rightarrow$  the original number

- Arithmetic is easy

- Subtraction = negation and addition
  - Easy to implement in hardware

Add	Invert and add	Invert and add
4    0100	4    0100	-4    1100
+3   +0011	-3   +1101	+3   +0011
=7   =0111	=1   10001	-1   1111
	drop carry =0001	

## Possible logic functions of two variables

- There are 16 possible functions of 2 input variables:
  - in general, there are  $2^{2^n}$  functions of  $n$  inputs



X	Y	16 possible functions (F0–F15)															
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Labels for functions (F0-F15) from left to right:
   
 X and Y (F1), X (F4), Y (F5), X xor Y (F6), X or Y (F7), X = Y (F9), X nor Y / not (X or Y) (F4), not Y (F11), not X (F12), X nand Y (F14), not (X and Y) (F15)

## Cost of different logic functions

- Different functions are easier or harder to implement
  - each has a cost associated with the number of switches needed
  - 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
  - X (F3) and Y (F5): require 0 switches, output is one of inputs
  - X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
  - X nor Y (F4) and X nand Y (F14): require 4 switches
  - X or Y (F7) and X and Y (F1): require 6 switches
  - X = Y (F9) and  $X \oplus Y$  (F6): require 16 switches
- thus, because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice



## Boolean algebra

- Boolean algebra
  - $B = \{0, 1\}$
  - variables
  - + is logical OR, • is logical AND
  - ' is logical NOT
- All algebraic axioms hold

## Logic functions and Boolean algebra

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: ', +, and •

X	Y	X • Y	X	Y	X'	X' • Y
0	0	0	0	0	1	0
0	1	0	0	1	1	1
1	0	0	1	0	0	0
1	1	1	1	1	0	0

X	Y	X'	Y'	X • Y	X' • Y'	(X • Y) + (X' • Y')
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \bullet Y) + (X' \bullet Y') \equiv X = Y$$

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

X, Y are Boolean algebra variables



## Axioms and theorems of Boolean algebra

- identity
  1.  $X + 0 = X$
  - 1D.  $X \cdot 1 = X$
- null
  2.  $X + 1 = 1$
  - 2D.  $X \cdot 0 = 0$
- idempotency:
  3.  $X + X = X$
  - 3D.  $X \cdot X = X$
- involution:
  4.  $(X')' = X$
- complementarity:
  5.  $X + X' = 1$
  - 5D.  $X \cdot X' = 0$
- commutativity:
  6.  $X + Y = Y + X$
  - 6D.  $X \cdot Y = Y \cdot X$
- associativity:
  7.  $(X + Y) + Z = X + (Y + Z)$
  - 7D.  $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

## Axioms and theorems of Boolean algebra (cont'd)

- distributivity:
  8.  $X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$
  - 8D.  $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$
- uniting:
  9.  $X \cdot Y + X \cdot Y' = X$
  - 9D.  $(X + Y) \cdot (X + Y') = X$
- absorption:
  10.  $X + X \cdot Y = X$
  - 10D.  $X \cdot (X + Y) = X$
  11.  $(X + Y') \cdot Y = X \cdot Y$
  - 11D.  $(X \cdot Y') + Y = X + Y$
- factoring:
  12.  $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$
  - 12D.  $X \cdot Y + X' \cdot Z = (X + Z) \cdot (X' + Y)$
- consensus:
  13.  $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$
  - 13D.  $(X + Y) \cdot (Y + Z) \cdot (X' + Z) = (X + Y) \cdot (X' + Z)$

## Axioms and theorems of Boolean algebra (cont'd)

- de Morgan's:  
14.  $(X + Y + \dots)' = X' \cdot Y' \cdot \dots$     14D.  $(X \cdot Y \cdot \dots)' = X' + Y' + \dots$
- generalized de Morgan's:  
15.  $f'(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) = f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)$
- establishes relationship between  $\cdot$  and  $+$

## Axioms and theorems of Boolean algebra (cont'd)

- Duality
  - a dual of a Boolean expression is derived by replacing
    - by  $+$ ,  $+$  by  $\cdot$ , 0 by 1, and 1 by 0, and leaving variables unchanged
  - any theorem that can be proven is thus also proven for its dual!
  - a meta-theorem (a theorem about theorems)
- duality:  
16.  $X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$
- generalized duality:  
17.  $f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$
- Different than deMorgan's Law
  - this is a statement about theorems
  - this is not a way to manipulate (re-write) expressions

## Proving theorems (rewriting)

- Using the axioms of Boolean algebra:

- e.g., prove the theorem:  $X \cdot Y + X \cdot Y' = X$

distributivity (8)  $X \cdot Y + X \cdot Y' = X \cdot (Y + Y')$

complementarity (5)  $X \cdot (Y + Y') = X \cdot (1)$

identity (1D)  $X \cdot (1) = X \checkmark$

- e.g., prove the theorem:  $X + X \cdot Y = X$

identity (1D)  $X + X \cdot Y = X \cdot 1 + X \cdot Y$

distributivity (8)  $X \cdot 1 + X \cdot Y = X \cdot (1 + Y)$

identity (2)  $X \cdot (1 + Y) = X \cdot (1)$

identity (1D)  $X \cdot (1) = X \checkmark$

## Activity

- Prove the following using the laws of Boolean algebra:

- $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$

## Proving theorems (perfect induction)


- Using perfect induction (complete truth table):
  - e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$	$X$	$Y$	$X'$	$Y'$	$(X + Y)'$	$X' \cdot Y'$
NOR is equivalent to AND with inputs complemented	0	0	1	1	1	1
	0	1	1	0	0	0
	1	0	0	1	0	0
	1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$	$X$	$Y$	$X'$	$Y'$	$(X \cdot Y)'$	$X' + Y'$
NAND is equivalent to OR with inputs complemented	0	0	1	1	1	1
	0	1	1	0	1	1
	1	0	0	1	1	1
	1	1	0	0	0	0
 
## A simple example: 1-bit binary adder

- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



$A$	$B$	$Cin$	$Cout$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$Cout = A' B Cin + A B' Cin + A B Cin' + A B Cin$$

## Apply the theorems to simplify expressions

- The theorems of Boolean algebra can simplify Boolean expressions
  - e.g., full adder's carry-out function (same rules apply to any function)

$$\begin{aligned}
 \text{Cout} &= A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\
 &= A' B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in} + A B C_{in}} \\
 &= A' B C_{in} + A B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\
 &= (A' + A) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\
 &= (1) B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in} \\
 &= B C_{in} + A B' C_{in} + A B C_{in}' + \boxed{A B C_{in} + A B C_{in}} \\
 &= B C_{in} + A B' C_{in} + A B C_{in} + A B C_{in}' + A B C_{in} \\
 &= B C_{in} + A (B' + B) C_{in} + A B C_{in}' + A B C_{in} \\
 &= B C_{in} + A (1) C_{in} + A B C_{in}' + A B C_{in} \\
 &= B C_{in} + A C_{in} + A B (C_{in}' + C_{in}) \\
 &= B C_{in} + A C_{in} + A B (1) \\
 &= B C_{in} + A C_{in} + A B
 \end{aligned}$$

adding extra terms  
creates new factoring  
opportunities

## Activity


- Fill in the truth-table for a circuit that checks that a 4-bit number is divisible by 2, 3, or 5


X8	X4	X2	X1	By2	By3	By5
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	0	1	0


- Write down Boolean expressions for By2, By3, and By5

## Activity

## From Boolean expressions to logic gates





- NOT  $X'$   $\bar{X}$   $\sim X$  

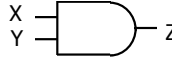X	Y
0	1
1	0
- AND  $X \cdot Y$   $XY$   $X \wedge Y$  

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1
- OR  $X + Y$   $X \vee Y$  

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

## From Boolean expressions to logic gates (cont'd)

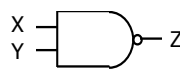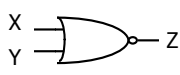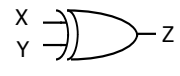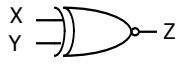
■ NAND		<table border="1" data-bbox="812 399 941 514"> <thead> <tr><th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	Z	0	0	1	0	1	1	1	0	1	1	1	0	
X	Y	Z																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
■ NOR		<table border="1" data-bbox="812 546 941 661"> <thead> <tr><th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	Z	0	0	1	0	1	0	1	0	0	1	1	0	
X	Y	Z																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
■ XOR $X \oplus Y$		<table border="1" data-bbox="812 693 941 808"> <thead> <tr><th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	X	Y	Z	0	0	0	0	1	1	1	0	1	1	1	0	$X \text{ xor } Y = X Y' + X' Y$ X or Y but not both ("inequality", "difference")
X	Y	Z																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
■ XNOR $X = Y$		<table border="1" data-bbox="812 840 941 955"> <thead> <tr><th>X</th><th>Y</th><th>Z</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	X	Y	Z	0	0	1	0	1	0	1	0	0	1	1	1	$X \text{ xnor } Y = X Y + X' Y'$ X and Y are the same ("equality", "coincidence")
X	Y	Z																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

## From Boolean expressions to logic gates (cont'd)

- More than one way to map expressions to gates


□ e.g.,  $Z = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$

$$\frac{\frac{\quad}{T2}}{T1}$$

 

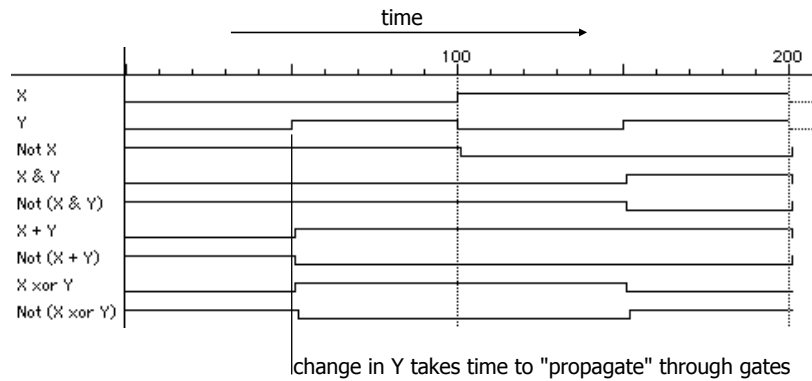
## Waveform view of logic functions

- Just a sideways truth table
  - but note how edges don't line up exactly
  - it takes time for a gate to switch its output!



## Choosing different realizations of a function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

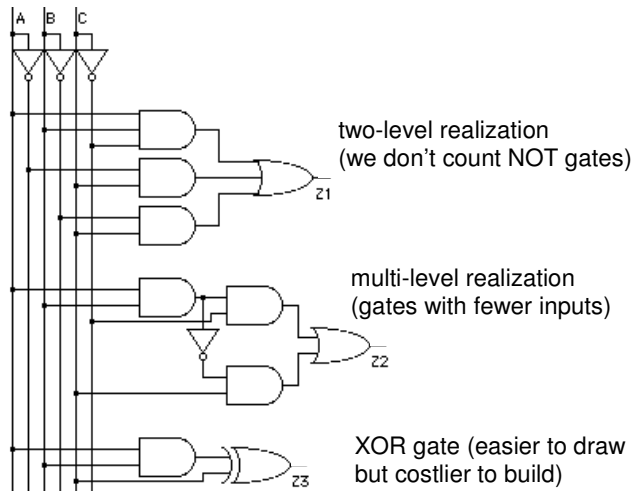



## Which realization is best?


- Reduce number of inputs
  - literal: input variable (complemented or not)
    - can approximate cost of logic gate as 2 transistors per literal
    - why not count inverters?
  - fewer literals means less transistors
    - smaller circuits
  - fewer inputs implies faster gates
    - gates are smaller and thus also faster
  - fan-ins (# of gate inputs) are limited in some technologies
- Reduce number of gates
  - fewer gates (and the packages they come in) means smaller circuits
    - directly influences manufacturing costs

## Which is the best realization? (cont'd)

- Reduce number of levels of gates
  - fewer level of gates implies reduced signal propagation delays
  - minimum delay configuration typically requires more gates
    - wider, less deep circuits
- How do we explore tradeoffs between increased circuit delay and size?
  - automated tools to generate different solutions
  - logic minimization: reduce number of gates and complexity
  - logic optimization: reduction while trading off against delay
 
## Are all realizations equivalent?

- Under the same input stimuli, the three alternative implementations have almost the same waveform behavior
  - delays are different
  - glitches (hazards) may arise – these could be bad, it depends
  - variations due to differences in number of gate levels and structure
- The three implementations are functionally equivalent



## Implementing Boolean functions

- Technology independent
  - canonical forms
  - two-level forms
  - multi-level forms
- Technology choices
  - packages of a few gates
  - regular logic
  - two-level programmable logic
  - multi-level programmable logic

## Canonical forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
- Canonical forms
  - standard forms for a Boolean expression
  - provides a unique algebraic signature

## Sum-of-products canonical forms

- Also known as disjunctive normal form
- Also known as minterm expansion

					$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$				
					$F = A'B'C + A'BC + AB'C + ABC' + ABC$				
A	B	C	F	F'					
0	0	0	0	1					
0	0	1	1	0					
0	1	0	0	1					
0	1	1	1	0					
1	0	0	0	1					
1	0	1	1	0					
1	1	0	1	0					
1	1	1	1	0					

$F' = A'B'C' + A'BC' + AB'C'$

## Sum-of-products canonical form (cont'd)

- Product term (or minterm)
  - ANDed product of literals – input combination for which output is true
  - each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms	
0	0	0	A'B'C'	m0
0	0	1	A'B'C	m1
0	1	0	A'BC'	m2
0	1	1	A'BC	m3
1	0	0	AB'C'	m4
1	0	1	AB'C	m5
1	1	0	ABC'	m6
1	1	1	ABC	m7

short-hand notation for  
minterms of 3 variables

F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \Sigma m(1,3,5,6,7) \\
 &= m1 + m3 + m5 + m6 + m7 \\
 &= A'B'C + A'BC + AB'C + ABC' + ABC
 \end{aligned}$$

canonical form  $\neq$  minimal form

$$\begin{aligned}
 F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\
 &= (A'B' + A'B + AB' + AB)C + ABC' \\
 &= ((A' + A)(B' + B))C + ABC' \\
 &= C + ABC' \\
 &= ABC' + C \\
 &= AB + C
 \end{aligned}$$

## Product-of-sums canonical form

- Also known as conjunctive normal form
- Also known as maxterm expansion

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}
 F &= \quad 000 \quad \quad \quad 010 \quad \quad \quad 100 \\
 F &= (A + B + C) (A + B' + C) (A' + B + C)
 \end{aligned}$$

$$F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C') (A' + B' + C')$$

## Product-of-sums canonical form (cont'd)

- Sum term (or maxterm)
  - ORed sum of literals – input combination for which output is false
  - each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	
0	0	0	A+B+C	M0
0	0	1	A+B+C'	M1
0	1	0	A+B'+C	M2
0	1	1	A+B'+C'	M3
1	0	0	A'+B+C	M4
1	0	1	A'+B+C'	M5
1	1	0	A'+B'+C	M6
1	1	1	A'+B'+C'	M7

short-hand notation for  
maxterms of 3 variables

F in canonical form:

$$\begin{aligned} F(A, B, C) &= \prod M(0,2,4) \\ &= M0 \cdot M2 \cdot M4 \\ &= (A + B + C) (A + B' + C) (A' + B + C) \end{aligned}$$


canonical form  $\neq$  minimal form

$$\begin{aligned} F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C) \end{aligned}$$

## S-o-P, P-o-S, and de Morgan's theorem


- Sum-of-products
  - $F' = A'B'C' + A'BC' + AB'C'$
- Apply de Morgan's
  - $(F')' = (A'B'C' + A'BC' + AB'C')'$
  - $F = (A + B + C) (A + B' + C) (A' + B + C)$
- Product-of-sums
  - $F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$
- Apply de Morgan's
  - $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C'))'$
  - $F = A'B'C' + A'BC' + AB'C' + ABC' + ABC$
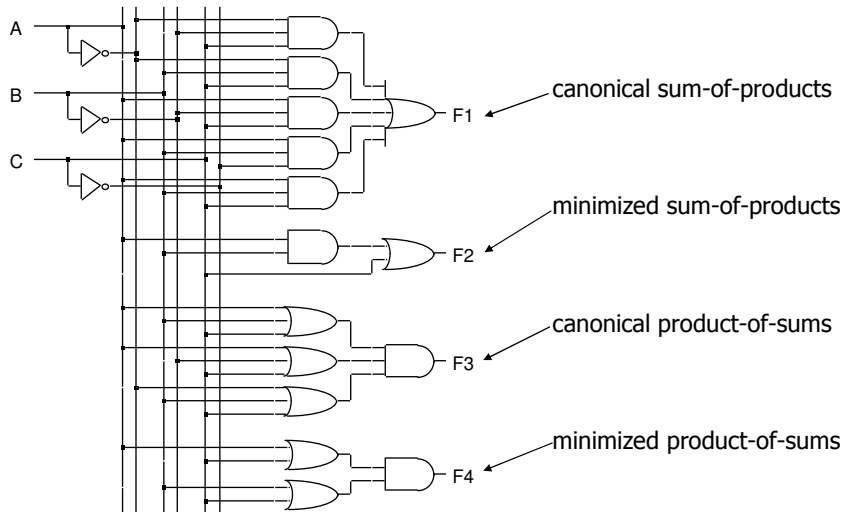
## Four alternative two-level implementations of $F = AB + C$


 
## Waveforms for the four alternatives

- Waveforms are essentially identical
  - except for timing hazards (glitches)
  - delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)



## Mapping between canonical forms

- Minterm to maxterm conversion
  - use maxterms whose indices do not appear in minterm expansion
  - e.g.,  $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm conversion
  - use minterms whose indices do not appear in maxterm expansion
  - e.g.,  $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm expansion of  $F$  to minterm expansion of  $F'$ 
  - use minterms whose indices do not appear
  - e.g.,  $F(A,B,C) = \sum m(1,3,5,6,7)$       $F'(A,B,C) = \sum m(0,2,4)$
- Maxterm expansion of  $F$  to maxterm expansion of  $F'$ 
  - use maxterms whose indices do not appear
  - e.g.,  $F(A,B,C) = \prod M(0,2,4)$       $F'(A,B,C) = \prod M(1,3,5,6,7)$

## Incompletely specified functions

- Example: binary coded decimal increment by 1
  - BCD digits encode the decimal digits 0 – 9 in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

off-set of W  
 on-set of W  
 don't care (DC) set of W  
 these inputs patterns should never be encountered in practice – **"don't care"** about associated output values, can be exploited in minimization

## Notation for incompletely specified functions

- Don't cares and canonical forms
  - so far, only represented on-set
  - also represent don't-care-set
  - need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
  - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
  - $Z = \Sigma [ m(0,2,4,6,8) + d(10,11,12,13,14,15) ]$
  - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
  - $Z = \Pi [ M(1,3,5,7,9) \cdot D(10,11,12,13,14,15) ]$

## Simplification of two-level combinational logic


- Finding a minimal sum of products or product of sums realization
  - exploit don't care information in the process
- Algebraic simplification
  - not an algorithmic/systematic procedure
  - how do you know when the minimum realization has been found?
- Computer-aided design tools
  - precise solutions require very long computation times, especially for functions with many inputs ( $> 10$ )
  - heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
  - to understand automatic tools and their strengths and weaknesses
  - ability to check results (on small examples)



## The uniting theorem


- Key tool to simplification:  $A(B' + B) = A$
- Essence of simplification of two-level logic
  - find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$

 
 
## Boolean cubes


- Visual technique for indentifying when the uniting theorem can be applied
- n input variables = n-dimensional "cube"



## Mapping truth tables onto Boolean cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

 


ON-set = solid nodes  
 OFF-set = empty nodes  
 DC-set = x'd nodes

## Three variable example

- Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


the on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$\text{Cout} = \text{BCin} + \text{AB} + \text{ACin}$$

## Higher dimensional cubes

- Sub-cubes of higher dimension than 2

 

$$F(A,B,C) = \Sigma m(4,5,6,7)$$

on-set forms a square  
i.e., a cube of dimension 2

*represents an expression in one variable  
i.e., 3 dimensions - 2 dimensions*

A is asserted (true) and unchanged  
B and C vary

This subcube represents the  
literal A

## m-dimensional cubes in a n-dimensional Boolean space

- In a 3-cube (three variables):
  - a 0-cube, i.e., a single node, yields a term in 3 literals
  - a 1-cube, i.e., a line of two nodes, yields a term in 2 literals
  - a 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
  - a 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
  - an m-subcube within an n-cube ( $m < n$ ) yields a term with  $n - m$  literals

## Karnaugh maps

- Flat map of Boolean cube
  - wrap-around at edges
  - hard to draw and visualize for more than 4 dimensions
  - virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
  - guide to applying the uniting theorem
  - on-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

	A	0	1
B	0	1	1
1	0	1	0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

## Karnaugh maps (cont'd)

- Numbering scheme based on Gray-code
  - e.g., 00, 01, 11, 10
  - only a single bit changes in code for adjacent map cells

	AB	00	01	11	10
C	0	0	2	6	4
1	0	1	3	7	5



	A	0	2	6	4
C	0	0	2	6	4
1	0	1	3	7	5

	A	0	4	12	8
C	0	0	4	12	8
1	0	1	5	13	9
2	0	3	7	15	11




$13 = 1101 = ABC'D$
  
## Adjacencies in Karnaugh maps




- Wrap from first to last column
- Wrap top row to bottom row



## Karnaugh map examples

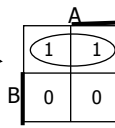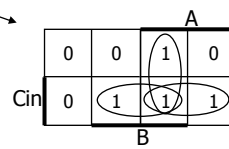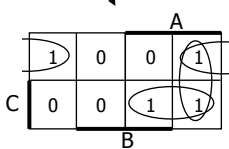- $F =$    $B'$
  - $C_{out} =$    $AB + AC_{in} + BC_{in}$
  - $f(A,B,C) = \Sigma m(0,4,5,7)$    $AC + B'C' + AB'$
- obtain the complement of the function by covering 0s with subcubes



## More Karnaugh map examples

   

## Karnaugh map: 4-variable example

■  $F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$

$F = C + A'BD + B'D'$

  

find the smallest number of the largest possible subcubes to cover the ON-set  
 (fewer terms with fewer inputs per term)

## Karnaugh maps: don't cares

- $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$ 
  - without don't cares
    - $f = A'D + B'C'D$

	A			
	0	0	X	0
	1	1	X	1
C	1	1	0	0
	0	X	0	0
	B			

## Karnaugh maps: don't cares (cont'd)

- $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$ 
  - $f = A'D + B'C'D$  without don't cares
  - $f = A'D + C'D$  with don't cares

	A			
	0	0	X	0
	1	1	X	1
C	1	1	0	0
	0	X	0	0
	B			

by using don't care as a "1"  
a 2-cube can be formed  
rather than a 1-cube to cover  
this node

don't cares can be treated as  
1s or 0s  
depending on which is more  
advantageous

## Activity

- Minimize the function  $F = \Sigma m(0, 2, 7, 8, 14, 15) + d(3, 6, 9, 12, 13)$

## Combinational logic summary

- Logic functions, truth tables, and switches
  - NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Axioms and theorems of Boolean algebra
  - proofs by re-writing and perfect induction
- Gate logic
  - networks of Boolean functions and their time behavior
- Canonical forms
  - two-level and incompletely specified functions
- Simplification
  - a start at understanding two-level simplification
- Later
  - automation of simplification
  - multi-level logic
  - time behavior
  - hardware description languages
  - design case studies