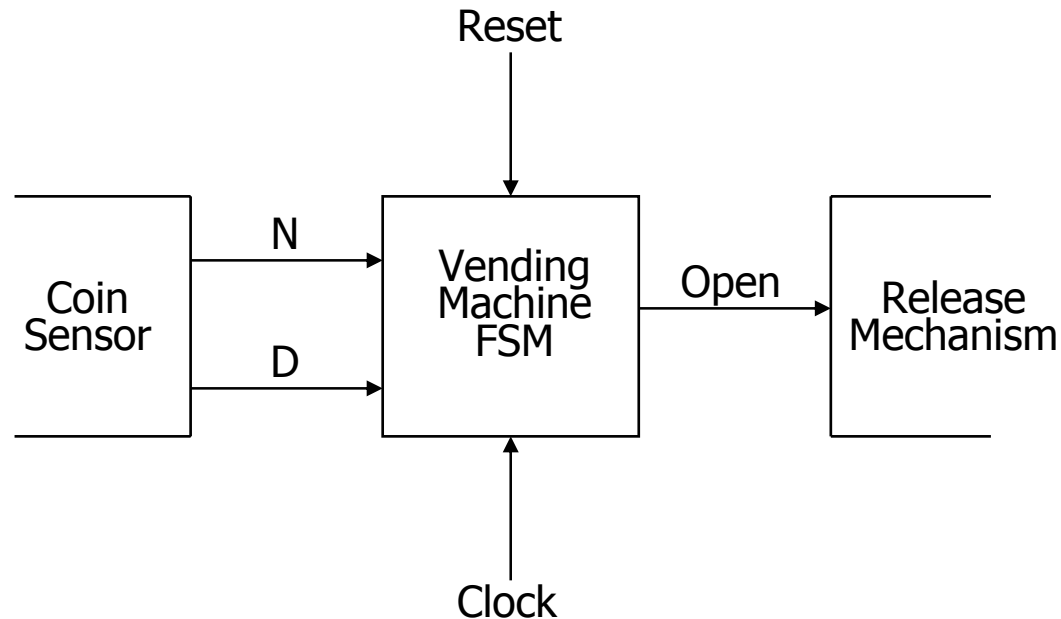



Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes, nickels
- No change



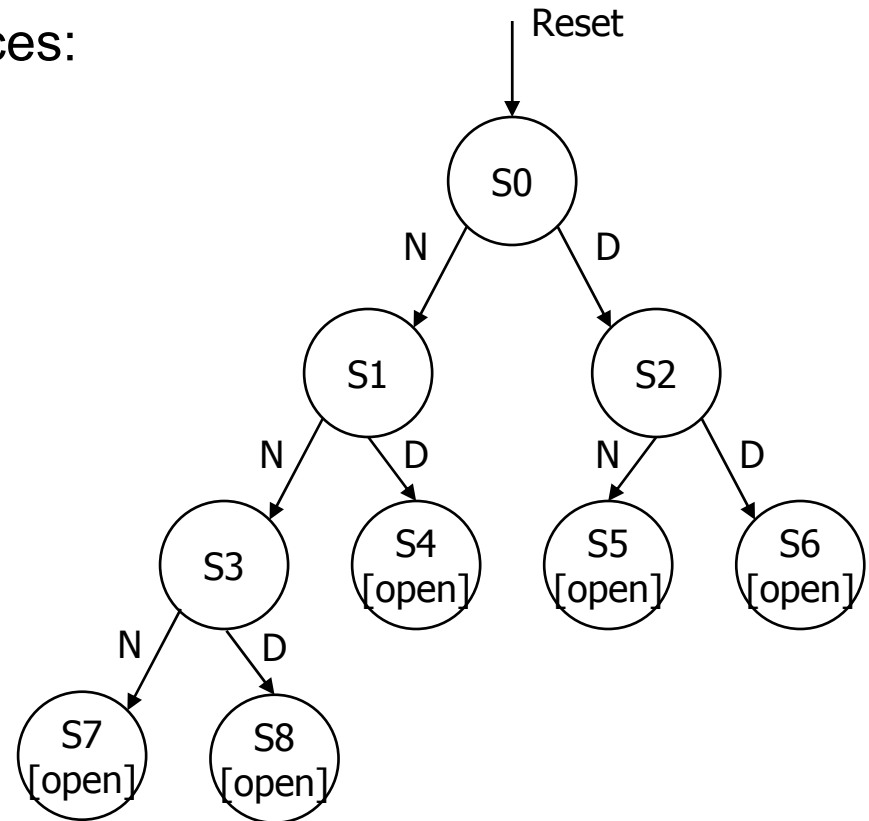
Example: vending machine (cont'd)

- Suitable abstract representation
 - tabulate typical input sequences:
 - 3 nickels
 - nickel, dime
 - dime, nickel
 - two dimes
 - draw state diagram:
 - inputs: N, D, reset
 - output: open chute
 - assumptions:
 - assume N and D asserted for one cycle
 - each state has a self loop for $N = D = 0$ (no coin)



 Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

symbolic state table

Example: vending machine (cont'd)

- Uniquely encode states

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	–	–	–
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	–	–	–
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	–	–	–
1	1	–	–	1	1	1


Example: Moore implementation

■ Mapping to logic

		<u>Q1</u>			
D1		0	0	1	1
		0	1	1	1
	D	X	X	1	X
		1	1	1	1
		<u>Q0</u>			

		<u>Q1</u>			
D0		0	1	1	0
		1	0	1	1
	D	X	X	1	X
		0	1	1	1
		<u>Q0</u>			

		<u>Q1</u>			
Open		0	0	1	0
		0	0	1	0
	D	X	X	1	X
		0	0	1	0
		<u>Q0</u>			

 

$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

Example: vending machine (cont'd)

- One-hot encoding

present state				inputs		next state				output
Q3	Q2	Q1	Q0	D	N	D3	D2	D1	D0	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	-
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
1	0	0	0	-	-	1	0	0	0	1

$$D0 = Q0 D' N'$$

$$D1 = Q0 N + Q1 D' N'$$

$$D2 = Q0 D + Q1 N + Q2 D' N'$$


$$D3 = Q1 D + Q2 D + Q2 N + Q3$$

$$OPEN = Q3$$

Equivalent Mealy and Moore state diagrams


- Moore machine

- outputs associated with state

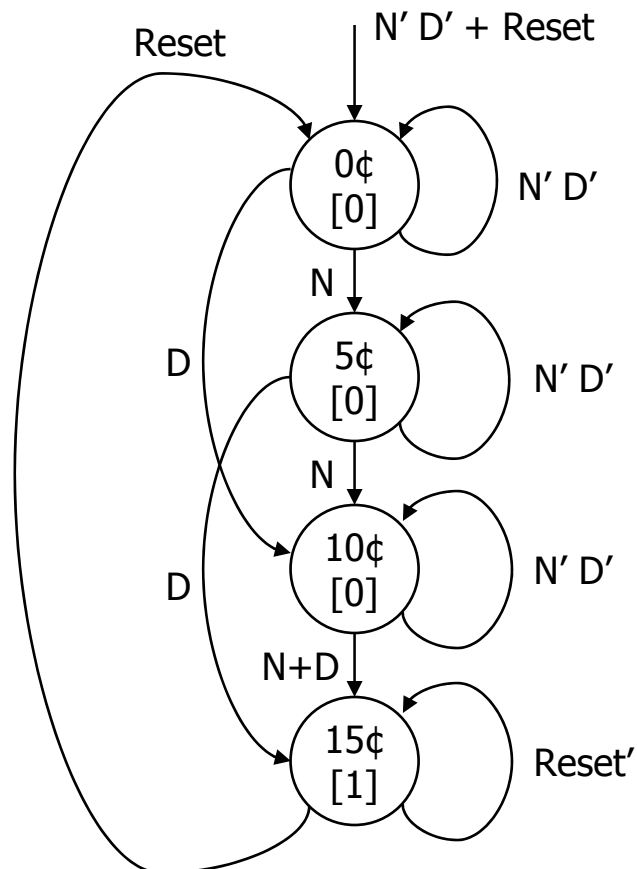


- Mealy machine

- outputs associated with transitions

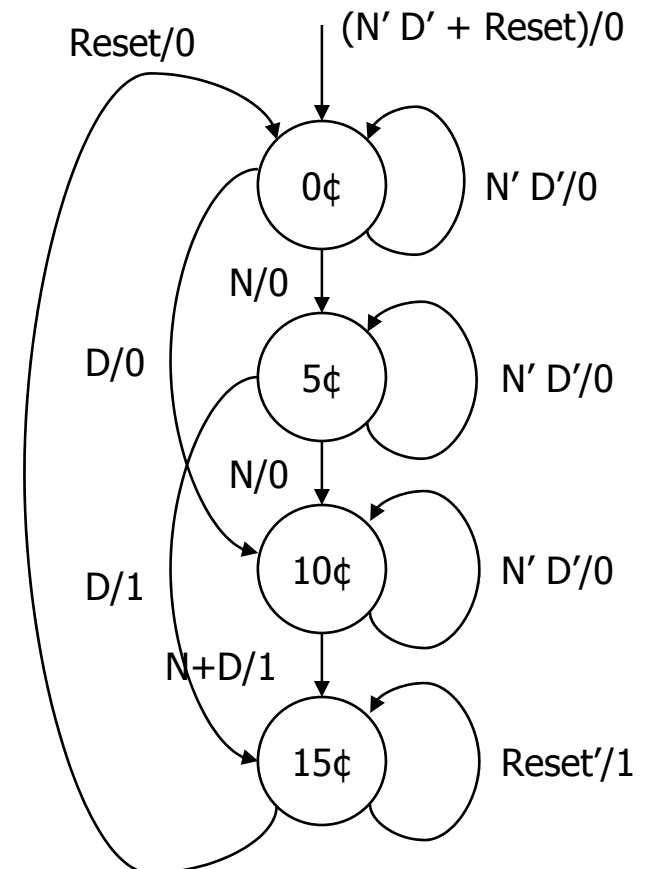

Example: Mealy implementation

 

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	-	-	-
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	1
		1	1	-	-	-
1	0	0	0	1	0	0
		0	1	1	1	1
		1	0	1	1	1
		1	1	-	-	-
1	1	-	-	1	1	1

		Q1		
Open		0	1	
	N	0	1	
	D	X	1	X
		0	1	
		Q0		



$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


Vending machine: Moore to synch. Mealy

- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$
- Implementation now looks like a synchronous Mealy machine
 - it is common for programmable devices to have FF at end of logic

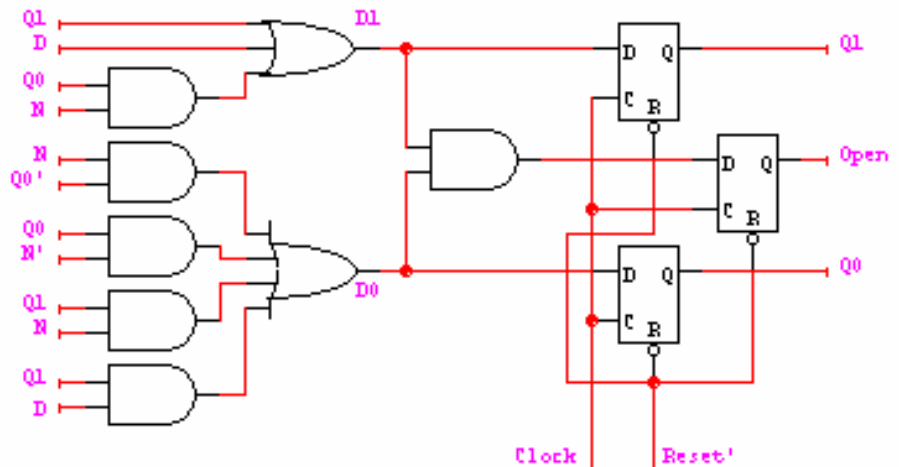 


Vending machine: Mealy to synch. Mealy

- $OPEN.d = Q1Q0 + Q1N + Q1D + Q0D$
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$

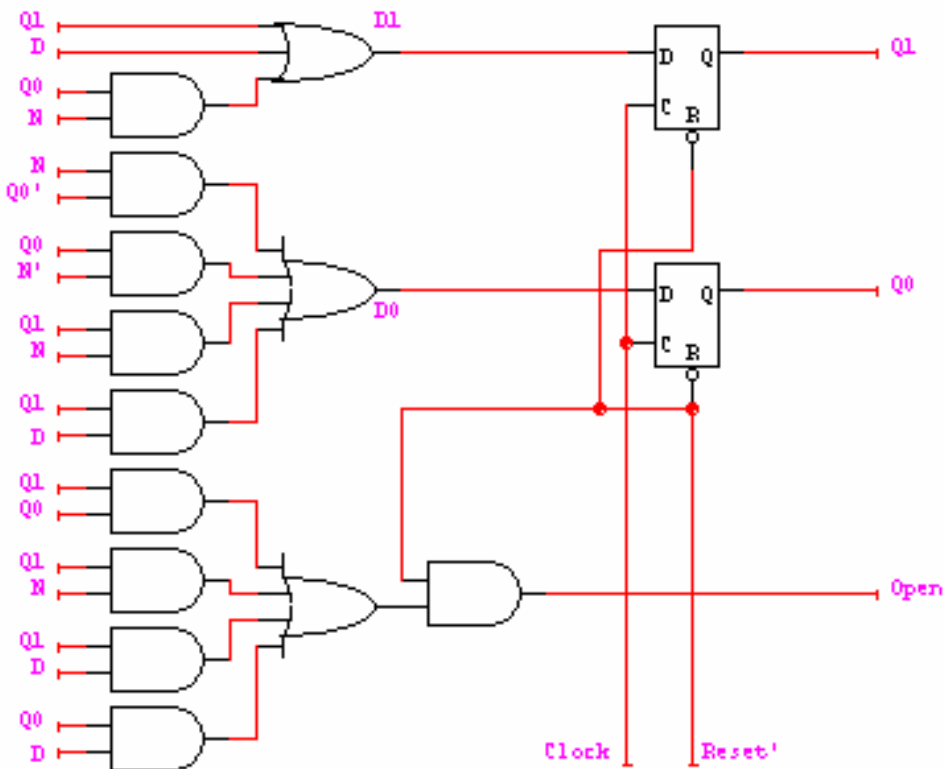

Spring 2005

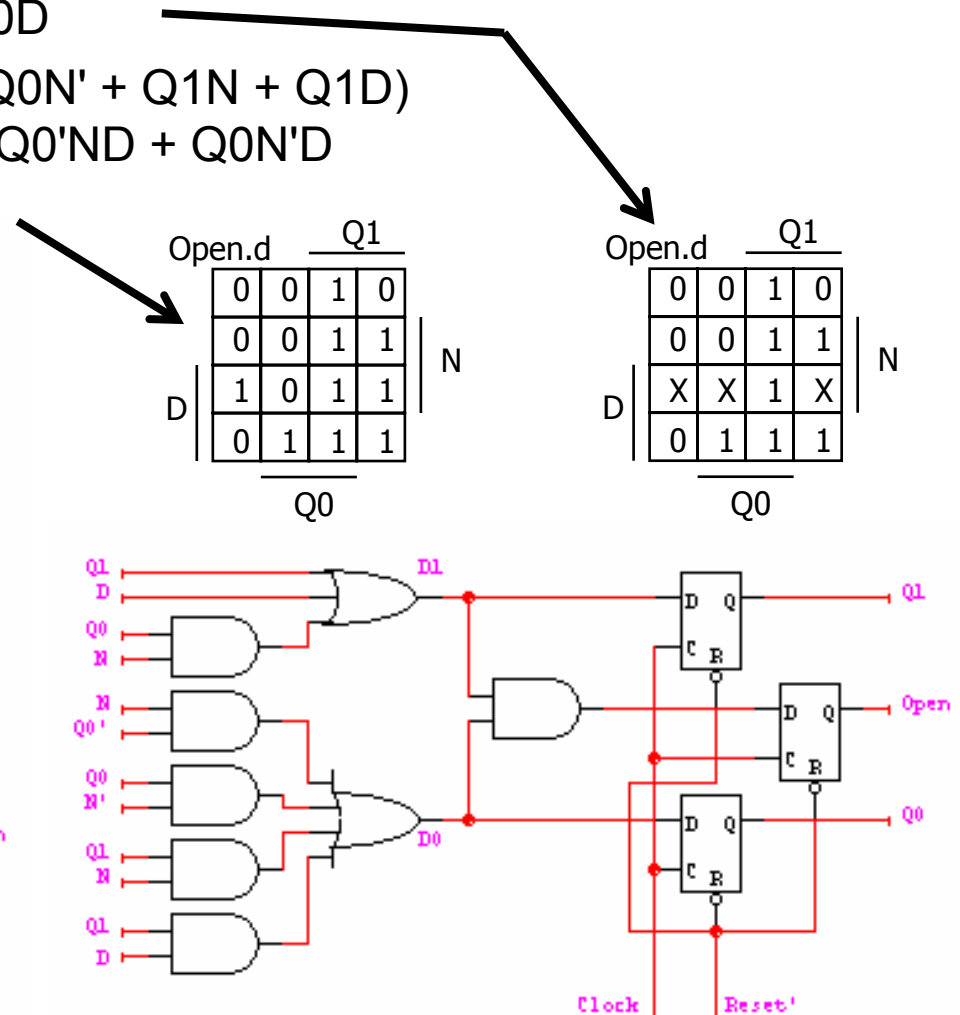

CSE370 - guest lecture



11

Hardware Description Languages and Sequential Logic

- Flip-flops
 - representation of clocks - timing of state changes
 - asynchronous vs. synchronous
- FSMs
 - structural view (FFs separate from combinational logic)
 - behavioral view (synthesis of sequencers – not in this course)
- Data-paths = data computation (e.g., ALUs, comparators) + registers
 - use of arithmetic/logical operators
 - control of storage elements

  Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input




Verilog FSM - Reduce 1s example

■ Moore machine

```
module reduce (clk, reset, in, out);  
  input clk, reset, in;  
  output out;  
  
  parameter zero = 2'b00;  
  parameter one1 = 2'b01;  
  parameter two1s = 2'b10;  
  
  reg out;  
  reg [2:1] state; // state variables  
  reg [2:1] next_state;  
  
  always @(posedge clk)  
    if (reset) state = zero;  
    else state = next_state;
```

 state assignment
(easy to change,
if in one place)



Moore Verilog FSM (cont'd)

```
always @(in or state)

case (state)
  zero:
  // last input was a zero
  begin
    if (in) next_state = one1;
    else   next_state = zero;
  end
  one1:
  // we've seen one 1
  begin
    if (in) next_state = twos;
    else   next_state = zero;
  end
  twos:
  // we've seen at least 2 ones
  begin
    if (in) next_state = twos;
    else   next_state = zero;
  end
endcase
```

crucial to include
all signals that are
input to state determination

note that output
depends only on state

```
always @(state)
case (state)
  zero: out = 0;
  one1: out = 0;
  twos: out = 1;
endcase
```


endmodule

Mealy Verilog FSM

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = zero;
    else      state = next_state;

   always @(in or state)
    case (state)
      zero:           // last input was a zero
      begin
        out = 0;
        if (in) next_state = one;
        else   next_state = zero;
      end
      one:           // we've seen one 1
      if (in) begin
        next_state = one; out = 1;
      end else begin
        next_state = zero; out = 0;
      end
    endcase
endmodule
```



Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;
    reg out;
    reg state; // state variables

    always @(posedge clk)
        if (reset) state = zero;
        else
            case (state)
                zero: // last input was a zero
                    begin
                        out = 0;
                        if (in) state = one;
                        else state = zero;
                    end
                one: // we've seen one 1
                    if (in) begin
                        state = one; out = 1;
                    end else begin
                        state = zero; out = 0;
                    end
            endcase
endmodule
```

State assignment

- Choose bit vectors to assign to each “symbolic” state
 - with n state bits for m states there are $2^n! / (2^n - m)!$
[$\log n \leq m \leq 2^n$]
 - 2^n codes possible for 1st state, $2^n - 1$ for 2nd, $2^n - 2$ for 3rd, ...
 - huge number even for small values of n and m
 - intractable for state machines of any size
 - heuristics are necessary for practical solutions
 - optimize some metric for the combinational logic
 - size (amount of logic and number of FFs)
 - speed (depth of logic and fanout)
 - dependencies (decomposition)

State assignment strategies


- Possible strategies
 - sequential – just number states as they appear in the state table
 - random – pick random codes
 - one-hot – use as many state bits as there are states (bit=1 → state)
 - output – use outputs to help encode states
 - heuristic – rules of thumb that seem to work in most cases
- No guarantee of optimality – another intractable problem

Current state assignment approaches

- For tight encodings using close to the minimum number of state bits
 - best of 10 random seems to be adequate (averages as well as heuristics)
 - heuristic approaches are not even close to optimality
 - used in custom chip design
- One-hot encoding
 - easy for small state machines
 - generates small equations with easy to estimate complexity
 - common in FPGAs and other programmable logic
- Output-based encoding
 - ad hoc - no tools
 - most common approach taken by human designers
 - yields very small circuits for most FSMs
 - popular in PLDs


State machines and PLDs

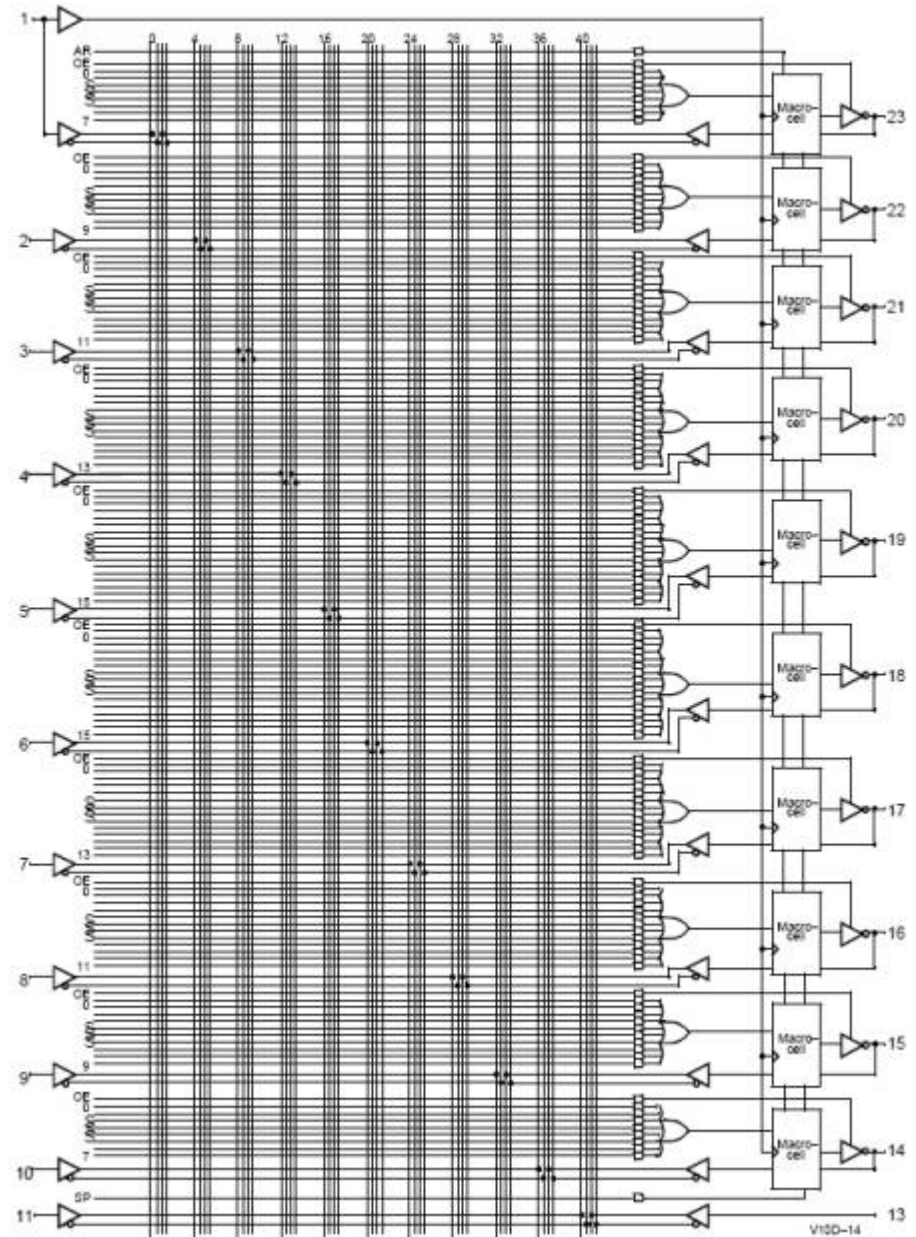- Moore and synchronous Mealy most common
- Output-directed state assignment
 - All outputs already have FFs and are fed back in as input to logic array
 - Use these as part of the state register
 - Add only as many extra states bits as needed to make all state codes unique



Implementation using PALs

 
- Programmable logic building block for sequential logic
 - macro-cell: FF + logic
 - D-FF
 - two-level logic capability like PAL (e.g., 8 product terms)



22V10 PAL


- Combinational logic elements (SoP)
- Sequential logic elements (D-FFs)
- Up to 10 outputs
- Up to 10 FFs
- Up to 22 inputs

Functional Logic Diagram for PALC22V10D

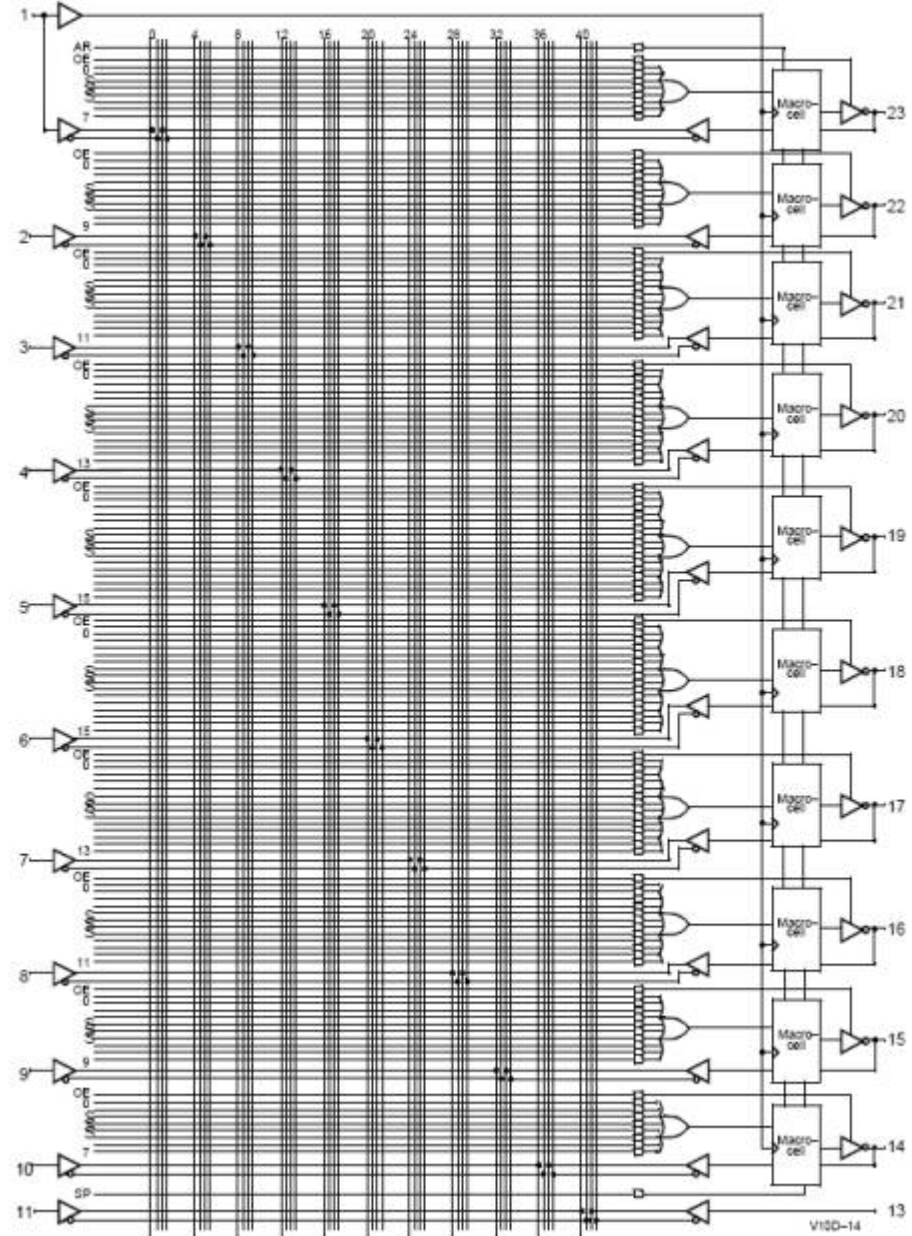

22V10 PAL Macro Cell

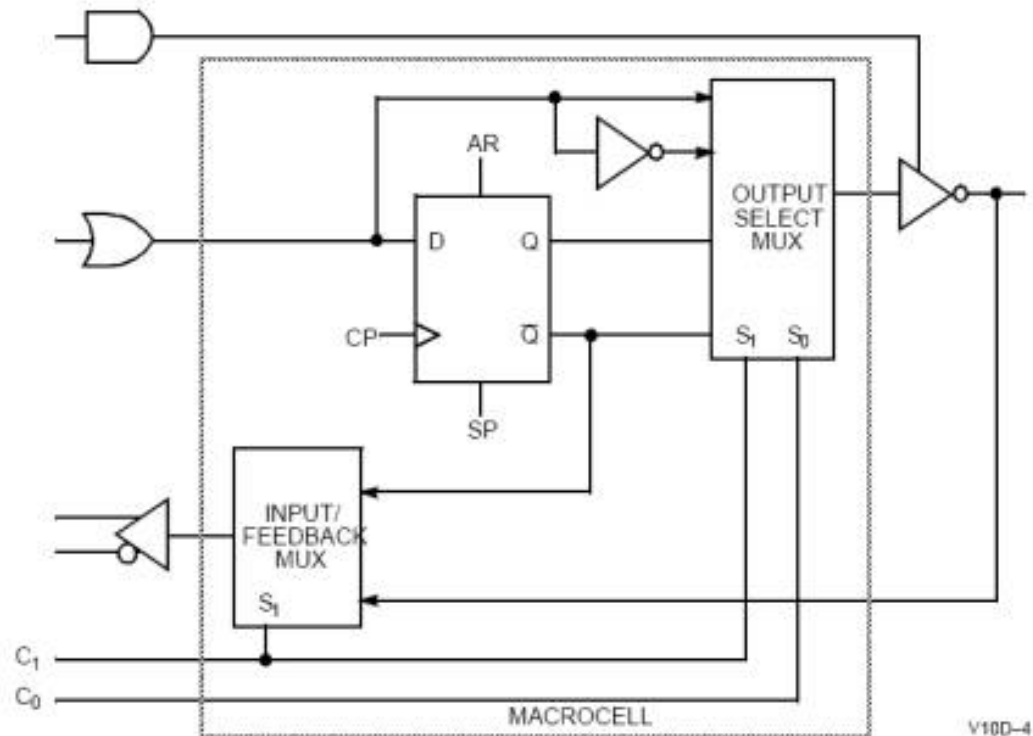- Sequential logic element + output/input selection



Vending machine example (Moore PLD mapping)

$$D0 = \text{reset}'(Q0'N + Q0N' + Q1N + Q1D)$$

$$D1 = \text{reset}'(Q1 + D + Q0N)$$

$$\text{OPEN} = Q1Q0$$

