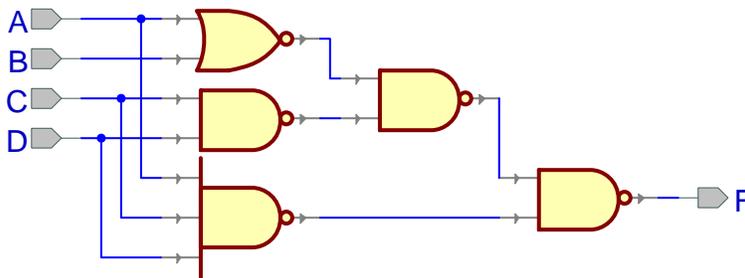


CSE370 Quiz 1 (21 January)

Name _____



Given the following schematic:



Write down the Boolean expression corresponding to F (in any form).

Write the expression in sum-of-products form (Σ notation).

Fill in the K-map below on the left.

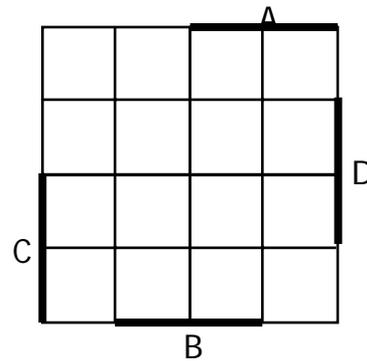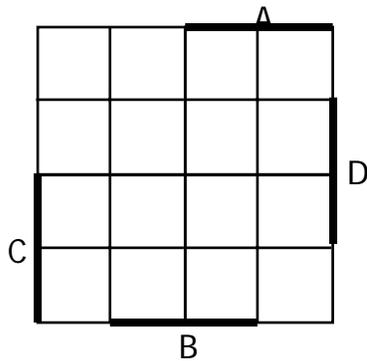

We also know that this function is a don't care for the cases where $A'CD$ is true. Fill in the modified K-map above on the right.

Find a minimum sum-of-products expression for this incompletely specified function.

Circle the essential prime implicants in your expression above.