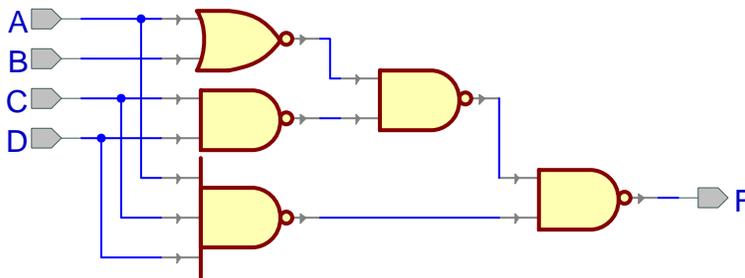


# CSE370 Quiz 1 (21 January)

Name \_\_\_\_\_ Solution \_\_\_\_\_

Given the following schematic:





Write down the Boolean expression corresponding to F (in any form).

$$\{ [(A+B)' (CD)']' (ACD)' \}' = (A+B)'(CD)' + ACD = A'B'(C' + D') + ACD = A'B'C' + A'B'D' + ACD$$

Write the expression in sum-of-products form ( $\Sigma$  notation).

$\Sigma m(0, 1, 2, 11, 15)$  - easier to get after filling in the K-map

Fill in the K-map below on the left.

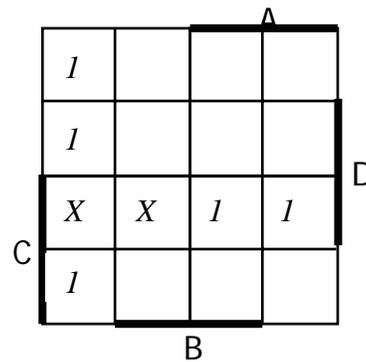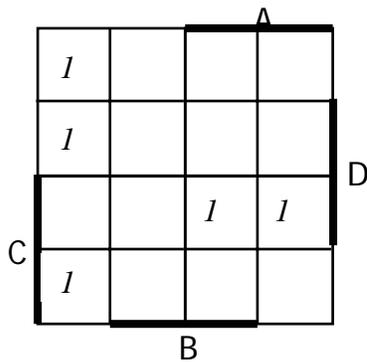

We also know that this function is a don't care for the cases where  $A'CD$  is true. Fill in the modified K-map above on the right.

Find a minimum sum-of-products expression for this incompletely specified function.

$$\textcircled{A'B'} + \textcircled{CD}$$

Circle the essential prime implicants in your expression above.