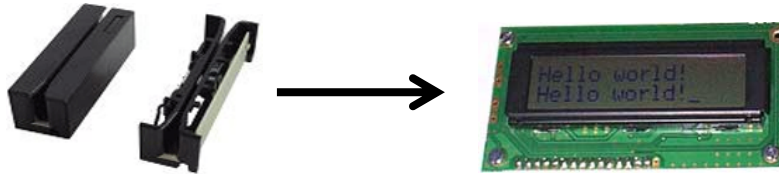


## Final Lab Project

- Magnetic stripe card reader to LCD display
- Solution will require four (4) 22V10 chips
- Given:
  - Schematic
  - test fixtures
- Your job:
  - Design the core of the PALs




Autumn 2006

CSE370 - IX - Final Project

1
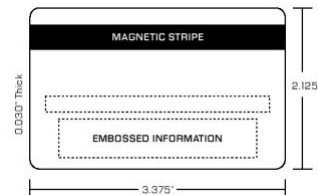
## Overview of Magnetic Stripe Cards

- Commonly used in credit, debit, transportation, and gift cards
- Magnetic material (iron-ion rich) is contained in a plastic-like film
  - Stripe is 5.66 mm from edge of card and is 9.52 mm wide
  - Contains three tracks, each 2.79 mm wide
    - Tracks one and three are typically recorded at 8.27 bits per mm
    - Track two typically has a recording density of 2.95 bits per mm
- Various ISO standards define format
  - 7810, 7811, 7812, 7813, and 4909
  - Defined by each industry



See [http://en.wikipedia.org/wiki/Magnetic\\_stripe\\_card](http://en.wikipedia.org/wiki/Magnetic_stripe_card) for details

0.223"	TRACK	Recording Density (Bits per inch)	Character Configuration (including parity bit)	Information Content (including control characters)
0.110"	1 IATA	210	7 bits per character	79 alphanumeric characters
0.110"	2 ABA	210	5 bits per character	40 numeric characters
0.110"	3 THRIFT	210	5 bits per character	107 numeric characters

Autumn 2006

CSE370 - IX - Final Project


2

# Overview of Magnetic Stripe Cards

- Data encoded as 7-bit characters
  - 6 bits for value (least significant bit first)
  - 1 bit for parity


BIT				CHARACTER SET			
b <sub>4</sub>	b <sub>3</sub>	b <sub>2</sub>	b <sub>1</sub>	b <sub>5</sub>	b <sub>6</sub>	b <sub>7</sub>	b <sub>8</sub>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	1
0	0	1	0	*	2	B	R
0	0	1	1	#	3	C	S
0	1	0	0	S	4	D	T
0	1	0	1	%	5	E	U
0	1	1	0	€	6	F	V
0	1	1	1	'	7	G	W
1	0	0	0	(	8	H	X
1	0	0	1	)	9	I	Y
1	0	1	0	*	:	J	Z
1	0	1	1	+	:	K	[
1	1	0	0	<	<	L	\
1	1	0	1	-	=	M	]
1	1	1	0	.	>	N	^
1	1	1	1	/	7	O	-

## Card Data Format - Track 1

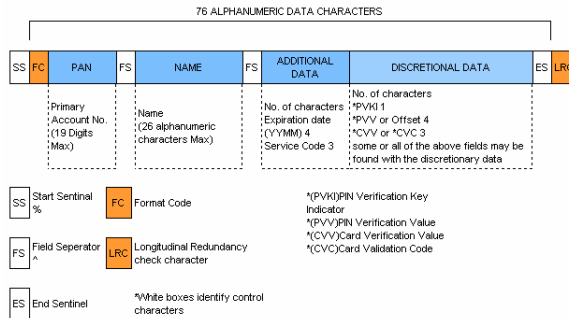

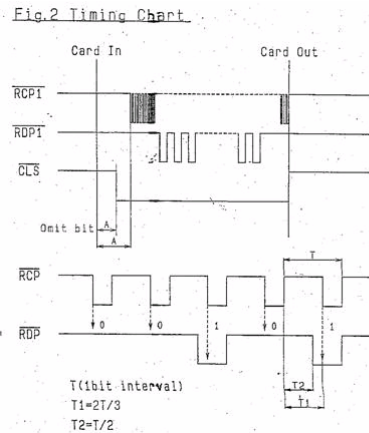
# Reader serial data format

- 3 signals
  - RCP – “clock”
    - RCP only oscillates if card is moving
  - RDP – data
    - CLS is only active if a card is present
- Decoding
  - Use RCP falling transition to sample RDP only when CLS is asserted



## Block diagram

- Major components
  - Reader outputs (simulation test fixture)
  - Reader buffer (logic that goes into XLA board's FPGA)
  - **LCD controller (Lab 9)**
  - **Reader signal decoder and serial-to-parallel converter (Lab 10)**
  - LCD display (simulation test fixture)

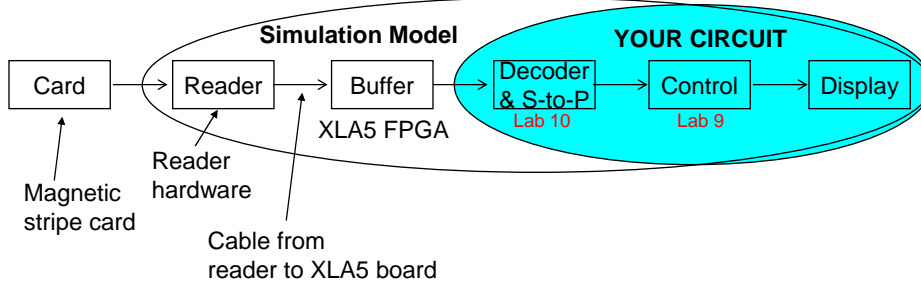


Autumn 2006

CSE370 - IX - Final Project


5
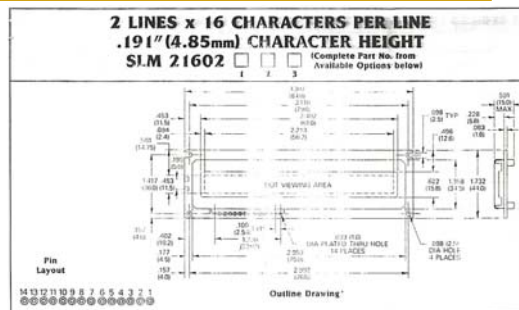
## LCD interface

- Eleven signal wires plus PWR/GND/ $V_o$ 
  - 1 mode input
  - 1 read/write control
  - 1 enable
  - 8 data lines



Interface Pin Connections

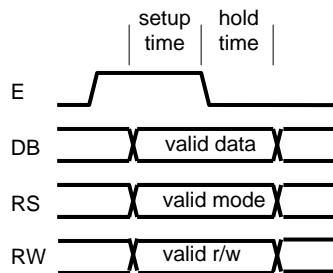

Pin No.	Symbol	Function
1	V <sub>SS</sub>	0V
2	V <sub>DD</sub>	+5V
3	V <sub>0</sub>	—
4	RS	H: Data input L: Instruction input
5	R/W	H: Read(MPU ← LCM) L: Write(MPU → LCM)
6	E	Enable signal
7	DB0	Data bus line
8	DB1	
9	DB2	
10	DB3	
11	DB4	
12	DB5	
13	DB6	
14	DB7	

Autumn 2006

CSE370 - IX - Final Project

6

## Basic LCD operations

- Requires sequence of 4 commands on initialization
- Many more commands
  - E.g., backup cursor, blink, etc.
- Data write prints character to display

Operation	RS	DB7...DB0
Clear Display	0	0000 0001
Function Set	0	0011 0011
Display On	0	0000 1100
Entry Mode Set	0	0000 0110
Write Character	1	DDDD DDDD

## ASCII codes


- Each character has a unique code
- Some codes could be used to issue commands to display
  - E.g., clear, backspace, etc.
  - These are extra credit

**CHARACTER FONT DATA CODES**  
UPPER 4-BIT HEXADECIMAL


	Higher 4-bit	0	1	2	3	4	5	6	7	A	B	C	D	E	F
	Lower 4-bit	0000	0010	0011	0100	0101	0110	0111	1010	1011	1100	1101	1110	1111	
	CS RAM (1)	0	1	2	3	4	5	6	7	8	9	A	B	C	D
0	xxxx0000														
1	xxxx0001	(2)	!	"	#	\$	%	&	'	(	)	*	+	,	-
2	xxxx0010	(3)	.	/	0	1	2	3	4	5	6	7	8	9	:
3	xxxx0011	(4)	@	A	B	C	D	E	F	G	H	I	J	K	L
4	xxxx0100	(5)	M	N	O	P	Q	R	S	T	U	V	W	X	Y
5	xxxx0101	(6)	Z	[	\	]	^	_	`	{		}	~		
6	xxxx0110	(7)													
7	xxxx0111	(8)													
8	xxxx1000	(9)													
9	xxxx1001	(A)													
A	xxxx1010	(B)													
B	xxxx1011	(C)													
C	xxxx1100	(D)													
D	xxxx1101	(E)													
E	xxxx1110	(F)													
F	xxxx1111	(F)													

LOWER 4-BIT HEXADECIMAL


## Block Diagram (lab 9)

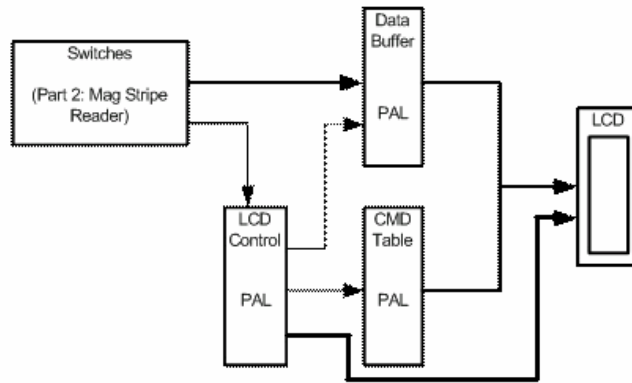

## Features of 22V10 PAL

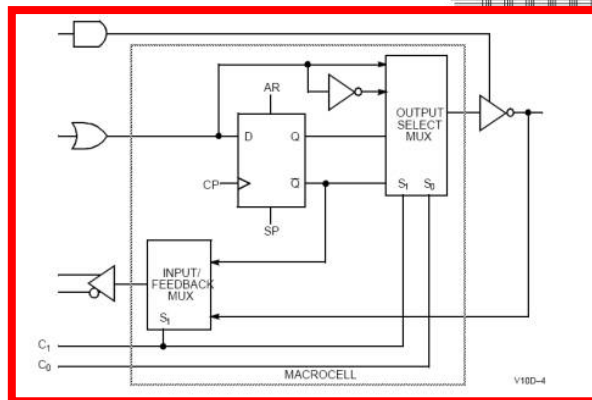

Functional Logic Diagram for PALC22V10D

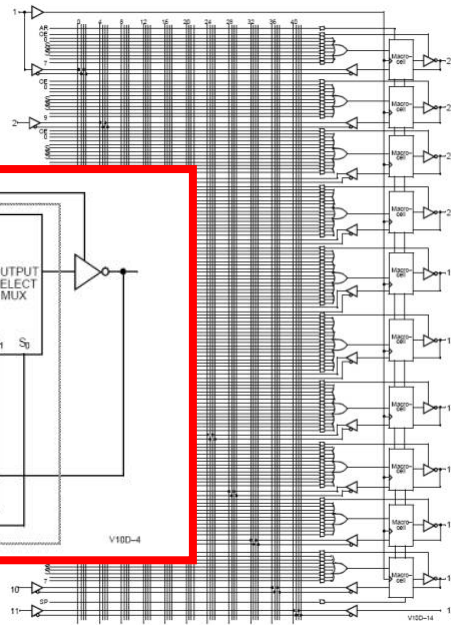

## Skeleton Verilog files

```
module lcd_control (clk, reset, write, EN, RS, CMD);
  input clk, reset;
  input write;      // Write a character to the LCD
  output EN, RS;   // Enable, RS signals of LCD
  output [1:0] CMD; // Index for current LCD command

  /* reg [??:??] state; */

  /* YOUR DECLARATIONS ETC. GO HERE */

  always @(posedge clk) begin
    /* YOUR SYNCHRONOUS CODE GOES HERE */
  end
endmodule
```

## Skeleton Verilog files (cont'd)

```
module lcd_cmd (RS, cmdIndex, lcdCMD);
  input RS;          // Used to tristate the LCD CMD
  input [1:0] cmdIndex; // Index of the command
  output [7:0] lcdCMD; // LCD command

  /* YOUR CODE HERE */
endmodule
```

```
module tri_driver (en, from, to);
  input en;
  input [7:0] from;
  output [7:0] to;

  assign to = (en) ? from : 8'bzzzzzzzz;
endmodule
```

## LCD test fixture (1 of 2)

```
module lcd_tf (reset, RS, EN, RW, data);
input reset, RS, EN, RW;
input [7:0] data;
reg [2:0] resetCnt; // Counts through the reset sequence
time dataTime, RSTime, ENTime, resetTime;
parameter CMD0 = 8'h1, CMD1 = 8'h33, CMD2 = 8'hC, CMD3 = 8'h6;
parameter hold = 7, setup = 7;

initial begin resetCnt = 0; dataTime = 0; RSTime = 0; ENTime = 0; end

always @(negedge reset) resetTime = $time;

always @(data) begin
dataTime = $time;
if (!reset && (dataTime != resetTime) && (EN==0) && (($time - ENTime) < hold)) begin
$display("Error: Data hold time not met: %t", ($time-ENTime));
$stop;
end
end

always @(RS) begin
RSTime = $time;
if (!reset && (RSTime != resetTime) && (EN==0) && ($time - ENTime) < hold) begin
$display("Error: RS hold time not met: %t", ($time-ENTime));
$stop;
end
end

always @(posedge EN) begin
ENTime = $time;
// Check RS setup time - there is no setup/hold wrt. data
if ((ENTime != resetTime) && ($time - RSTime) < setup) begin
$display("Error: RS setup time not met: %t", ($time-RSTime));
$stop;
end
end

end

...
endmodule
```


13

## LCD test fixture (2 of 2)

```
always @(negedge EN) begin
if (reset == 0) begin
ENTime = $time;
if (($time - dataTime) < setup) begin
$display("Error: Data setup time not met: %t", ($time-dataTime)); $stop;
end
if (($time - RSTime) < setup) begin
$display("Error: RS setup time not met: %t", ($time-RSTime)); $stop;
end
if (RW != 0) begin
$display("Error: RW should be 0"); $stop;
end
if (RS == 0) begin // Writing a command
case (resetCnt)
0: begin // First reset
if (data == CMD0) begin $display("Display cleared"); resetCnt = 1;
end else begin $display("Error: Invalid reset command 0"); $stop;
end
end
1: begin
if (data == CMD1) begin $display("Display function set"); resetCnt = 2;
end else begin $display("Error: Invalid reset command 1"); $stop;
end
end
2: begin
if (data == CMD2) begin $display("Display turned on"); resetCnt = 3;
end else begin $display("Error: Invalid reset command 2"); $stop;
end
end
3: begin
if (data == CMD3) begin $display("Display entry mode set"); resetCnt = 4;
end else begin $display("Error: Invalid reset command 3"); $stop;
end
end
default: begin $display("Error: Too many reset commands"); $stop; end
endcase // case(resetCnt)
end else if (RS == 1) begin // Writing a character
if (resetCnt != 4) begin $display("Display has not been properly reset"); end
$display("Write Character: %c", data);
end // else: !if(RS == 0)
end // if (reset == 0)
end // always @ (negedge EN)
endmodule
```

14

## Block Diagram (lab 10)

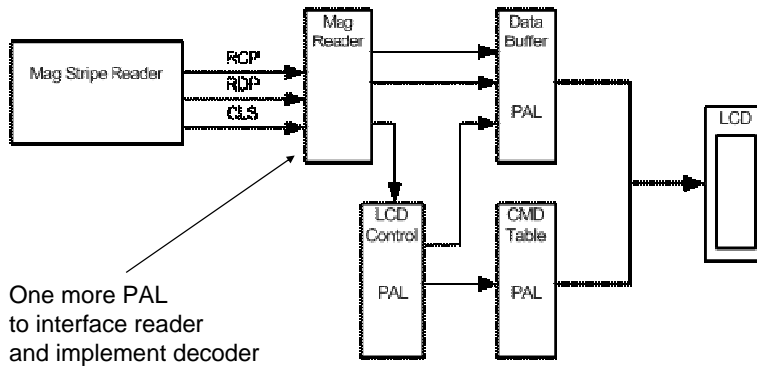

## Magnetic stripe reader test fixture (1 of 2)

```

module magreader_tf (reset, clk, outRCP, outRDP, outCLS);
input reset, clk;
output outRCP, outRDP, outCLS;
reg outCLS, outReset;

reg intrCP;
assign outRCP = intrCP;

integer delay = 0; // Generate delays
integer count = 0; // Count bits we have sent
parameter CLS_STATE = 0;

// These specify the delays in terms of clock cycles
parameter BEFORECLS = 14, // From reset to CLS asserted
AFTERCLS = 25, // From reset to first clock
CPHIGH = 1, CPLOW = 3, // Clock high and low time
CLSDONE = 4; // From end of data to CLS off

parameter BUFSIZE = 64; // Number of bits sent

// Buffer for input data bits
reg [BUFSIZE-1:0] data;
// RDP output from data buffer
assign outRDP = ~data[0];

// States used to generate data
parameter CLS = 0, DATA = 1, DONE = 2;

reg [1:0] state;

...

```



## Magnetic stripe reader test fixture (2 of 2)

```
always @(posedge clk) begin
  if (reset) begin
    // Make sure the low order bits are the sentinel character.
    // data[0] is the first high bit for initialization
    data <= 64'b00000_0000001_0000001_0010000_0101100_0101100_0100101_1101000_1000101_000;
    state <= CLS; // Start by asserting CLS
    delay <= 0;
    count <= 0;
    outCLS <= 1;
    intrCP <= 1;
    outReset <= 1;
  end else begin
    delay <= delay + 1;
    case (state)
      CLS: begin
        outReset <= 0;
        if (delay == BEFORECLS) begin outCLS <= 0;
        end else if (delay == AFTERCLS) begin state <= DATA; delay <= 0;
        end
      end // case: CLS
      DATA: begin
        if (delay == CPHIGH) begin intrCP <= 0;
        end else if (delay == (CPHIGH+CPLOW)) begin
          delay <= 0;
          intrCP <= 1;
          count <= count + 1;
          data <= { 1'b0, data[(BUFSIZE-1):1] }; // Shift data right
          if (count == (BUFSIZE-1)) state <= DONE;
        end
      end // case: DATA
      DONE: begin
        if (~outCLS && (delay == CLSDONE)) begin outCLS <= 1; end
      end // case: DONE
    endcase // case(state)
  end // else: !if(reset)
end // always @ (posedge clk)
endmodule // magreader_tf
```

## Purpose of the project

- Learn how to build a realistic system
- Read data sheets
- Communicating state machines
- Deal with existing code/components