 


# CSE 370 Spring 2006

## Introduction to Digital Design

### Lecture 9: Multilevel Logic



#### Last Lecture

- Introduction to Verilog

#### Today

- Multilevel Logic
- Hazards

## Administrivia

- Hand in Homework #3
- Homework #3 posted this afternoon
- Lab #4 posted.

- A note from Adrienne:

When it says write an expression in canonical minterm form or canonical maxterm form, unless it explicitly says to use the shorthand m and M notation, please write a Boolean expression. (Not deducted for in HW#2-#3 or on the Quiz.)

## Sequential Verilog-- Blocking and non-blocking assignments

- Blocking assignments ( $Q = A$ )
  - Variable is assigned immediately
  - New value is used by subsequent statements
- Non-blocking assignments ( $Q <= A$ )
  - Variable is assigned after all scheduled statements are executed
  - Value to be assigned is computed but saved for later
- Usual use: Register assignment
  - Registers simultaneously take new values after the clock edge

- Example: Swap

```
always @(posedge CLK)
begin
    temp = B;
    B = A;
    A = temp;
end
```


```
always @(posedge CLK)
begin
    A <= B;
    B <= A;
end
```

## Sequential Verilog-- Assignments- watch out!

- Blocking versus Non-blocking


```
reg B, C, D;

 always @(posedge clk)
begin
    B = A;
    C = B;
    D = C;
end
```





```
reg B, C, D;

 always @(posedge clk)
begin
    B <= A;
    C <= B;
    D <= C;
end
```



  
# Timing diagrams

- “Sideways” truth tables
  - Show time-response of circuits
  - Real gates have real delays
- Example:  $A' \cdot A = 0$ 
  - Delays cause transient  $F=1$




Some texts call timing diagrams “waveforms”

# Example: $F=A+BC$ in 2-level logic

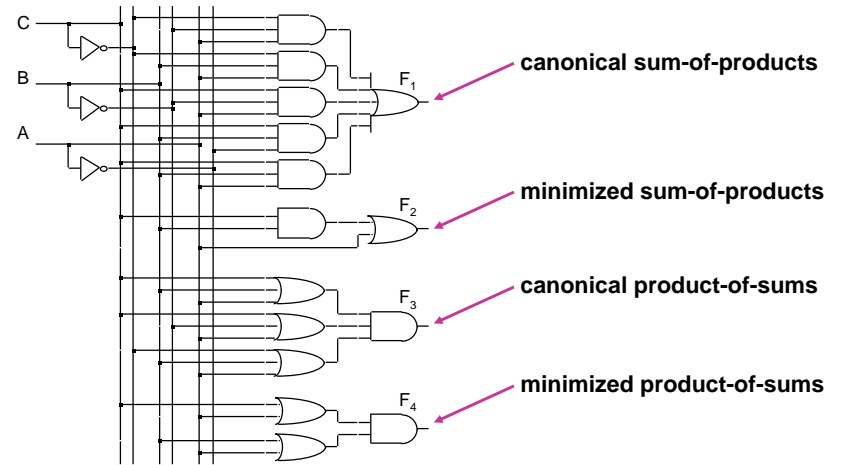
 
# Timing diagram for $F = A + BC$

- Time waveforms for  $F_1 - F_4$  are identical
  - Except for timing hazards (glitches)
  - More on this shortly...



# Multilevel logic

- Basic idea: Simplify logic using >2 gate levels
  - Time-space (speed versus gate count) tradeoff
- Two-level logic *usually*
  - Has smaller delays (faster circuits)
    - But more gates and more wires (more circuit area)
    - Sometimes has large fan-ins (slow)
  - Easier to eliminate hazards
- Multilevel logic *usually*
  - Has less gates (smaller circuits)
    - But can be slower (more gate delays)
  - Harder to eliminate hazards

# Multilevel logic example

## Function X

SOP:  $X = ADF + AEF + BDF + BEF + CDF + CEF + G$


X is minimized!

Six 3-input ANDs; one 7-input OR; 25 wires

Multilevel:  $X = (A+B+C)(D+E)F + G$


Factored form

 One 3-input OR, two 2-input OR's, one 3-input AND; 10 wires




# Multilevel NAND/NAND conversion

$$F = A(B+CD) + BC'$$

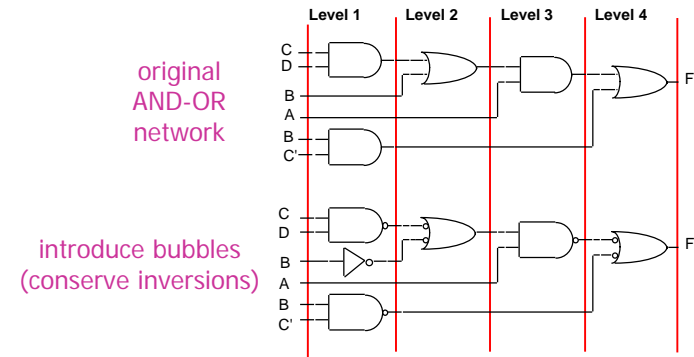


# Multilevel NOR/NOR conversion

$$F = A(B+CD) + BC'$$

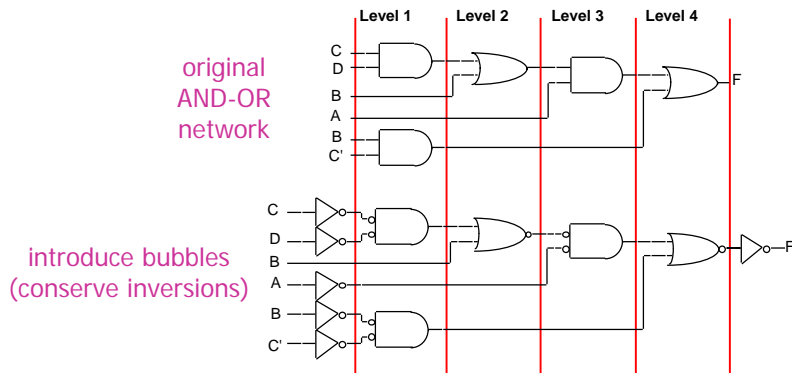



# Generic multilevel conversion

$$F = ABC + BC + D = AX + X + D$$

 
  
# AND-OR-Invert and OR-AND-Invert blocks


- AOI and OAI are dense 3-level building blocks
  - 2x2 AOI uses only 8 transistors
  - Minimal delay


 
# Using AOI and OAI blocks

- Approach
  - Start by finding  $F'$ 
    - If using AOI, find  $F'$  in minimized SOP form
    - If using OAI, find  $F'$  in minimized POS form

- Form AOI as  $(F')'$
- Example:  $F = A'B + AB'$ 
  - SOP form:  $F' = A'B' + AB$
  - AOI form:  $F = (A'B' + AB)'$




# Example: AOI and OAI

		<u>A</u>			
		0	1	1	1
C		0	0	1	0
		<u>B</u>			

AOI form – Use SOP

$$F' = A'B' + A'C + B'C$$


$$F = (A'B' + A'C + B'C)'$$

 

OAI form – Use POS

$$F' = (B'+C)(A'+C)(A'+B')$$

$$F = [(B'+C)(A'+C)(A'+B')]'$$

 

# Issues with multilevel design

- No global definition of “optimal” multilevel circuit
  - Optimality depends on user-defined goals
  - **Synthesize** an implementation that meets design goals
- Synthesis requires CAD-tool help
  - No simple hand methods like K-maps
  - CAD tools manipulate Boolean expressions
    - Factoring, decomposition, etc.
  - Covered in more detail in CSE467

## Multilevel logic summary

- Advantages over 2-level logic
  - Smaller circuits
  - Reduced fan-in
  - Less wires
- Disadvantages w.r.t 2-level logic
  - More difficult design
  - Less powerful optimizing tools
  - Dynamic hazards
- What you should know for CSE370
  - The basic multilevel idea
  - Multilevel NAND/NAND and NOR/NOR conversion
  - AOI gates

## Hazards/glitches

- Hazards/glitches: Undesired output switching
  - Occurs when different pathways have different delays
  - Wastes power; causes circuit noise
  - Dangerous if logic makes a decision while output is unstable
  - Dangerous if using asynchronous circuits
- Solutions
  - Design hazard-free circuits
    - Difficult when logic is multilevel
  - Wait until signals are stable
  - Use synchronous circuits

## Types of hazards


- Static 1-hazard
  - Output should stay logic 1
  - Gate delays cause brief glitch to logic 0



- Static 0-hazard
  - Output should stay logic 0
  - Gate delays cause brief glitch to logic 1





 - Dynamic hazards
  - Output should toggle cleanly
  - Gate delays cause multiple transitions


  
## Static hazards


- Occur when a literal and its complement momentarily assume the same value
  - Through different paths with different delays
  - Causes an (ideally) static output to *glitch*



static-0 hazard
 
## Dynamic hazards


- Occur when a literal assumes multiple values
  - Through different paths with different delays
  - Causes an output to toggle multiple times



## Eliminating static hazards

- In 2-level logic circuits
  - Assuming single-bit changes
- Key idea: Glitches happen when a changing input spans separate k-map encirclements
  - Example: 1101 to 0101 change can cause a static-1 glitch

$$F = AC' + A'D$$

 


		A			
	AB	00	01	11	10
C	00	0	0	1	1
	01	1	1	1	1
	11	1	1	0	0
	10	0	0	0	0
		B		D	

## Eliminating static hazards (con't)

- Solution: Add redundant k-map encirclements
  - Ensure that all single-bit changes are covered
  - First eliminate static-1 hazards: Use SOP form

$$F = AC' + A'D + C'D$$

 

		A			
	AB	00	01	11	10
C	00	0	0	1	1
	01	1	1	1	1
	11	1	1	0	0
	10	0	0	0	0
		B		D	

## Summary of hazards

- We can eliminate static hazards in 2-level logic
  - For single-bit changes
  - Eliminating static hazards also eliminates dynamic hazards
- Hazards are a difficult problem
  - Multiple-bit changes in 2-level logic are hard
  - Static hazards in multilevel logic are harder
  - Dynamic hazards in multilevel logic are harder yet
- CAD tools and simulation/testing are indispensable
  - Test vectors probe a design for hazards

