 


# CSE 370 Spring 2006

## Introduction to Digital Design

### Lecture 25: Computer Organization



#### Last Lecture

- Design Examples


#### Today

- Computer Organization

The following is a state transition table for a FSM which takes as input one bit, X and outputs one bit O. The machine is a Moore machine.

Current State	Current O	Next State	
		X=0	X=1
S1	0	S2	S4
S2	0	S2	S7
S3	0	S7	S4
S4	1	S3	S6
S5	0	S2	S4
S6	0	S7	S4
S7	1	S6	S3

 $S_1 \equiv S_8$   
 $S_5 \equiv S_2$   
 $\Downarrow$   
 $S_1 \equiv S_2$



$S_1 \equiv S_8 \equiv S_2$   
 $S_5 \equiv S_6$   
 $S_4 \equiv S_7$

## Administrivia

- Homework 9 out. Due June 2.

Extra Credit  
 → extra quiz  
 → HW points


Posted Tonight

## Computer organization

- Computer design – an application of digital logic design procedures
- Computer = processing unit + memory system
- Processing unit = control + datapath
- Control = finite state machine
  - inputs = machine instruction, datapath conditions
  - outputs = register transfer control signals, ALU operation codes
  - instruction interpretation = instruction fetch, decode, execute
- Datapath = functional units + registers
  - functional units = ALU, multipliers, dividers, etc.
  - registers = program counter, shifters, storage registers


# Structure of a computer

## Block diagram view

 
 
# Registers

- Selectively loaded – EN or LD input
- Output enable – OE input
- Multiple registers – group 4 or 8 in parallel




OE asserted causes FF state to be connected to output pins; otherwise they are left unconnected (high impedance)

LD asserted during a lo-to-hi clock transition loads new data into FFs

# Register transfer

 
## Point-to-point connection

- dedicated wires
- muxes on inputs of each register



 
## Common input from multiplexer

- load enables for each register
- control signals for multiplexer


 
## Common bus with output enables

- output enables and load enables for each register




# Register files

## Collections of registers in one package

- two-dimensional array of FFs
- address used as index to a particular word
- can have separate read and write addresses so can do both at same time

 
## 4 by 4 register file

- 16 D-FFs
- organized as four words of four bits each
- write-enable (load)
- read-enable (output enable)


 
## Memories

- Larger collections of storage elements
  - implemented not as FFs but as much more efficient latches
  - high-density memories use 1 to 5 switches (transistors) per memory bit
- Static RAM – 1024 words each 4 bits wide
  - once written, memory holds forever (not true for denser dynamic RAM)
  - address lines to select word (10 lines for 1024 words)
  - read enable
    - same as output enable
    - often called chip select
    - permits connection of many chips into larger array
  - write enable (same as load enable)
  - bi-directional data lines
    - output when reading, input when writing



## Instruction sequencing

- Example – an instruction to add the contents of two registers (Rx and Ry) and place result in a third register (Rz)
- Step 1: get the ADD instruction from memory into an instruction register
- Step 2: decode instruction
  - instruction in IR has the code of an ADD instruction
  - register indices used to generate output enables for registers Rx and Ry
  - register index used to generate load signal for register Rz
- Step 3: execute instruction
  - enable Rx and Ry output and direct to ALU
  - setup ALU to perform ADD operation
  - direct result to Rz so that it can be loaded into register

## Instruction types

- Data manipulation
  - add, subtract
  - increment, decrement
  - multiply
  - shift, rotate
  - immediate operands
- Data staging
  - load/store data to/from memory
  - register-to-register move
- Control
  - conditional/unconditional branches in program flow
  - subroutine call and return

## Elements of the control unit (aka instruction unit)

- Standard FSM elements
  - state register
  - next-state logic
  - output logic (datapath/control signalling)
  - Moore or synchronous Mealy machine to avoid loops unbroken by FF
- Plus additional "control" registers
  - instruction register (IR)
  - program counter (PC)
- Inputs/outputs
  - outputs control elements of data path
  - inputs from data path used to alter flow of program (test if zero)

# Instruction execution


- Control state diagram (for each diagram)

- reset
- fetch instruction
- decode
- execute

- Instructions partitioned into three classes

- branch
- load/store
- register-to-register

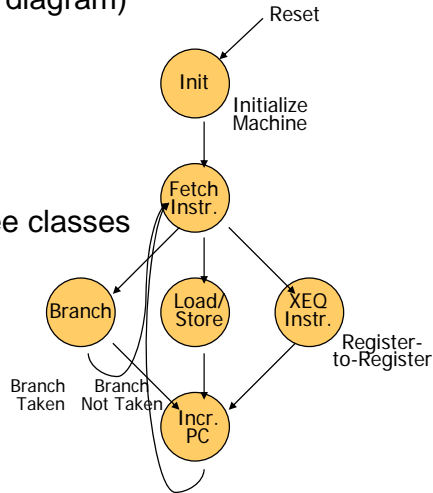
- Different sequence through diagram for each instruction type


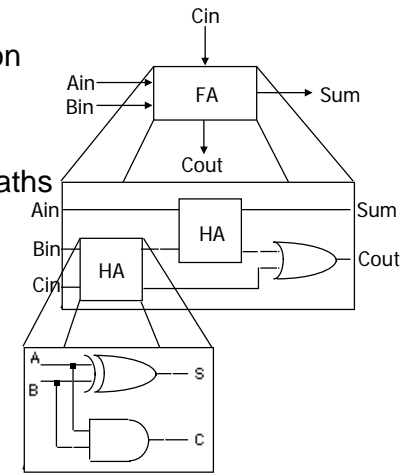
# Data path (hierarchy)

- Arithmetic circuits constructed in hierarchical and modular fashion


- each bit in datapath is functionally identical
- 4-bit, 8-bit, 16-bit, 32-bit datapaths


 
# Data path (ALU)

- ALU block diagram

- input: data and operation to perform
- output: result of operation and status information



# Data path (ALU + registers)

- Accumulator


- special register
- one of the inputs to ALU
- output of ALU stored back in accumulator

- One-address instructions

- operation and address of one operand
- other operand and destination is accumulator register
- $AC \leftarrow AC \text{ op Mem}[\text{addr}]$
- "single address instructions" (AC implicit operand)


- Multiple registers

 - part of instruction used to choose register operands


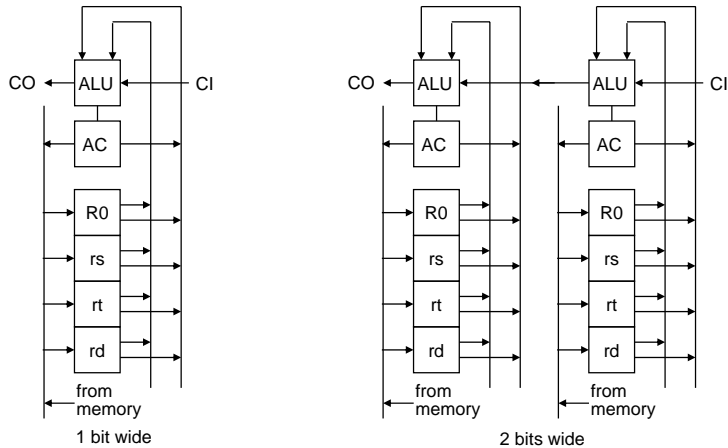
## Data path (bit-slice)

- Bit-slice concept – replicate to build n-bit wide datapaths



## Instruction path


- Program counter (PC)
  - keeps track of program execution
  - address of next instruction to read from memory
  - may have auto-increment feature or use ALU
- Instruction register (IR)
  - current instruction
  - includes ALU operation and address of operand
  - also holds target of jump instruction
  - immediate operands
- Relationship to data path
  - PC may be incremented through ALU
  - contents of IR may also be required as input to ALU – immediate operands

## Data path (memory interface)

- Memory
  - separate data and instruction memory (Harvard architecture)
    - two address busses, two data busses
  - single combined memory (Princeton architecture)
    - single address bus, single data bus
- Separate memory
  - ALU output goes to data memory input
  - register input from data memory output
  - data memory address from instruction register
  - instruction register from instruction memory output
  - instruction memory address from program counter
- Single memory
  - address from PC or IR
  - memory output to instruction and data registers
  - memory input from ALU output
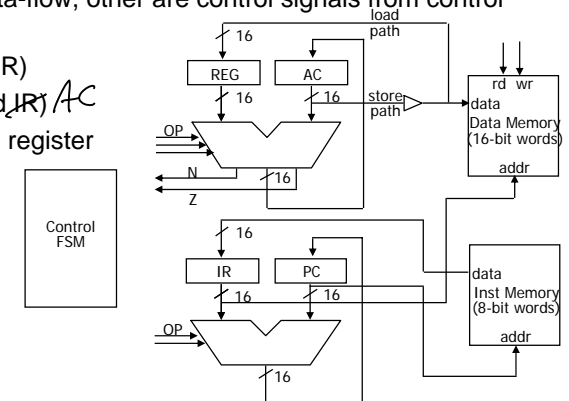
## Block diagram of processor (Harvard)

- Register transfer view of Harvard architecture
  - which register outputs are connected to which register inputs
  - arrows represent data-flow, other are control signals from control FSM
  - two MARs (PC and IR)
  - two MBRs (REG and IR)
  - load control for each register



# Block diagram of processor (Princeton)

## ■ Register transfer view of Princeton architecture

- which register outputs are connected to which register inputs
- arrows represent data-flow, other are control signals from control FSM
- MAR may be a simple multiplexer
- rather than separate register
- MBR is split in two (REG and IR)
- load control for each register

