 


# CSE 370 Spring 2006

## Introduction to Digital Design

### Lecture 26: Computer Organization



#### Last Lecture

- Computer Organization


#### Today

- More Computer Organization

# Administrivia

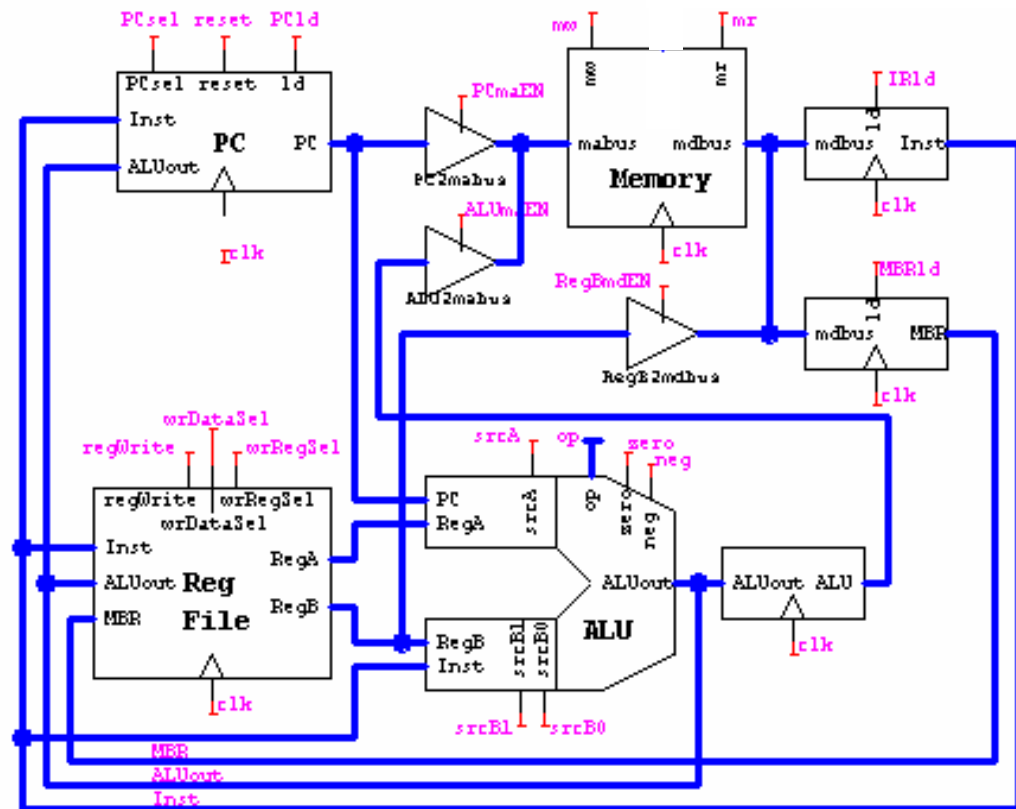
# A simplified processor data-path and memory

- Princeton architecture
- Register file
- Instruction register
- PC incremented through ALU
- Modeled after MIPS rt000 (used in 378 textbook by Patterson & Hennessy)
  - really a 32-bit machine
  - we'll do a 16-bit version


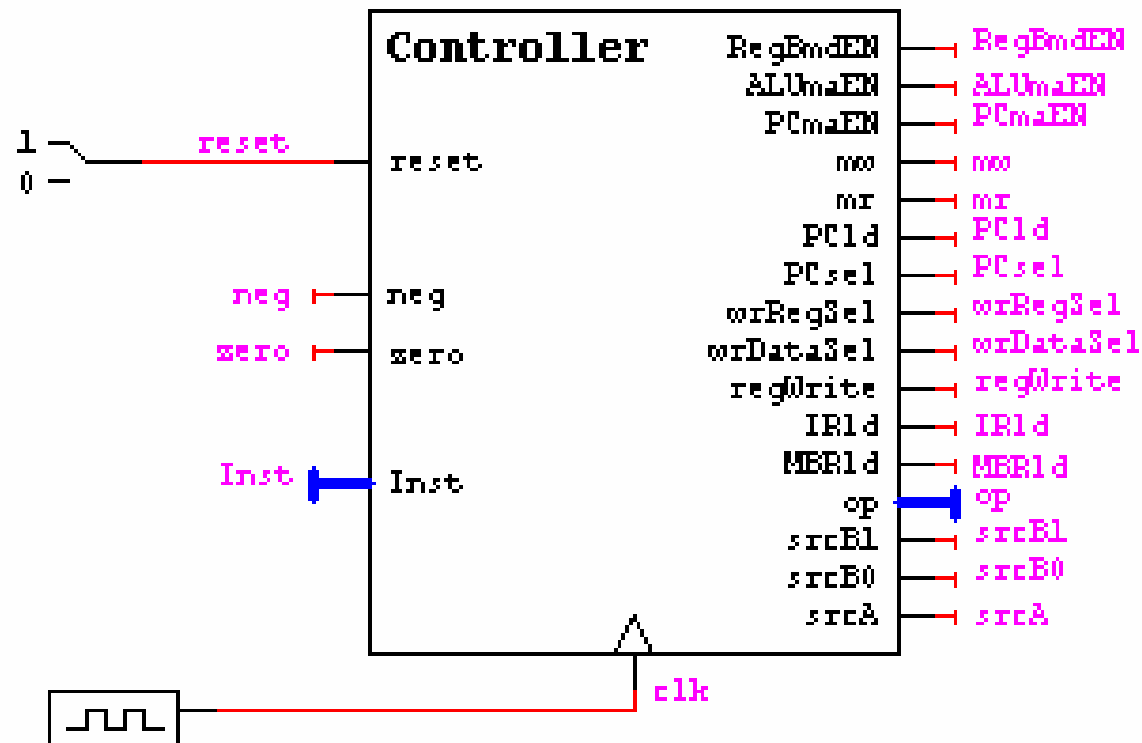
# Processor control

- Synchronous Mealy or Moore machine
- Multiple cycles per instruction



# Processor instructions

- Three principal types (16 bits in each instruction)

type	op	rs	rt	rd	funct
R(egister)	3	3	3	3	4
I(mmediate)	3	3	3	7	
J(ump)	3	13			

- Some of the instructions

R	add	0	rs	rt	rd	0	$rd = rs + rt$
	sub	0	rs	rt	rd	1	$rd = rs - rt$
	and	0	rs	rt	rd	2	$rd = rs \& rt$
	or	0	rs	rt	rd	3	$rd = rs   rt$
	slt	0	rs	rt	rd	4	$rd = (rs < rt)$
I	lw	1	rs	rt	offset		$rt = mem[rs + offset]$
	sw	2	rs	rt	offset		$mem[rs + offset] = rt$
	beq	3	rs	rt	offset		$pc = pc + offset, \text{ if } (rs == rt)$
	addi	4	rs	rt	offset		$rt = rs + offset$
J	j	5	target address				$pc = \text{target address}$
	halt	7	-				stop execution until reset

# Tracing an instruction's execution

- Instruction:  $r3 = r1 + r2$

R    

0	rs=r1	rt=r2	rd=r3	funct=0
---	-------	-------	-------	---------

- 1. instruction fetch
  - move instruction address from PC to memory address bus
  - assert memory read
  - move data from memory data bus into IR
  - configure ALU to add 1 to PC
  - configure PC to store new value from ALUout
- 2. instruction decode
  - op-code bits of IR are input to control FSM
  - rest of IR bits encode the operand addresses (rs and rt)
    - these go to register file

# Tracing an instruction's execution (cont'd)

- Instruction:  $r3 = r1 + r2$


R 

0	rs=r1	rt=r2	rd=r3	funct=0
---	-------	-------	-------	---------

- 3. instruction execute
  - set up ALU inputs
  - configure ALU to perform ADD operation
  - configure register file to store ALU result (rd)

# Tracing an instruction's execution (cont'd)


## ■ Step 1

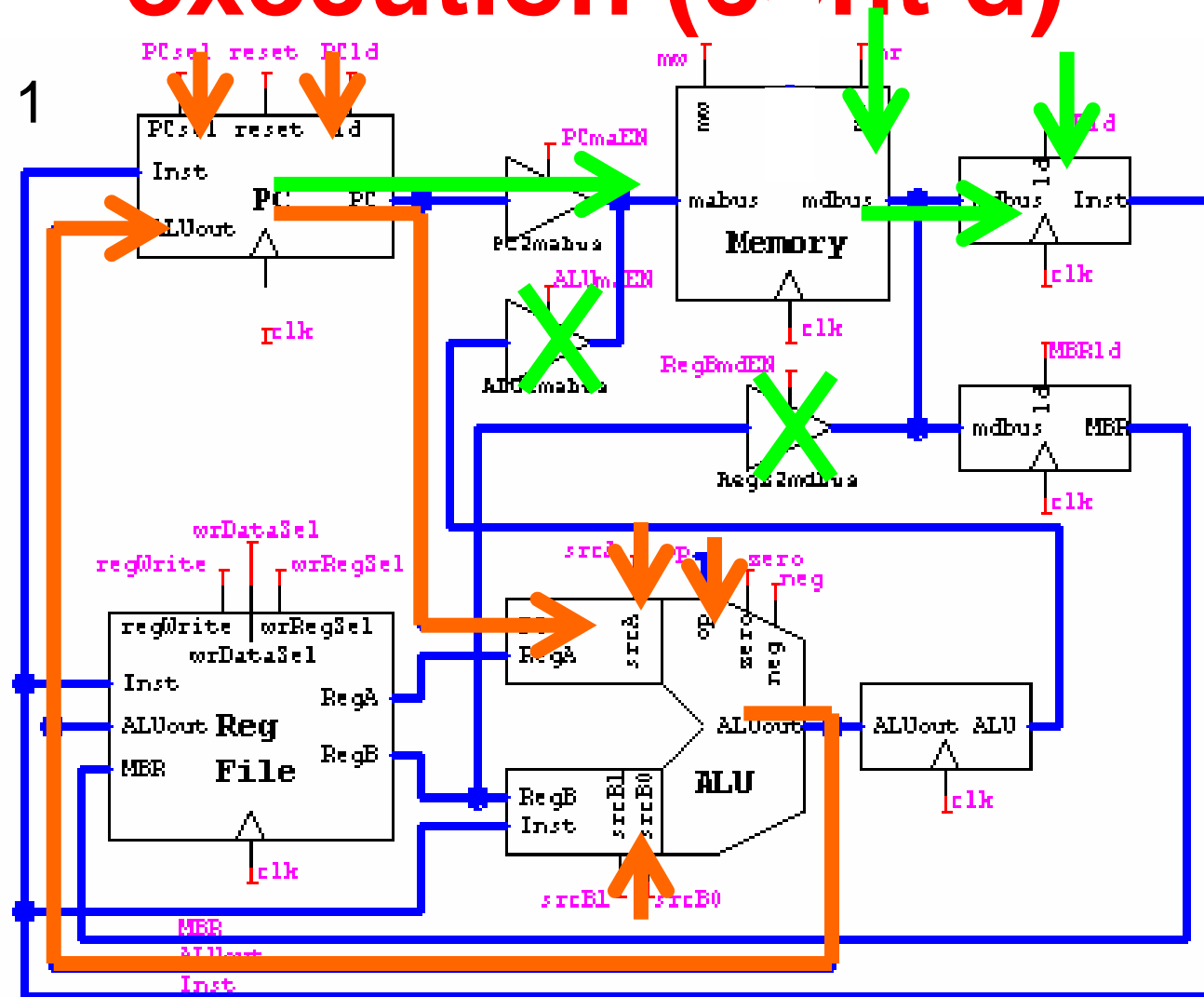




# Tracing an instruction's execution (cont'd)

## ■ Step 2

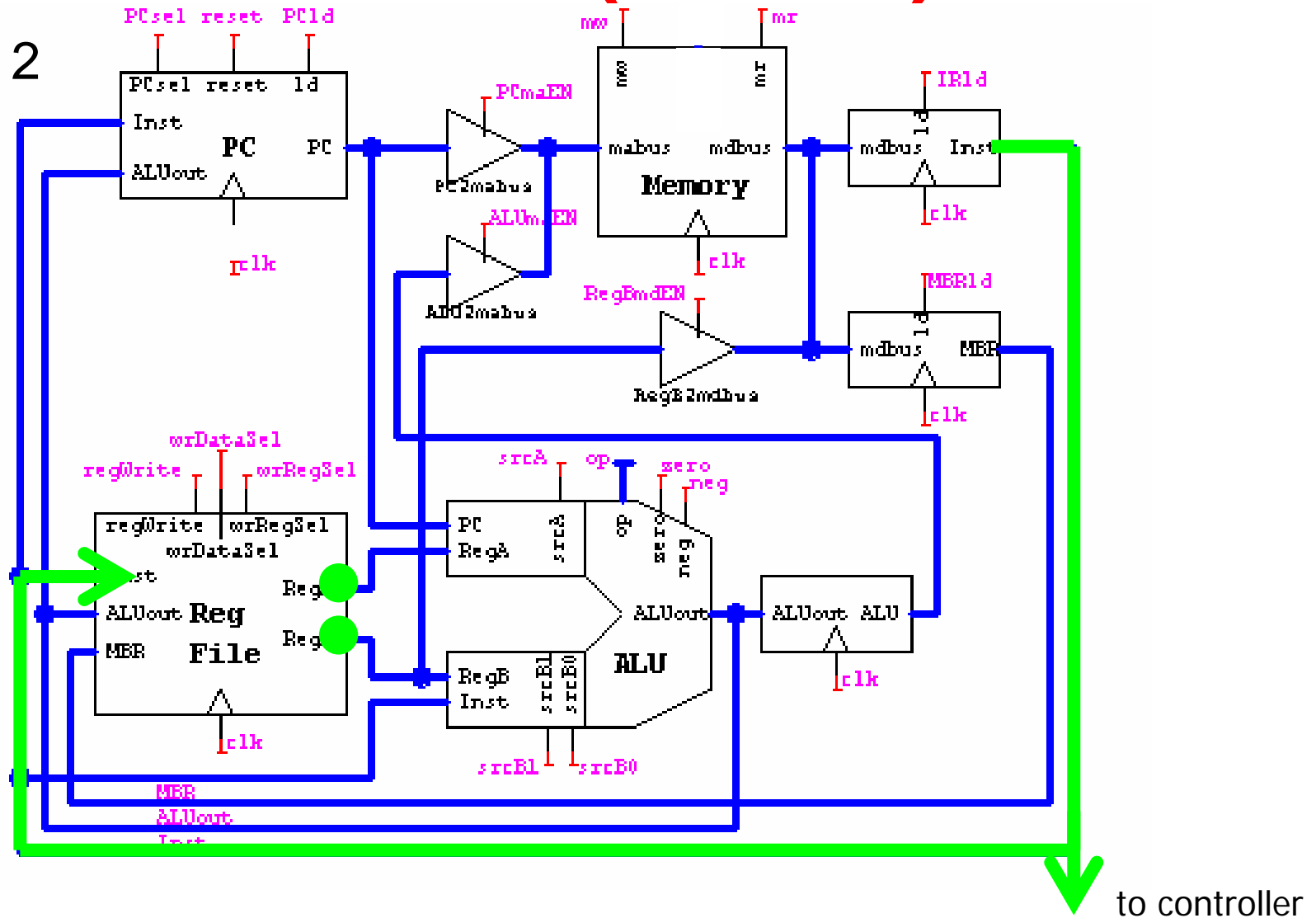

# Tracing an instruction's execution (cont'd)

## ■ Step 3

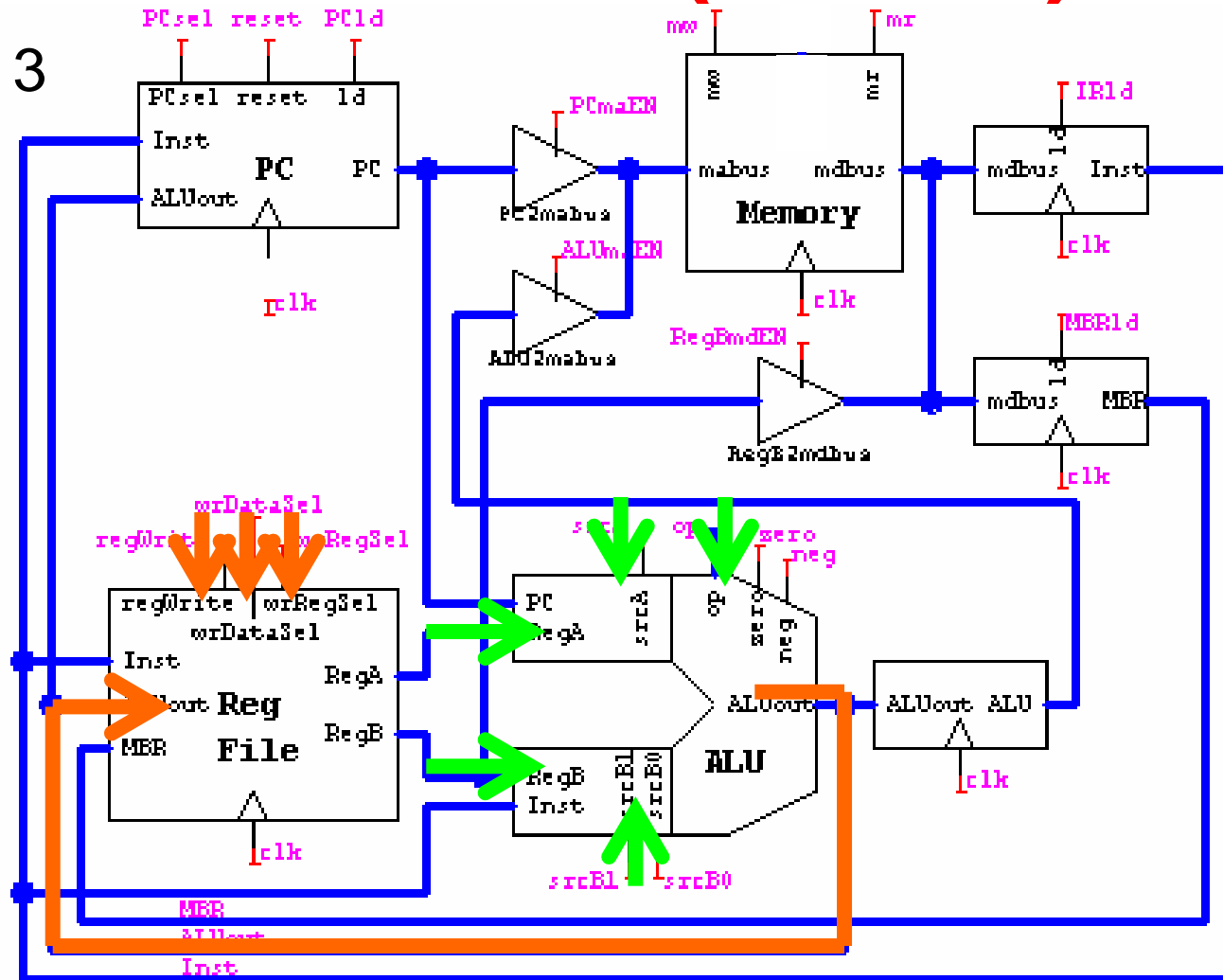


# Register-transfer-level description

- Control
  - transfer data between registers by asserting appropriate control signals
- Register transfer notation - work from register to register
  - instruction fetch:
    - mabus  $\leftarrow$  PC; – move PC to memory address bus (PCmaEN, ALUmaEN)
    - memory read; – assert memory read signal (mr, RegBmdEN)
    - IR  $\leftarrow$  memory; – load IR from memory data bus (IRld)
    - op  $\leftarrow$  add – send PC into A input, 1 into B input, add (srcA, srcB0, scrB1, op)
    - PC  $\leftarrow$  ALUout – load result of incrementing in ALU into PC (PCld, PCsel)
  - instruction decode:
    - IR to controller
    - values of A and B read from register file (rs, rt)
  - instruction execution:
    - op  $\leftarrow$  add – send regA into A input, regB into B input, add (srcA, srcB0, scrB1, op)
    - rd  $\leftarrow$  ALUout – store result of add into destination register (regWrite, wrDataSel, wrRegSel)

# Register-transfer-level description (cont'd)

- How many states are needed to accomplish these transfers?
  - data dependencies (where do values that are needed come from?)
  - resource conflicts (ALU, busses, etc.)
- In our case, it takes three cycles
  - one for each step
  - all operation within a cycle occur between rising edges of the clock
- How do we set all of the control signals to be output by the state machine?
  - depends on the type of machine (Mealy, Moore, synchronous Mealy)


# Review of FSM timing

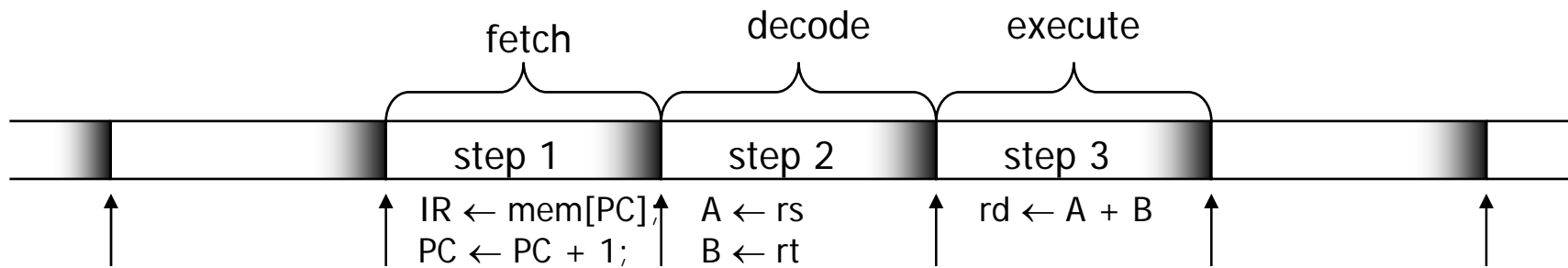

to configure the data-path to do this here,  
when do we set the control signals?
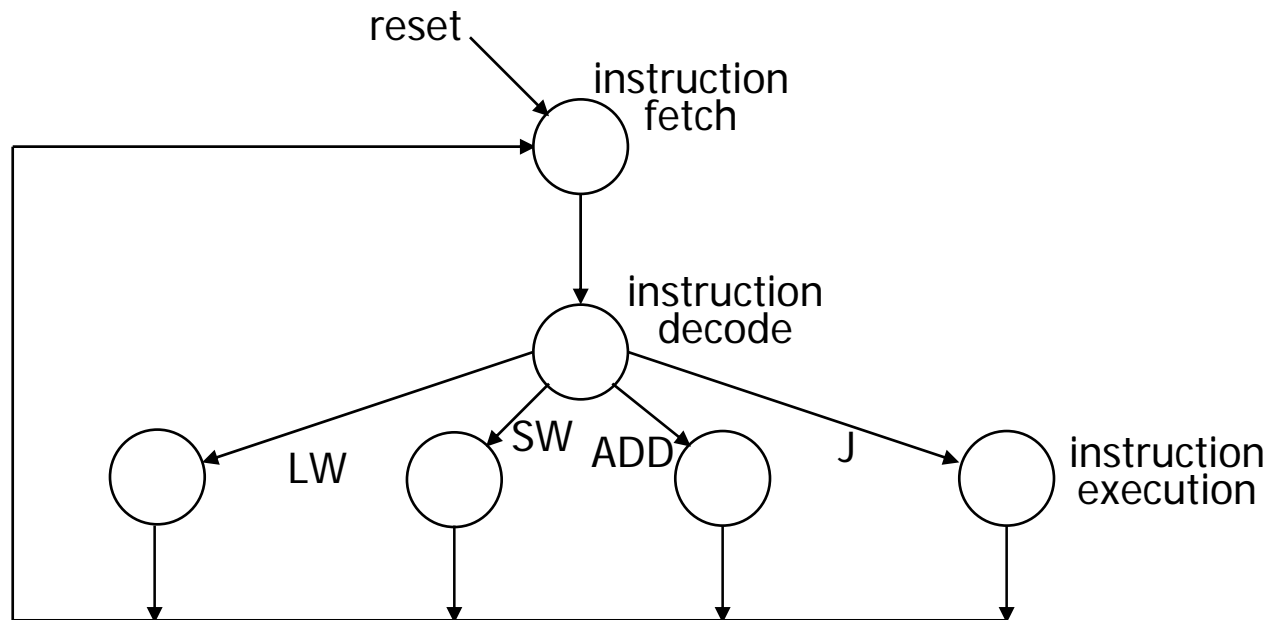
# FSM controller for CPU (skeletal Moore FSM)


- First pass at deriving the state diagram (Moore machine)
  - these will be further refined into sub-states


 
# FSM controller for CPU (reset and inst. fetch)


- Assume Moore machine
  - outputs associated with states rather than arcs
- Reset state and instruction fetch sequence
- On reset (go to Fetch state)
  - start fetching instructions
  - PC will set itself to zero

mabus  $\leftarrow$  PC;  
memory read;  
IR  $\leftarrow$  memory data bus;  
PC  $\leftarrow$  PC + 1;


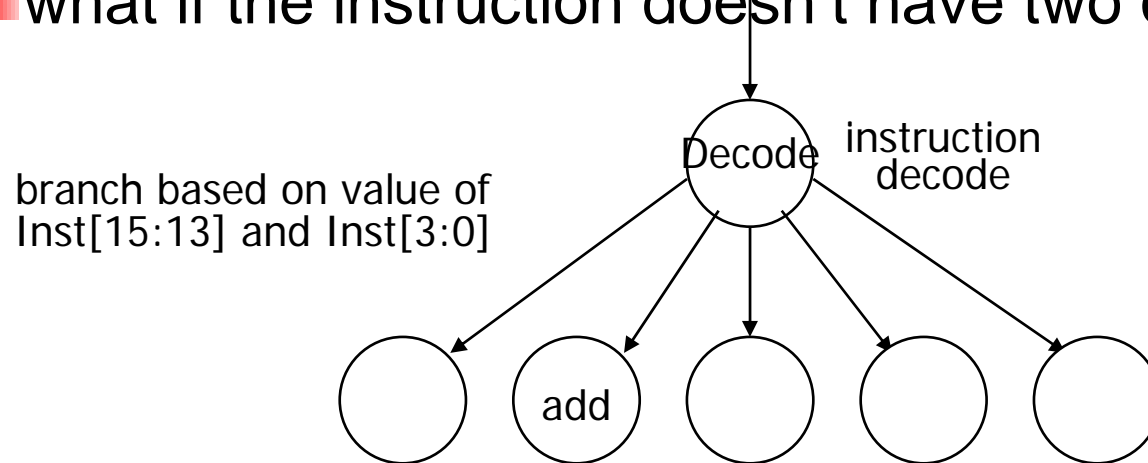
# FSM controller for CPU (decode)

- Operation decode state
  - next state branch based on operation code in instruction
  - read two operands out of register file
  - what if the instruction doesn't have two operands?






# FSM controller for CPU (instruction execution)

- For add instruction
  - configure ALU and store result in register

$$rd \leftarrow A + B$$

 
- other instructions may require multiple cycles


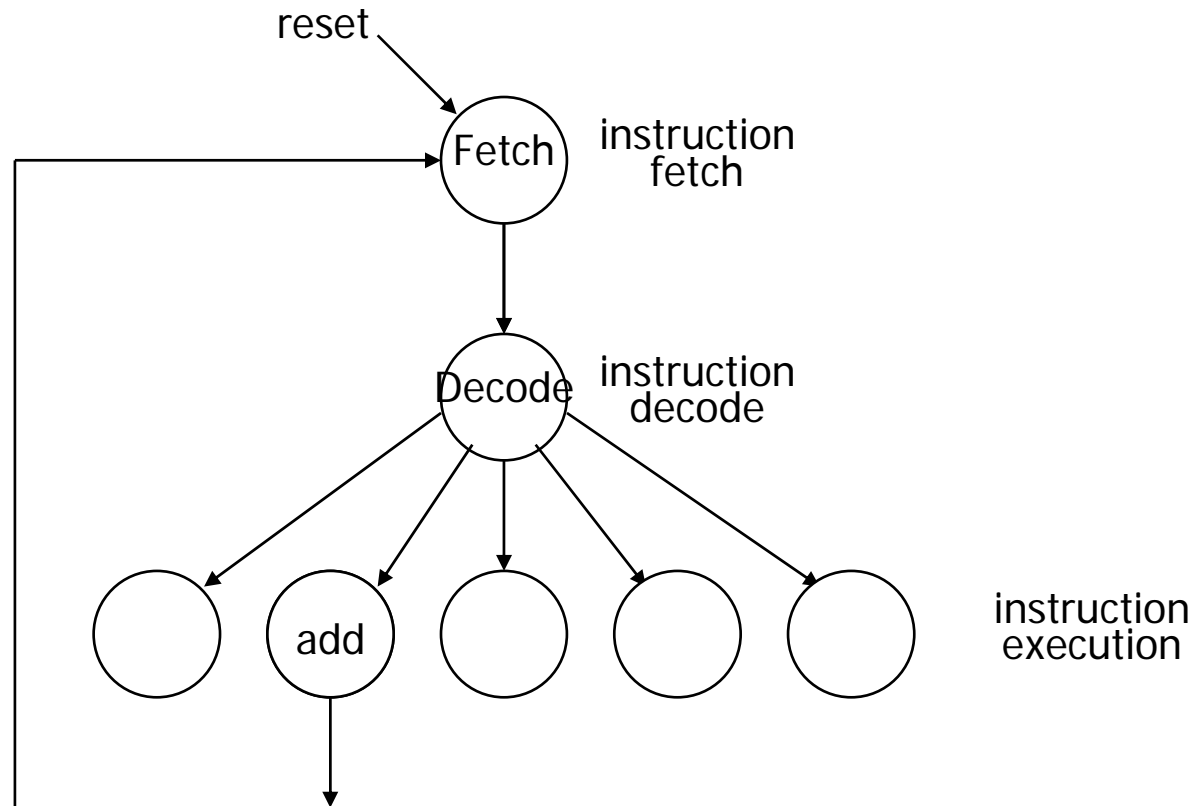
# FSM controller for CPU (add instruction)


- Putting it all together and closing the loop

- the famous instruction fetch decode execute cycle


 
# FSM controller for CPU

- Now we need to repeat this for all the instructions of our processor
  - fetch and decode states stay the same
  - different execution states for each instruction
    - some may require multiple states if available
    - register transfer paths require sequencing of steps




RD = RA op RB


ALU instruction

This design needs to be run with a clock period of 20ns.  
To single-step, set the simulation step to 20ns.

GND

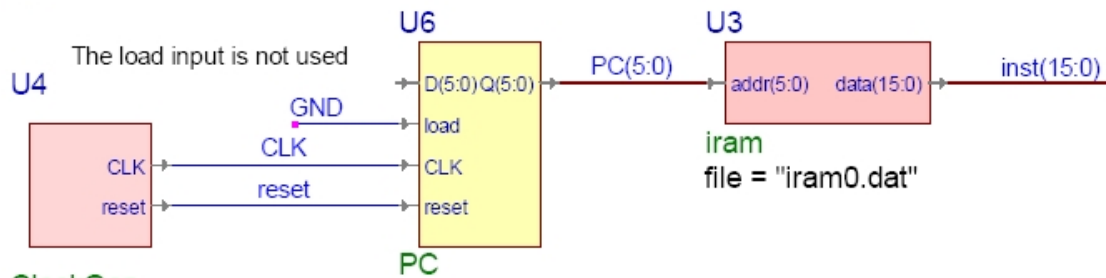

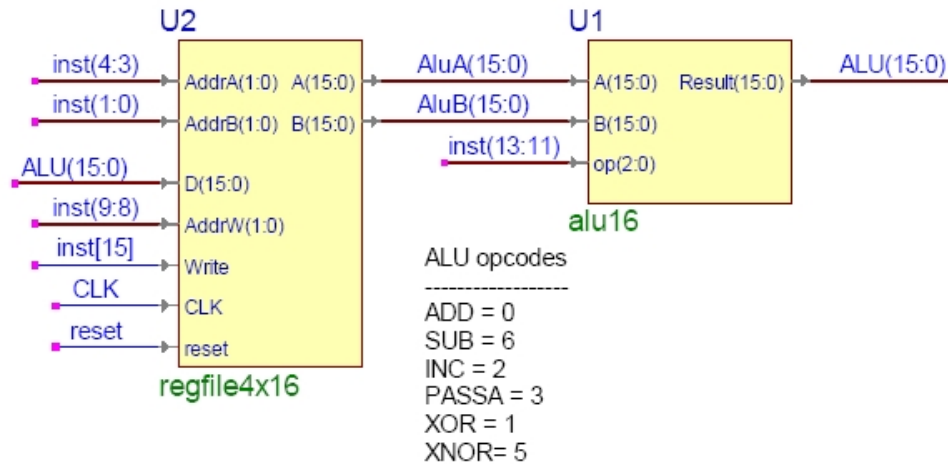
**ClockGen**  
 period = 10  
 number = 1000000  
 number =  
 period = 20


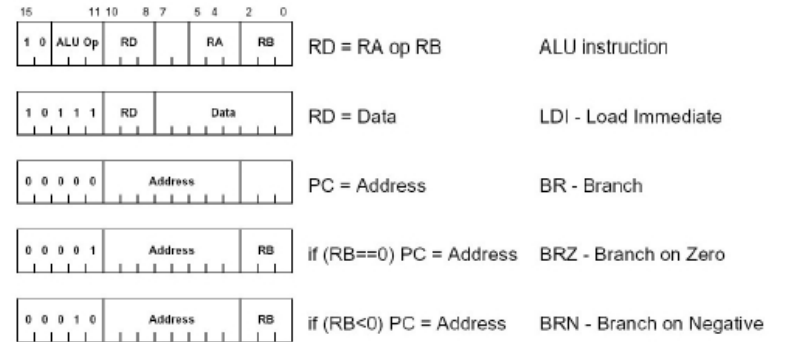
### Instruction Fields

```

wire [4:0] opcode = inst[15:11];
assign ALUopcode = inst[13:11];
assign RA = inst[4:3]; // only 4 registers
assign RB = inst[1:0]; // => 2-bit register address
assign RD = inst[9:8];
assign data = inst[7:0];
    
```



This design needs to be run with a clock period of 20ns. To single-step, set the simulation step to 20ns.

### Branch Logic


```

assign Branch = BR ||
    (BRZ && (AluB==0)) ||
    (BRN && (AluB[15]==1));
    
```
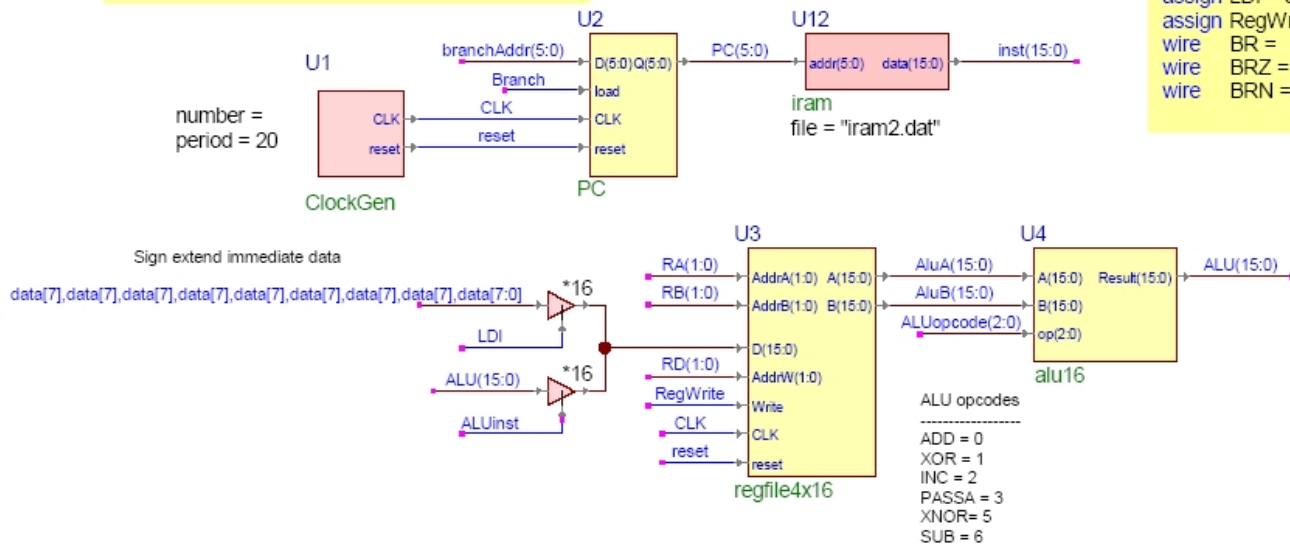
### Instruction Decode

```

assign ALUinst = ALUopcode != 7; // ALU performs first six op co ...
assign LDI = opcode == 'h17; // Load immediate op code
assign RegWrite = opcode[4]; // Write to register
wire BR = opcode == 0;
wire BRZ = opcode == 1;
wire BRN = opcode == 2;
    
```



### Instruction Fields

```

wire [4:0] opcode = inst[15:11];
assign ALUopcode = inst[13:11];
assign RA = inst[4:3]; // only 4 registers
assign RB = inst[1:0]; // => 2-bit register address
assign RD = inst[9:8];
assign data = inst[7:0];
    
```

This design needs to be run with a clock period of 20ns.  
To single-step, set the simulation step to 20ns.

### Branch Logic

```


assign Branch = BR ||
    (BRZ && (AluB==0)) ||
    (BRN && (AluB[15]==1));
    
```


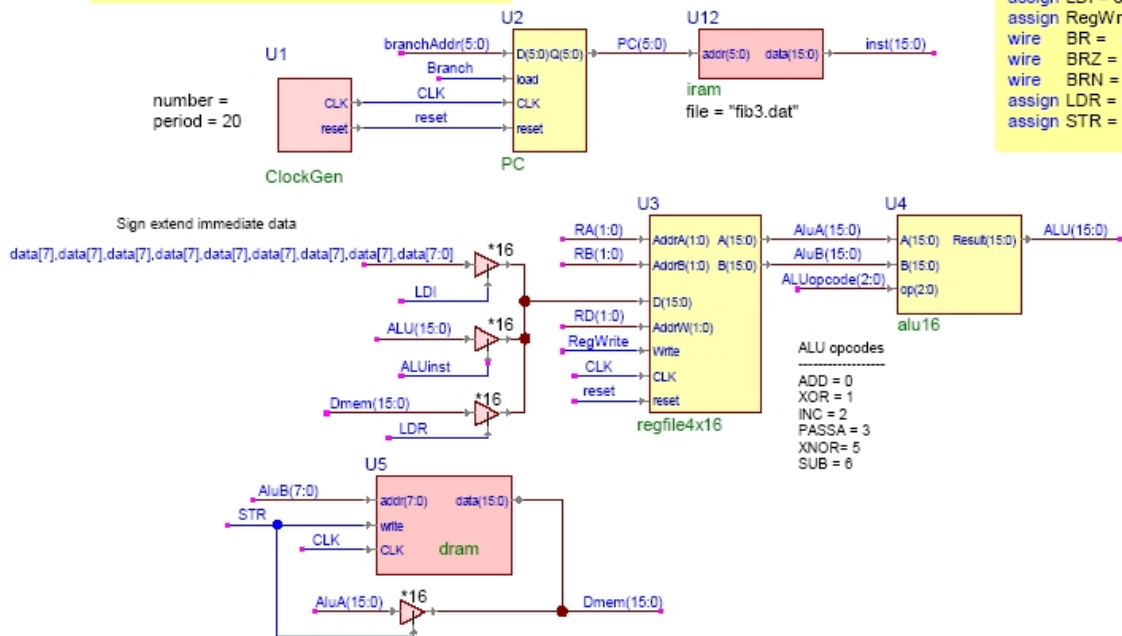
### Instruction Decode

```

assign ALUinst = ALUopcode != 7; // ALU performs first six op co ...
assign LDI = opcode == 'h17; // Load immediate op code
assign RegWrite = opcode[4]; // Write to register
wire BR = opcode == 0;
wire BRZ = opcode == 1;
wire BRN = opcode == 2;
assign LDR = opcode == 'h1f;
assign STR = opcode == 'hf;
    
```



(C)ALDEC, Inc 2260 Corporate Circle Henderson, NV 89074		 The Design Verification Company
Created:	8/24/2004	
Title:	x370 processor version 3	