

# Lecture II: Multi-Level Logic

CSE 370, Autumn 2007  
Benjamin Ylvisaker

---


## Where We Are

- Last lecture: Quine-McCluskey Minimization
- This lecture: Multi-Level Logic
- Next lecture: Circuit Delay and Timing
- Homework 4 in progress
- Lab 3 done; lab 4 next week


## 2-Level Minimum Circuits are Not Always the Best Solution

- Important circuit metrics:
  - Size
  - Speed
  - Complexity
  - Energy efficiency
- How we approximate these metrics:
  - Number and kind of gates
  - Number of gate inputs
  - Circuit depth

## Example: Full Adder Sum Output

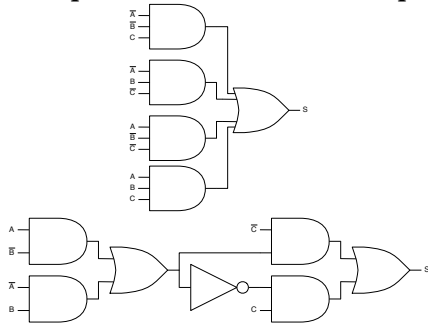

## More Extreme Example: 2-Bit Adder

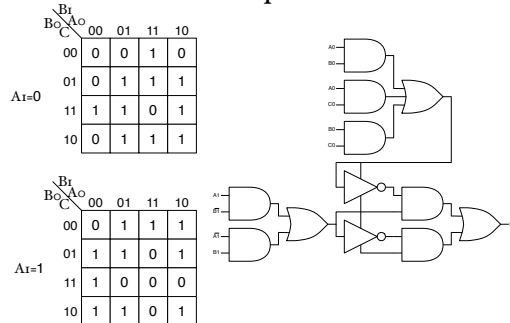


## No Simple Methods

- For 2-level minimization we have:
  - K-maps
  - Quine-McCluskey
  - Espresso
- For multi-level minimization we have:
  - Lots of heuristics
  - SIS

## Factoring

- $Z = ADF + AEF + BDF + BEF + CDF + CEF + G$ 
  - AND3: 6 OR7: 1 Depth: 2
- $Z = (AD + AE + BD + BE + CD + CE)F + G$ 
  - AND2: 7 OR6: 1 OR2: 1 Depth: 4
- $Z = (AD + BD + CD + AE + BE + CE)F + G$ 
  - AND2: 7 OR6: 1 OR2: 1 Depth: 4
- $Z = [(A + B + C)D + (A + B + C)E]F + G$ 
  - OR3: 2 AND2: 3 OR2: 2 Depth: 5
- $Z = (A + B + C)(D + E)F + G$ 
  - OR3: 1 OR2: 2 AND3: 1 Depth: 3
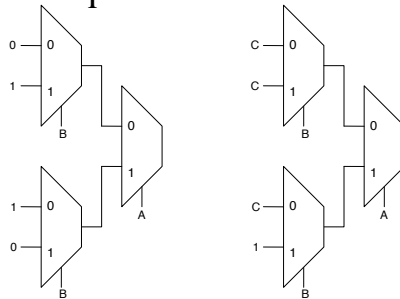
## Using Multiplexors to Implement Functions




## Cofactoring

- $Z = ACE + A-C-D + -AB-E + -A-BD$ 
  - Cofactor A
- $Z = A(CE + -C-D) + -A(B-E + -BD)$ 
  - Cofactor C in the left expression and B in the right expression
- $Z = A(C(E) + -C(-D)) + -A(B(-E) + -B(D))$
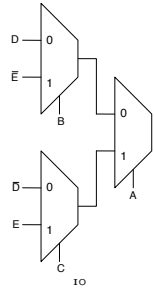
## Translating to Muxes

- $A(C(E) + \neg C(\neg D)) + \neg A(B(\neg E) + \neg B(D))$



## Thank You for Your Attention

- Start reading lab 4
- Start looking at homework 4
- Continue reading the book