


Where We Are

Lecture 12: Time and Glitches

CSE 370, Autumn 2007
Benjamin Ylvisaker



- Last lecture: Multi-Level Logic
- This lecture: Circuit Delay and Timing
- Next lecture: Adders, Comparators, ALUs
- Exam 1 on Wednesday
- Homework 4 in progress
- Lab 4 this week

Sometimes Time Matters

 


Glitches and Hazards


$$F = AC' + A'D$$

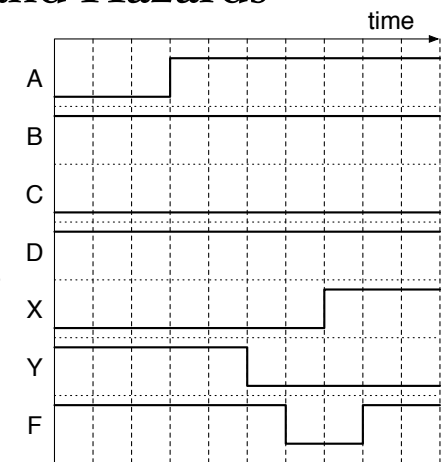 


Where Glitches Come From

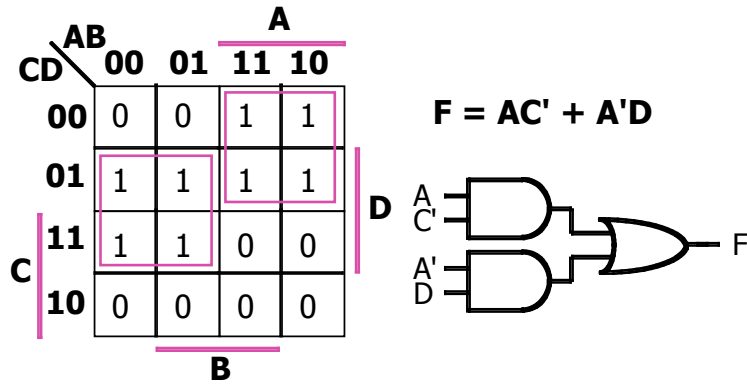

Avoiding Glitches in 2-Level Circuits

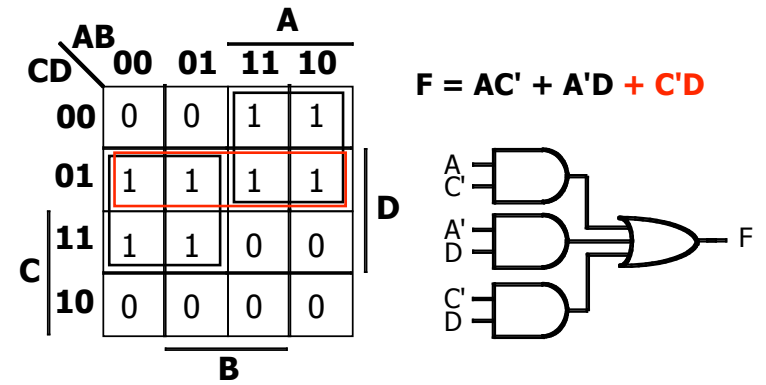


Additional Gate Prevents Glitches

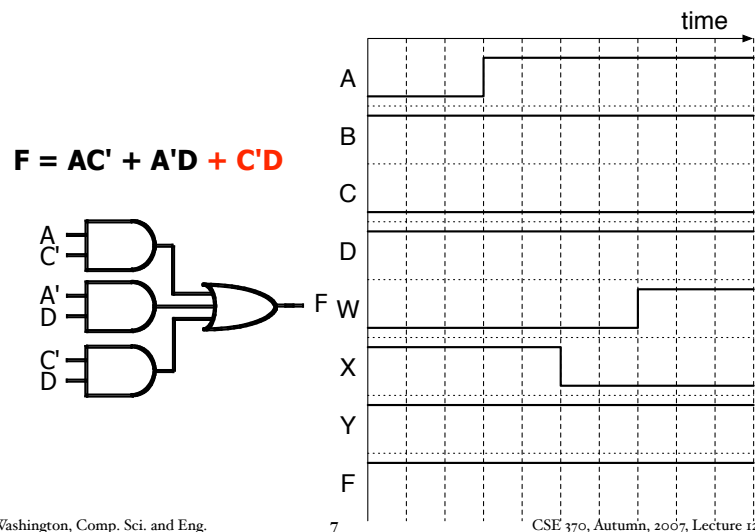

Terminology of Hazards

- Static 1-Hazard
- Static 0-Hazard
- Dynamic Hazards

A Dynamic Hazard

 

Avoiding Dynamic Hazards

- Very hard
- Automated tools can help
- In practice, use 2-level circuits if you must avoid hazards at all costs

Now You Try

- $F(A,B,C,D) = \neg AB + A\neg CD + \neg BCD$
- Draw waves that illustrate one input pattern/transition that can cause a glitch, and identify which gates would have to be slow or fast
- Change the circuit to make it hazard-free and draw the resulting circuit

Thank You for Your Attention

- Read lab 4
- Study for the exam
- Continue working on homework 4
- Continue reading the book