

Canonical forms

- ◆ Last lecture
 - Logic gates and truth tables
 - Implementing logic functions
 - CMOS switches
- ◆ Today's lecture
 - deMorgan's theorem
 - NAND and NOR
 - Canonical forms
 - ▣ Sum-of-products (minterms)
 - ▣ Product-of-sums (maxterms)

de Morgan's theorem

- ◆ Replace
 - • with +, + with •, 0 with 1, and 1 with 0
 - All variables with their complements
- ◆ Example 1: $Z = A'B' + A'C'$
$$\begin{aligned}Z' &= (A'B' + A'C')' \\ &= (A'B')' \cdot (A'C')' \\ &= (A+B) \cdot (A+C)\end{aligned}$$
- ◆ Example 2: $Z = A'B'C + A'BC + AB'C + ABC'$
$$\begin{aligned}Z' &= (A'B'C + A'BC + AB'C + ABC')' \\ &= (A'B'C)' \cdot (A'BC)' \cdot (AB'C)' \cdot (ABC')' \\ &= (A+B+C) \cdot (A+B'+C') \cdot (A'+B+C) \cdot (A'+B'+C)\end{aligned}$$

NAND and NOR

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND
 with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR
 with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0


NAND, NOR, and de Morgan's theorem

◆ de Morgan's

- Standard form: $A'B' = (A + B)'$ $A' + B' = (AB)'$
- Inverted: $A + B = (A'B)'$ $(AB) = (A' + B')$

- AND with complemented inputs \equiv NOR
- OR with complemented inputs \equiv NAND
- OR \equiv NAND with complemented inputs
- AND \equiv NOR with complemented inputs

pushing
the
bubble

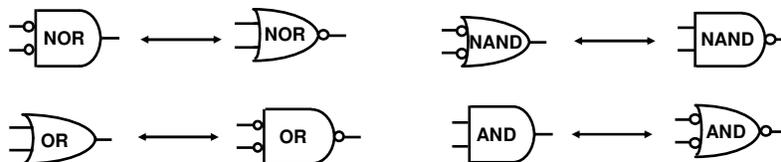

Converting between forms



- ◆ Introduce inversions ("bubbles")

- Introduce bubbles in pairs
 - ✦ Conserve inversions
 - ✦ Do not alter logic function

- ◆ Example

- AND/OR to NAND/NAND

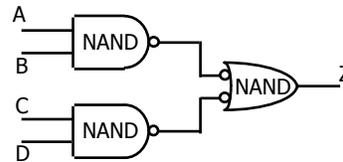
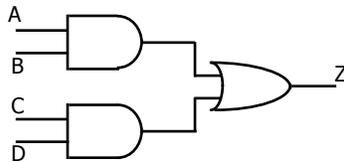
$$\begin{aligned}
 Z &= AB + CD \\
 &= (A'+B')'+(C'+D)' \\
 &= [(A'+B')(C'+D)'] \\
 &= [(AB)'(CD)']
 \end{aligned}$$



Converting between forms (con't)


- ◆ Example: AND/OR network to NOR/NOR
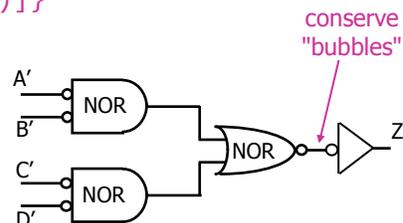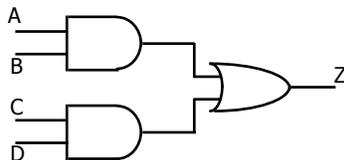
$$\begin{aligned}
 Z &= AB+CD \\
 &= (A'+B')'+(C'+D)' \\
 &= [(A'+B')+(C'+D)'] \\
 &= \{[(A'+B')+(C'+D)']\}'
 \end{aligned}$$




Converting between forms (con't)

- ◆ Example: OR/AND to NAND/NAND

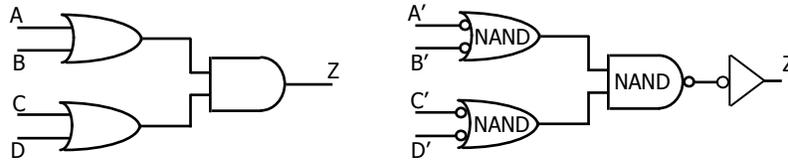

Converting between forms (con't)


- ◆ Example: OR/AND to NOR/NOR

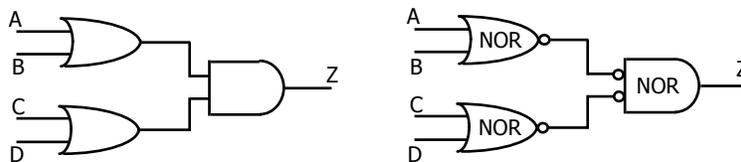



Why convert between forms?

- ◆ CMOS logic gates are inverting

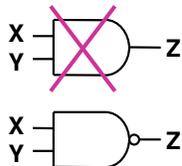- Get NAND, NOR, NOT
- Don't get AND, OR, Buffer



X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

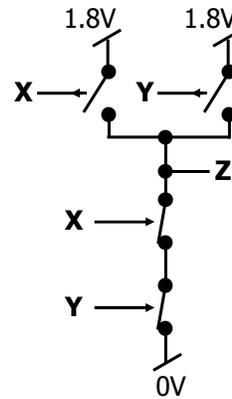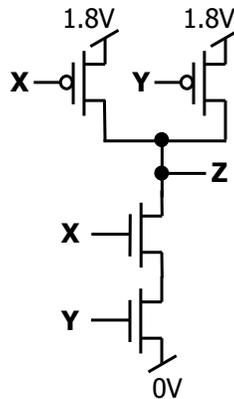

CSE370, Lecture 5

9

Canonical forms

- ◆ Canonical forms

- Standard forms for Boolean expressions
- Unique algebraic signatures
- Generally not the simplest forms
 - ✦ Can be minimized
- Derived from truth table

- ◆ Two canonical forms

- Sum-of-products (minterms)
- Product-of-sum (maxterms)

CSE370, Lecture 5

10

Sum-of-products canonical form

- ◆ Also called disjunctive normal form
 - Commonly called a **minterm expansion**

						001	011	101	110	111
						$F = A'B'C + A'BC + AB'C + ABC' + ABC$				
A	B	C	F	F'						
0	0	0	0	1						
0	0	1	1	0						
0	1	0	0	1						
0	1	1	1	0						
1	0	0	0	1						
1	0	1	1	0						
1	1	0	1	0						
1	1	1	1	0						

$F' = A'B'C' + A'BC' + AB'C'$

Minterms

- ◆ Variables appears exactly once in each minterm
 - In true or inverted form (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$ m0
0	0	1	$A'B'C$ m1
0	1	0	$A'BC'$ m2
0	1	1	$A'BC$ m3
1	0	0	$AB'C'$ m4
1	0	1	$AB'C$ m5
1	1	0	ABC' m6
1	1	1	ABC m7

short-hand notation

F in canonical form:

$$\begin{aligned}
 F(A,B,C) &= \sum m(1,3,5,6,7) \\
 &= m1 + m3 + m5 + m6 + m7 \\
 &= A'B'C + A'BC + AB'C + ABC' + ABC
 \end{aligned}$$

canonical form \rightarrow minimal form

$$\begin{aligned}
 F(A,B,C) &= A'B'C + A'BC + AB'C + ABC' + ABC \\
 &= (A'B' + A'B + AB' + AB)C + ABC' \\
 &= ((A' + A)(B' + B))C + ABC' \\
 &= ABC' + C \\
 &= AB + C
 \end{aligned}$$

Product-of-sums canonical form

- ◆ Also called conjunctive normal form
 - Commonly called a **maxterm expansion**

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F = (\overset{000}{A + B + C}) (\overset{010}{A + B' + C}) (\overset{100}{A' + B + C})$

$F' = (A+B+C')(A+B'+C')(A'+B+C)(A'+B'+C)(A'+B+C')$

Maxterms

- ◆ Variables appears exactly once in each maxterm
 - In true or inverted form (but not both)

A	B	C	maxterms
0	0	0	A+B+C M0
0	0	1	A+B+C' M1
0	1	0	A+B'+C M2
0	1	1	A+B'+C' M3
1	0	0	A'+B+C M4
1	0	1	A'+B+C' M5
1	1	0	A'+B'+C M6
1	1	1	A'+B'+C' M7

short-hand notation


F in canonical form:

$$\begin{aligned}
 F(A,B,C) &= \prod M(0,2,4) \\
 &= M0 \cdot M2 \cdot M4 \\
 &= (A+B+C)(A+B'+C)(A'+B+C)
 \end{aligned}$$

canonical form → minimal form

$$\begin{aligned}
 F(A,B,C) &= (A+B+C)(A+B'+C)(A'+B+C) \\
 &= (A+B+C)(A+B'+C) \cdot \\
 &\quad (A+B+C)(A'+B+C) \\
 &= (A + C)(B + C)
 \end{aligned}$$

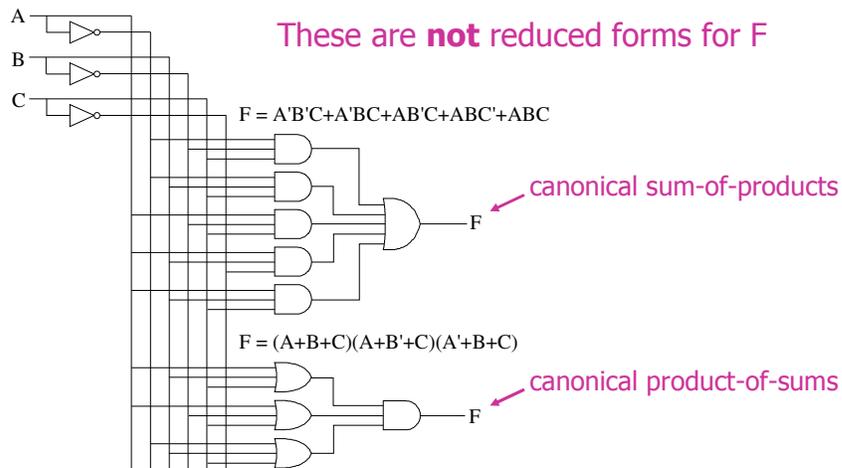Canonical implementations of $F = AB + C$



SOP, POS, and de Morgan's theorem

◆ Sum-of-products

- $F' = A'B'C' + A'BC' + AB'C'$

◆ Apply de Morgan's to get POS

- $(F')' = (A'B'C' + A'BC' + AB'C')'$
- $F = (A+B+C)(A+B'+C)(A'+B+C)$

◆ Product-of-sums

- $F' = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C')$

◆ Apply de Morgan's to get SOP

- $(F')' = ((A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C'))'$
- $F = A'B'C + A'BC + AB'C + ABC' + ABC$

Conversion between canonical forms

- ◆ Minterm to maxterm
 - Use maxterms that aren't in minterm expansion
 - $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- ◆ Maxterm to minterm
 - Use minterms that aren't in maxterm expansion
 - $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- ◆ Minterm of F to minterm of F'
 - Use minterms that don't appear
 - $F(A,B,C) = \sum m(1,3,5,6,7) \quad F'(A,B,C) = \sum m(0,2,4)$
- ◆ Maxterm of F to maxterm of F'
 - Use maxterms that don't appear
 - $F(A,B,C) = \prod M(0,2,4) \quad F'(A,B,C) = \prod M(1,3,5,6,7)$