

Lecture 12

◆ Logistics

- HW4 was due yesterday
- HW5 was out yesterday (due next Wednesday)
- Feedback: thank you!
- Things to work on: Big picture, Book chapters, Exam comments

◆ Last lecture


- Adders

◆ Today

- Clarification of Adders
- Summary of Combinational Logic
- Introduction to Sequential Logic
 - The basic concepts
 - A simple example


Adders allow computers to add numbers

2-bit ripple-carry adder

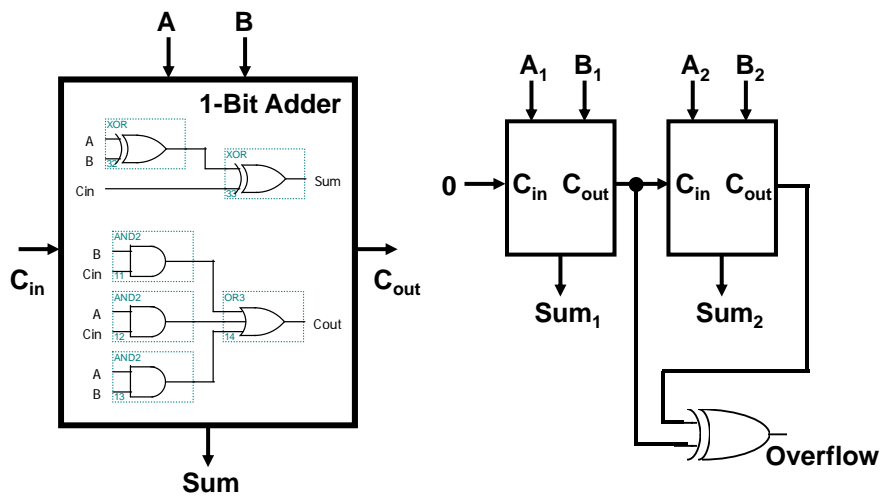

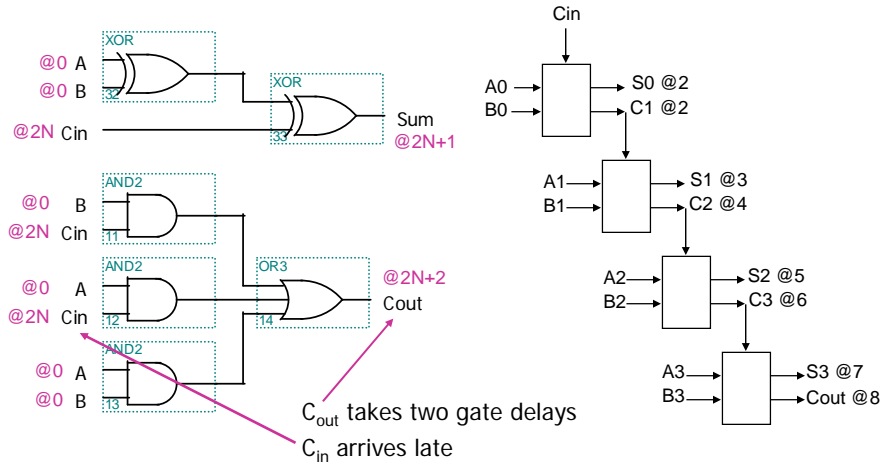Problem: Ripple-carry delay

- ◆ Carry propagation limits adder speed (we want to add fast)




CSE370, Lecture 12

3

One Solution: Carry lookahead logic

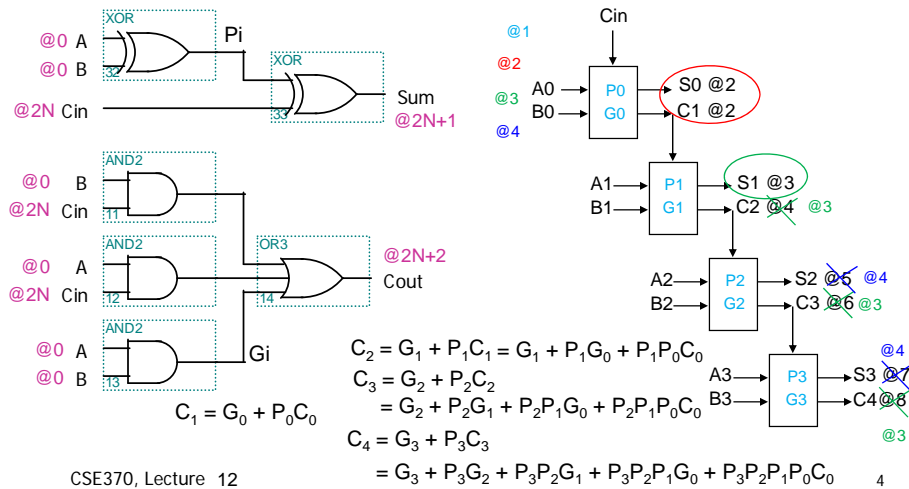- ◆ Get P_i (propagate) and G_i (generate)




CSE370, Lecture 12

4


Cascaded carry-lookahead adder (in your HW5)

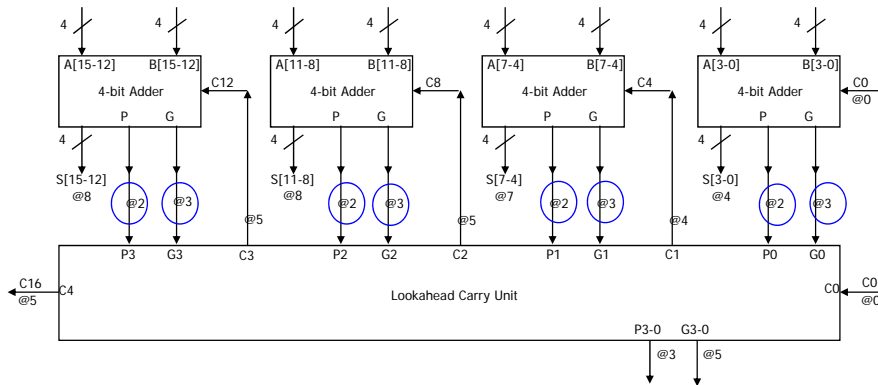- ◆ 4 four-bit adders with internal carry lookahead
 - Second level lookahead extends adder to 16 bits



Another solution: Carry-select adder

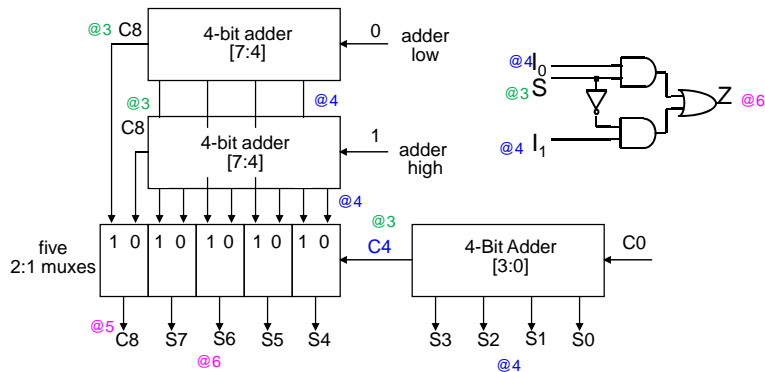- ◆ Redundant hardware speeds carry calculation
 - Compute two high-order sums while waiting for carry-in (C4)
 - Select correct high-order sum after receiving C4



We've finished combinational logic...

◆ What you should know

- Twos complement arithmetic
- Truth tables
- Basic logic gates
- Schematic diagrams
- Timing diagrams
- Minterm and maxterm expansions (canonical, minimized)
- de Morgan's theorem
- AND/OR to NAND/NOR logic conversion
- K-maps, logic minimization, don't cares
- Multiplexers/demultiplexers
- PLAs/PALs
- ROMs
- Adders

We had no way to store memory:
When the input changed, the output changed

Next: Sequential logic can store memory...


Sequential Logic (next 5 weeks!)

◆ We learn the details

- Latches, flip-flops, registers (**storage**)
- Shift registers, counters (**we can count now!**)
- State machines
- Timing and timing diagrams
 - ↳ **timing more important than combinational logic**
- Synchronous and asynchronous inputs
 - ↳ Metastability (**problem!**)
- Moore and Mealy machines (**types of state machines**)

- More...

Sequential versus combinational

 


Apply fixed inputs A, B
Wait for clock edge
Observe C
Wait for another clock edge
Observe C again


Combinational: C will stay the same
Sequential: C may be different

Sequential versus combinational (again)

 - ◆ Combinational systems are **memoryless**
 - Outputs depend only on the present inputs




 - ◆ Sequential systems have **memory**
 - Outputs depend on the present **and** the previous inputs




Synchronous sequential systems

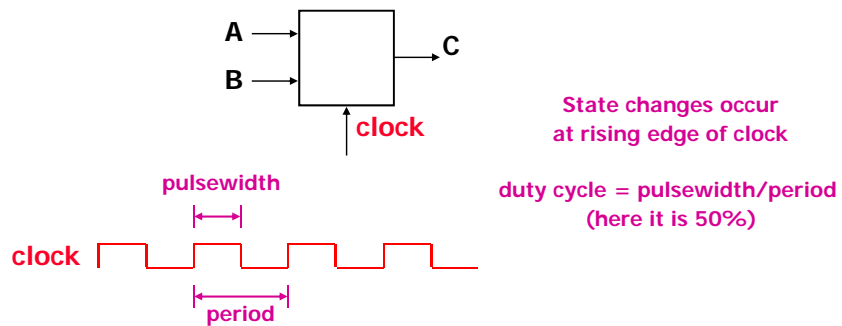- ◆ **Memory** holds a system's *state*
 - Changes in state occur at specific times
 - A periodic signal times or **clocks** the state changes
 - The clock period is the time between state changes



Steady-state abstraction

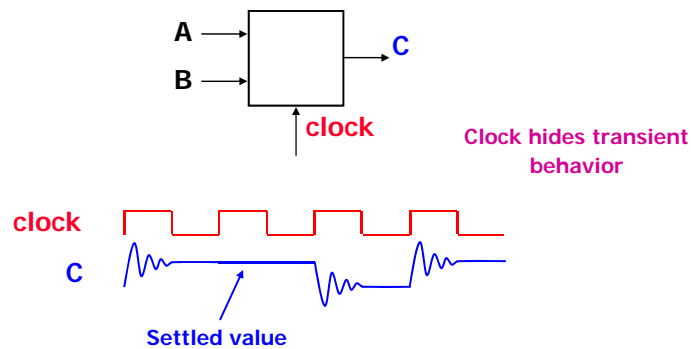- ◆ Outputs retain their *settled values*
 - The clock period must be long enough for all voltages to settle to a **steady state** before the next state change



What did I just say about sequential logic?


- ◆ Has clock
 - **Synchronous** = clocked
 - Exception: Asynchronous
- ◆ Has state
 - **State** = memory
- ◆ Employs **feedback**
- ◆ Assumes **steady-state** signals
 - Signals are valid after they have settled
 - State elements hold their settled output values

Example: A sequential system

- ◆ Door combination lock
 - Enter 3 numbers in sequence and the door opens
 - If there is an error the lock must be reset
 - After the door opens the lock must be reset
 - Inputs: Sequence of numbers, reset
 - Outputs: Door open/close
 - Memory: Must remember the combination


Understand the problem

 - ◆ Consider I/O and unknowns
 - How many bits per input?
 - How many inputs in sequence?
 - How do we know a new input is entered?
 - How do we represent the system states?



Implement using sequential logic

 - ◆ Behavior
 - Clock tells us when to look at inputs
 - ☛ After inputs have settled
 - Sequential: Enter sequence of numbers
 - Sequential: Remember if error occurred
- ◆ Need a finite-state diagram
 - Assume synchronous inputs
 - State sequence
 - ☛ Enter 3 numbers serially
 - ☛ Remember if error occurred
 - All states have outputs
 - ☛ Lock open or closed




Finite-state diagram

- ◆ States: 5
 - Each state has outputs
- ◆ Outputs: open/closed
- ◆ Inputs: reset, new, results of comparisons
 - Assume synchronous inputs


We use state diagrams to represent sequential logic

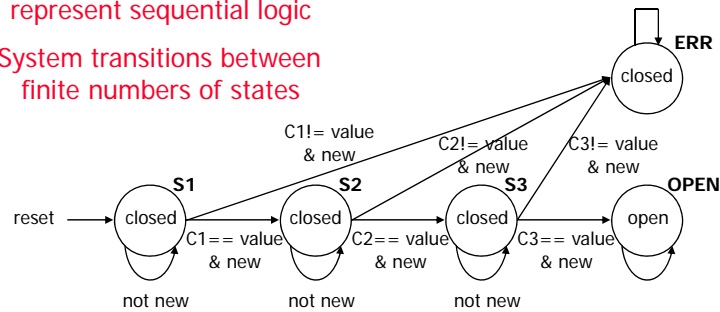System transitions between finite numbers of states




Separate data path and control

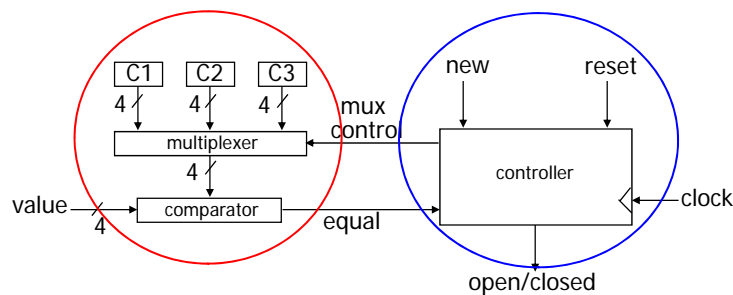- ◆ **Data path**
 - Stores combination
 - Compares inputs with combination
- ◆ **Control**
 - Finite state-machine controller
 - Control for data path
 - State changes clocked



Refine diagram; generate state table

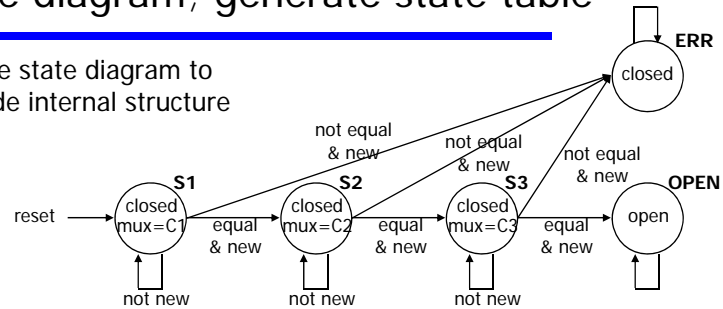- ◆ Refine state diagram to include internal structure



- ◆ Generate state table

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open
...						