

## Lecture 13

---


- ◆ Logistics
  - HW5 due Wednesday
- ◆ Last lecture
  - Finished combinational logic
  - Introduction to sequential logic and systems
- ◆ Today
  - Finish the example from last time
  - Latches
  - Flip-flops

## Example from last time: Combination lock

---

- ◆ Door combination lock
  - Enter 3 numbers in sequence and the door opens
  - If there is an error the lock must be reset
  - After the door opens the lock must be reset
  - Inputs: Sequence of numbers, reset
  - Outputs: Door open/close
  - Memory: Must remember the combination

## State diagram and state table

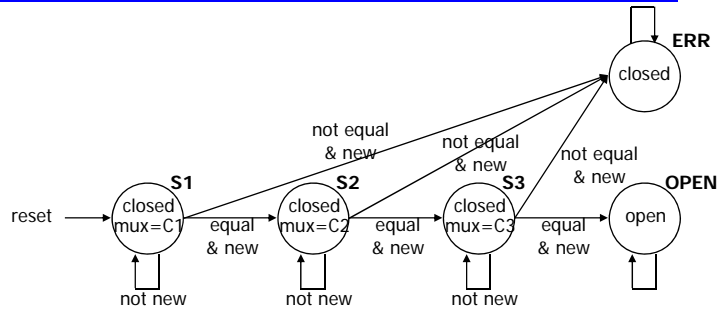


reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
...						
0	1	1	S3	OPEN	-	open

CSE370, Lecture 13 ...

3

## Combination lock system design


 


CSE370, Lecture 13

4
  
## Designing the datapath


- Four 3:1 multiplexers
  - 2-input ANDs and 3-input OR
- Four single-bit comparators
  - 2-input XNORs
- 4-input AND


 
## Designing the controller

- We will learn how to design the controller given the encoded state-transition table

special circuit element, called a register, for storing inputs when told to by the clock





## Now we will learn how to store things!

- ◆ First, we will learn several different logic elements (like how you had to learn AND and OR before you could do functional things)
  - D latch
  - D flip flop
  - T flip flop
  - SR latch
  
- ◆ Be patient --- once you know these components, you can do a lot in combinational logic!

  
## The D latch

- ◆ Output depends on clock
  - Clock high: Input passes to output
  - Clock low: Latch holds its output
- ◆ Latches are level sensitive and transparent



 
## How do we make a latch?

- ◆ Two inverters hold a bit
  - As long as power is applied




 - ◆ Storing a new memory
  - Temporarily break the feedback path



 
## The D flip-flop

- ◆ Input sampled at clock edge
  - Rising edge: Input passes to output
  - Otherwise: Flip-flop holds its output



 
- ◆ Flip-flops are rising-edge triggered, falling-edge triggered, or master-slave



## How do we make a D flip flop?

 
### ◆ Edge triggering is difficult

- You can do this at home:
  - ✦ Label the internal nodes
  - ✦ Draw a timing diagram
  - ✦ Start with CLK=1




## Terminology & notation


### Rising-edge triggered D flip-flop

 


### Positive D latch

 


### Falling-edge triggered D flip-flop

 

### Negative D latch

 


## Latches versus flip-flops

 

behavior is the same **unless** input changes while the clock is high
 
## T flip-flop

- ◆ Full name: Toggle flip-flop
- ◆ Output toggles when input is asserted
  - If  $T=1$ , then  $Q \rightarrow Q'$  when  $CLK \uparrow$
  - If  $T=0$ , then  $Q \rightarrow Q$  when  $CLK \uparrow$





Input( $t$ )	Q( $t$ )	Q( $t + \Delta t$ )
0	0	0
0	1	1
1	0	1
1	1	0
  
# The SR latch


◆ Cross-coupled NOR gates

- Can set ( $S=1, R=0$ ) or reset ( $R=1, S=0$ ) the output




# SR latch behavior

◆ Truth table and timing

 

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	disallow

 



## SR latch is glitch sensitive

---

- ◆ Static 0 hazards can set/reset latch
  - Glitch on S input sets latch
  - Glitch on R input resets latch

