

Lecture 16

◆ Logistics

- HW6 due Wednesday
- Midterm 2 creeping up (next week Wednesday 5/21)
- Midterm 2 covers materials up to Friday lecture & HW7
- Review next Tuesday 6:30pm?

◆ Last lecture

- Timing issues for asynchronous inputs
- Registers/counters
- Wrapped up on sequential logic building blocks


◆ Today

- Introduction to finite state machines
- Counters as finite state machines

“States” for finite state machines are kept in the storage elements


◆ Combinational logic and storage elements

 - Localized feedback loops
- Choice of storage elements alters the logic





Finite-state machines (FSMs)

 - ◆ States: Possible storage-element values
- ◆ Transitions: Changes in state
 - Clock synchronizes the state changes
- ◆ Sequential logic
 - Sequences through a series of states
 - Based on inputs and present state



Drawing state diagrams

  - ◆ Show input values on transition arcs
- ◆ Show output values in state nodes



Counters revisited

- ◆ Great simple examples of state machines
 - Output is the counter's state
- ◆ Next state is well defined
 - Does not depend on input (no inputs)




FSM design procedure (using counters)

1. Draw a state diagram
2. Draw a state-transition table
3. Encode the next-state functions
 - Minimize the logic using k-maps
4. Implement the design

We will use a '3-bit up counter' as an example
in two different ways today

1. Draw a state diagram

 

2. Draw a state-transition table

- ◆ Like a truth-table
 - State encoding is easy for counters → Use count value

	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

3. Encode the next state functions

- ◆ Assume D flip-flops as state elements

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

	C3			
N1	1	1	1	1
C1	0	0	0	0
	C2			

$$N1 := C1'$$

$$N2 := C1C2' + C1'C2$$

$$:= C1 \text{ xor } C2$$

$$N3 := C1C2C3' + C1'C3 + C2'C3$$

$$:= C1C2C3' + (C1' + C2')C3$$


$$:= (C1C2) \text{ xor } C3$$

	C3			
N2	0	1	1	0
C1	1	0	0	1
	C2			

	C3			
N3	0	0	1	1
C1	0	1	0	1
	C2			

 4. Implement the design


- ◆ 3 flip-flops hold state
 - Counter is synchronously clocked
- ◆ Minimized logic computes next state



Another example: 3-bit up counter with T flip flops

1. Draw a state diagram
2. Draw a state-transition table
3. Encode the next-state functions
 - Minimize the logic using k-maps
4. Implement the design


1. Draw a state diagram

 

 2. Draw a state-transition table

◆ Like a truth-table


- State encoding is easy for counters → Use count value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

3. Encode the next state functions

T flip-flops

 

$T_1 := 1$
 $T_2 := C_1$
 $T_3 := C_1 C_2$

C3	C2	C1	N3	N2	N1	T3	T2	T1
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

T1	C3			
	1	1	1	1
C1	1	1	1	1
	C2			

T2	C3			
	0	0	0	0
C1	1	1	1	1
	C2			

T3	C3			
	0	0	0	0
C1	0	1	1	0
	C2			

4. Implement the design

