

Lecture 25 Last lecture

◆ Logistics

- HW9 and Ant extra credit problem are due now
- All lab must be done by 6pm today.
- Review session tomorrow CSE403 11:30am
- Final Exam 6/9 here 8:30am

◆ Today

- Review materials from the entire class
- Announcement of final exam extra credit problem
- Evaluation: me and Nikhil (leave last 15 min for this)
- Tomorrow: can take more questions and go over examples.

What you should know

◆ Combinational logic basics

- Binary/hex/decimal numbers
- Ones and twos complement arithmetic
- Truth tables
- Boolean algebra
- Basic logic gates
- Schematic diagrams
- Timing diagrams
- de Morgan's theorem
- AND/OR to NAND/NOR logic conversion
- K-maps (up to 4 variables), logic minimization, don't cares
- SOP, POS
- Minterm and maxterm expansions (canonical, minimized)

What you should know

- ◆ Combinational logic applications
 - Combinational design
 - ✍ Input/output encoding
 - ✍ Truth table
 - ✍ K-map
 - ✍ Boolean equation
 - ✍ Schematics
 - Multiplexers/demultiplexers
 - PLAs/PALs
 - ROMs
 - Adders

What you should know

- ◆ Sequential logic building blocks
 - Latches (R-S and D)
 - Flip-flops (D and T)
 - Latch and flip-flop timing (setup/hold time, prop delay)
 - Timing diagrams
 - Asynchronous inputs and metastability
 - Registers

What you should know

◆ Counters

- Timing diagrams
- Shift registers
- Ring counters
- State diagrams and state-transition tables
- Counter design procedure
 1. Draw a state diagram
 2. Draw a state-transition table
 3. Encode the next-state functions
 4. Implement the design
- Self-starting counters


What you should know

◆ Finite state machines


- Timing diagrams (synchronous FSMs)
- Moore versus Mealy versus synchronized Mealy
- FSM design procedure
 1. State diagram
 2. state-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design
- State minimization
- One-hot / output-oriented encoding
- FSM design guidelines
 - ↳ Separate datapath and control
- Pipelining, retiming partitioning basics

Partitioning rules

 Rule #1: Source-state transformation
 Replace by transition to idle state (SA)




 Rule #2: Destination state transformation
 Replace with exit transition from idle state




Partitioning rules (con't)

 Rule #3: Multiple transitions with same source or destination
 Source \Rightarrow Replace by transitions to idle state (SA)
 Destination \Rightarrow Replace with exit transitions from idle state



 Rule #4: Hold condition for idle state
 OR exit conditions and invert



Example: 6 state up/down counter (con't)

- ◆ Count sequence $S_0, S_1, S_2, S_3, S_4, S_5$
 - S_2 goes to S_A and holds, leaves after S_5
 - S_5 goes to S_B and holds, leaves after S_2
 - Down sequence is similar

