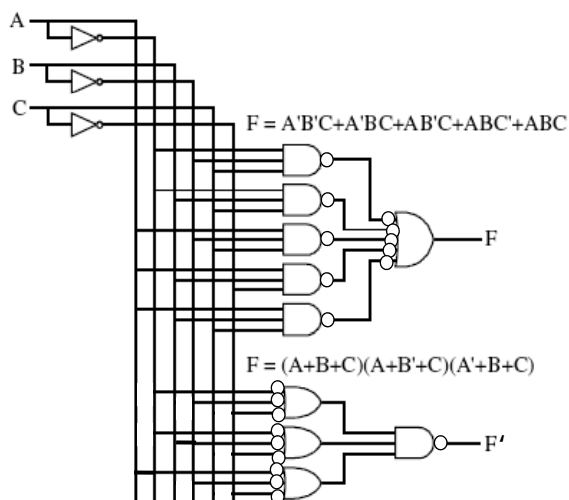



Lecture 6

- ◆ Logistics
 - HW2 out, due 4/16 Wednesday
 - Lab 2 ongoing
- ◆ Last lecture
 - Canonical forms
 - NAND and NOR
- ◆ Today's lecture
 - One more pushing bubble example
 - Logic simplification
 - ✦ Boolean cubes
 - ✦ Karnaugh maps

Example of bubble pushing: NAND/NAND



Example of bubble pushing: NOR/NOR

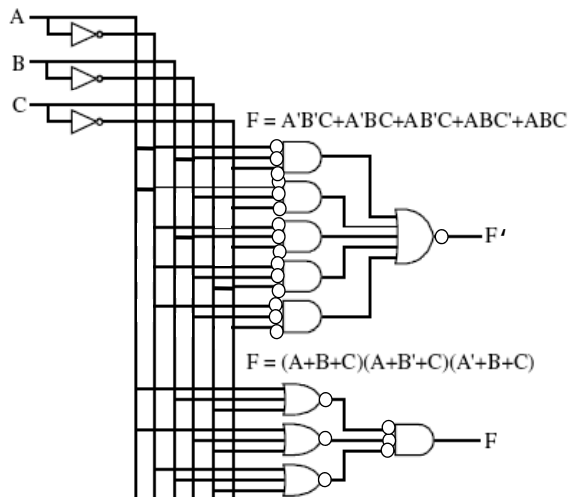

CSE370, Lecture 6

3

Goal: Minimize two-level logic expression

- ◆ Algebraic simplification
 - not a systematic procedure
 - hard to know when we reached the minimum
- ◆ Computer-aided design tools
 - require very long computation times (NP hard)
 - heuristic methods employed – “educated guesses”
- ◆ Visualization methods are useful
 - our brain is good at figuring things out over computers
 - many real-world problems are solvable by hand

CSE370, Lecture 6

4

Key tool: The Uniting Theorem

- ◆ The uniting theorem $\rightarrow A(B'+B) = A$
- ◆ The approach:
 - Find some variables don't change (the A's above) and others do (the B's above)
 - Eliminate the changing variables (the B's)

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0


A has the same value in both "on-set" rows
 \Rightarrow keep A

B has a different value in the two rows
 \Rightarrow eliminate B

$$F = A'B' + A'B = A'(B+B') = A'$$

Boolean cubes

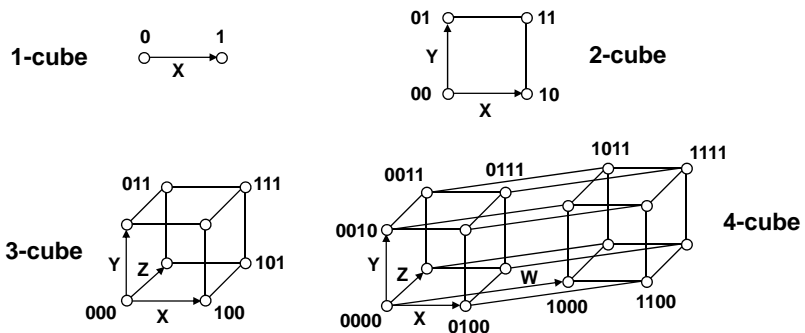
- ◆ Visualization tool for the uniting theorem
 - n input variables = n-dimensional "cube"



Mapping truth tables onto Boolean cubes

- ◆ ON set = solid nodes
- ◆ OFF set = empty nodes

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

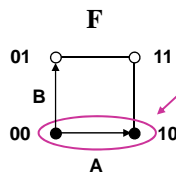

Look for on-set adjacent to each other

Sub-cube (a line) comprises two nodes


A varies within the sub-cube; B does not

This sub-cube represents B'

Example using Boolean cube

- ◆ Binary full-adder carry-out logic
 - On-set is covered by the OR of three 2-D subcubes

A	B	C _{in}	C _{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

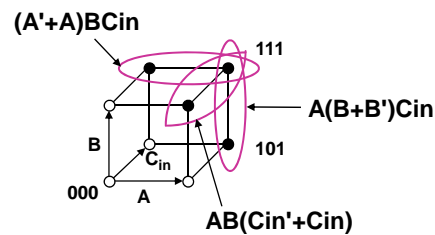


$$C_{out} = BC_{in} + AB + AC_{in}$$

M-dimensional cubes in n-dimensional space

◆ In a 3-cube (three variables):

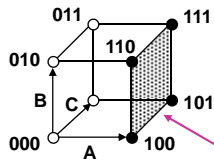- A 0-cube (a single node) yields a term in 3 literals
- A 1-cube (a line of two nodes) yields a term in 2 literals
- A 2-cube (a plane of four nodes) yields a term in 1 literal
- A 3-cube (a cube of eight nodes) yields a constant term "1"



$$F(A,B,C) = \sum m(4,5,6,7)$$

On-set forms a square (a 2-D cube)

A is asserted (true) and unchanging
B and C vary

This sub-cube represents the literal A

Karnaugh maps (K-map)

◆ Flat representation of Boolean cubes

- Easy to use for 2– 4 dimensions
- Hard for 4 – 6 dimensions
- Virtually impossible for 6+ dimensions
 - ✦ Use CAD tools

◆ Help visualize adjacencies


- On-set elements that have one variable changing are adjacent

	A	B	F
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	0

B \ A	0	1
0	0 1	2 1
1	1 0	3 0


2, 3, and 4 dimensional K-maps

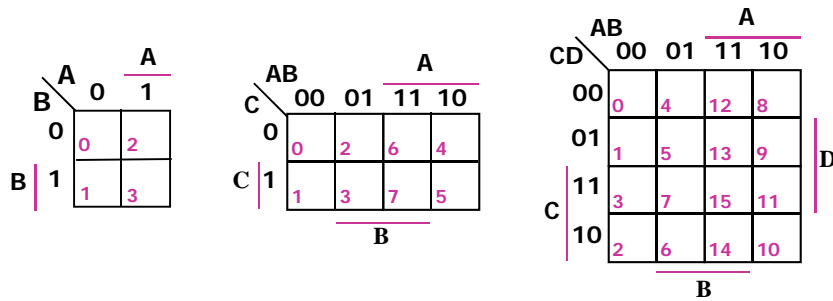- ◆ Uses Gray code: Only one bit changes between cells
 - Example: 00 → 01 → 11 → 10



Adjacencies

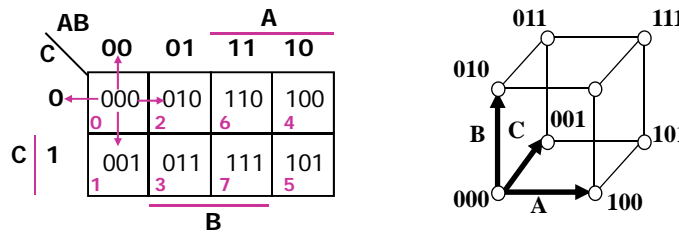- ◆ Wrap-around at edges
 - First column to last column
 - Top row to bottom row



K-map minimization example: 2 variables

	A	B	F
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	0

		A	
		0	1
B	0	1	1
	1	0	0

$$F = B'$$

K-map minimization example: 3 variables

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		A			
		00	01	11	10
Cin	0	0	0	1	0
	1	0	1	1	1

$$Cout = AB + BCin + ACin$$

K-map minimization example: minterms

$$F(A,B,C) = \sum m(0,4,5,7) \\ = B'C' + AC$$

	AB		A	
	00	01	11	10
C				
0	0 1	2 0	6 0	4 1
1	1 0	3 0	7 1	5 1
	B			

K-map minimization example: complement

	AB		A	
	00	01	11	10
C				
0	0 1	2 0	6 0	4 1
1	1 0	3 0	7 1	5 1
	B			


$$F(A,B,C) = \sum m(0,4,5,7) \\ = B'C' + AC$$

$$F'(A,B,C) = \sum m(1,2,3,6) \\ = A'C + BC'$$

K-map minimization example: 4 variables

- ◆ Minimize $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$
 - Find the least number of subcubes, each as large as possible, that cover the ON-set


	AB		A		
CD	00	01	11	10	
00	1 0	0 4	0 12	1 8	
01	0 1	1 5	0 13	0 9	D
11	1 3	1 7	1 15	1 11	
10	1 2	1 6	1 14	1 10	
		B			

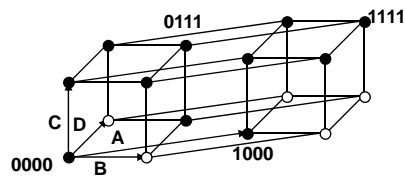

K-map minimization example: 4 variables

- ◆ Minimize $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$
- ◆ Answer: $F = C + A'BD + B'D'$

	AB		A		
CD	00	01	11	10	
00	1	0	0	1	
01	0	1	0	0	D
11	1	1	1	1	
10	1	1	1	1	
		B			

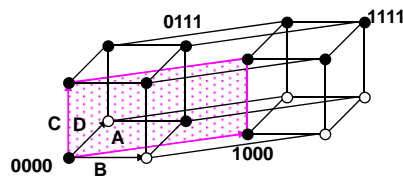

K-map minimization examples: do it yourself

$$F(A,B,C) = \Sigma m(0,3,6,7)$$

$$F(A,B,C) =$$
$$F'(A,B,C) =$$

	AB			
C	00	01	11	10
0				
1				

$$F(A,B,C,D) = \Sigma m(0,3,7,8,11,15)$$

$$F(A,B,C,D) =$$
$$F'(A,B,C,D) =$$

	AB			
CD	00	01	11	10
00				
01				
11				
10				