

Overview

- ◆ Last lecture
 - Logic simplification
 - ↳ Boolean cubes
 - ↳ Karnaugh maps
- ◆ Today
 - Incompletely specified functions
 - Design examples
 - k-maps for POS minimization

Incompletely specified functions

- ◆ Functions of n inputs have 2^n possible configurations
 - Some combinations may be unused
 - Call unused combinations "don't cares"
 - Exploit don't cares during logic minimization
 - Don't care \neq no output
- ◆ Example: A BCD increment-by-1
 - Function F computes the next number in a BCD sequence
 - ↳ If the input is 0010_2 , the output is 0011_2
 - BCD encodes decimal digits 0–9 as 0000_2 – 1001_2
 - ↳ Don't care about binary numbers 1010_2 – 1111_2

Truth table for a BCD increment-by-1

INPUTS				OUTPUTS			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

off-set for W: m_0 – m_6 , m_9

on-set for W: m_7 and m_8

Don't care set for W:
We **don't care**
about the output values

Notation

- ◆ Don't cares in canonical forms
 - Three distinct logical sets
 - ↳ {on}, {off}, {don't care}
- ◆ Canonical representations of a BCD increment-by-1
 - Minterm expansion
 - ↳ $W = m_7 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - Maxterm expansion
 - ↳ $W = M_0 \cdot M_1 \cdot M_2 \cdot M_3 \cdot M_4 \cdot M_5 \cdot M_6 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$

Karnaugh maps and don't cares

- ◆ Can treat don't cares as 0s or 1s
 - Depending on which is more advantageous
- ◆ $F(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - Example: Minimize F with and without don't cares

		A						
		00	01	11	10			
C	CD	00	0	4	0	X	8	0
		01	1	5	1	X	13	9
	11	3	7	1	15	0	11	0
	10	2	6	X	14	0	10	0
		B						

CSE370, Lecture 7

5

Karnaugh maps and don't cares (con't)

- ◆ $F(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - $F = A'D + B'C'D$ *without using don't cares*
 - $F = A'D + C'D$ *using don't cares*


		A				
		00	01	11	10	
C	CD	00	0	0	X	0
		01	1	1	X	1
	11	1	1	0	0	
	10	0	X	0	0	
		B				

Assign X == "1"
⇒ allows a 2-cube rather than a 1-cube

CSE370, Lecture 7

6

Design example: A two-bit comparator

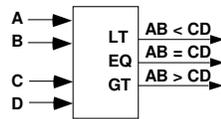

block diagram
truth table

A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

Need a 4-variable Karnaugh map for each of the 3 output functions

CSE370, Lecture 7

7

Two-bit comparator (con't)

K-map for LT

		A					
		00	01	11	10		
C	CD	00	0	4	0	8	0
		01	1	5	0	13	9
	11	3	7	1	15	11	0
	10	2	6	1	14	10	0
		B					

LT = ?

K-map for EQ

		A					
		00	01	11	10		
C	CD	00	1	0	0	0	0
		01	1	0	1	0	0
	11	0	0	1	0	0	
	10	0	0	0	1	0	
		B					

EQ = ?

K-map for GT

		A					
		00	01	11	10		
C	CD	00	0	1	1	1	1
		01	1	0	0	1	1
	11	0	0	0	0	0	
	10	0	0	1	0	0	
		B					

GT = ?

CSE370, Lecture 7

8

Two-bit comparator (con't)

CD		AB		A	
		00	01	11	10
C	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

$$LT = A'B'D + A'C + B'CD$$

$$EQ = A'B'C'D' + A'BC'D + ABCD + AB'CD'$$


$$= (A \text{ xnor } C) \bullet (B \text{ xnor } D)$$

CSE370, Lecture 7

9

Two-bit comparator (con't)


- Two ways to implement EQ:

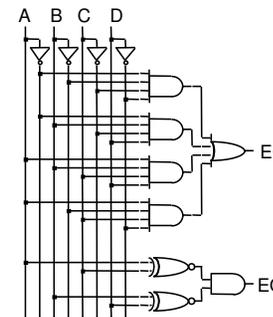

$$EQ = A'B'C'D' + A'BC'D + ABCD + AB'CD'$$

$$= (A \text{ xnor } C) \bullet (B \text{ xnor } D)$$

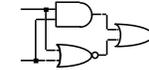
- XNOR approach looks simpler
But XNORs are complex
- Example: XNOR constructed from 3 simple gates



CSE370, Lecture 7

10


Two-bit comparator design

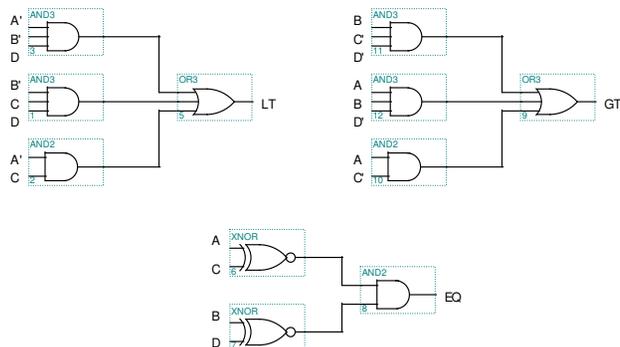

CSE370, Lecture 7

11

Design example: Two-bit multiplier

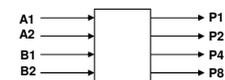



block diagram
truth table

A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
	0	1	0	0	0	0	0
	1	0	0	0	0	0	0
	1	1	0	0	0	0	0
0	1	0	0	0	0	0	0
	0	1	0	0	0	0	1
	1	0	0	0	0	1	0
	1	1	0	0	1	1	0
1	0	0	0	0	0	0	0
	0	1	0	0	0	1	0
	1	0	0	0	1	0	0
	1	1	0	0	1	1	0
1	1	0	0	0	0	0	0
	0	1	0	0	1	1	1
	1	0	0	0	1	1	0
	1	1	1	0	0	1	1

Need a 4-variable Karnaugh map
for each of the 4 output functions

CSE370, Lecture 7

12

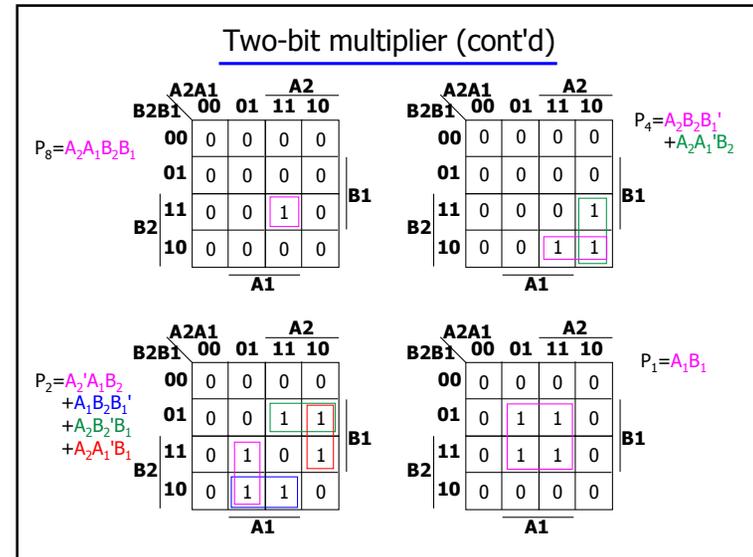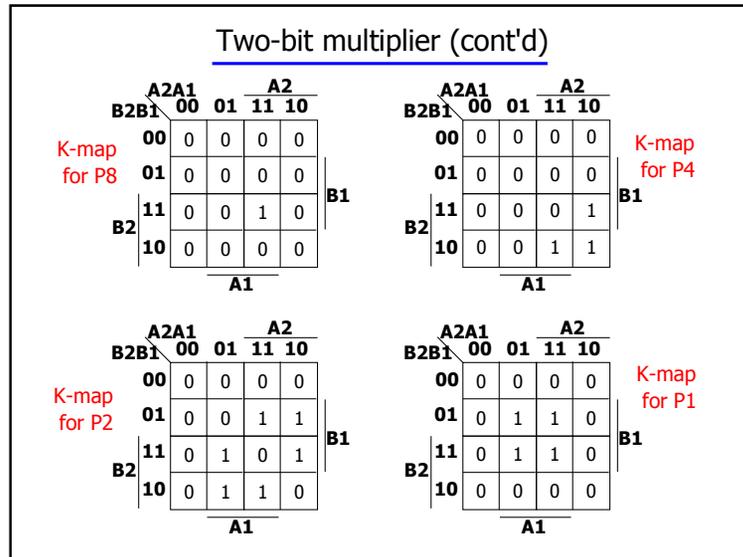

Two-bit multiplier design

- ◆ Draw the circuit schematic
 - $P_8 = A_2 A_1 B_2 B_1$
 - $P_4 = A_2 B_2 B_1' + A_2 A_1' B_2$
 - $P_2 = A_2' A_1 B_2 + A_1 B_2 B_1' + A_2 B_2' B_1 + A_2 A_1' B_1$
 - $P_1 = A_1 B_1$

CSE370, Lecture 7 15

Design example: BCD increment by 1

block diagram

I8	I4	I2	I1	O8	O4	O2	O1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

truth table

Need a 4-variable Karnaugh map for each of the 4 output functions

CSE370, Lecture 7 16

BCD increment by 1 (con't)

	I8					I8						
O8	0	0	X	1	I1	0	0	1	X	0	I1	
	1	0	0	X		0	1	0	1	X		0
I2	2	0	0	X	X	I2	2	0	0	X	X	I2
	3	0	1	X	X		3	0	1	X	X	
	I4					I4						

	I8					I8						
O2	0	0	X	0	I1	0	1	1	X	1	I1	
	1	1	1	X		0	1	0	0	X		0
I2	2	0	0	X	X	I2	2	0	0	X	X	I2
	3	0	1	X	X		3	0	1	X	X	
	I4					I4						

CSE370, Lecture 7

17

BCD increment by 1 (con't)

	I8					I8				
O8	0	0	X	1	I1	0	1	X	0	I1
	1	0	0	X		0	1	0	X	
I2	2	0	X	X	I2	2	0	X	X	I2
	3	0	X	X		3	0	X	X	
	I4					I4				

	I8					I8				
O2	0	0	X	0	I1	1	1	X	1	I1
	1	1	X	0		0	0	X	0	
I2	2	0	X	X	I2	0	0	X	X	I2
	3	1	X	X		1	1	X	X	
	I4					I4				

We **greatly** simplify the logic by using the don't cares

CSE370, Lecture 7

18

BCD increment by 1 design

◆ Draw the circuit schematic

- $O_8 = I_4 I_2 I_1 + I_8 I_1'$
- $O_4 = I_4 I_2' + I_4 I_1' + I_4' I_2 I_1$
- $O_2 = I_8 I_2' I_1 + I_2 I_1'$
- $O_1 = I_1'$

CSE370, Lecture 7

19

Loose end: POS minimization using k-maps

◆ Using k-maps for POS minimization

- Encircle the zeros in the map
- Interpret indices complementary to SOP form

			A		
	AB	00	01	11	10
CD	00	1	0	0	1
	01	0	1	0	0
C	11	1	1	1	1
	10	1	1	1	1
		B			

$$F = (B'+C+D)(B+C+D')(A'+B'+C)$$

Check using de Morgan's on SOP

$$F' = BC'D' + B'C'D + ABC'$$

$$(F')' = (BC'D' + B'C'D + ABC)'$$

$$F = (BC'D')'(B'C'D)')(ABC)'$$

$$F = (B'+C+D)(B+C+D')(A'+B'+C)$$

CSE370, Lecture 7

20