

## Overview

- ◆ Last lecture
  - PLDs
  - ROMs
  - Tristates
  - Design examples
- ◆ Today
  - Adders
    - ⇒ Ripple-carry
    - ⇒ Carry-lookahead
    - ⇒ Carry-select
  - The conclusion of combinational logic!!!



## Arithmetic circuits

- ◆ General-purpose building blocks
  - Critical components in processor datapaths
    - ⇒ Adders
    - ⇒ Multipliers (integer, floating-point)
    - ⇒ ALUs
  - Perform most computer instructions
  - Time ↔ space tradeoff
    - ⇒ Fast circuits usually require more logic

## Binary half adder

- ◆ 1-bit half adder
  - Computes sum, carry-out
    - ⇒ No carry-in
  - Sum =  $A'B + AB' = A \text{ xor } B$
  - Cout =  $AB$



A	B	S	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  

## Binary full adder

- ◆ 1-bit full adder
  - Computes sum, carry-out
    - ⇒ Carry-in allows cascaded adders
  - Sum =  $C_{in} \text{ xor } A \text{ xor } B$
  - Cout =  $AC_{in} + BC_{in} + AB$

A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

  

## Full adder: Alternative implementation


### ◆ Multilevel logic

- Slower
- Less gates
  - ↳ 2 XORs, 2 ANDs, 1 OR

$$\text{Sum} = (A \oplus B) \oplus \text{Cin}$$

$$\begin{aligned} \text{Cout} &= A\text{Cin} + B\text{Cin} + AB \\ &= (A \oplus B)\text{Cin} + AB \end{aligned}$$


A	B	C <sub>in</sub>	S	C <sub>out</sub>	C <sub>out</sub>
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1

 

CSE370, Lecture 12

5

## 2-bit ripple-carry adder

 


CSE370, Lecture 12

6

## 4-bit ripple-carry adder/subtractor
 
### ◆ Circuit adds or subtracts

- 2s complement:  $A - B = A + (-B) = A + B' + 1$




CSE370, Lecture 12

7

## Problem: Ripple-carry delay
 
### ◆ Carry propagation limits adder speed




CSE370, Lecture 12

8

## Ripple-carry adder timing diagram
 
### ◆ Critical delay

- Carry propagation
- 1111 + 0001 = 10000 is worst case



CSE370, Lecture 12

9

## One solution: Carry lookahead logic

### ◆ Compute all the carries in parallel

- Derive carries from the data inputs
  - ⇒ Not from intermediate carries
  - ⇒ Use two-level logic
- Compute all sums in parallel


### ◆ Cascade simple adders to make large adders

### ◆ Speed improvement

- 16-bit ripple-carry: ~32 gate delays
- 16-bit carry-lookahead: ~8 gate delays

### ◆ Issues



- Complex combinational logic

 

CSE370, Lecture 12

10

## Full adder again

  

CSE370, Lecture 12

11

## Carry-lookahead logic

### ◆ Carry generate: $G_i = A_i B_i$

- Generate carry when  $A = B = 1$

### ◆ Carry propagate: $P_i = A_i \text{ xor } B_i$

- Propagate carry-in to carry-out when  $(A \text{ xor } B) = 1$

### ◆ Sum and Cout in terms of generate/propagate:

$$\begin{aligned} S_i &= A_i \text{ xor } B_i \text{ xor } C_i \\ &= P_i \text{ xor } C_i \end{aligned}$$

$$\begin{aligned} C_{i+1} &= A_i B_i + C_i (A_i \text{ xor } B_i) \\ &= G_i + C_i P_i \end{aligned}$$

CSE370, Lecture 12

12

## Carry-lookahead logic (cont'd)

- ◆ Re-express the carry logic in terms of G and P

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1G_0 + P_1P_0C_0$$


$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

$$C_4 = G_3 + P_3C_3 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0$$

- ◆ Implement each carry equation with two-level logic


- Derive intermediate results directly from inputs
  - ⇨ Rather than from carries
- Allows "sum" computations to proceed in parallel
 
## Implementing the carry-lookahead logic



 
## Cascaded carry-lookahead adder

- ◆ 4 four-bit adders with internal carry lookahead
  - Second level lookahead extends adder to 16 bits


 
## Another solution: Carry-select adder

- ◆ Redundant hardware speeds carry calculation
  - Compute two high-order sums while waiting for carry-in (C4)
  - Select correct high-order sum after receiving C4



## We've finished combinational logic...

---

### ◆ What you should know

- Twos complement arithmetic
- Truth tables
- Basic logic gates
- Schematic diagrams
- Timing diagrams
- Minterm and maxterm expansions (canonical, minimized)
- de Morgan's theorem
- AND/OR to NAND/NOR logic conversion
- K-maps, logic minimization, don't cares
- Multiplexers/demultiplexers
- PLAs/PALs
- ROMs
- Adders