
 


Overview

- ◆ Last lecture
 - Introduction to sequential logic and systems
 - ⇒ The basic concepts
 - ⇒ A simple example
- ◆ Today
 - Latches
 - Flip-flops
 - ⇒ Edge-triggered D
 - ⇒ Master-slave
 - Timing diagrams
 - T flip-flops and SR latches



The D latch

 - ◆ Output depends on clock
 - Clock high: Input passes to output
 - Clock low: Latch holds its output
- ◆ Latches are level sensitive and transparent




The D flip-flop

  - ◆ Input sampled at clock edge
 - Rising edge: Input passes to output
 - Otherwise: Flip-flop holds its output
- ◆ Flip-flops are rising-edge triggered, falling-edge triggered, or master-slave




Terminology & notation


Rising-edge triggered
D flip-flop

 


Positive D latch

 


Falling-edge triggered
D flip-flop

 

Negative D latch

 


Latches versus flip-flops

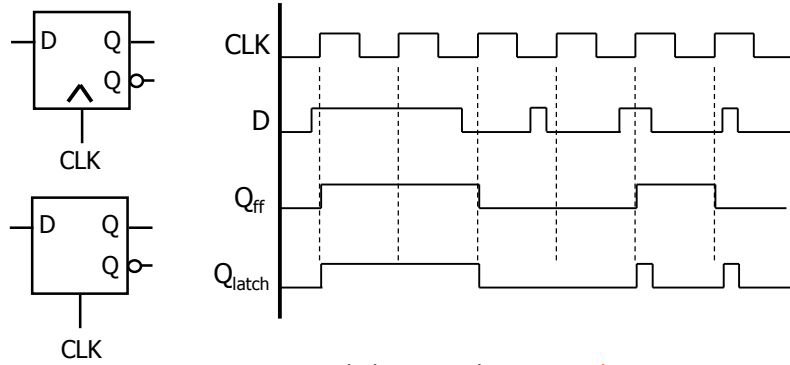

behavior is the same **unless** input changes while the clock is high


The master-slave D

 


Class example: Draw the timing diagram

Flip-flop timing

 - Setup time t_{su} : Amount of time the input must be stable before the clock transitions high (or low for negative-edge triggered FF)
- Hold time t_h : Amount of time the input must be stable after the clock transitions high (or low for negative-edge triggered FF)




 There is a timing "window" around the clock edge during which the input **must** remain stable






Flip-flop timing (cont'd)

 - ◆ Timing constraints
 - Must meet setup and hold times
 - Must meet minimum clock width
 - Will have propagation delays (low to high & high to low)




Latches versus flip-flops

   

behavior is the same **unless** input changes while the clock is high


The master-slave D

 


Class example: Draw the timing diagram

How do we make a latch?

 - ◆ Two inverters hold a bit
 - As long as power is applied




 - ◆ Storing a new memory
 - Temporarily break the feedback path




How do we make a D F/F?

 - ◆ Edge triggering is difficult
 - Label the internal nodes
 - Draw a timing diagram
 - Start with $\text{Clk}=1$



T flip-flop

 
- ◆ Full name: Toggle flip-flop
- ◆ Output toggles when input is asserted
 - If $T=1$, then $Q \rightarrow Q'$ when $\text{CLK} \uparrow$
 - If $T=0$, then $Q \rightarrow Q$ when $\text{CLK} \uparrow$




Input(t)	Q(t)	Q($t + \Delta t$)
0	0	0
0	1	1
1	0	1
1	1	0

The SR latch

 - ◆ Cross-coupled NOR gates
 - Can set ($S=1, R=0$) or reset ($R=1, S=0$) the output




 - ◆ Cross-coupled NAND gates
 - Can set ($S=1, R=0$) or reset ($R=1, S=0$) the output




SR latch behavior

◆ Truth table and timing

 

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	disallow

 


CSE370, Lecture 14

15

SR latch is glitch sensitive

◆ Static 0 hazards can set/reset latch

 - Glitch on S input sets latch
- Glitch on R input resets latch



CSE370, Lecture 14

16

Clear and preset in flip-flops

- ◆ **Clear** and **Preset** set flip-flop to a known state
 - Used at startup, reset
- ◆ **Clear** or **Reset** to a logic 0
 - Synchronous: $Q=0$ when next clock edge arrives
 - Asynchronous: $Q=0$ when reset is asserted
 - ⇒ Doesn't wait for clock
 - ⇒ Quick but dangerous
- ◆ **Preset** or **Set** the state to logic 1
 - Synchronous: $Q=1$ when next clock edge arrives
 - Asynchronous: $Q=1$ when reset is asserted
 - ⇒ Doesn't wait for clock
 - ⇒ Quick but dangerous