

Overview

- ◆ Last lecture
 - Sequential Logic Examples
- ◆ Today
 - State encoding
 - ↙ One-hot encoding
 - ↙ Output encoding
 - ↙ FSM partitioning

State encoding

- ◆ Assume n state bits and m states
 - $2^n! / (2^n - m)!$ possible encodings [$m \geq n \geq \log_2(m)$]
 - ↙ From binomial expansion
 - ↙ Example: 3 state bits, 4 states, 1680 possible state assignments
- ◆ Hard problem, with no known algorithmic solution
 - Can try heuristic approaches
 - Can try to optimize some metric
 - ↙ FSM size (amount of logic and number of FFs)
 - ↙ FSM speed (depth of logic and fanout)
 - ↙ FSM dependencies (decomposition)
- ◆ Need to consider startup
 - Self-starting FSM or explicit reset input

State-encoding strategies

- ◆ No guarantee of optimality
 - An intractable problem
- ◆ Most common strategies
 - Binary (sequential) – number states as in the state table
 - Random – computer tries random encodings
 - Heuristic – rules of thumb that seem to work well
 - ↙ e.g. Gray-code – try to give adjacent states (states with an arc between them) codes that differ in only one bit position
 - **One-hot** – use as many state bits as there are states
 - **Output** – use outputs to help encode states

One-hot encoding



- ◆ One-hot: Encode n states using n flip-flops
 - Assign a single "1" for each state
 - ↳ Example: 0001, 0010, 0100, 1000
 - Propagate a single "1" from one flip-flop to the next
 - ↳ All other flip-flop outputs are "0"
- ◆ The inverse: One-cold encoding
 - Assign a single "0" for each state
 - ↳ Example: 1110, 1101, 1011, 0111
 - Propagate a single "0" from one flip-flop to the next
 - ↳ All other flip-flop outputs are "1"
- ◆ "almost one-hot" encoding
 - Use no-hot (000...0) for the initial (reset state)
 - Assumes you never revisit the reset state

One-hot encoding (con't)

- ◆ Often the best approach for FPGAs
 - FPGAs have many flip-flops
 - One-hot machines use the least next-state logic
- ◆ Draw FSM directly from the state diagram
 - One product term per incoming arc
 - But complex state diagram \Rightarrow complex design
- ◆ One-hot designs have many possible failure modes
 - All states that aren't one-hot
 - Can create logic to reset the FSM if it enters illegal state
- ◆ Large machines require many flip-flops
 - Decompose design into smaller one-hot encoded sub-designs
 - ↳ $n+m$ states for two machines versus $n*m$ states for one

Vending machine again...

 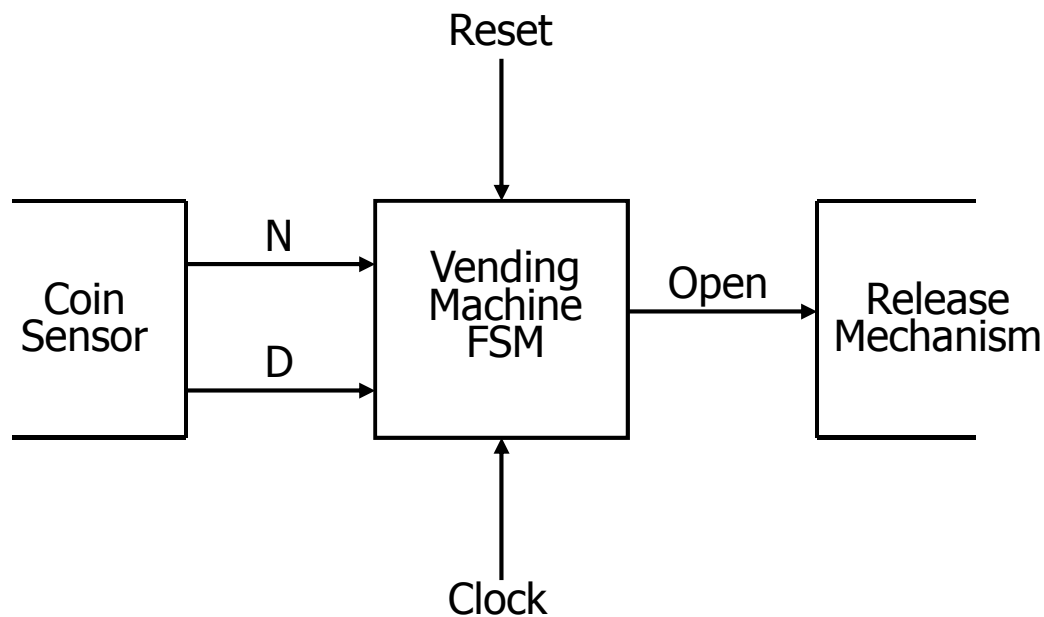- ◆ Release item after receiving 15 cents
 - Single coin slot for dimes and nickels
 - ↳ Sensor specifies coin type
 - Machine does not give change



One-hot encoded transition table

present state				inputs		next state				output
Q_3	Q_2	Q_1	Q_0	D	N	D_3	D_2	D_1	D_0	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	-
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
1	0	0	0	-	-	1	0	0	0	1

$$D_0 = Q_0 D' N'$$


$$D_1 = Q_0 N + Q_1 D' N'$$

$$D_2 = Q_0 D + Q_1 N + Q_2 D' N'$$

$$D_3 = Q_1 D + Q_2 D + Q_2 N + Q_3$$

$$\text{OPEN} = Q_3$$

One-hot encoded vending machine

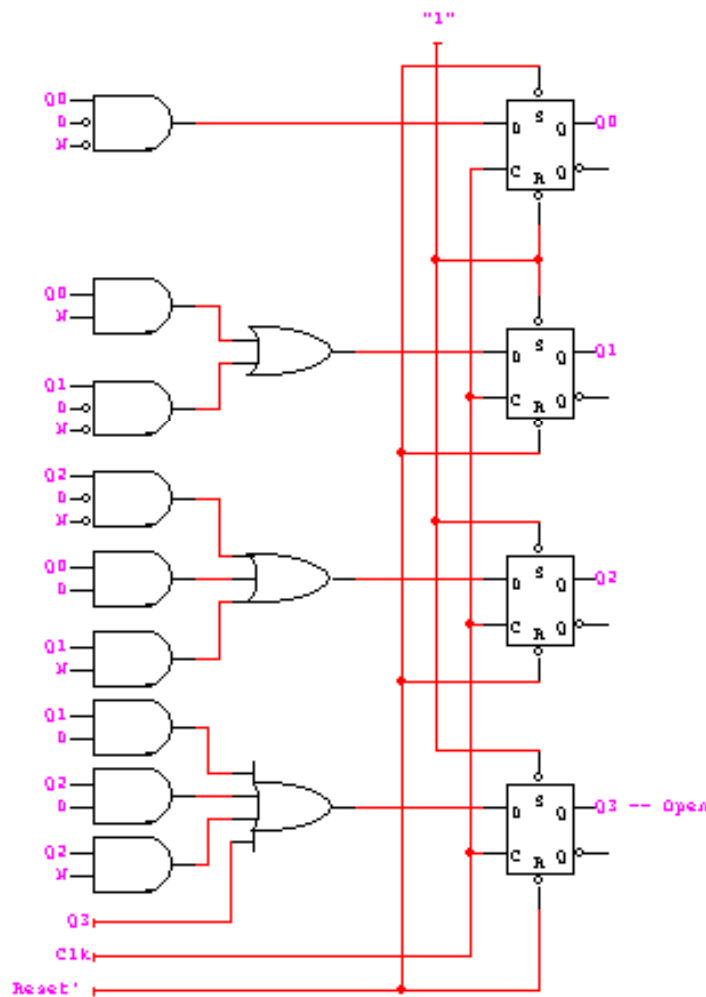

$$D_0 = Q_0 D' N'$$


$$D_1 = Q_0 N + Q_1 D' N'$$

$$D_2 = Q_0 D + Q_1 N + Q_2 D' N'$$

$$D_3 = Q_1 D + Q_2 D + Q_2 N + Q_3$$

$$\text{OPEN} = Q_3$$

Designing from the state diagram

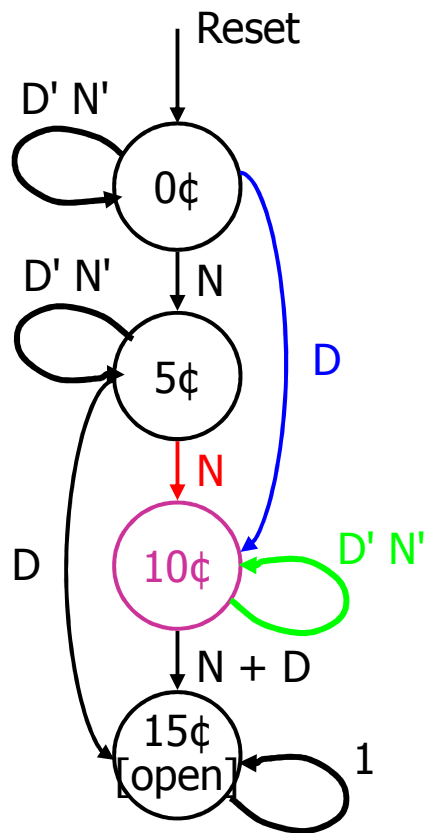


$$D_0 = Q_0 D' N'$$

$$D_1 = Q_0 N + Q_1 D' N'$$

$$D_2 = Q_0 D + Q_1 N + Q_2 D' N'$$

$$D_3 = Q_1 D + Q_2 D + Q_2 N + Q_3$$

$$\text{OPEN} = Q_3$$

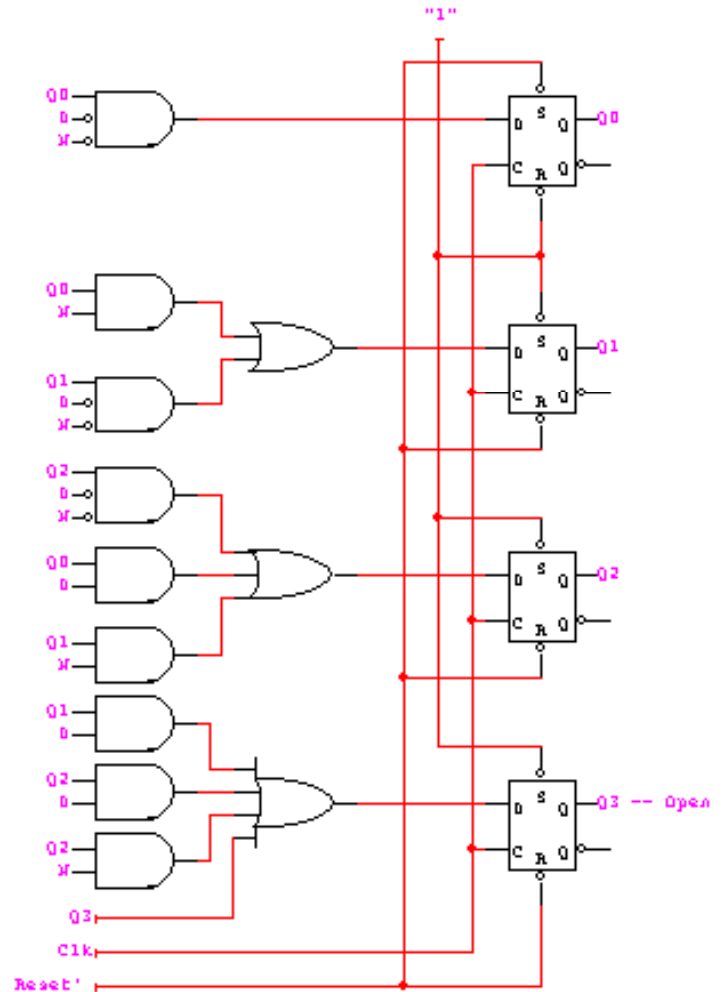

Output encoding


- ◆ Reuse outputs as state bits
 - Why create new functions when you can use outputs?
 - Bits from state assignments are the outputs for that state
 - ↳ Take outputs directly from the flip-flops
- ◆ ad hoc - no tools
 - Yields small circuits for most FSMs
 - Fits nicely with synchronous Mealy machines

FSM partitioning

- ◆ Break a large FSM into two or more smaller FSMs
- ◆ Rationale
 - Less states in each partition
 - ↳ Simpler minimization and state assignment
 - ↳ Smaller combinational logic
 - ↳ Shorter critical path
 - But more logic overall
- ◆ Goal
 - Minimize communication between partitions
 - ↳ Minimize wires & I/O
- ◆ Partitions are synchronous
 - Same clock!!!


Example: Partition the machine

- ◆ Partition into two halves

 


Introduce idle states

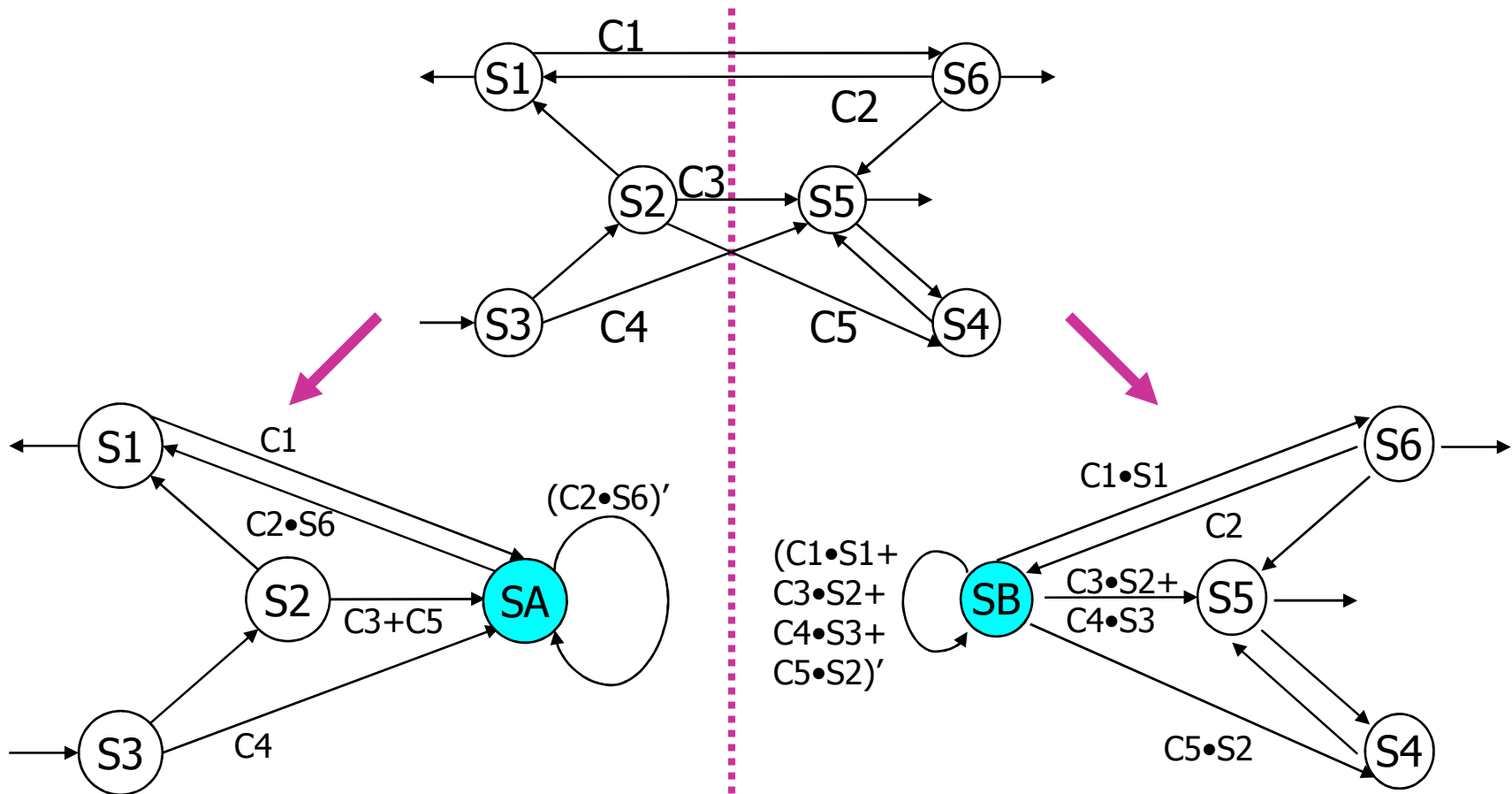- ◆ SA and SB handoff control between machines




Partitioning rules

 Rule #1: Source-state transformation
Replace by transition to idle state (SA)




 Rule #2: Destination state transformation
Replace with exit transition from idle state




Partitioning rules (con't)

 Rule #3: Multiple transitions with same source or destination
 Source \Rightarrow Replace by transitions to idle state (SA)
 Destination \Rightarrow Replace with exit transitions from idle state



 Rule #4: Hold condition for idle state
 OR exit conditions and invert




Mealy versus Moore partitions

- ◆ Mealy machines **undesirable**
 - Inputs can affect outputs immediately
 - ↳ “output” can be a handoff to another machine!!!
 - **Inputs can ripple through several machines in one clock cycle**
- ◆ Moore or synchronized Mealy **desirable**
 - Input-to-output path always broken by a flip-flop
 - But...may take several clocks for input to propagate to output
 - ↳ Output may derive from other side of a partition

Example: Six-state up/down counter



- ◆ Break into 2 parts

U \equiv count up
D \equiv count down

 

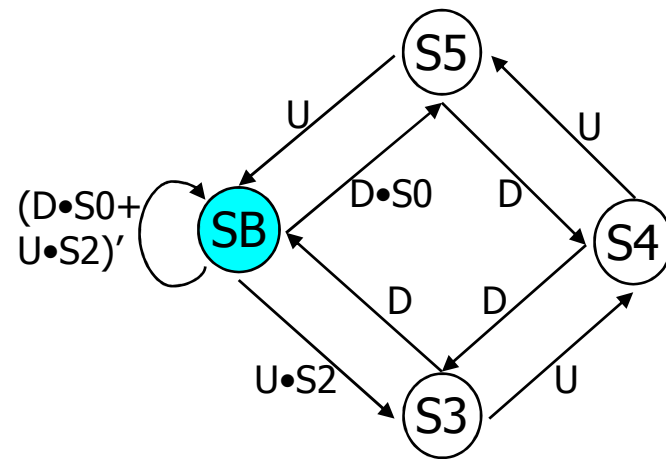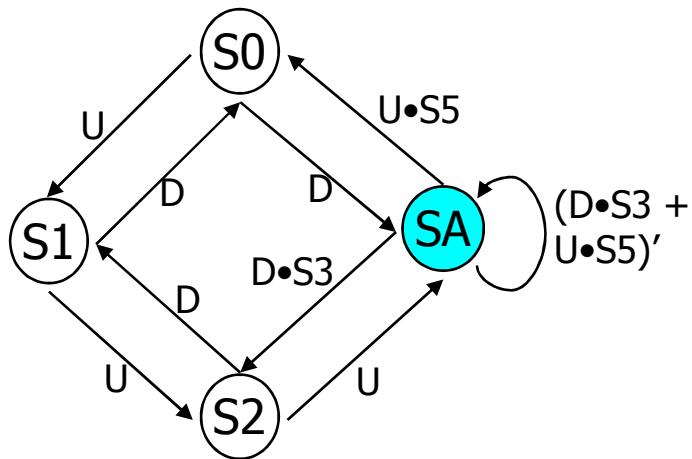Example: 6 state up/down counter (con't)

- ◆ Count sequence $S_0, S_1, S_2, S_3, S_4, S_5$
 - S_2 goes to S_A and holds, leaves after S_5
 - S_5 goes to S_B and holds, leaves after S_2
 - Down sequence is similar



Minimize communication between partitions

- ◆ Ideal world: Two machines handoff control
 - Separate I/O, states, etc.
- ◆ Real world: Minimize handoffs and common I/O
 - Minimize number of state bits that cross boundary
 - Merge common outputs
- ◆ Look for:
 - Disjoint inputs used in different regions of state diagram
 - Outputs active in only one region of state diagram
 - Isomorphic portions of state diagram
 - ↙ Add states, if necessary, to make them so
 - Regions of diagram with a single entry and single exit point

Sequential logic: What you should know

◆ Sequential logic building blocks

- Latches (R-S and D)
- Flip-flops (master/slave D, edge-triggered D & T)
- Latch and flip-flop timing (setup/hold time, prop delay)
- Timing diagrams
- Flip-flop clocking
- Asynchronous inputs and metastability
- Registers

Sequential logic: What you should know

◆ Counters

- Timing diagrams
- Shift registers
- Ripple counters
- State diagrams and state-transition tables
- Counter design procedure
 1. Draw a state diagram
 2. Draw a state-transition table
 3. Encode the next-state functions
 4. Implement the design
- Self-starting counters

Sequential logic: What you should know

◆ Finite state machines

- Timing diagrams (synchronous FSMs)
- Moore versus Mealy versus registered Mealy
- FSM design procedure
 1. Understand the problem (state diagram & state-transition table)
 2. Determine the machine's states (minimize the state diagram)
 3. Encode the machine's states (state assignment)
 4. Design the next-state logic (minimize the combinational logic)
 5. Implement the FSM
- FSM design guidelines
 - ↳ Separate datapath and control
- One-hot encoding
- FSM partitioning procedure