

Lecture 5

- Converting to use NAND and NOR
- Minimizing functions using Boolean cubes

Minimal set

- Can implement any logic function from NOT, NOR, and NAND
- In fact, can do it with only NORs and NANDs
 - NOT is just NAND or NOR with two identical inputs

X	Y	X nor Y	X	Y	X nand Y
0	0	1	0	0	1
1	1	0	1	1	0

Why NAND/NOR?

- NAND/NOR preferred for real hardware implementation
 - More efficient (less switches per gate)
- But how do we convert from the canonical forms that are expressed in AND/OR?

NAND/NOR truth tables

$(X + Y)' = X' \cdot Y'$
 NOR is equivalent to AND with inputs complemented


X	Y	X'	Y'	(X + Y)'	X' • Y'
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
 NAND is equivalent to OR with inputs complemented

X	Y	X'	Y'	(X • Y)'	X' + Y'
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Pushing the bubble

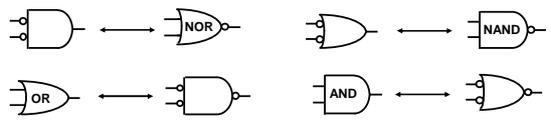
- Apply DeMorgan's
 - $A'B' = (A + B)'$
 - $A + B = (A'B)'$
 - $A' + B' = (AB)'$
 - $(AB) = (A' + B')'$



Converting to NAND/NOR


- Introduce inversions ("bubbles")
 - Introduce bubbles in pairs
 - Conserve inversions
 - Do not alter logic function

AND/OR to NAND/NAND

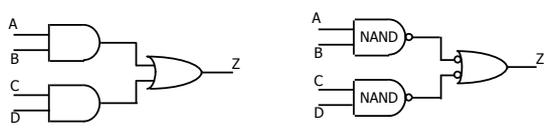


$$\begin{aligned}
 Z &= AB + CD \\
 &= (A'+B')+(C'+D)' \\
 &= [(A'+B')(C'+D)]' \\
 &= [(AB)(CD)]'
 \end{aligned}$$

AND/OR to NOR/NOR

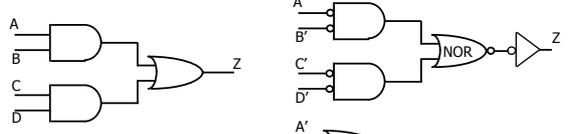


$$\begin{aligned}
 Z &= AB + CD \\
 &= (A'+B')+(C'+D)' \\
 &= [(A'+B')+(C'+D)]'' \\
 &= \{[(A'+B')+(C'+D)]'\}'
 \end{aligned}$$

OR/AND to NAND/NAND

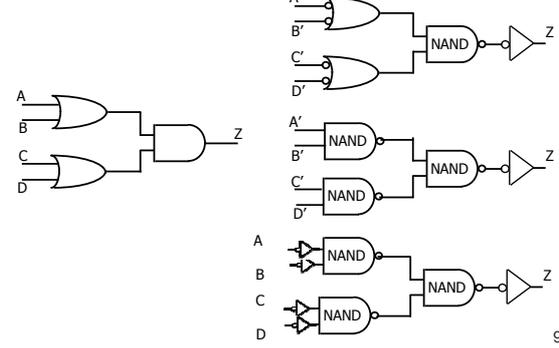

OR/AND to NOR/NOR

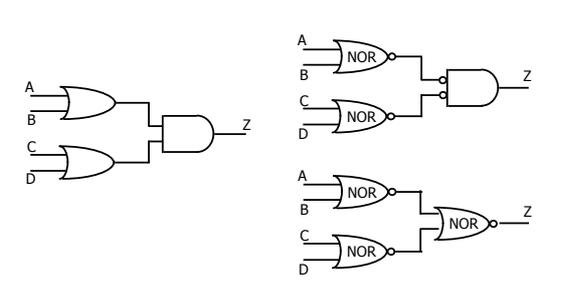

Goal: Logic minimization

- Algebraic simplification
 - Not a systematic procedure
 - Hard to know when we reached the minimum
- Computer-aided design tools
 - Require very long computation times (NP hard)
 - Heuristic methods employed—"educated guesses"

Goal: Logic minimization

- Visualization methods are useful
 - Our brain is good at figuring "simple" things out
 - Many real-world problems are solvable by hand

Key tool: Uniting Theorem


- Uniting theorem: $A(B'+B) = A$
- The approach:
 - Find where some variables don't change (the A's above) and others do (the B's above)
 - Eliminate the changing variables (the B's)

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

A has the same value in both "on-set" rows
 \Rightarrow keep A
 B has a different value in the both rows
 \Rightarrow eliminate B
 $F = A'B'+A'B = A'(B'+B) = A'$


Boolean cubes

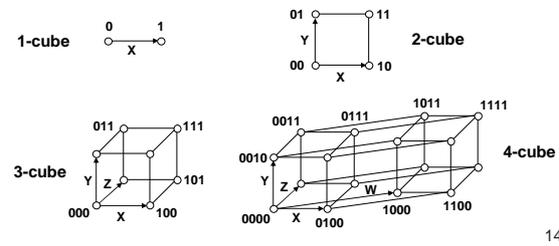- Visualization tool for the uniting theorem
 - n input variables = n-dimensional "cube"




Mapping to Boolean cubes

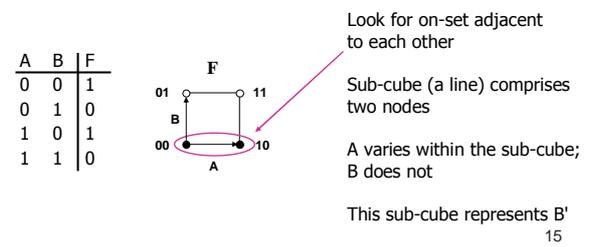- ON set = solid nodes
- OFF set = empty nodes



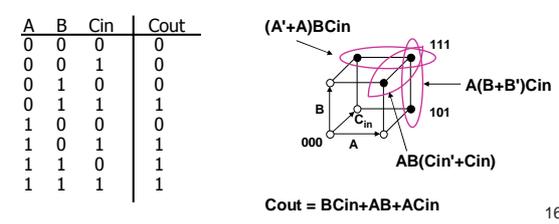
Example: Full adder carry-out

- Binary full-adder carry-out logic
 - On-set is covered by the OR of three 1-D subcubes



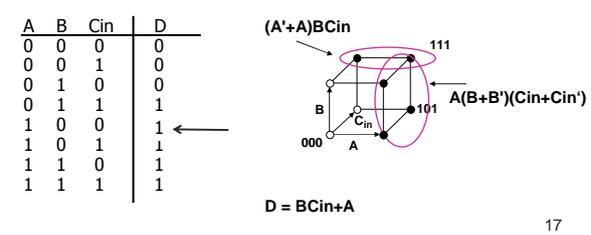Example

- Changed one bit from the previous function
 - On-set is covered by the OR of one 2-D subcube and one 3-D subcube



M-D cubes in N-D space

- In a 3-cube (three variables):
 - A 0-cube (a single node) yields a term in 3 literals
 - A 1-cube (a line of two nodes) yields a term in 2 literals
 - A 2-cube (a plane of four nodes) yields a term in 1 literal
 - A 3-cube (a cube of eight nodes) yields a constant term "1"

