

Lecture 6


- Karnaugh maps (K-maps)
- K-maps with “don't cares”

Karnaugh map (K-map)

- Flat representation of Boolean cubes
 - Easy to use for 2– 4 dimensions
 - Harder for 5 – 6 dimensions
 - Virtually impossible for >6 dimensions
 - Use CAD tools
- Help visualize adjacencies
 - On-set elements that have one variable changing are adjacent

Karnaugh map (K-map)




	A	B	F
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	0

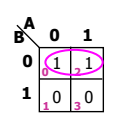

$F = B'$



2, 3, and 4 dimensional K-maps

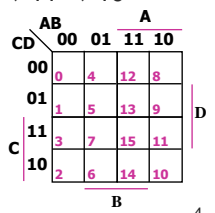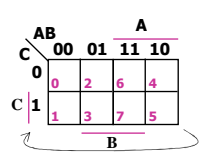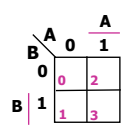- Uses Gray code: Only one bit changes between cells
 - Example: 00 → 01 → 11 → 10



Adjacencies

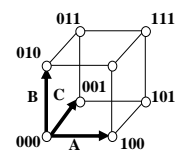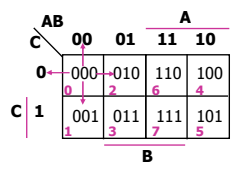- Wrap-around at edges
 - First column to last column
 - Top row to bottom row



K-map minimization

- Find the least number of subcubes, each as large as possible, that cover the ON-set.
- Make sure subcubes contain 1, 2, 4, or 8 items (remember the Boolean cube)

Example 1

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	1	0
0	1	0	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		A			
		00	01	11	10
Cin	0	0	0	1	0
	1	0	1	1	1

Cout = AB + BCin + ACin

Example 2

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

		A			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	1

D = A + BC

Example 3

$F(A,B,C) = \Sigma m(0,4,5,7)$
 $= B'C + AC$

		A			
		00	01	11	10
C	0	1	0	0	1
	1	1	0	1	1

Finding the complement

		A			
		00	01	11	10
C	0	1	0	0	1
	1	0	0	1	1

$F(A,B,C) = \Sigma m(0,4,5,7)$
 $= B'C + AC$

$F'(A,B,C) = \Sigma m(1,2,3,6)$
 $= A'C + BC'$

Example: 4 variables

- Minimize $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$
- Answer: $F = C + A'BD + B'D'$

		A			
		00	01	11	10
CD	00	1	0	0	1
	01	1	0	0	0
11	11	1	1	1	1
	10	1	1	1	1

Exercise

$F(A,B,C) = \Sigma m(0,3,6,7)$

$F(A,B,C) =$

$F'(A,B,C) =$

$F(A,B,C,D) = \Sigma m(0,3,7,8,11,15)$

$F(A,B,C,D) =$


$F'(A,B,C,D) =$

		AB			
		00	01	11	10
C	0				
	1				

		AB			
		00	01	11	10
CD	00				
	01				
11	11				
	10				

6-dimensions

K-maps become 3D for 5 & 6 variables

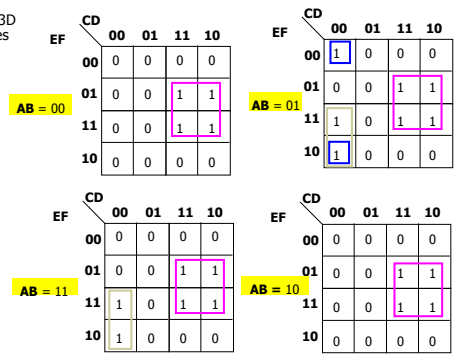

Incompletely specified functions

- Functions of n inputs have 2^n possible configurations
 - Some combinations may be unused
 - Call unused combinations "don't cares"
 - Exploit don't cares during logic minimization
 - Don't care \neq no output
 - There will always be an output signal

Don't cares

- Example: A BCD increment-by-1
 - Function F computes the next number in a BCD sequence
 - If the input is 0010_2 , the output is 0011_2
 - BCD encodes decimal digits 0-9 as 0000_2-1001_2
 - Don't care about binary numbers 1010_2-1111_2

BCD increment-by-one

INPUTS				OUTPUTS			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

off-set for W: m_0-m_6, m_9

on-set for W: m_7 and m_8

Don't care set for W:
We don't care about the output values

Don't care notation

- Minterm expansion

$$W = m_7+m_8+d_{10}+d_{11}+d_{12}+d_{13}+d_{14}+d_{15}$$


$$= \Sigma m(7,8) + d(10,11,12,13,14,15)$$
- Maxterm expansion

$$W = M_0 \cdot M_1 \cdot M_2 \cdot M_3 \cdot M_4 \cdot M_5 \cdot M_6 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$$

$$= \Pi M(0,1,2,3,4,5,6,9) \cdot D(10,11,12,13,14,15)$$
- In K-maps, can treat 'don't cares' as 0s or 1s depending on which is more advantageous

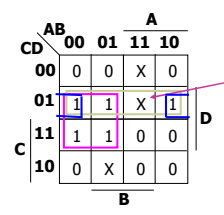Example

- $F(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - $F = A'D + B'C'D$ without using don't cares
 - $F = A'D + C'D$ using don't cares



Assign X == "1"
 \Rightarrow allows a 2-cube rather than a 1-cube