

# Lecture 8

- K-map minimization examples
- POS minimization with K-map
- Design example
- "Switching network" logic blocks (multiplexers/demultiplexers)

# Example: BCD increment-by-1

I8	I4	I2	I1	O8	O4	O2	O1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Need a 4-variable Karnaugh map for each of the 4 output functions

# BCD increment-by-1: K-maps

$$O_8 = I_8 I_2 I_1 + I_8 I_1'$$

$$O_4 = I_4 I_2' + I_4 I_1' + I_4' I_2 I_1$$

$$O_2 = I_8' I_2' I_1 + I_2' I_1'$$

$$O_1 = I_1'$$

We greatly simplify the logic by using the don't cares

# Example: Two-bit multiplier

A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	1	1
1	1	0	1	0	1	1	0
1	1	1	0	0	1	1	1
1	1	1	1	0	0	1	1

Need a 4-variable Karnaugh map for each of the 4 output functions

$$P_8 = A_2 A_1 B_2 B_1 + A_1 B_2 B_1' + A_2 A_1' B_2$$

$$P_4 = A_2 A_1 B_2 + A_1 B_2 B_1' + A_2 B_2' B_1 + A_2 A_1' B_1$$


# POS minimization with K-maps

- Encircle the zeros in the map
- Interpret indices complementary to SOP form

$$F = (B' + C + D)(B + C + D')(A' + B' + C)$$

Same idea as with truth tables

## Design example: Comparator

 


A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	1

block diagram  
truth table

Need a 4-variable Karnaugh map for each of the 3 output functions

7

## Comparator: K-maps

 


$$LT = A'B'D + A'C + B'CD$$

$$GT = BC'D + AC' + ABD'$$

$$EQ = A'B'CD' + A'BC'D + ABCD + AB'CD' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$$

8

## Comparator: Implementing EQ

 


Option 1:  
 $EQ = A'B'CD' + A'BC'D + ABCD + AB'CD'$

5 gates but they require lots of inputs

Option 2:  
 $EQ = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$


XNOR is constructed from 3 simple gates

 

7 gates but they all have 2 inputs each

9

## Comparator: Circuit schematics

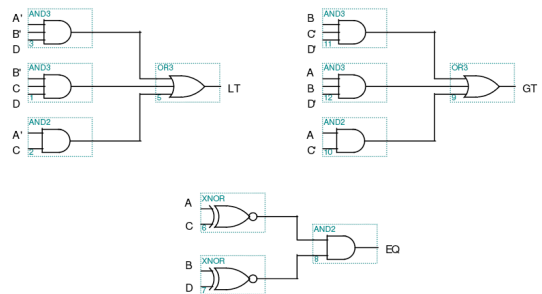


10

## Switching networks logic blocks

 
### Multiplexer (MUX)

- Routes one of many inputs to a single output
- Also called a *selector*


 
### Demultiplexer (DEMUX)

- Routes a single input to one of many outputs
- Also called a *decoder*



11

## Multiplexers

### Basic concept


- $2^n$  data inputs;  $n$  control inputs ("selects"); 1 output
- Connects one of  $2^n$  inputs to the output
- "Selects" decide which input connects to output

12

# Multiplexers: Truth tables

- Two alternative truth-tables: **Functional** and **Logical**

 
Example: A 2:1 Mux      **Functional** truth table      **Logical** truth table




S	Z	In <sub>1</sub>	In <sub>0</sub>	S	Z
0	In <sub>0</sub>	0	0	0	0
1	In <sub>1</sub>	0	0	1	0
		0	1	0	1
		0	1	1	0
		1	0	0	0
		1	0	1	1
		1	1	0	1
		1	1	1	1

# Multiplexers

 - 2:1 mux:  $Z = S_0'In_0 + S_0In_1$
- 4:1 mux:  $Z = S_1'S_0'In_0 + S_1'S_0In_1 + S_1S_0'In_2 + S_1S_0In_3$
- 8:1 mux:  $Z = S_2'S_1'S_0'In_0 + S_2'S_1'S_0In_1 + \dots$




# Multiplexers: Implementation

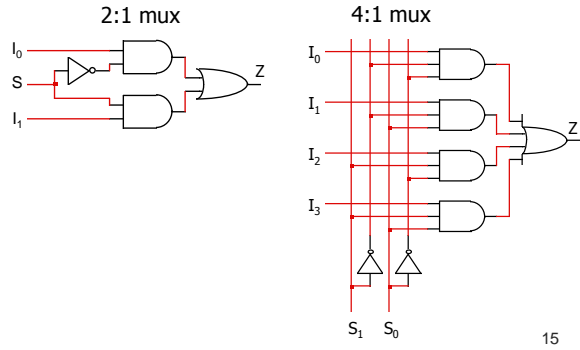
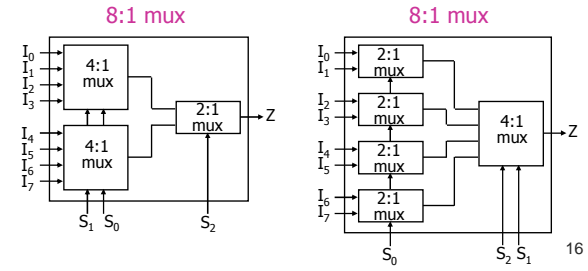
# Cascading multiplexers

- Can form large multiplexers from smaller ones (many implementation options)




# Multiplexer as logic block

- A  $2^n:1$  mux can implement any function of  $n$  variables as a lookup table

$F(A,B,C) = m_0 + m_2 + m_6 + m_7$   
 $= A'B'C' + A'BC' + ABC' + ABC$


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

# Multiplexer as logic block

- Can also use a  $2^n:1$  mux to implement a function of  $n$  variables
  - ( $n-1$ ) mux control variables  $S_0 - S_{n-2}$
  - One data variable  $S_{n-1}$
  - Four possible values for each data input: 0, 1,  $S_{n-1}$ ,  $S_{n-1}'$

A	B	C	F
0	0	0	1 C'
0	0	1	0 C'
0	1	0	1 C'
0	1	1	0 C'
1	0	0	0 0
1	0	1	0 0
1	1	0	1 1'
1	1	1	1 1'

 

# Multiplexer as logic block

- $F(A,B,C,D)$  implemented using an 8:1 mux

	AB		A		
	00	01	11	10	
CD	00	1	0	1	1
	01	1	0	0	0
C	11	1	1	0	1
	10	0	1	1	0
		B			D

Choose A,B,C as control variables  
 Choose D as a data variable

