

# Lecture 14


- Memory storage elements
  - Latches
  - Flip-flops
- State Diagrams

# Example from last time

- Door combination lock
  - Inputs: Sequence of numbers, reset, new
  - Outputs: Door open/close
  - Memory: Must remember combination
  - Memory: Must remember current state
 
# How do we store information?


- Feedback
- Example: Two inverters can hold a bit (as long as power is applied)



- What is missing?
  - How do we change the stored bit?


 
# How do we store information?

- Storing a new memory
  - Temporarily break the feedback path



  
# SR latch

- Cross-coupled NOR gates
  - Can set (S=1, R=0) or reset (R=1, S=0) the output




S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	disallow

# SR latch behavior

 


S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	disallow

 
 
## [ SR latch is glitch sensitive ]

- Static 0 glitches can set/reset latch
  - Glitch on S input sets latch
  - Glitch on R input resets latch




7

## [ State diagrams ]

- How do we characterize logic circuits?
  - Combinational circuits: **Truth tables**
  - Sequential circuits: **State diagrams**
- First draw the states
  - **States** ≡ Unique circuit configurations
- Second draw the transitions between states
  - **Transitions** ≡ Changes in state caused by inputs

8


## [ Example: SR latch ]

 

9
 
## [ Observed SR latch behavior ]


- The 1–1 state is transitory
  - Either R or S “gets ahead”
  - Latch settles to 0–1 or 1–0 state ambiguously
  - Race condition → non-deterministic transition
    - Disallow (R,S) = (1,1)



10

 
## [ D ("data") latch ]

- Output depends on clock
  - Clock high: Input passes to output
  - Clock low: Latch holds its output



11


## [ Making a D latch ]

 

12

 
## D flip-flop

- Input sampled at clock edge
  - Rising edge: Input passes to output
  - Otherwise: Flip-flop holds its output
- Flip-flops can be rising-edge triggered or falling-edge triggered



13


## Master-slave D-type flip-flop

 

- How to make into negative edge-triggered D-type flip-flop?

14


## Latches versus flip-flops

 

behavior is the same unless input changes while the clock is high

15


## Terminology and notation

 

16
 
## How to make a D flip-flop?

- Edge triggering is difficult
  - Label the internal nodes
  - Draw a timing diagram
  - Start with  $Clk=1$



17


## How to make a D flip flop?

### Falling edge-triggered flip-flop

If  $Clk=1$  then  $X=Y=0$  and SR latch block holds previous values of  $Q, Q'$ , also  $Z=D'$  and  $W=Z'=D$ .

When  $Clk \rightarrow 0$  then Y (set for SR latch block) becomes  $Z'=D$  and X (reset for SR latch block) becomes  $W'=D'$  so Q becomes D.

 
While  $Clk=0$ , if D switches then Z becomes 0 (because inputs to Z are D and D') and X and W hold their previous values and  $Y=X'=D$  as before.



18
 
## T ("toggle") flip-flop

- Output toggles when input is asserted
  - If  $T=1$ , then  $Q \rightarrow Q'$  when  $CLK \uparrow$
  - If  $T=0$ , then  $Q \rightarrow Q$  when  $CLK \uparrow$



Input( $t$ )	Q( $t$ )	Q( $t + \Delta t$ )
0	0	0
0	1	1
1	0	1
1	1	0