

Lecture 16

- Timing
 - Terminology
 - Timing issues
 - Asynchronous inputs

1

Terminology

- **Setup time t_{su}** : Amount of time the input must be stable before the clock transitions high (or low for negative-edge triggered FF)
- **Hold time t_h** : Amount of time the input must be stable after the clock transitions high (or low for negative-edge triggered FF)


2

Terminology

- **Clock width t_w** : Minimum clock width that must be met in order for FF to work properly
- Propagation delays t_{p-lh} and t_{p-hl} : Delay between clocking event and change in output (high to low, low to high)
 - Longer than hold time


3

Terminology

 

4

Cascading flip-flops

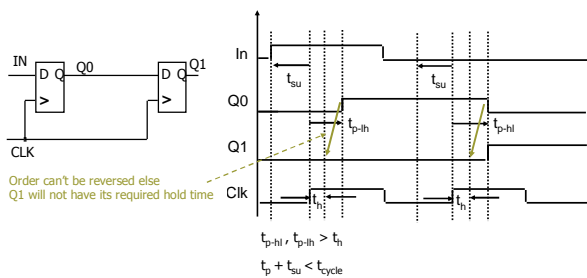

5

Cascading flip-flops

- Flip-flop propagation delays exceed hold times
 - Second stage commits its input before Q0 changes

6

System considerations

- Basic rules for correct timing
 - Clock flip-flops synchronously (all at the same time)
 - No flip-flop changes state more than once per clock cycle
 - FF propagation delay > hold time
 - Avoid mixing positive-edge triggered and negative-edge triggered flip-flops in the same circuit

7


System considerations

- Use edge-triggered flip-flops wherever possible
 - Avoid latches
 - Most common: Master-slave D

8

Clock skew

 - Goal: Clock all flip-flops at the same time



Original state: IN = 0, Q0 = 1, Q1 = 1
 Next state: Q0 = 0, Q1 = 0 (should be Q1 = 1)

9

Clock skew

- Difficult to achieve in high-speed systems
 - Clock delays (wire, buffers) are comparable to logic delays

- $T_p > T_h \rightarrow T_p > T_{skew} + T_h$
- If $T_{skew} < 0$, $T_{period} + T_{skew} > T_p + T_{su}$

10

Asynchronous versus synchronous

- **Asynchronous**
 - State changes occur when state inputs change
 - Feedback elements may be wires or delays
- **Synchronous**
 - State changes occur synchronously
 - Feedback elements are clocked

11

Asynchronous inputs

- Clocked circuits are **synchronous**
 - Circuit changes state only at clock edges
 - Signals (voltages) settle in-between clock edges
- Unclocked circuits or signals are **asynchronous**
 - No master clock
 - Real-world inputs (e.g. a keypress) are asynchronous

12

Asynchronous inputs

- Synchronous circuits have asynchronous inputs
 - Reset signal, memory wait, user input, etc.
 - Inputs can change at any time
 - We must **synchronize the input** to our clock
 - Inputs will violate flip-flop setup/hold times


13

Synchronizer failure

- Occurs when FF input changes near clock edge
 - Input is neither 1 or 0 when clock goes high
 - Output may be neither 0 or 1
 - May stay undefined for a long time
 - Undefined state is called **metastability**

14


Synchronizer failure

 

15

Minimizing synchronizer failure

 
- Failure probability can never be zero
 - Cascade two (or more) flip-flops
 - Effectively synchronizes twice
 - Both would have to fail for system to fail



16

Handling asynchronous inputs

 - **Never fan-out asynchronous inputs**
 - Synchronize at circuit boundary
 - Fan-out synchronized signal



17

Summary

- For sequential logic circuits, timing issues have to be considered.
- Inputs are often asynchronous and can cause problems.
- Different amount of delay at different part of the circuit can cause problems also.
- Solutions:
 - Cascade flip flops in series
 - Design to keep timing alignment in mind (length of wires, etc)

18