


Lecture 19

- A bigger FSM example: Hungry Robot Ant in Maze

1

Robotic ant in a maze

 - Help the ant escape the maze to find food!
 - Maze has no islands



2


Robotic ant specifics

- Sensors
 - L and R antennae, 1 if touching wall
- Actuators
 - F - forward step, TL/TR - turn left/right
- What strategy should we use?
 - Right-hand rule! (It works in physics and pretty much everywhere else...)

3

Right-hand rule


- Keep the wall to the right of the ant

 

4

Special cases: What to do?


- Left (L) antenna touching the wall

 

5

Special cases: What to do?


- Ant lost (not adjacent to any wall)

 

6


Special cases: What to do?

- Ant lost (not adjacent to any wall)

 

7

Robot ant behavior

 

8

Notes and strategy

- Notes
 - Maze has no islands
 - Corridors are wider than ant
 - Don't worry about startup
 - Assume a Moore machine
 - Assume D flip-flops
- Strategy
 - Right-hand rule!

9

FSM design procedure

- State diagram
- State-transition table
- State minimization
- State encoding
- Next-state logic minimization
- Implement the design


10

Notations

- Sensors on L and R antennae
 - Sensor = "1" if touching wall; "0" if not touching wall
 - L'R' ≡ no wall
 - L'R ≡ wall on right
 - LR' ≡ wall on left
 - LR ≡ wall in front
- Movement
 - F ≡ forward one step
 - TL ≡ turn left slightly
 - TR ≡ turn right slightly

11

1. State diagram

 

Make certain that transitions from all states are defined on all possible inputs

12


2. State transition table

state	L	R	next state	outputs
LOST	0	0	LOST	F
LOST	X	1	E	F
LOST	1	0	G	F
E	0	0	B	TL
E	X	1	E	TL
E	1	0	G	TL
G	0	0	B	TL
G	X	1	E	TL
G	1	0	G	TL
A	0	0	B	TL, F
A	0	1	A	TL, F
A	1	0	G	TL, F
A	1	1	E	TL, F
B	0	0	B	TR, F
B	0	1	A	TR, F
B	1	0	G	TR, F
B	1	1	E	TR, F

Same outputs and transitions
 ⇒ can merge states

13

3. State minimization

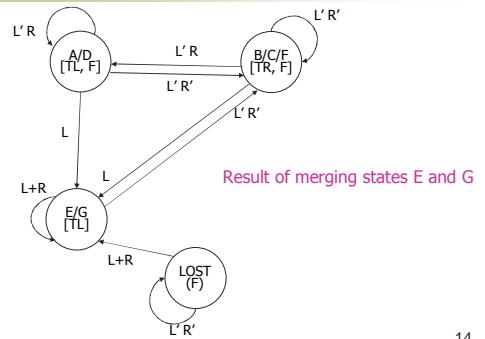

14

4. State encoding

state	L	R	next state	outputs	state	L	R	next state	outputs			
					X	Y		X+	Y+	F	TR	TL
LOST	0	0	LOST	F	0	0	0	0	0	1	0	0
LOST	X	1	E	F	0	0	X	1	0	1	0	0
LOST	1	0	E	F	0	0	1	0	0	1	0	0
E	0	0	B	TL	0	1	0	0	1	0	0	1
E	X	1	E	TL	0	1	X	1	0	0	0	1
E	1	0	E	TL	0	1	1	0	0	0	0	1
A	0	0	B	TL, F	1	0	0	0	1	1	0	1
A	0	1	A	TL, F	1	0	0	1	1	0	1	0
A	1	X	E	TL, F	1	0	1	X	0	1	1	0
B	0	0	B	TR, F	1	1	0	0	1	1	1	0
B	0	1	A	TR, F	1	1	0	1	1	0	1	0
B	1	X	E	TR, F	1	1	1	X	0	1	1	0

15

5. Next-state logic minimization


state	L	R	next state	outputs			
X	Y		X+	Y+	F	TR	TL
0	0	0	0	0	1	0	0
0	0	X	1	0	1	0	0
0	0	1	0	1	1	0	0
0	1	0	0	1	1	0	0
0	1	0	1	1	0	0	1
0	1	X	1	0	0	0	1
0	1	1	0	1	0	0	1
1	0	0	0	1	1	0	1
1	0	0	1	1	1	0	1
1	0	1	1	0	1	0	1
1	0	X	0	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	X	0	1	1	0

Why are the 1's in the last 3 K-maps in vertical columns?

16

 6. Implement the design

- Outputs are a function of the current state only - Moore machine



17