

Overview

- ◆ Logistics
 - HW5 due today
 - HW6 due next Friday
- ◆ Last lecture
 - Finish basic latches and Flip-flops
 - Registers
 - ↳ Shift registers
 - ↳ Counters
 - Basic state machine design
- ◆ Today
 - Sequential Verilog

Variables

- ◆ wire
 - Connects components together
- ◆ reg
 - Saves a value
 - ↳ Part of a behavioral description
 - Does **NOT** necessarily become a register when you synthesize
 - ↳ May become a wire
- ◆ The rule
 - Declare a variable as reg if it is a target of an assignment statement inside an always block
 - ↳ Continuous assign doesn't count

Sequential Verilog

- ◆ Sequential circuits: Registers & combinational logic
 - Use positive edge-triggered registers
 - Avoid latches and negative edge-triggered registers
- ◆ Register is triggered by "posedge clk"

```
module register(Q, D, clock);
  input  D, clock;
  output Q;
  reg   Q;

  always @(posedge clock) begin
    Q <= D;
  end
endmodule
```

Example: A D flip-flop

A real register. Holds Q between clock edges

always block

- ◆ A construct that describes a circuit's behavior
 - Can contain multiple statements
 - Can contain *if*, *for*, *while*, *case*
 - Triggers at the specified conditions
 - *begin/end* groups statements within *always* block

```
module register(Q, D, clock);
  input  D, clock;
  output Q;
  reg   Q;

  always @(posedge clock) begin
    Q <= D;
  end
endmodule
```

always example

```
module and_gate(out, in1, in2);
  input  in1, in2;
  output out;
  reg   out;

  always @(in1 or in2) begin
    out = in1 & in2;
  end
endmodule
```

Not a real register!
Holds assignment in
always block

The compiler will not synthesize
this code to a register, because
out changes whenever *in1* or *in2*
change. Can instead simply write
wire out, in1, in2;
and (out, in1, in2);

specifies when block is executed
i.e. triggered by changes in *in1* or *in2*

Incomplete sensitivity list or incomplete assignment

- ◆ What if you omit an input trigger (e.g. *in2*)
 - Compiler will insert a latch to hold the state
 - Becomes a sequential circuit — **NOT** what you want

```
module and_gate (out, in1, in2);
  input  in1, in2;
  output out;
  reg   out;

  always @(in1) begin
    out = in1 & in2;
  end
endmodule
```

Real state! Holds *out*
because *in2* isn't specified
in *always* sensitivity list

2 rules:

- 1) Include all inputs in the trigger list
- 2) Use complete assignments
 - ⇒ Every path must lead to an assignment for *out*
 - ⇒ Otherwise *out* needs a state element

Incomplete sensitivity lists

- ◆ • always @(a or b) // it's or, not ||
f = a & b;
- ◆ • always @(a)
f = a & b;
- ◆ • always
f = a & b;
- ◆ • Just use always@(*) for combinational logic

Assignments

- ◆ Be careful with always assignments
 - Which of these statements generate state?

```
always @(c or x) begin
  if (c) begin
    value = x;
  end
  y = value;
end
```

```
always @(c or x) begin
  value = x;
  if (c) begin
    value = 0;
  end
  y = value;
end
```

```
always @(c or x) begin
  if (c)
    value = 0;
  else if (x)
    value = 1;
end
```

```
always @(a or b)
  f = a & b & c;
end
```

2 rules:

- 1) Include all inputs in the sensitivity list
- 2) Use complete assignments
 - ⇒ Every path must lead to an assignment for *out*
 - ⇒ Otherwise *out* needs a state element

Another way: Use functions

- ◆ Functions for combinational logic
 - Functions can't have state

```
module and_gate (out, in1, in2);
  input in1, in2;
  output out;

  assign out = myfunction(in1, in2);
  function myfunction;
    input in1, in2;
    begin
      myfunction = in1 & in2;
    end
  endfunction
endmodule
```

Benefits:

- Functions force a result
 - ⇒ Compiler will fail if function does not generate a result
 - ⇒ If you build a function wrong the circuit will not synthesize. If you build an always block wrong you get a register

if

- ◆ Same as C *if* statement

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    if (sel == 2'b00) Y = A;
    else if (sel == 2'b01) Y = B;
    else if (sel == 2'b10) Y = C;
    else if (sel == 2'b11) Y = D;
endmodule
```

- ⇒ Single *if* statements synthesize to multiplexers
- ⇒ Nested *if/else* statements usually synthesize to logic

if (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    if (sel[0] == 0)
      if (sel[1] == 0) Y = A;
      else Y = B;
    else
      if (sel[1] == 0) Y = C;
      else Y = D;
endmodule
```

case

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
  input [1:0] sel; // 2-bit control signal
  input A, B, C, D;
  output Y;
  reg Y; // target of assignment

  always @(sel or A or B or C or D)
    case (sel)
      2'b00: Y = A;
      2'b01: Y = B;
      2'b10: Y = C;
      2'b11: Y = D;
    endcase
endmodule
```

- case* executes sequentially
 - ⇒ First match executes
 - ⇒ Don't need to break out of *case*
 - case* statements synthesize to muxes

case (another way)

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel; // 2-bit control signal
input A, B, C, D;
output Y;

assign out = mymux(sel, A, B, C, D);
function mymux;
input [1:0] sel, A, B, C, D;
begin
  case (sel)
    2'b00: mymux = A;
    2'b01: mymux = B;
    2'b10: mymux = C;
    2'b11: mymux = D;
  endcase
end
endfunction
endmodule
```

Note: You can define a function in a file
Then include it into your Verilog module

CSE370, Lecture 16

13

default case

```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
  case (A)
    8'b00000001: Y = 0;
    8'b00000010: Y = 1;
    8'b00000100: Y = 2;
    8'b00001000: Y = 3;
    8'b00010000: Y = 4;
    8'b00100000: Y = 5;
    8'b01000000: Y = 6;
    8'b10000000: Y = 7;
    default: Y = 3'bx; // Don't care about other cases
  endcase
endmodule
```

If you omit the *default*, the compiler will
create a latch for Y
⇒ Either list all 256 cases
⇒ Or use a function (compiler will
warn you of missing cases)

CSE370, Lecture 16

14

case executes sequentially

```
// Priority encoder
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment

always @(A)
  case (1'b1)
    A[0]: Y = 0;
    A[1]: Y = 1;
    A[2]: Y = 2;
    A[3]: Y = 3;
    A[4]: Y = 4;
    A[5]: Y = 5;
    A[6]: Y = 6;
    A[7]: Y = 7;
    default: Y = 3'bx; // Don't care when input is all 0's
  endcase
endmodule
```

Case statements execute sequentially
⇒ Take the first alternative that matches

CSE370, Lecture 16

15

for

```
// simple encoder
module encode (A, Y);
input [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
reg [2:0] Y; // target of assignment
integer i; // Temporary variables for program
reg [7:0] test;

always @(A) begin
  test = 8b'00000001;
  Y = 3'bx;
  for (i = 0; i < 8; i = i + 1) begin
    if (A == test) Y = i;
    test = test << 1; // Shift left, pad with 0s
  end
end
endmodule
```

for statements synthesize as
cascaded combinational logic
⇒ Verilog unrolls the loop

CSE370, Lecture 16

16

Verilog while/ repeat/ forever

- ◆ *while* (expression) statement
 - execute statement while expression is true
- ◆ *repeat* (expression) statement
 - execute statement a fixed number of times
- ◆ *forever* statement
 - execute statement forever

CSE370, Lecture 16

17

Blocking and non-blocking assignments

- ◆ Blocking assignments ($Q = A$)
 - Variable is assigned immediately
 - New value is used by subsequent statements
- ◆ Non-blocking assignments ($Q <= A$)
 - Variable is assigned after all scheduled statements are executed
 - Value to be assigned is computed but saved for later
- ◆ Example: Swap

```
always @(posedge CLK)
begin
  temp = B;
  B = A;
  A = temp;
end


always @(posedge CLK)
begin
  A <= B;
  B <= A;
end
```

CSE370, Lecture 16


18

Blocking and non-blocking assignments
 
```
reg B, C, D;
always @(posedge clk)
begin
  B = A;
  C = B;
  D = C;
end
```


 
```
reg B, C, D;
always @(posedge clk)
begin
  B <= A;
  C <= B;
  D <= C;
end
```



Swap

◆ The following code executes incorrectly

- One block executes first
- Loses previous value of variable

```
always @(posedge CLK)
begin
  A = B;
end
always @(posedge CLK)
begin
  B = A;
end
```

◆ Non-blocking assignment fixes this

- Both blocks are scheduled by posedge CLK

```
always @(posedge CLK)
begin
  A <= B;
end
always @(posedge CLK)
begin
  B <= A;
end
```

A simple stateful example

```
module stateful_and (out, in, clk);
input in, clk;
output out;
reg out;


always @(posedge clk) begin
  out <= in & out;
end
endmodule
```

Parallel versus serial execution

◆ **assign** statements are implicitly parallel

- "=" means continuous assignment
- Example
 
```
assign E = A & D;
assign A = B & C;
```
- A and B change if B changes



◆ **always** blocks execute in parallel

- always @(posedge clock)


◆ Procedural block internals not necessarily parallel

- "=" is a blocking assignment (sequential)
- "<=" is a nonblocking assignment (parallel)
- Examples of procedures: always, function, etc.

Synthesis examples

```
wire [3:0] x, y, a, b, c, d;
```
 
```
assign apr = ^a;
assign y = a & ~b;
assign x = (a == b) ?
  a + c : d + a;
```



Verilog tips and traps

Constants: 32 bits, decimal

- wire [7:0] foo = 127; // synthesis warning!
- wire [7:0] foo = 8'd127;
- wire [7:0] foo = 8'b11111111;
- wire [7:0] foo = 8'hff;
- wire [7:0] foo = 8'hFF;
- watch out: 1010 looks like 4'b1010!

Truncation

```
wire [7:0] a = 8'hAB;
wire b;      // oops! forgot width
wire [7:0] c;
assign b = a; // synthesis warning if lucky.
assign c = a;
```

TIP: (blocking) = vs. <= (non-blocking)

- ◆ • Simple rule:
 - • If you want sequential logic, use always @(posedge clk) with <= (non-blocking)
 - • If you want combinational logic, use always @(*) with = (blocking)

Verilog Stratified Event Queue [1]

- ◆ Region 1: Active Events
 - Most events except those explicitly in other regions
 - Includes \$display system tasks
- ◆ Region 2: Inactive Events
 - Processed after all active events
 - #0 delay events (**bad!**)
- ◆ Region 3: Non-blocking Assign Update Events
 - Evaluation previously performed
 - Update is after all active and inactive events complete
- ◆ Region 4: Monitor Events
 - Caused by \$monitor and \$strobe system tasks
- ◆ Region 5: Future Events
 - Occurs at some future simulation time
 - Includes future events of other regions
 - Other regions only contain events for CURRENT simulation time

Verilog Stratified Event Queue [2]

