

Lecture 19


- ◆ Logistics
 - Lab 8 this week to be done in pairs
 - ↳ Find a partner before your lab period
 - ↳ Otherwise you will have to wait for a pairing which will slow you down
 - HW5 and HW6 solutions out today
 - HW7 out today due Wednesday March 4
 - Midterm 2 Wednesday
 - ↳ Covers material up to simple FSM
 - ↳ Review session tomorrow, 4:30 here, EEB 037
- ◆ Last lecture
 - Counter FSM design
 - General Finite State Machine Design
 - ↳ Vending machine example
- ◆ Today
 - Moore/Mealy machines
 - Midterm 2 topics and logistics

The "WHY" slide


- ◆ Moore/Mealy machines
 - There are two different ways to express the FSMs with respect to the output. Both have different advantages so it is good to know them.

Generalized FSM model: Moore and Mealy

 - ◆ Combinational logic computes next state and outputs
 - Next state is a function of current state and inputs
 - Outputs are functions of
 - ↳ Current state (**Moore** machine)
 - ↳ Current state and inputs (**Mealy** machine)



Moore versus Mealy machines

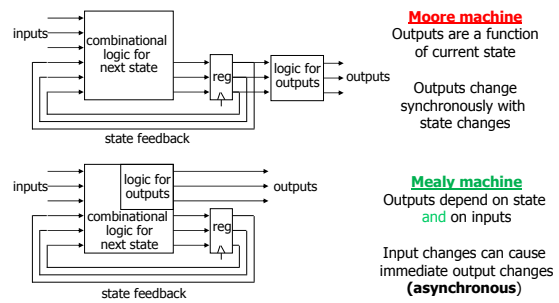

Impacts start of the FSM design procedure

- Counter-design procedure
 1. State diagram
 2. State-transition table
 3. Next-state logic minimization
 4. Implement the design
- FSM-design procedure
 1. State diagram
 2. State-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design

State Diagrams


- ◆ Moore machine
 - Each state is labeled by a pair:

$$\text{state-name/output} \quad \text{or} \quad \text{state-name} [\text{output}]$$
- ◆ Mealy machine
 - Each transition arc is labeled by a pair:

$$\text{input-condition/output}$$

 Example 10 → 01: Moore or Mealy?


- ◆ Circuits recognize AB=10 followed by AB=01
 - What kinds of machines are they?



CSE370, Lecture 19

 Example "01 or 10" detector: a Moore machine


- ◆ Output is a function of state only
 - Specify output in the state bubble



CSE370, Lecture 19

 Example "01 or 10" detector: a Mealy machine

- ◆ Output is a function of state and inputs
 - Specify outputs on transition arcs



CSE370, Lecture 19


Comparing Moore and Mealy machines

- ◆ Moore machines
 - + Safer to use because outputs change at clock edge
 - May take additional logic to decode state into outputs
- ◆ Mealy machines
 - + Typically have fewer states
 - + React faster to inputs — don't wait for clock
 - Asynchronous outputs can be dangerous
- ◆ We often design synchronous Mealy machines
 - Design a Mealy machine
 - Then register the outputs

CSE370, Lecture 19

Synchronous (registered) Mealy machine

 
- ◆ Registered state and registered outputs
 - No glitches on outputs
 - No race conditions between communicating machines




CSE370, Lecture 19

Example "=01": Moore or Mealy?

- ◆ Recognize AB = 01
 - Mealy or Moore?

 

Registered Mealy (actually Moore)

 

Moore

CSE370, Lecture 19


Example: A parity checker

- ◆ Serial input string
 - OUT=1 if odd # of 1s in input
 - OUT=0 if even # of 1s in input
- ◆ Let's do this for Moore and Mealy


Example: A parity checker

1. State diagram

Moore

 

Mealy

 

Example: A parity checker

1. State-transition table

Moore

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	0
Odd	0	Odd	1
Odd	1	Even	1

Mealy

Present State	Input	Next State	Present Output
Even	0	Even	0
Even	1	Odd	1
Odd	0	Odd	1
Odd	1	Even	0

Example: A parity checker

3. State minimization: Already minimized

- Need both states (even and odd)
- Use one flip-flop

Example: A parity checker

4. State encoding

Moore

Present State	Input	Next State	Present Output
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1

Assignment
Even 0
Odd 1

Mealy


Present State	Input	Next State	Present Output
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

Example: A parity checker

5. Next-state logic minimization

- Assume D flip-flops
- Next state = (present state) XOR (present input)

6. Implement the design

 

What was covered after midterm 1

- ◆ Combinational logic applications
 - PLAs/PALs
 - ROMs
 - Adders
 - Multi-level logic
 - Timing diagrams
 - Hazards

*1010
+ 0110

????*

What was covered after midterm 1

- ◆ Sequential logic building blocks
 - Latches (R-S and D)
 - Flip-flops (D and T)
 - Latch and flip-flop timing (setup/hold time, prop delay)
 - Timing diagrams
 - Asynchronous inputs and metastability
 - Registers

*Remember that
the last number was 1*

What was covered after midterm 1

- ◆ Counters
 - Timing diagrams
 - Shift registers
 - Ring counters
 - State diagrams and state-transition tables
 - Counter design procedure
 1. Draw a state diagram
 2. Draw a state-transition table
 3. Encode the next-state functions
 4. Implement the design
 - Self-starting counters

1, 2, 3, 4, ...

What was covered after midterm 1

- ◆ Finite state machines
 - FSM design procedure
 1. State diagram
 2. State-transition table
 3. State minimization
 4. State encoding
 5. Next-state logic minimization
 6. Implement the design
 - No Mealy machines

*The last coin was 25cents and
already had 50cents deposited
so let's pop out a soda*

Don't expect to know a ton of FSM.
Just understand what was presented in the lectures.

Midterm 2 logistics

- ◆ 45 minutes long (starts 10:35)
- ◆ Materials covered from
 - Lectures 9 to 18 (but not Sequential Verilog or Moore/Mealy)
 - HW 4, 5, and 6
- ◆ Closed book/notes, no calculator
- ◆ Scratch papers provided
- ◆ Just have your pencil/pen and eraser
- ◆ Raise hand for questions (don't walk to get help)